

Lecture 22

OUTLINE

- Differential Amplifiers
 - General considerations
 - BJT differential pair
 - Qualitative analysis
 - Large-signal analysis
 - Small-signal analysis
 - Frequency response
- Reading: Chapter 10.1-10.2


EE105 Spring 2008

Lecture 22, Slide 1

Prof. Wu, UC Berkeley

"Humming" Noise in Audio Amplifier

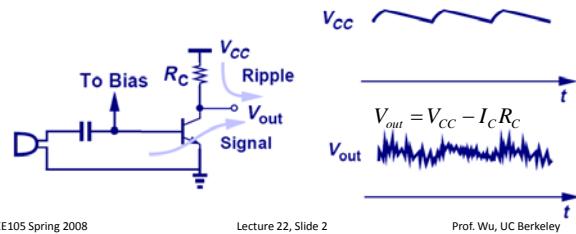- Consider the amplifier below which amplifies an audio signal from a microphone.
- If the power supply (V_{CC}) is time-varying, it will result in an additional (undesirable) voltage signal at the output, perceived as a "humming" noise by the user.




EE105 Spring 2008

Lecture 22, Slide 2

Prof. Wu, UC Berkeley

Supply Ripple Rejection

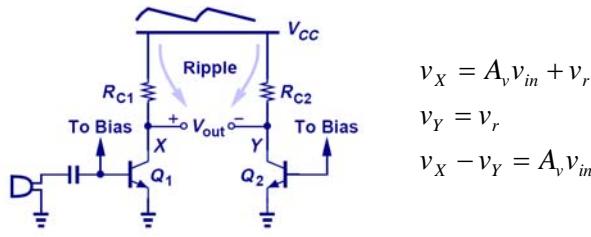- Since node X and Y each see the voltage ripple, their voltage difference will be free of ripple.




EE105 Spring 2008

Lecture 22, Slide 3

Prof. Wu, UC Berkeley

Ripple-Free Differential Output

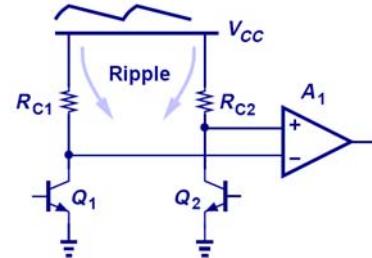- If the input signal is to be a voltage difference between two nodes, an amplifier that senses a **differential signal** is needed.




EE105 Spring 2008

Lecture 22, Slide 4

Prof. Wu, UC Berkeley

Common Inputs to Differential Amp.

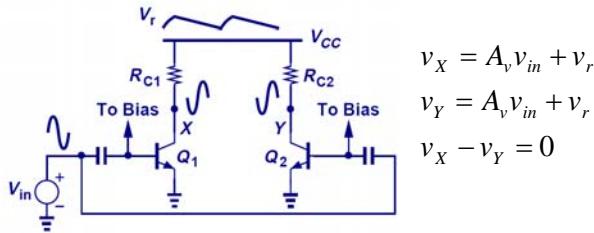- The voltage signals applied to the input nodes of a differential amplifier cannot be in phase; otherwise, the differential output signal will be zero.




EE105 Spring 2008

Lecture 22, Slide 5

Prof. Wu, UC Berkeley

Differential Inputs to Differential Amp.

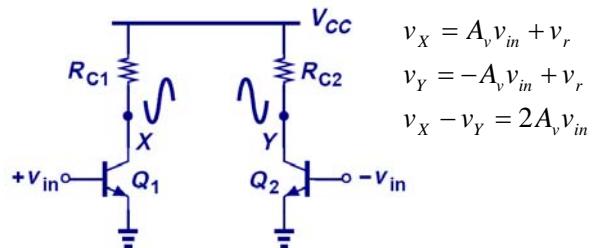- When the input voltage signals are 180° out of phase, the resultant output node voltages are 180° out of phase, so that their difference is enhanced.




EE105 Spring 2008

Lecture 22, Slide 6

Prof. Wu, UC Berkeley

Differential Signals

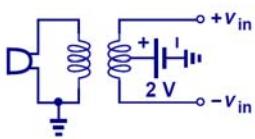
- Differential signals share the same average DC value and are equal in magnitude but opposite in phase.
- A pair of differential signals can be generated, among other ways, by a transformer.




EE105 Spring 2008

Lecture 22, Slide 7

Prof. Wu, UC Berkeley

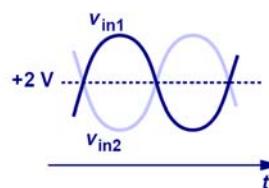

Single-Ended vs. Differential Signals

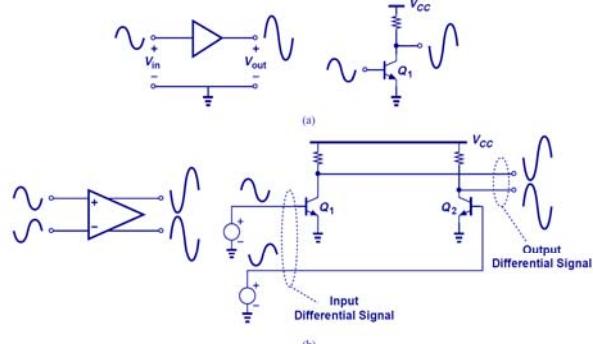

EE105 Spring 2008

Lecture 22, Slide 8

Prof. Wu, UC Berkeley

Differential Pair

The circuit shows two transistors, Q₁ and Q₂, connected in a differential pair. The drain of Q₁ is connected to node X, and the drain of Q₂ is connected to node Y. Both nodes X and Y are connected to ground through resistors R_{C1} and R_{C2} respectively. The source of Q₁ is connected to input V_{in1}, and the source of Q₂ is connected to input V_{in2}. A tail current source I_{EE} is connected between the emitters of Q₁ and Q₂.

- With the addition of a tail current, the circuits above operate as an elegant, yet robust differential pair.

EE105 Spring 2008 Lecture 22, Slide 9 Prof. Wu, UC Berkeley

Common-Mode Response

The circuit shows two transistors, Q₁ and Q₂, connected in a differential pair. The drain of Q₁ is connected to node X, and the drain of Q₂ is connected to node Y. Both nodes X and Y are connected to ground through resistors R_{C1} and R_{C2} respectively. The source of Q₁ is connected to input V_{in1}, and the source of Q₂ is connected to input V_{in2}. A tail current source I_{EE} is connected between the emitters of Q₁ and Q₂. A common-mode voltage source V_{CM} is connected between the bases of Q₁ and Q₂.

$V_{BE1} = V_{BE2}$
 $I_{C1} = I_{C2} = \frac{I_{EE}}{2}$
 $V_X = V_Y = V_{CC} - R_C \frac{I_{EE}}{2}$
 $R_{C1} = R_{C2} = R_C$

EE105 Spring 2008 Lecture 22, Slide 10 Prof. Wu, UC Berkeley

Differential Response

The circuit shows two transistors, Q₁ and Q₂, connected in a differential pair. The drain of Q₁ is connected to node X, and the drain of Q₂ is connected to node Y. Both nodes X and Y are connected to ground through resistors R_C respectively. The source of Q₁ is connected to input V_{in1} (+2 V), and the source of Q₂ is connected to input V_{in2} (+1 V). A tail current source I_{EE} is connected between the emitters of Q₁ and Q₂.

$V_{CC} = 2.5 \text{ V}$
 $V_{out} = +0.5 \text{ V}$
 $I_{C1} = I_{EE}$
 $I_{C2} = 0$
 $V_X = V_{CC} - R_C I_{EE}$
 $V_Y = V_{CC}$

EE105 Spring 2008 Lecture 22, Slide 11 Prof. Wu, UC Berkeley

Differential Response (cont'd)


The circuit shows two transistors, Q₁ and Q₂, connected in a differential pair. The drain of Q₁ is connected to node X, and the drain of Q₂ is connected to node Y. Both nodes X and Y are connected to ground through resistors R_C respectively. The source of Q₁ is connected to input V_{in1} (+1 V), and the source of Q₂ is connected to input V_{in2} (+2 V). A tail current source I_{EE} is connected between the emitters of Q₁ and Q₂.

$V_{CC} = 2.5 \text{ V}$
 $V_{out} = +1.5 \text{ V}$
 $I_{C2} = I_{EE}$
 $I_{C1} = 0$
 $V_Y = V_{CC} - R_C I_{EE}$
 $V_X = V_{CC}$

EE105 Spring 2008 Lecture 22, Slide 12 Prof. Wu, UC Berkeley

Differential Pair Characteristics

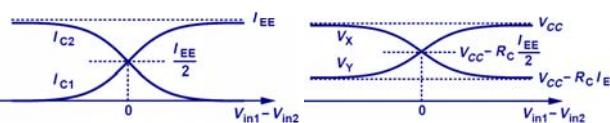- A differential input signal results in variations in the output currents and voltages, whereas a common-mode input signal does not result in any output current/voltage variations.




EE105 Spring 2008

Lecture 22, Slide 13

Prof. Wu, UC Berkeley

Virtual Ground

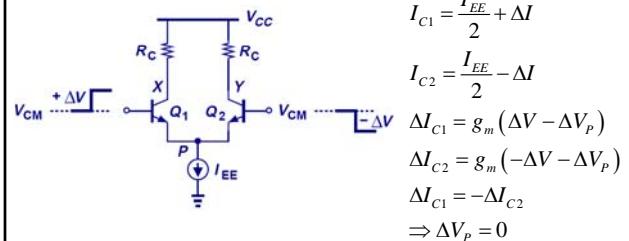- For small input voltages ($+\Delta V$ and $-\Delta V$), the g_m values are \sim equal, so the increase in I_{C1} and decrease in I_{C2} are \sim equal in magnitude. Thus, the voltage at node P is constant and can be considered as AC ground.




EE105 Spring 2008

Lecture 22, Slide 14

Prof. Wu, UC Berkeley

Extension of Virtual Ground

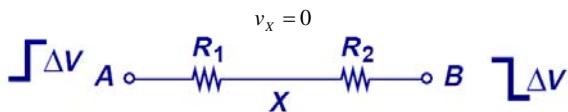- It can be shown that if $R_1 = R_2$, and the voltage at node A goes up by the same amount that the voltage at node B goes down, then the voltage at node X does not change.




EE105 Spring 2008

Lecture 22, Slide 15

Prof. Wu, UC Berkeley

Small-Signal Differential Gain

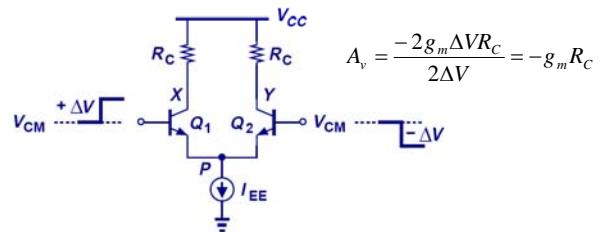- Since the output signal changes by $-2g_m\Delta V R_C$ when the input signal changes by $2\Delta V$, the small-signal voltage gain is $-g_m R_C$.
- Note that the voltage gain is the same as for a CE stage, but that the power dissipation is doubled.




EE105 Spring 2008

Lecture 22, Slide 16

Prof. Wu, UC Berkeley

Large-Signal Analysis

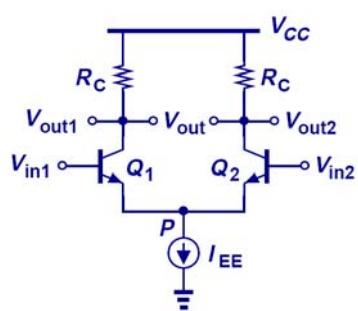


$$\begin{aligned}
 V_{m1} - V_{in2} &= V_{BE1} - V_{BE2} \\
 &= V_T \ln\left(\frac{I_{C1}}{I_S}\right) - V_T \ln\left(\frac{I_{C2}}{I_S}\right) \\
 &= V_T \ln\left(\frac{I_{C1}}{I_{C2}}\right) \\
 I_{C1} + I_{C2} &= I_{EE} \\
 I_{C1} &= \frac{I_{EE} e^{\frac{V_{in1}-V_{in2}}{V_T}}}{1 + e^{\frac{V_{in1}-V_{in2}}{V_T}}} \\
 I_{C2} &= \frac{I_{EE}}{1 + e^{\frac{V_{in1}-V_{in2}}{V_T}}}
 \end{aligned}$$

EE105 Spring 2008

Lecture 22, Slide 17

Prof. Wu, UC Berkeley

Input/Output Characteristics

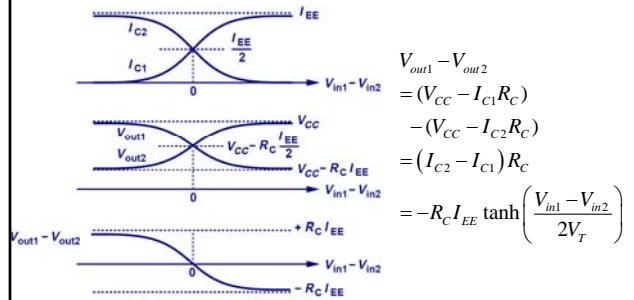


EE105 Spring 2008

Lecture 22, Slide 18

Prof. Wu, UC Berkeley

Linear/Nonlinear Regions of Operation


Amplifier operating in linear region

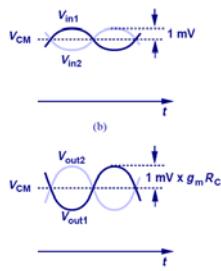

EE105 Spring 2008


Lecture 22, Slide 19

Amplifier operating in non-linear region

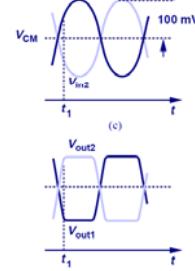

Prof. Wu, UC Berkeley

Small-Signal Analysis

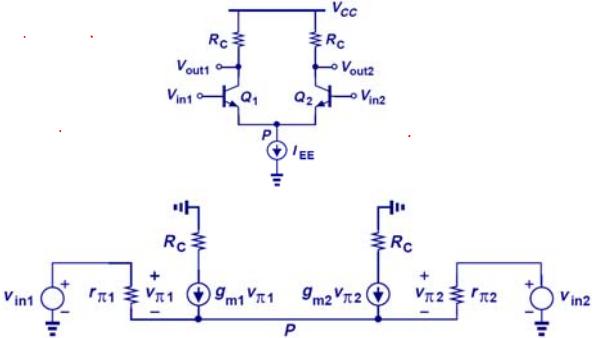


EE105 Spring 2008

Lecture 22, Slide 20

Prof. Wu, UC Berkeley

Half Circuits

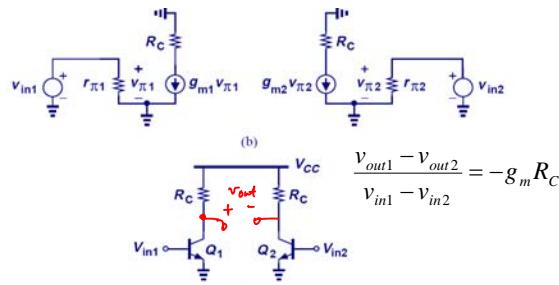- Since node P is AC ground, we can treat the differential pair as two CE "half circuits."




EE105 Spring 2008

Lecture 22, Slide 21

Prof. Wu, UC Berkeley

Half Circuit Example 1

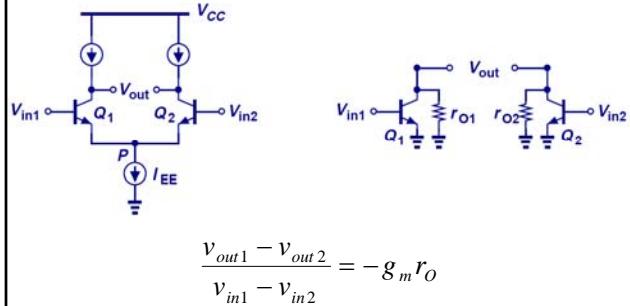


EE105 Spring 2008

Lecture 22, Slide 22

Prof. Wu, UC Berkeley

Half Circuit Example 2

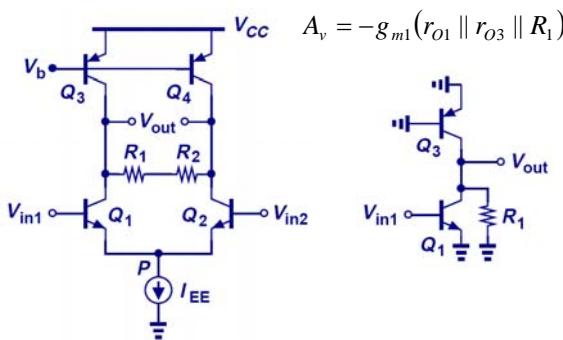


EE105 Spring 2008

Lecture 22, Slide 23

Prof. Wu, UC Berkeley

Half Circuit Example 3

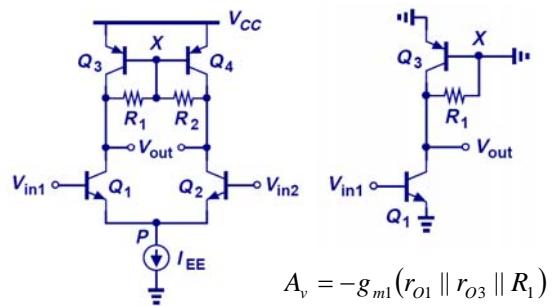


EE105 Spring 2008

Lecture 22, Slide 24

Prof. Wu, UC Berkeley

Half Circuit Example 4

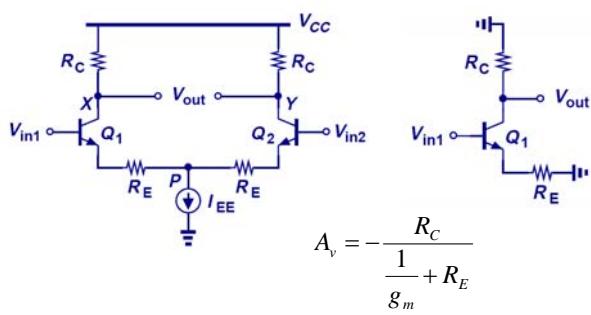


EE105 Spring 2008

Lecture 22, Slide 25

Prof. Wu, UC Berkeley

Differential Pair Frequency Response

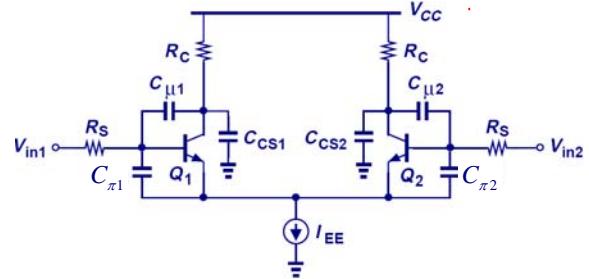- Since the differential pair can be analyzed using its half circuit, its transfer function, I/O impedances, locations of poles/zeros are the same as that of its half circuit.



EE105 Spring 2008

Lecture 22, Slide 26

Prof. Wu, UC Berkeley