

## Lecture 23

---

OUTLINE

- BJT Differential Amplifiers (cont'd)
  - Cascode differential amplifiers
  - Common-mode rejection
  - Differential pair with active load
- Reading: Chapter 10.4-10.6.1

EE105 Spring 2008      Lecture 23, Slide 1      Prof. Wu, UC Berkeley

## Cascode Differential Pair

---

$$R_{out} = [1 + g_{m3}(r_{O1} \parallel r_{\pi3})]r_{O3} + r_{O1} \parallel r_{\pi3}$$

$$R_{out} \cong g_{m3}(r_{O1} \parallel r_{\pi3})r_{O3} + r_{O1} \parallel r_{\pi3}$$

**Half circuit for ac analysis**

$$A_v = -g_{m1}R_{out} \cong -g_{m1}[g_{m3}(r_{O1} \parallel r_{\pi3})r_{O3} + r_{O1} \parallel r_{\pi3}]$$

EE105 Spring 2008      Lecture 23, Slide 2      Prof. Wu, UC Berkeley

## Telescopic Cascode Differential Pair

---

**Half circuit for ac analysis**

$$A_v \approx -g_{m1}[g_{m3}r_{O3}(r_{O1} \parallel r_{\pi3})] \parallel [g_{m5}r_{O5}(r_{O7} \parallel r_{\pi5})]$$

EE105 Spring 2008      Lecture 23, Slide 3      Prof. Wu, UC Berkeley

## Example

---

$$R_{op} = \left[ 1 + g_{m5} \left( r_{O7} \parallel r_{\pi5} \parallel \frac{R_1}{2} \right) \right] r_{O5} + r_{O7} \parallel r_{\pi5} \parallel \frac{R_1}{2}$$

$$A_v = -g_{m1} \left[ [g_{m3}r_{O3}(r_{O1} \parallel r_{\pi3})] \parallel R_{op} \right]$$

**Half circuit for ac analysis**

EE105 Spring 2008      Lecture 23, Slide 4      Prof. Wu, UC Berkeley

## Effect of Finite Tail Impedance

---

- If the tail current source is not ideal, then when an input common-mode voltage is applied, the currents in  $Q_1$  and  $Q_2$  and hence the output common-mode voltage will change.

$$\frac{\Delta V_{out,CM}}{\Delta V_{in,CM}} = \frac{(R_C/2)}{\frac{1}{2g_m} + R_{EE}} = \frac{R_C}{g_m + 2R_{EE}} \leftarrow \text{Common-mode gain should be small}$$

EE105 Spring 2008      Lecture 23, Slide 5      Prof. Wu, UC Berkeley

## Effect of Input CM Noise Ideal Tail Current

---

- There is no effect of the input CM noise at the output.

EE105 Spring 2008      Lecture 23, Slide 6      Prof. Wu, UC Berkeley

### Effect of Input CM Noise

#### Non-Ideal Tail Current

- The single-ended outputs are corrupted by the input CM noise.

$$I_{TAIL} = I_{EE} + \frac{V_P}{R_{EE}}$$

• Tail current,  $I_{TAIL}$ , now changes with  $V_P$  and  $V_P$  is affected by  $V_{CM}$

EE105 Spring 2008      Lecture 23, Slide 7      Prof. Wu, UC Berkeley

### Comparison

Ideal Tail Current	Non-Ideal Tail Current

- The differential output voltage signal is the same for both cases.
- For small input CM noise, the differential pair is not affected.

EE105 Spring 2008      Lecture 23, Slide 8      Prof. Wu, UC Berkeley

### CM to DM Conversion; gain $A_{CM-DM}$

- If finite tail impedance and asymmetry (e.g. in load resistance) are both present, then the differential output signal will contain a portion of the input common-mode signal.

$$\Delta V_{CM} = \Delta V_{BE} + 2\Delta I_C R_{EE} = \frac{\Delta I_C}{g_m} + 2\Delta I_C R_{EE}$$

$$\Rightarrow \Delta I_C = \frac{\Delta V_{CM}}{\frac{1}{g_m} + 2R_{EE}}$$

$$\Delta V_{out1} = -\Delta I_C R_C$$

$$\Delta V_{out2} = -\Delta I_C (R_C + \Delta R_C)$$

$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta I_C \Delta R_C$$

$$\frac{\Delta V_{out}}{\Delta V_{CM}} = \frac{\Delta R_C}{(1/g_m) + 2R_{EE}}$$

EE105 Spring 2008      Lecture 23, Slide 9      Prof. Wu, UC Berkeley

### Example

$$A_{CM-DM} = \frac{\Delta R_C}{\frac{1}{g_m} + 2\{[1 + g_m(R_1 \parallel r_{e3})]R_{O3} + R_1 \parallel r_{e3}\}}$$

EE105 Spring 2008      Lecture 23, Slide 10      Prof. Wu, UC Berkeley

### Common-Mode Rejection Ratio

- CMRR is the ratio of the wanted amplified differential input signal to the unwanted converted input common-mode noise that appears at the output.

$$CMRR \equiv \frac{A_{DM}}{A_{CM-DM}}$$

EE105 Spring 2008      Lecture 23, Slide 11      Prof. Wu, UC Berkeley

### Differential to Single-Ended Conversion


- Many circuits require a differential to single-ended conversion.

- This topology is not very good; its most critical drawback is supply noise corruption, since no common-mode cancellation mechanism exists. Also, we lose half of the voltage signal.

EE105 Spring 2008      Lecture 23, Slide 12      Prof. Wu, UC Berkeley
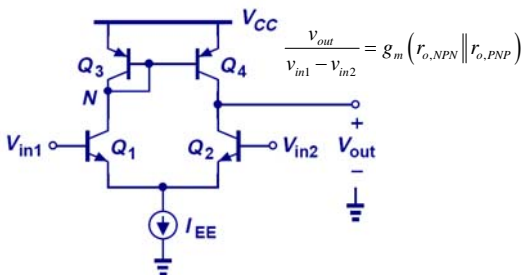
### ... A Better Alternative

- This circuit topology performs differential to single-ended conversion with no loss of gain.




$$\frac{v_{out}}{v_{in1} - v_{in2}} = g_m (r_{o,NPN} \parallel r_{o,PNP})$$

EE105 Spring 2008      Lecture 23, Slide 13      Prof. Wu, UC Berkeley
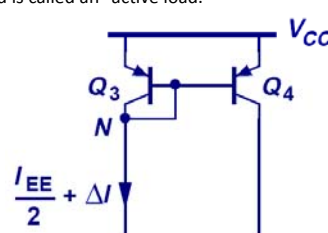
### Active Load

- With a current mirror as the load, the signal current produced by  $Q_1$  can be replicated onto  $Q_4$ .
- This type of load is different from the conventional "static load" and is called an "active load."




$$\frac{I_{EE}}{2} + \Delta I$$

EE105 Spring 2008      Lecture 23, Slide 14      Prof. Wu, UC Berkeley
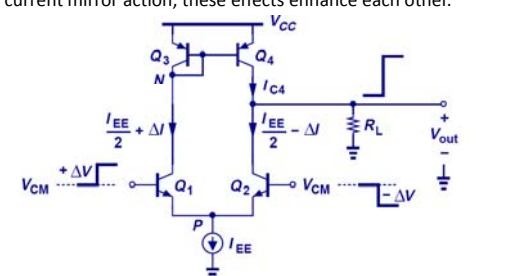
### Differential Pair with Active Load


- The input differential pair decreases the current drawn from  $R_L$  by  $\Delta I$ , and the active load pushes an extra  $\Delta I$  into  $R_L$  by current mirror action; these effects enhance each other.



EE105 Spring 2008      Lecture 23, Slide 15      Prof. Wu, UC Berkeley
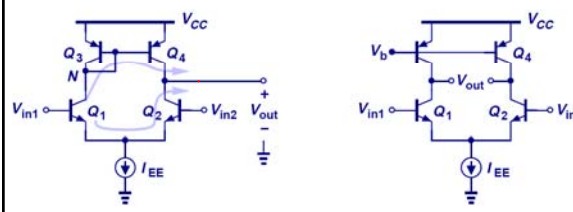
### Active Load vs. Static Load

- The load in the circuit on the left responds to the input signal and enhances the single-ended output, whereas the load in the circuit on the right does not.



EE105 Spring 2008      Lecture 23, Slide 16      Prof. Wu, UC Berkeley