

Lecture 24

OUTLINE

- MOSFET Differential Amplifiers
- Reading: Chapter 10.3-10.6


EE105 Spring 2008

Lecture 24, Slide 1

Prof. Wu, UC Berkeley

Common-Mode (CM) Response

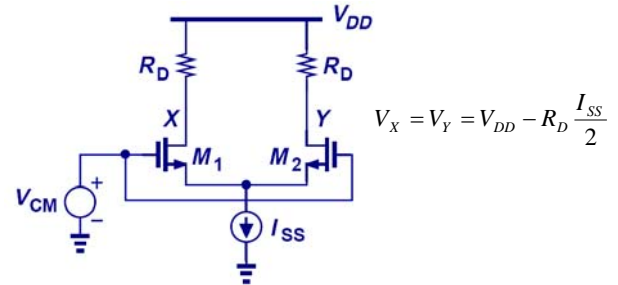- Similarly to its BJT counterpart, a MOSFET differential pair produces zero differential output




EE105 Spring 2008

Lecture 24, Slide 2

Prof. Wu, UC Berkeley

Equilibrium Overdrive Voltage

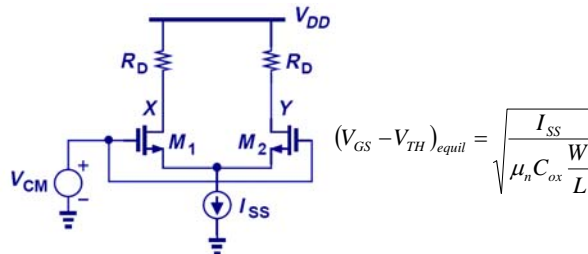- The **equilibrium overdrive voltage** is defined as $V_{GS} - V_{TH}$ when M_1 and M_2 each carry a current of $I_{SS}/2$.




EE105 Spring 2008

Lecture 24, Slide 3

Prof. Wu, UC Berkeley

Minimum CM Output Voltage

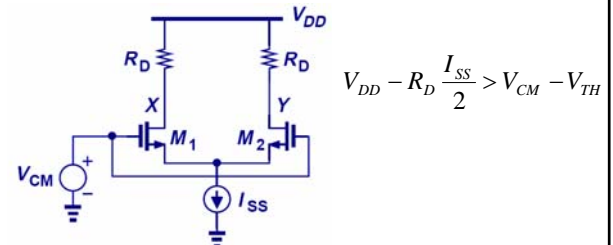- In order to maintain M_1 and M_2 in saturation, the common-mode output voltage cannot fall below $V_{CM} - V_{TH}$.
- This value usually limits voltage gain.




EE105 Spring 2008

Lecture 24, Slide 4

Prof. Wu, UC Berkeley

Differential Response

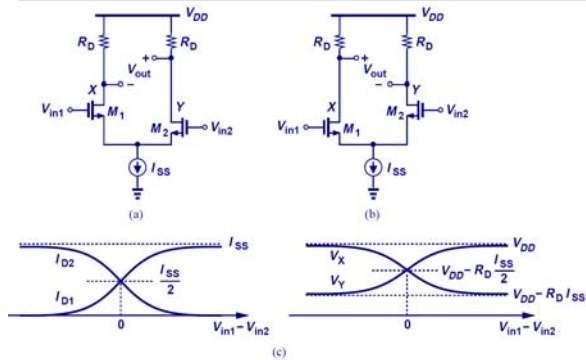


EE105 Spring 2008

Lecture 24, Slide 5

Prof. Wu, UC Berkeley

Small-Signal Response

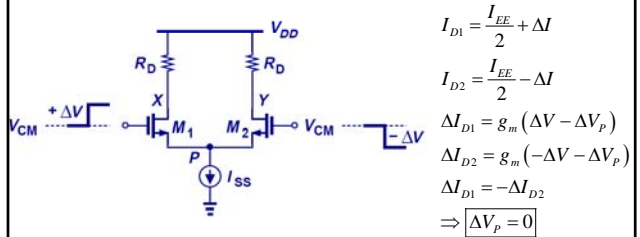- For small input voltages ($+\Delta V$ and $-\Delta V$), the g_m values are \sim equal, so the increase in I_{D1} and decrease in I_{D2} are \sim equal in magnitude. Thus, the voltage at node P is constant and can be considered as AC ground.




EE105 Spring 2008

Lecture 24, Slide 6

Prof. Wu, UC Berkeley

Small-Signal Differential Gain

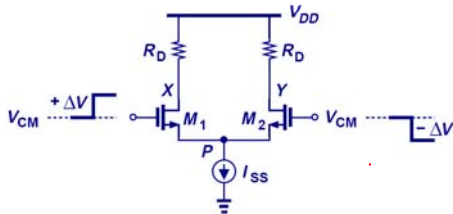- Since the output signal changes by $-2g_m \Delta V R_D$ when the input signal changes by $2\Delta V$, the small-signal voltage gain is $-g_m R_D$.
- Note that the voltage gain is the same as for a CS stage, but that the power dissipation is doubled.




EE105 Spring 2008

Lecture 24, Slide 7

Prof. Wu, UC Berkeley

Large-Signal Analysis

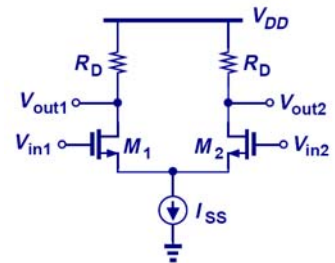

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$


EE105 Spring 2008

Lecture 24, Slide 8

Prof. Wu, UC Berkeley

Maximum Differential Input Voltage

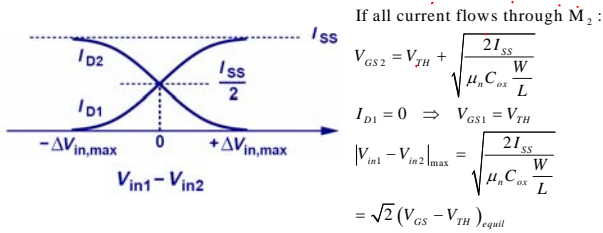- There exists a finite differential input voltage that completely steers the tail current from one transistor to the other. This value is known as the **maximum differential input voltage**.




EE105 Spring 2008

Lecture 24, Slide 9

Prof. Wu, UC Berkeley

MOSFET vs. BJT Differential Pairs

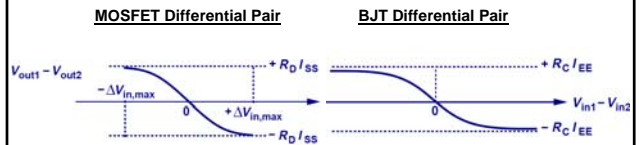- In a MOSFET differential pair, there exists a finite differential input voltage to completely switch the current from one transistor to the other, whereas in a BJT differential pair that voltage is infinite.




EE105 Spring 2008

Lecture 24, Slide 10

Prof. Wu, UC Berkeley

Effect of Doubling the Tail Current

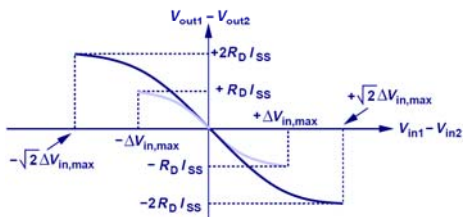- If I_{SS} is doubled, the equilibrium overdrive voltage for each transistor increases by $\sqrt{2}$, thus $\Delta V_{in,max}$ increases by $\sqrt{2}$ as well. Moreover, the differential output swing will double.




EE105 Spring 2008

Lecture 24, Slide 11

Prof. Wu, UC Berkeley

Effect of Doubling W/L

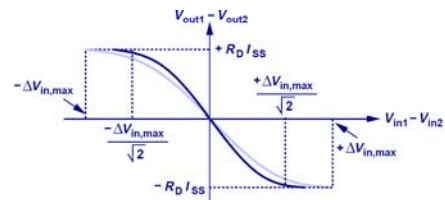- If W/L is doubled, the equilibrium overdrive voltage is lowered by $\sqrt{2}$, thus $\Delta V_{in,max}$ will be lowered by $\sqrt{2}$ as well. The differential output swing will be unchanged.



EE105 Spring 2008

Lecture 24, Slide 12

Prof. Wu, UC Berkeley

Small-Signal Analysis


- When the input differential signal is small compared to $4I_{SS}/\mu_n C_{ox}(W/L)$, the output differential current is ~ linearly proportional to it:

$$I_{D1} - I_{D2} \approx \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\mu_n C_{ox} \frac{W}{L}} I_{SS} (V_{in1} - V_{in2})$$

- We can use the small-signal model to prove that the change in tail node voltage (v_p) is zero:

$$V_{in1} = -V_{in2} \Rightarrow v_1 + v_p = -(v_2 + v_p) \Rightarrow v_1 = -v_2$$
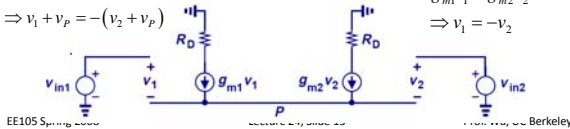
$$g_{m1}v_1 + g_{m2}v_2 = 0 \Rightarrow v_1 = -v_2$$




EE105 Spring 2008

Lecture 24, Slide 13

Prof. Wu, UC Berkeley

Virtual Ground and Half Circuit

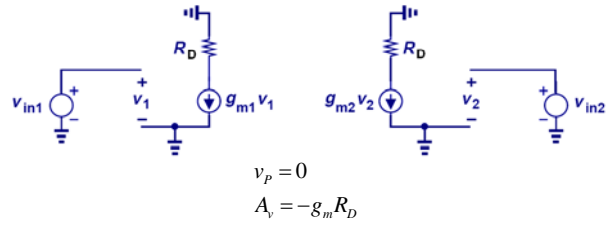- Since the voltage at node P does not change for small input signals, the half circuit can be used to calculate the voltage gain.



$$v_p = 0$$

$$A_v = -g_m R_D$$


EE105 Spring 2008

Lecture 24, Slide 14

Prof. Wu, UC Berkeley

MOSFET Diff. Pair Frequency Response

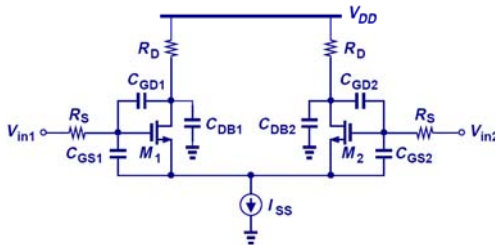- Since the MOSFET differential pair can be analyzed using its half-circuit, its transfer function, I/O impedances, locations of poles/zeros are the same as that of the half circuit's.




EE105 Spring 2008

Lecture 24, Slide 15

Prof. Wu, UC Berkeley

Example

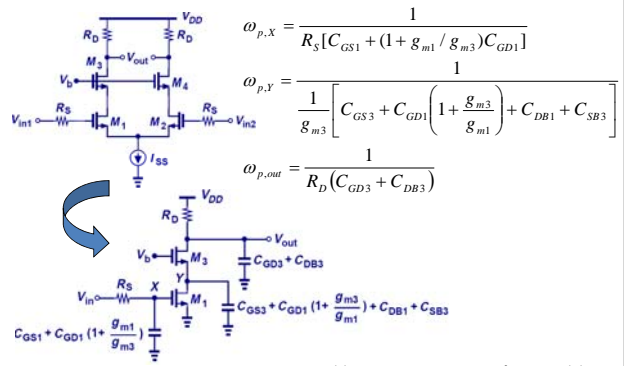

EE105 Spring 2008

Lecture 24, Slide 16

Prof. Wu, UC Berkeley

Half Circuit Example 1

$\lambda \neq 0$ Half circuit for small-signal analysis

$$A_v = -g_{m1} \left(\frac{1}{g_{m3}} \parallel r_{O3} \parallel r_{O1} \right)$$

EE105 Spring 2008 Lecture 24, Slide 17 Prof. Wu, UC Berkeley

Half Circuit Example 2

$\lambda = 0$ Half circuit for small-signal analysis

$$A_v = -\frac{R_{DD}/2}{(1/g_m) + (R_{SS}/2)}$$

EE105 Spring 2008 Lecture 24, Slide 18 Prof. Wu, UC Berkeley

MOSFET Cascode Differential Pair

Half circuit for small-signal analysis

$$A_v \approx -g_{m1} r_{O3} g_{m3} r_{O1}$$

EE105 Spring 2008 Lecture 24, Slide 19 Prof. Wu, UC Berkeley

MOSFET Telescopic Cascode Amplifier

Half circuit for small-signal analysis

$$A_v \approx -g_{m1} \left[(g_{m3} r_{O3} r_{O1}) \parallel (g_{m5} r_{O5} r_{O7}) \right]$$

EE105 Spring 2008 Lecture 24, Slide 20 Prof. Wu, UC Berkeley

CM to DM Conversion Gain, A_{CM-DM}

- If finite tail impedance and asymmetry are both present, then the differential output signal will contain a portion of the input common-mode signal.

$$\Delta V_{CM} = \Delta V_{GS} + 2\Delta I_D R_{SS} = \frac{\Delta I_D}{g_m} + 2\Delta I_D R_{SS}$$

$$\Rightarrow \Delta I_D = \frac{\Delta V_{out}}{\frac{1}{g_m} + 2R_{SS}}$$

$$\Delta V_{out1} = -\Delta I_D R_D$$

$$\Delta V_{out2} = -\Delta I_D (R_D + \Delta R_D)$$

$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta I_D \Delta R_D$$

$\frac{\Delta V_{out}}{\Delta V_{CM}}$	$= \frac{\Delta R_D}{(1/g_m) + 2R_{SS}}$
--	--


EE105 Spring 2008

Lecture 24, Slide 21

Prof. Wu, UC Berkeley

MOS Diff. Pair with Active Load

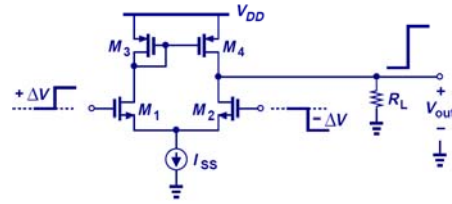- Similarly to its BJT counterpart, a MOSFET differential pair can use an active load to enhance its single-ended output.




EE105 Spring 2008

Lecture 24, Slide 22

Prof. Wu, UC Berkeley

Asymmetric Differential Pair

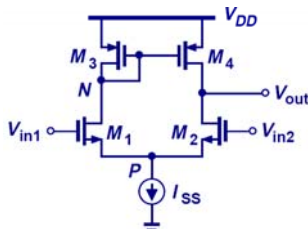- Because of the vast difference in magnitude of the resistances seen at the drains of M_1 and M_2 , the voltage swings at these two nodes are different and therefore node P cannot be viewed as a virtual ground...




EE105 Spring 2008

Lecture 24, Slide 23

Prof. Wu, UC Berkeley

Thevenin Equivalent of the Input Pair

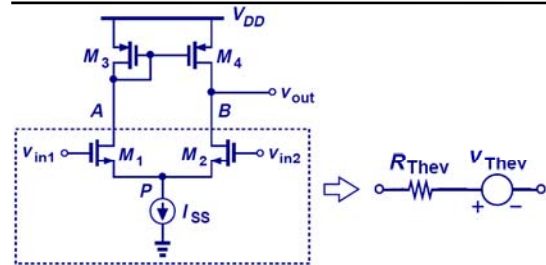

$$v_{Thev} = -g_{mN} r_{oN} (v_{in1} - v_{in2})$$


$$R_{Thev} = 2r_{oN}$$

EE105 Spring 2008

Lecture 24, Slide 24

Prof. Wu, UC Berkeley

Simplified Diff. Pair w/ Active Load

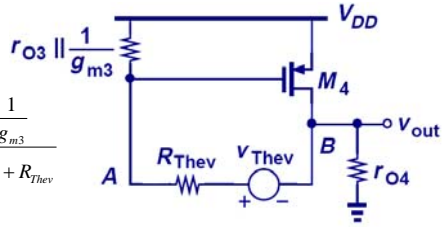

$$v_A = (v_{out} + v_{Thev}) \frac{\frac{1}{g_{m3}}}{\frac{1}{g_{m3}} + R_{Thev}}$$

$$\approx \frac{v_{out} + v_{Thev}}{g_{m3} \cdot 2r_{oN}}$$

$$\text{KCL at } v_{out} : g_{m4}v_A + \frac{v_{out}}{r_{o4}} + \frac{v_{out} + v_{Thev}}{\frac{1}{g_{m3}} + R_{Thev}} = 0 \quad \frac{v_{out}}{v_{in1} - v_{in2}} = g_{mN}(r_{oN} \parallel r_{oP})$$

EE105 Spring 2008

Lecture 24, Slide 25

Prof. Wu, UC Berkeley