

# Lecture 5


---

## OUTLINE

- Bipolar Junction Transistor (BJT) (Cont'd)
  - BJT operation in saturation mode
  - PNP BJT
  - Examples of small signal models


Reading: Chapter 4.5-4.6

# Bipolar Transistor in Saturation

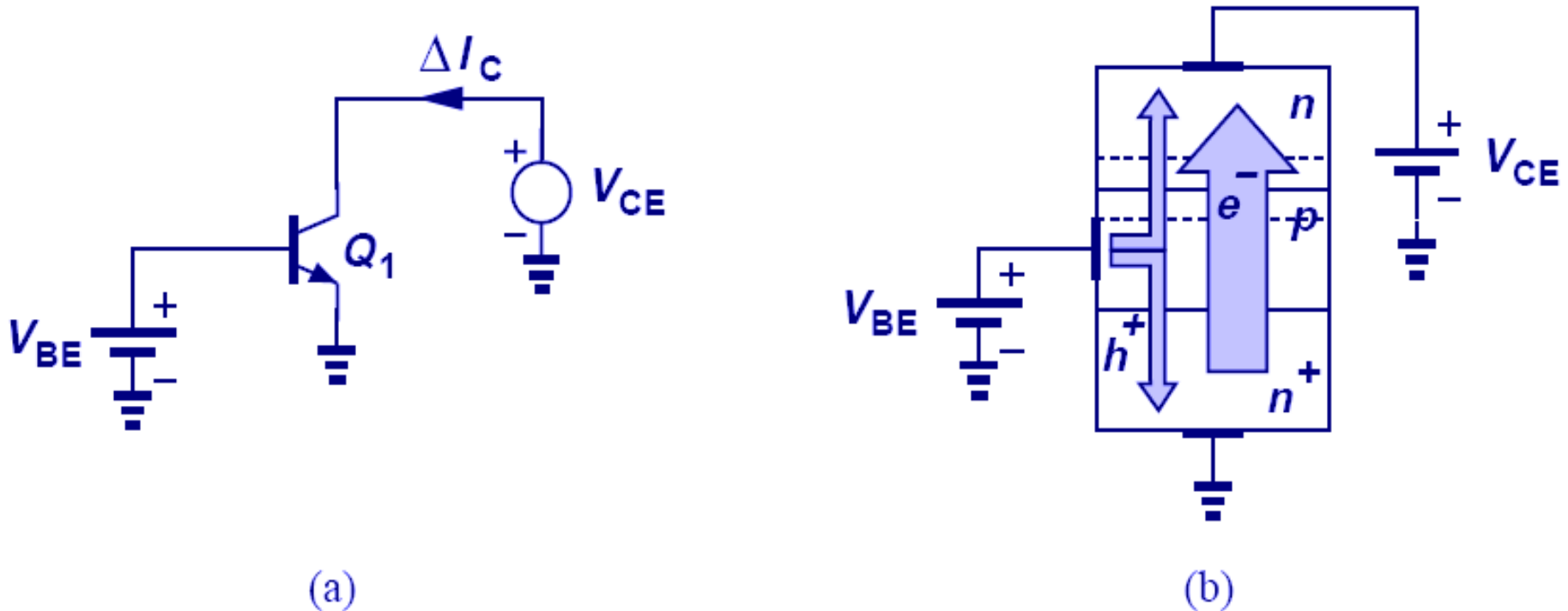


- When collector voltage drops below base voltage and forward biases the collector-base junction, base current increases and the current gain factor,  $\beta$ , decreases.
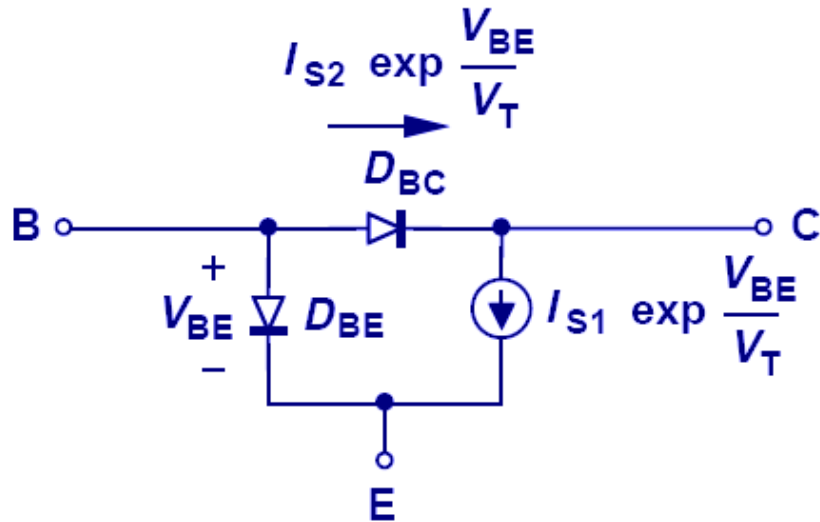
# Large-Signal Model for Saturation Region




(a)

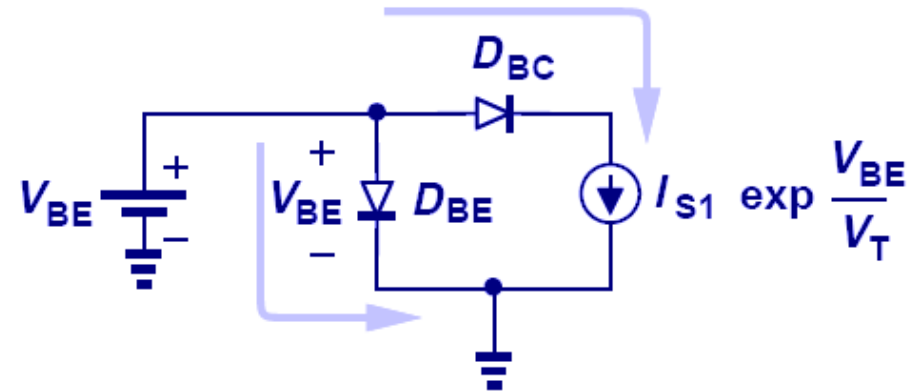

(b)


# Overall I/V Characteristics

---

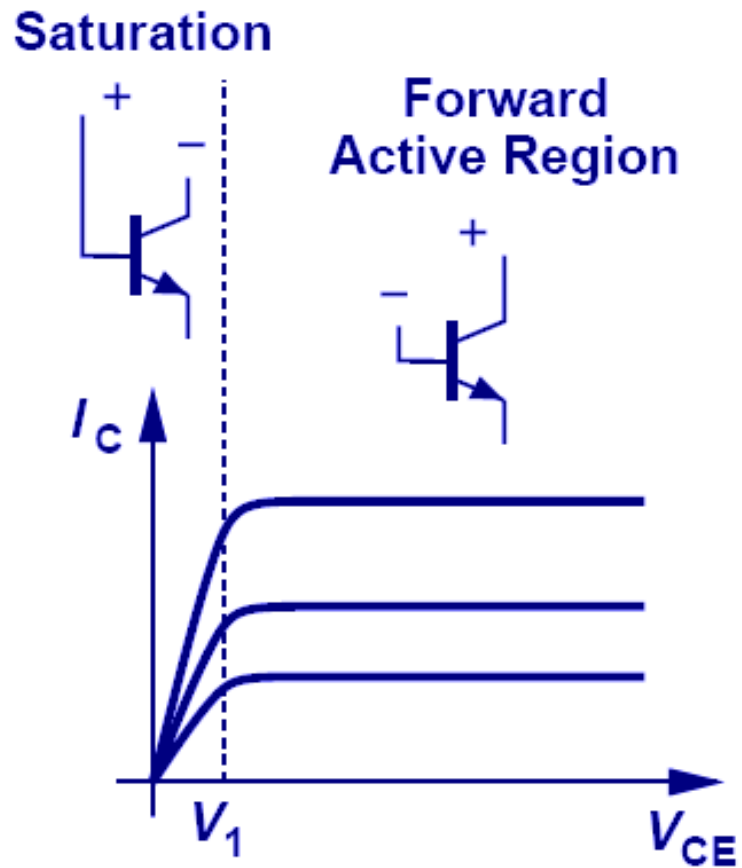

- The speed of the BJT also drops in saturation.

# Example: Acceptable VCC Region

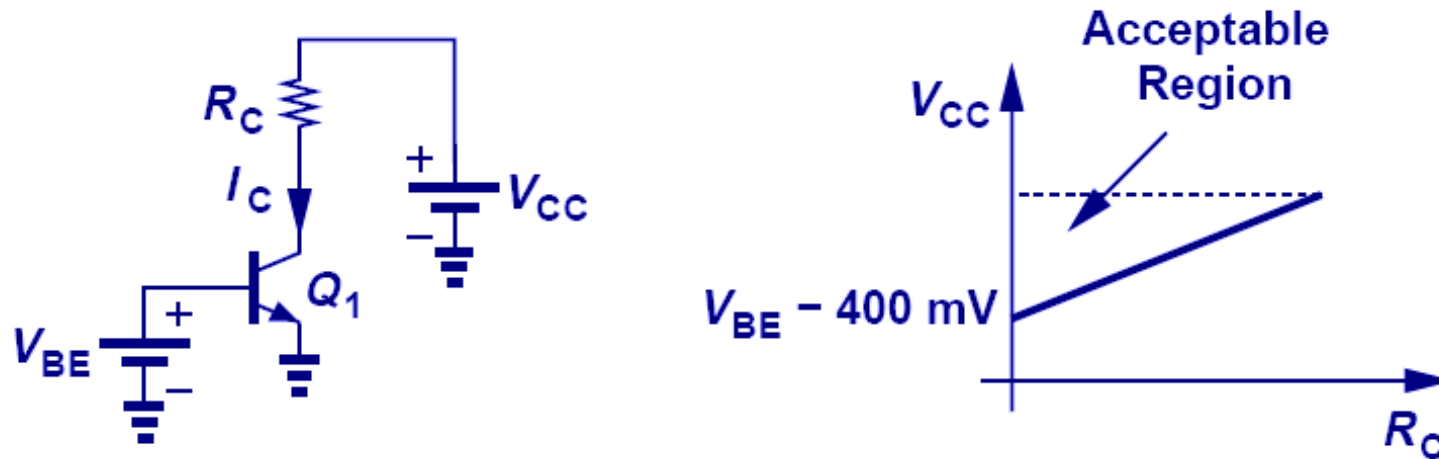


$$V_{CC} \geq I_C R_C + (V_{BE} - 400\text{mV})$$

- In order to keep BJT at least in soft saturation region, the collector voltage must not fall below the base voltage by more than 400mV.
- A linear relationship can be derived for  $V_{CC}$  and  $R_C$  and an acceptable region can be chosen.


# Deep Saturation

---

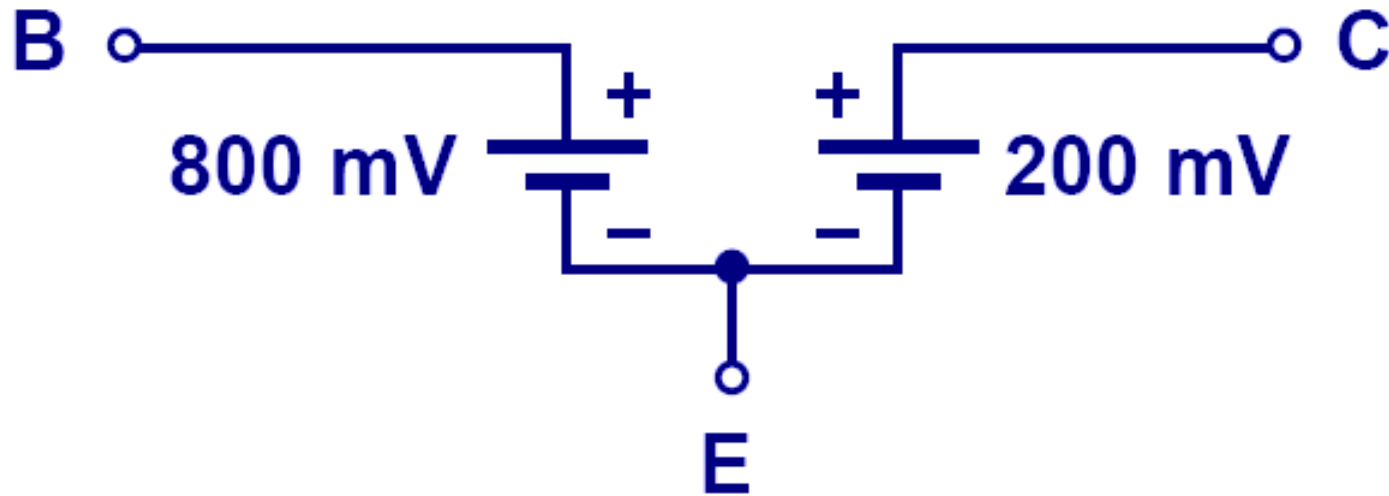


- In deep saturation region, the transistor loses its voltage-controlled current capability and  $V_{CE}$  becomes constant.


# PNP Transistor

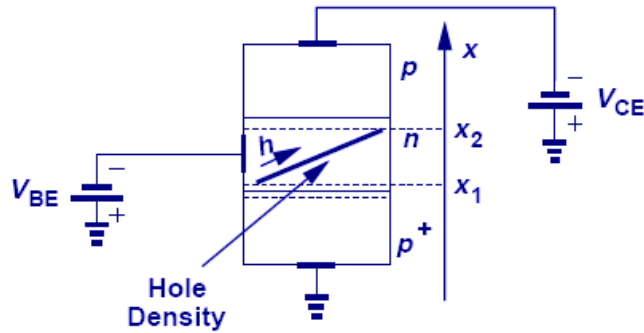


(a)

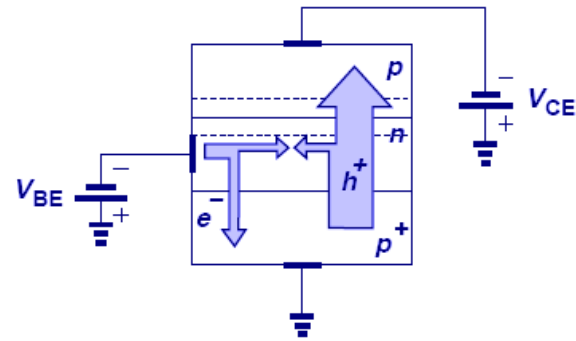

(b)

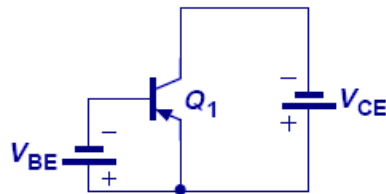


(c)

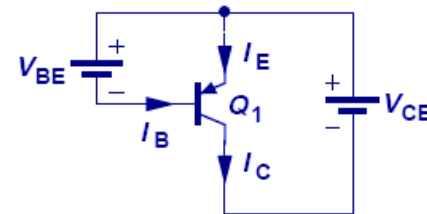

(d)

- With the polarities of emitter, collector, and base reversed, a PNP transistor is formed.
- All the principles that applied to NPN's also apply to PNP's, with the exception that emitter is at a higher potential than base and base at a higher potential than collector.
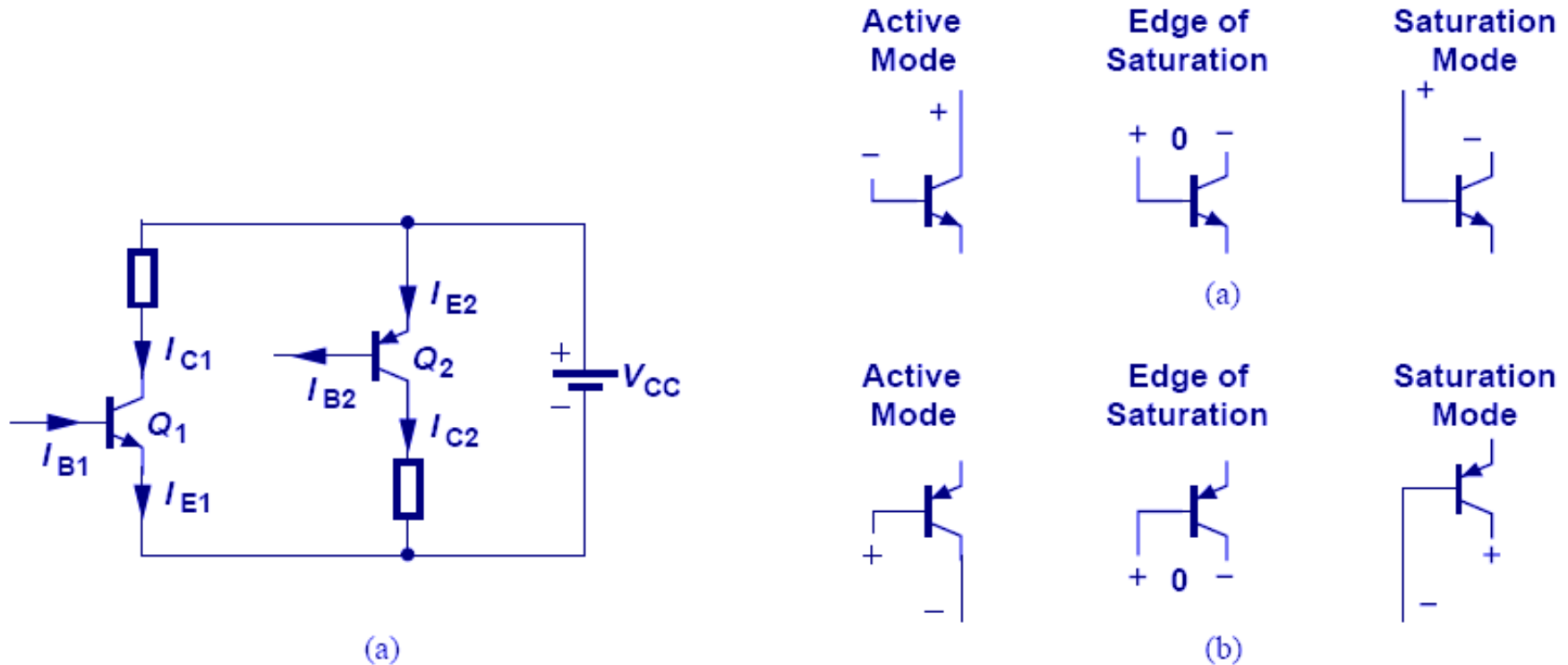
# A Comparison between NPN and PNP Transistors



- The figure above summarizes the direction of current flow and operation regions for both the NPN and PNP BJT's.



# PNP Equations with Early Effect

---

$$I_C = I_S \exp \frac{V_{EB}}{V_T}$$


$$I_B = \frac{I_S}{\beta} \exp \frac{V_{EB}}{V_T}$$

$$I_E = \frac{\beta + 1}{\beta} I_S \exp \frac{V_{EB}}{V_T}$$

$$I_C = \left( I_S \exp \frac{V_{EB}}{V_T} \right) \left( 1 + \frac{V_{EC}}{V_A} \right)$$


# Large Signal Model for PNP

---

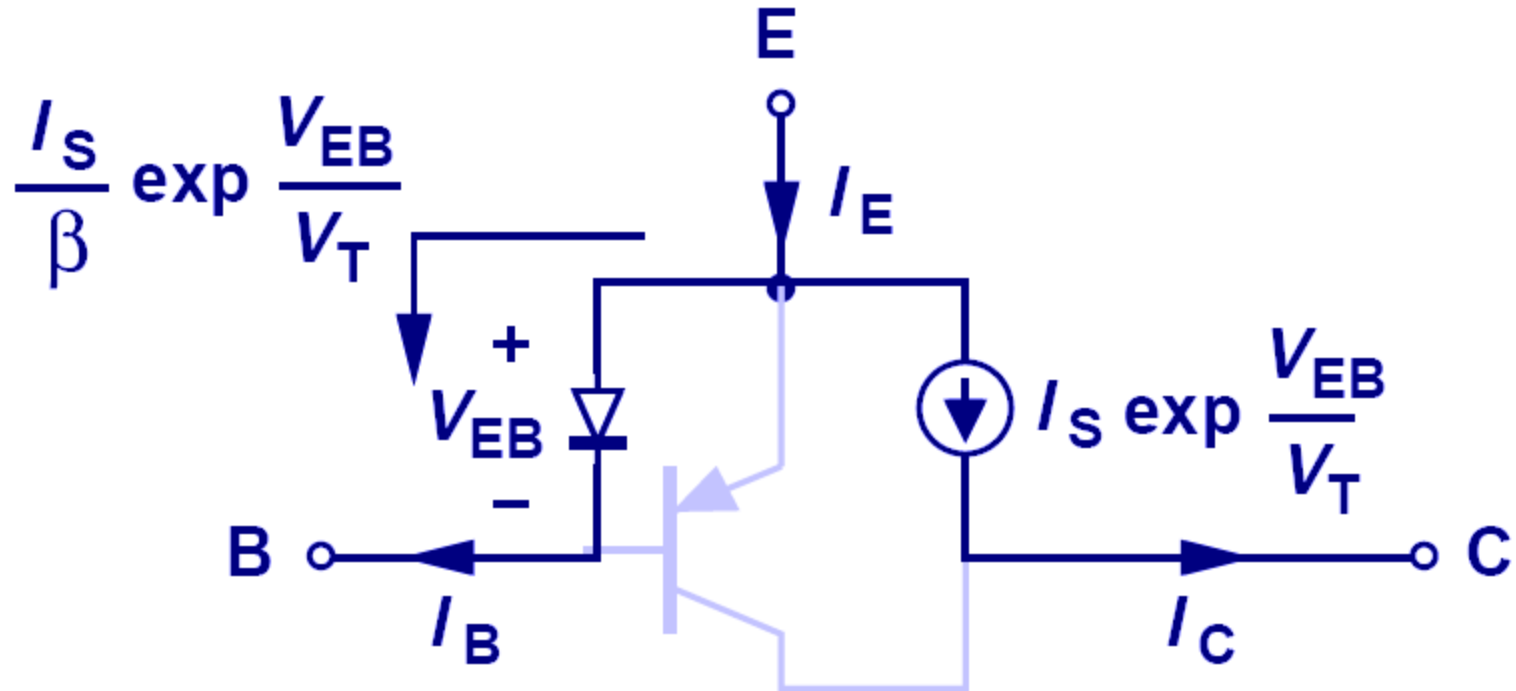

# PNP Biasing


---

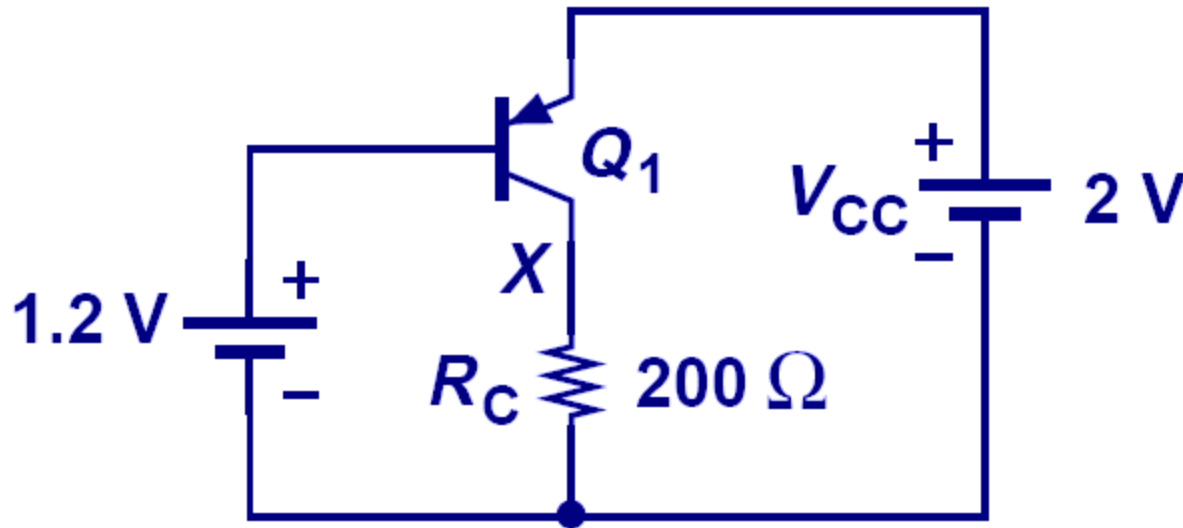



- Note that the emitter is at a higher potential than both the base and collector.

# Small Signal Analysis

---


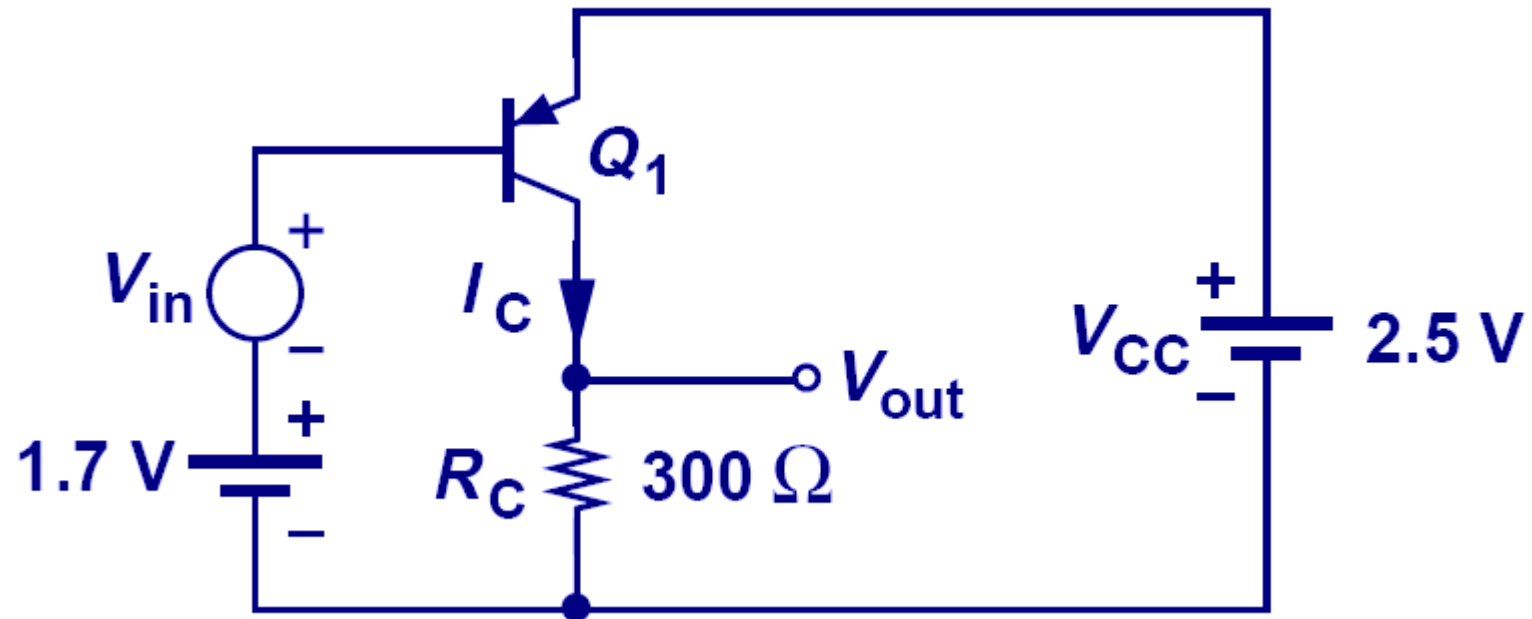


# Small-Signal Model for PNP Transistor

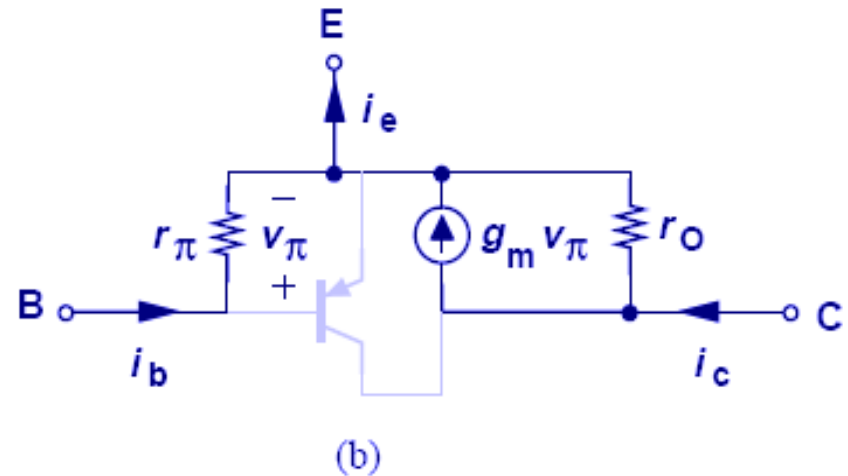
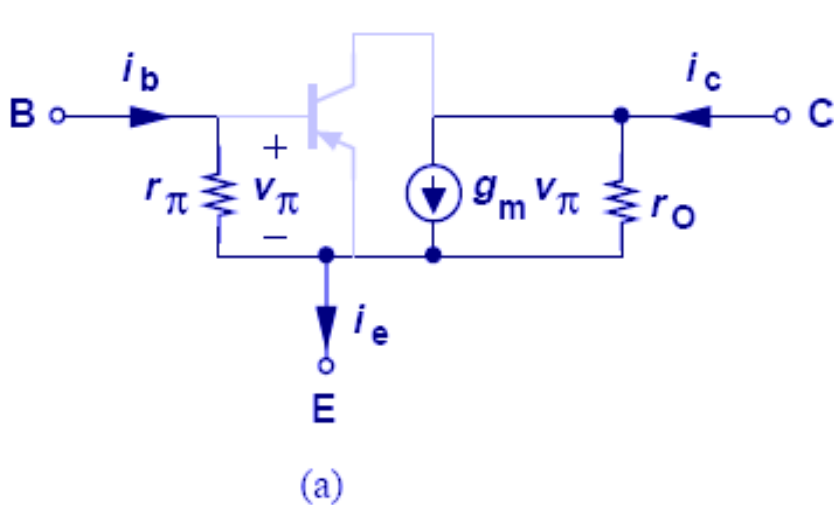


- The small signal model for PNP transistor is exactly IDENTICAL to that of NPN. This is not a mistake because the current direction is taken care of by the polarity of  $V_{BE}$ .

# Small Signal Model Example I

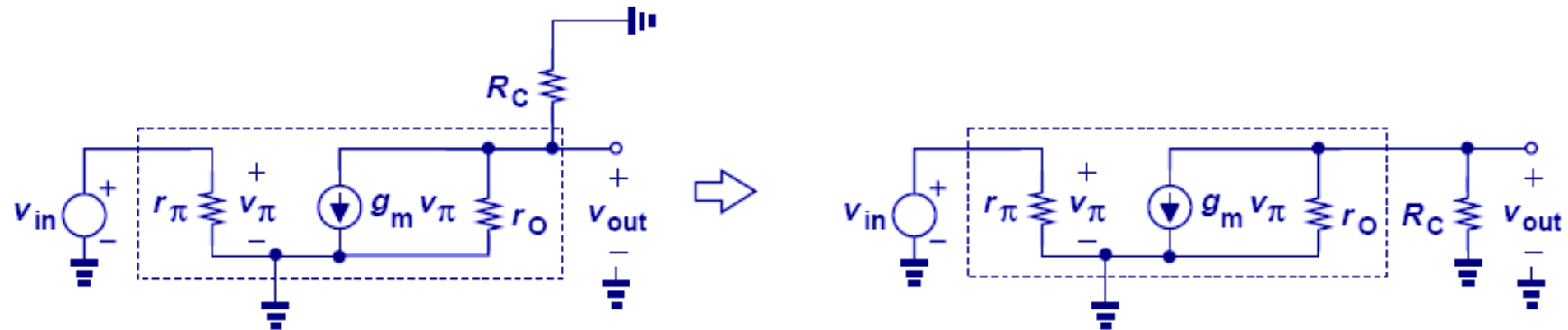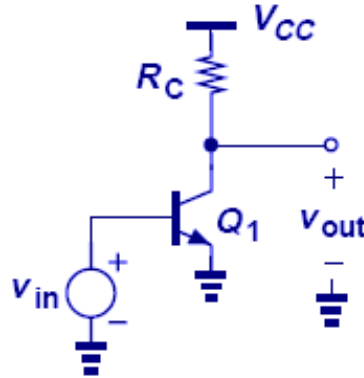


# Small Signal Model Example II

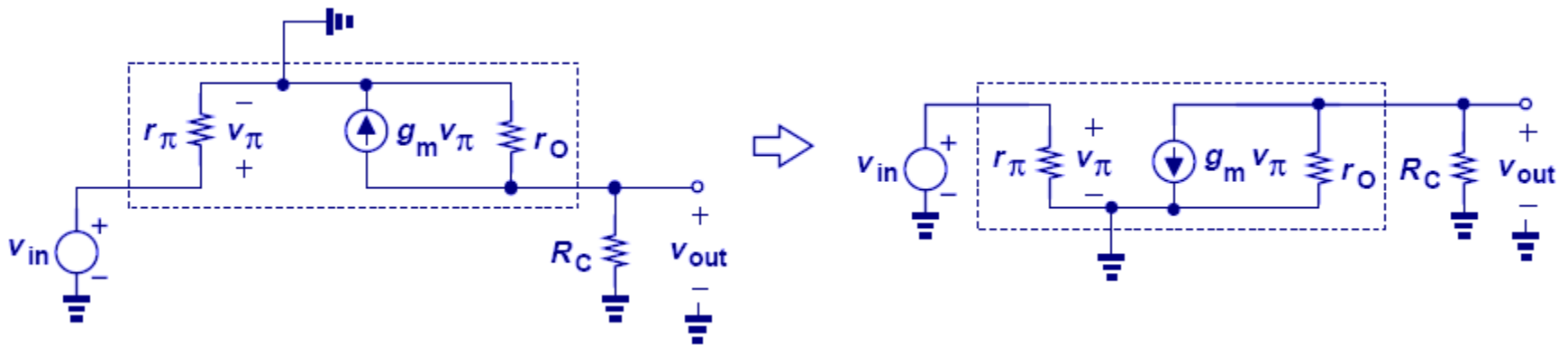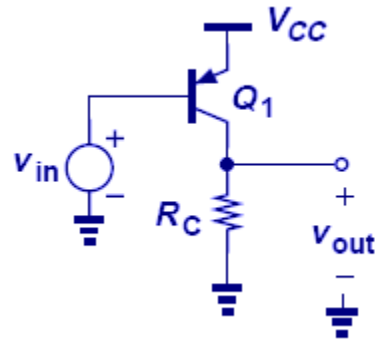

- Small-signal model is identical to the previous ones.



# Small Signal Model Example III

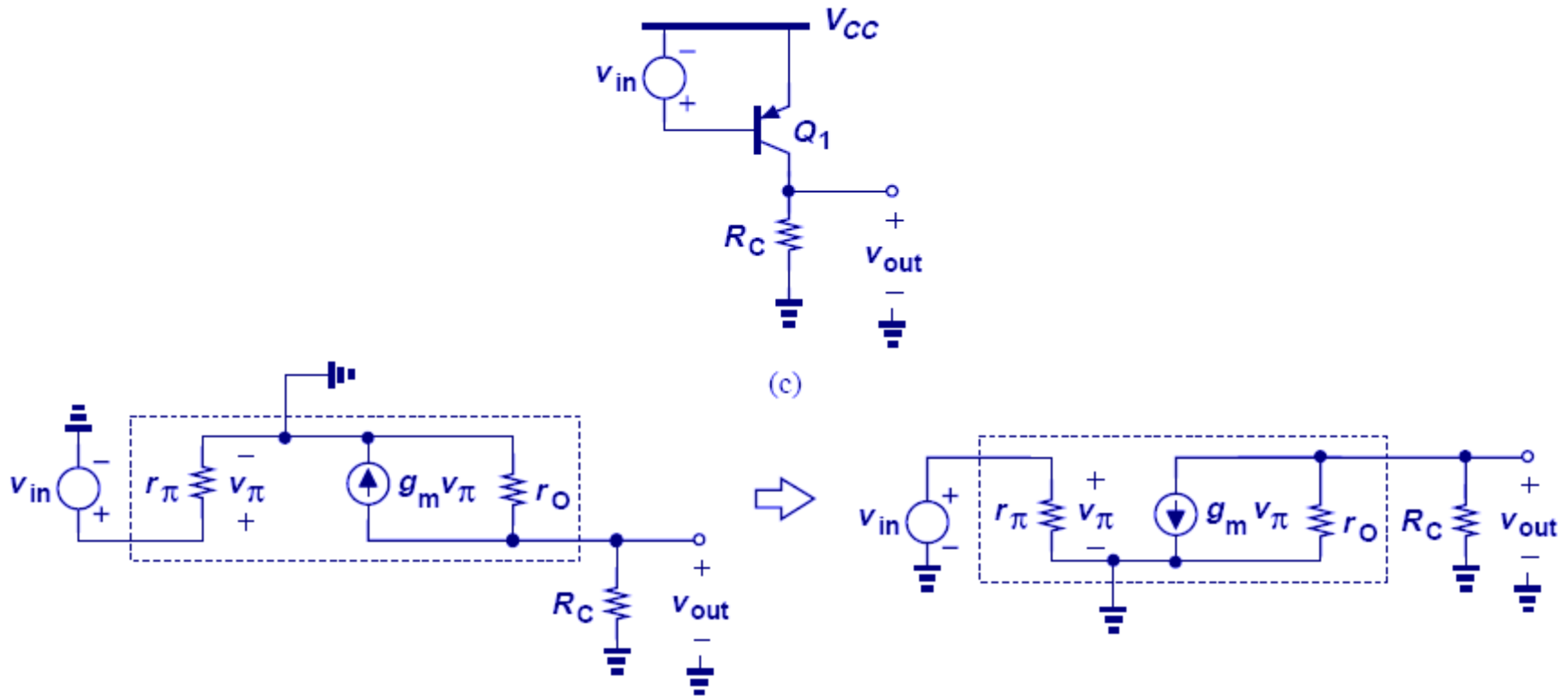

- Since during small-signal analysis, a constant voltage supply is considered to be AC ground, the final small-signal model is identical to the previous two.



# Small Signal Model Example IV

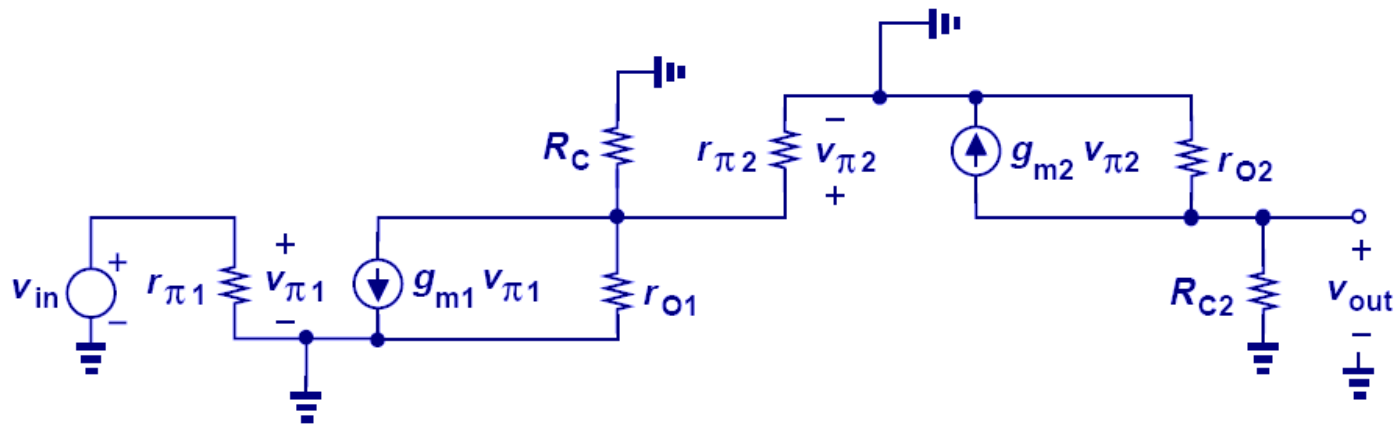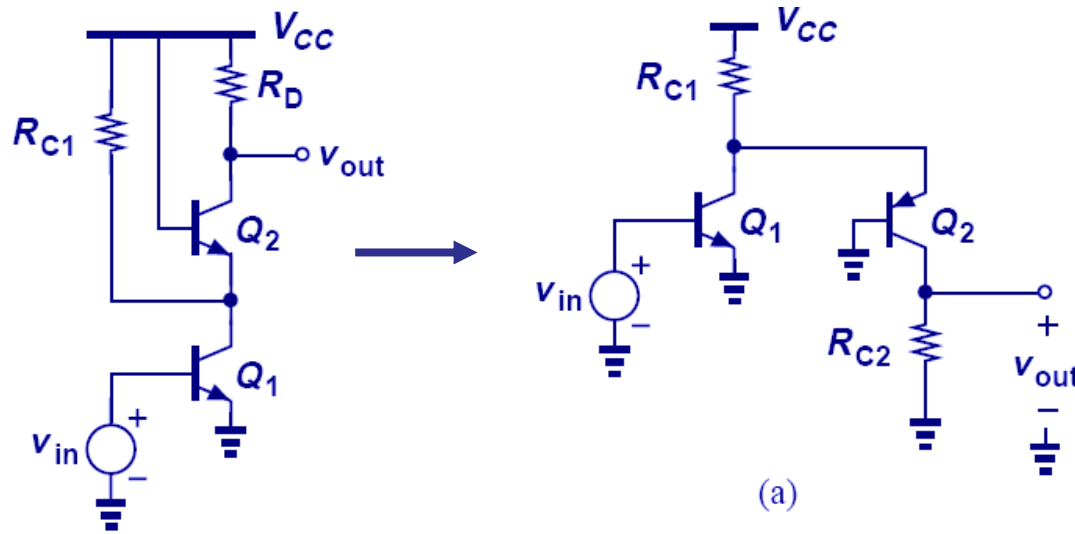

(b)