

## Lecture 8

---

### OUTLINE

- Bipolar Amplifier Topologies (Cont'd)
  - Common-Emitter Amplifiers

Reading: Chapter 5.3.1

EE105 Spring 2008      Lecture 8, Slide 1      Prof. Wu, UC Berkeley

### Output Impedance of Degenerated Stage with Finite $V_A$

---

(a)

$$R_{out} = [1 + g_m (R_E \parallel r_\pi)] r_o + R_E \parallel r_\pi$$

$$R_{out} = r_o + (g_m r_o + 1)(R_E \parallel r_\pi)$$

$$R_{out} \approx r_o [1 + g_m (R_E \parallel r_\pi)]$$

- Emitter degeneration boosts the output impedance by a factor of  $1 + g_m (R_E \parallel r_\pi)$ .
- This improves the gain of the amplifier and makes the circuit a better current source.

EE105 Spring 2008      Lecture 8, Slide 2      Prof. Wu, UC Berkeley

### Two Special Cases

---

- (1)  $R_E \gg r_\pi$   
 $R_{out} \approx r_o (1 + g_m r_\pi) \approx \beta r_o$
- (2)  $R_E \ll r_\pi$   
 $R_{out} \approx (1 + g_m R_E) r_o$

EE105 Spring 2008      Lecture 8, Slide 3      Prof. Wu, UC Berkeley

### Analysis by Inspection

---


$$R_{out} = R_1 \parallel R_{out1} \rightarrow R_{out1} = [1 + g_m (R_2 \parallel r_\pi)] r_o \rightarrow R_{out} = [1 + g_m (R_2 \parallel r_\pi)] r_o \parallel R_1$$

- This seemingly complicated circuit can be greatly simplified by first recognizing that the capacitor creates an AC short to ground, and gradually transforming the circuit to a known topology.

EE105 Spring 2008      Lecture 8, Slide 4      Prof. Wu, UC Berkeley

### Example: Degeneration by Another Transistor

---


$$R_{out} = [1 + g_{m1} (r_{o2} \parallel r_{\pi1})] r_{o1}$$

- Called a “cascode”, the circuit offers many advantages that are described later in the book.

EE105 Spring 2008      Lecture 8, Slide 5      Prof. Wu, UC Berkeley

### Bad Input Connection

---

- Since the microphone has a very low resistance that connects from the base of  $Q_1$  to ground, it attenuates the base voltage and renders  $Q_1$  without a bias current.

EE105 Spring 2008      Lecture 8, Slide 6      Prof. Wu, UC Berkeley

### Use of Coupling Capacitor

---

• Capacitor isolates the bias network from the microphone at DC but shorts the microphone to the amplifier at higher frequencies.

EE105 Spring 2008      Lecture 8, Slide 7      Prof. Wu, UC Berkeley

### DC and AC Analysis

---


$$A_v = -g_m(R_C \parallel r_o)$$

$$R_{in} = r_\pi \parallel R_B$$

$$R_{out} = R_C \parallel r_o$$

• Coupling capacitor is open for DC calculations and shorted for AC calculations.

EE105 Spring 2008      Lecture 8, Slide 8      Prof. Wu, UC Berkeley

### Bad Output Connection

---

• Since the speaker has an inductor, connecting it directly to the amplifier would short the collector at DC and therefore push the transistor into deep saturation.

EE105 Spring 2008      Lecture 8, Slide 9      Prof. Wu, UC Berkeley

### Still No Gain!!!

---

• In this example, the AC coupling indeed allows correct biasing. However, due to the speaker's small input impedance, the overall gain drops considerably.

EE105 Spring 2008      Lecture 8, Slide 10      Prof. Wu, UC Berkeley

### CE Stage with Biasing

---


$$A_v = -g_m(R_C \parallel r_o)$$

$$R_{in} = r_\pi \parallel R_1 \parallel R_2$$

$$R_{out} = R_C \parallel r_o$$

EE105 Spring 2008      Lecture 8, Slide 11      Prof. Wu, UC Berkeley

### CE Stage with Robust Biasing

---

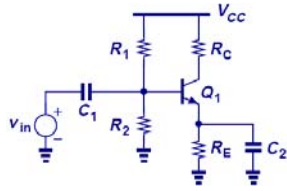

$$A_v = \frac{-R_C}{\frac{1}{g_m} + R_E}$$

$$R_{in} = [r_\pi + (\beta + 1)R_E] \parallel R_1 \parallel R_2$$

$$R_{out} = R_C$$

EE105 Spring 2008      Lecture 8, Slide 12      Prof. Wu, UC Berkeley

### Removal of Degeneration for Signals at AC



$$A_v = -g_m R_C$$

$$R_{in} = r_\pi \parallel R_1 \parallel R_2$$

$$R_{out} = R_C$$


- Capacitor shorts out RE at higher frequencies and removes degeneration.

EE105 Spring 2008

Lecture 8, Slide 13

Prof. Wu, UC Berkeley

### Complete CE Stage

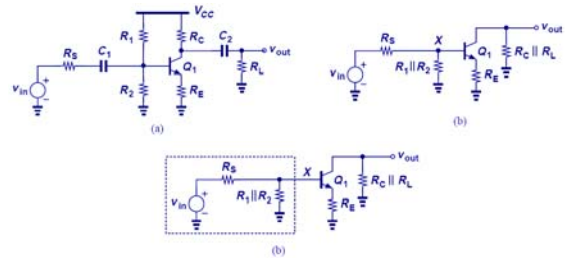


$$A_v = \frac{-R_C \parallel R_L}{\frac{1}{g_m} + R_E + \frac{R_s \parallel R_1 \parallel R_2}{\beta + 1}}$$

EE105 Spring 2008

Lecture 8, Slide 14

Prof. Wu, UC Berkeley

### Summary of CE Concepts

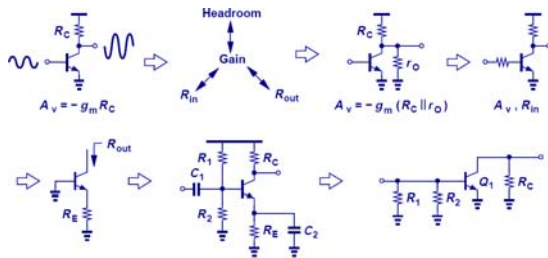

EE105 Spring 2008

Lecture 8, Slide 15

Prof. Wu, UC Berkeley