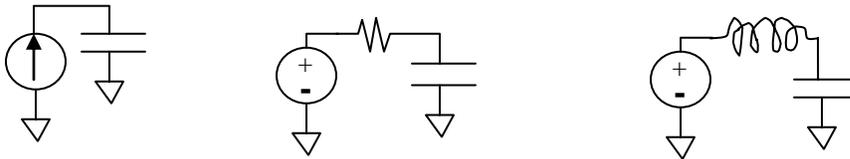


Homework Assignment #4

Due in the 105 box on the 2nd floor of Cory, 5pm Friday 2/11/2010

Problem 1: On a single graph on a piece of graph paper, draw a linear voltage axis from 0 to 2V, and a linear time axis from 0 to 3ns and plot the time response of the following circuits:



- a 1mA step function current source feeding a 1pF capacitor.
- a 1k Ω resistor hooked to a 1V step function supply on one side, and a 1pF capacitor on the other.
- a 1 μ H inductor (I'm not so good at drawing inductors) from a 1V step function supply feeding a 1pF capacitor.

Problem 2: Consider an NPN transistor with $I_S=10$ fA and a β of 100.

- If the device is biased in the forward active region at room temperature, ignore the Early effect and calculate the base-emitter voltage required to get a collector current of 1 μ A. Don't use a calculator! What is the base current that corresponds to this bias point?
- If V_A for this transistor is 50V, approximately what is the worst-case error in your calculations if this transistor is operating in a circuit powered by two AA alkaline batteries? (hint: alkaline batteries start life at 1.6V, and have useful storage down to around 0.9V)
- Same as part (a), but 100 μ A collector current. Using the formulas derived in class, estimate the small signal input resistance, r_{π} , output resistance, r_o , and transconductance g_m at this bias point. No calculators! Draw the low frequency small signal model, labeling all currents, voltages, and components.
- Assuming $V_A=50$ V, use your calculator to calculate the base and collector currents at the following three bias points: ($V_{BE}= 600$ mV, $V_{CE}= 1$ V), ($V_{BE}= 601$ mV, $V_{CE}= 1$ V), ($V_{BE}= 600$ mV, $V_{CE}= 2$ V) and use only those currents and voltages to make your best estimate of the small signal input resistance, output resistance, and transconductance.
- how do your answers in c) and d) compare? Why?

Problem 3: Draw the low-frequency small-signal model for a bipolar common-emitter amplifier with a resistive load. If $V_{CC} = 11$ V and $R_C=1$ M Ω what is the current necessary to achieve an output bias point of 10V? 1V? What are the small-signal values for g_m and r_o if the output bias point is 10V? 1V? What is the voltage gain, assuming that $V_A \gg V_{CC}$, at an output bias point of 10V? 1V?