

EE105 Lab Experiments

## Experiment 3: Single Stage CE & CS Amplifier Pre-Lab Worksheet

### 1 Pre-Lab

To make the plots more readable and to save on printer toner, change the background color of your plots to white before printing your plot. In WaveView, click *Config* → *Preferences* to change the WaveView program settings. Next, click the *Waveview* tab, and find the *Waveview Background* option and set it to *White*.

#### 1.1 Attenuation Network

Attenuation Ratio  $V_{in}/V_{source}$ : \_\_\_\_\_

Equivalent Impedance  $R_{in}$ : \_\_\_\_\_

Draw Thevenin equivalent model:

#### 1.2 Single Stage CE BJT Amplifier

Explain the function of  $R_e$ :

Small Signal Circuit:

Expression of middle band gain  $A_v$ : \_\_\_\_\_

Expression of output impedance of the amplifier  $R_{out}$ : \_\_\_\_\_

Expression of high cutoff frequency  $f_H$ : \_\_\_\_\_

**Table 1:** Component Design

Component Design	Hand Calculation	Hspice Simulation
$R_{b1}$		
$R_{b2}$		
$R_c$		
$R_e$		

**Table 2:** Performance Verification

Performance	Hand Calculation	Hspice Simulation
Middle Band Gain( $A_{mid}$ )		
High Cutoff Frequency( $f_H$ )		
Output Swing(SW)		
Total Power Consumption( $P_{total}$ )		

Plot Amplifier Gain(in dB20) v.s. Frequency (in log scale)

Plot Input and Output Waveforms showing the Output Swing

### 1.3 Single Stage CS MOSFET Amplifier

Explain the function of  $R_s$ :

Small Signal Circuit:

Expression of middle band gain  $A_v$ : \_\_\_\_\_

Expression of output impedance of the amplifier  $R_{out}$ : \_\_\_\_\_

Expression of high cutoff frequency  $f_H$ : \_\_\_\_\_

**Table 3:** Component Design

Component Design	Hand Calculation	Hspice Simulation
$R_{g1}$		
$R_{g2}$		
$R_d$		
$R_s$		

**Table 4:** Performance Verification

Performance	Hand Calculation	Hspice Simulation
Middle Band Gain( $A_{mid}$ )		
High Cutoff Frequency( $f_H$ )		
Output Swing(SW)		
Total Power Consumption( $P_{total}$ )		

Plot Amplifier Gain(in dB20) v.s. Frequency (in log scale)

Plot Input and Output Waveforms showing the Output Swing