

EE105 Lab Experiments

Lab 6: Differential Amplifier Pre-Lab Worksheet

1 Pre-Lab

1.1 Differential Input Stage

Please draw the equivalent "half circuit" for the differential signals.

Please write down the expression of the differential voltage gain ($A_{dm} = (V_{o1} - V_{o2})/V_{dm}$): _____

Please write down the expression of differential gain high cutoff frequency ($f_{H_{dm}}$): _____

Please write down the expression of maximum differential output swing and express it in terms of DC base voltage V_b :

For hand calculation only:

Resistor load R1 and R2: _____

Tail Current Source I_{bias} : _____

1.2 Widlar Current Source

Please write down the expression that relates I_{ref} , I_{bias} , V_t and R4:

Please write down the expression that relates I_{ref} , V_{be3} , R3, VDD and VSS:

Please write down the output impedance of current mirror (R_{out}):

Please write down the expression of the minimum allowable voltage on the collector of Q4:

According to the I_{bias} from previous section, select proper R3 and R4: _____

Verify the performance of the current source by Hspice simulation:

Design Parameter	Hand Calculation	HSPICE Simulation
I_{bias}		
I_{ref}		
R_{out}		

Table 1: Widlar Current Source Design

1.3 Common Mode Characterization

Please draw the equivalent "half circuit" for common mode signal.

Please write down the expression of the common mode gain with 0.1% load resistor mismatch ($A_{cm} = (V_{o1} - V_{o2})/V_{dm}$): _____

The expression of minimal common input voltage: _____

The expression of maximum common input voltage: _____

1.4 Putting it all together

Now connect the current source and differential pair together and verify its performance in Hspice

Performance	Hand Calculation	HSPICE Simulation
Differential Mode Gain (A_{dm})		
Differential Mode Gain High Cutoff Frequency (f_H)		
Differential Output Swing (SW)		
Common Mode Gain (A_{cm}) with mismatch		
Common Mode rejection Ratio (CMRR) with mismatch		

Table 2: Overall performance verification

Attach the plot of transient waveform of $(V_{o1} - V_{o2})$ v.s. V_{dm} at a frequency below the cutoff frequency.

Attach the plot showing evidence of a 2V differential output swing.

Attach the plot of the frequency response of A_{dm} from 10Hz to 100kHz.

Attach the plot of transient waveform of $(V_{o1} - V_{o2})$ v.s. V_{cm} with 0.1% load resistor mismatch.

Attach the plot of the frequency response of A_{cm} with 0.1% load resistor mismatch from 10Hz to 100kHz.