

UNIVERSITY OF CALIFORNIA, BERKELEY
 College of Engineering
 Department of Electrical Engineering and Computer Sciences

EE 105: Microelectronic Devices and Circuits

Fall 2017

Prof. Ming Wu

MIDTERM EXAMINATION #2

Time allotted: 80 minutes

NAME: _____
 (print) Last First Signature

STUDENT ID#: _____

INSTRUCTIONS:


1. **SHOW YOUR WORK.** (Make your methods clear to the grader!)
2. **Clearly mark (underline or box) your answers.**
3. **Specify the units of your answer to receive full credit.**
4. **Unless stated in the problem, use the values of physical constants provided below.**
5. **You can use approximations within 20% accuracy any time.**
6. **Calculator is allowed. (Cell phone is not allowed).**

**** If you need more space for your answer, use the blank pages in the back. Clearly label which problem is your answer for ****


Commonly used constants and physical parameters:		
Electronic charge	q	1.6×10^{-19} C
Boltzmann's constant	k	8.62×10^{-5} eV/K
Thermal voltage at 300K	$V_T = kT/q$	0.025 V
Relative permittivity of Si	$\epsilon_{r,Si}$	12
Relative permittivity of SiO ₂	$\epsilon_{r,ox}$	4
Vacuum permittivity	ϵ_0	8.854×10^{-14} F/cm

Points	Problem 1	25	
	Problem 2	25	
	Problem 3	25	
	Problem 4	25	
	Total	100	


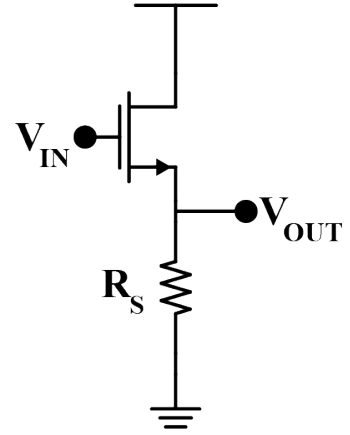
- 1) **Small Signal Response.** Consider the amplifier on the right, with the NMOS transistor operating in saturation.
- Draw the small signal equivalent circuit, indicating very clearly the dependent sources. Include r_0 , the FET drain-to-source resistance. Clearly label the three terminals of the FET.
 - Find the small signal voltage gain (v_{out} / v_{in}) of the amplifier assuming $r_0 = \infty$. Express your answer in terms of the transistor g_m and R_s ONLY.
 - What happens to the voltage gain as $R_s \rightarrow \infty$?



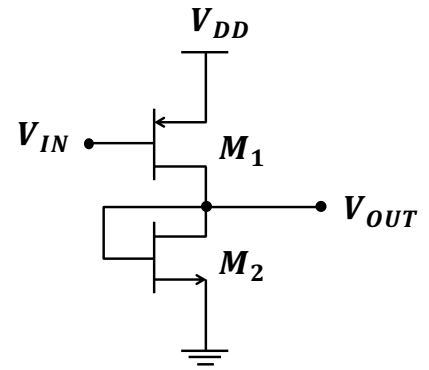
- 2) **Large Signal Response:** Assuming V_{Tp} , V_{Tn} , k_p , k_n are given for the PMOS and NMOS devices in the circuit on the right. The power supply voltage is V_{DD} .
- What are the operating regions for M_2 (Saturation or triode)? Why?
 - Find values of V_{in} such that M_1 is in the saturation region (in terms of the given parameters).
 - What is the DC value of V_{out} (again, in terms of the given parameters)?



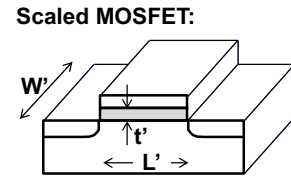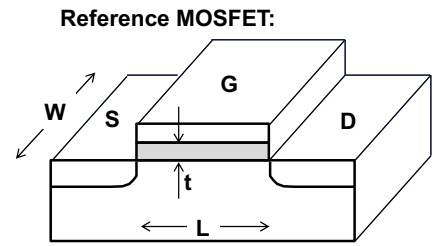- 3) A MOSFET has a channel length L , width W , oxide thickness t , threshold voltage V_t , and power supply voltage V_{DD} . Now consider a modified transistor with
- Channel length scaling:** L are changed by a factor of k (i.e. $L'=kL$). All other parameters remain the same. How do the maximum drain current I_D (at $V_{GS} = V_{DD}$) and transconductance g_m (also at $V_{GS} = V_{DD}$) change? Express your answers in scale factor, k . Show your derivation.
 - Uniform scaling:** W , L , t , V_t and V_{DD} are all changed by a factor of k . How does I_D and g_m change? Show your derivation.



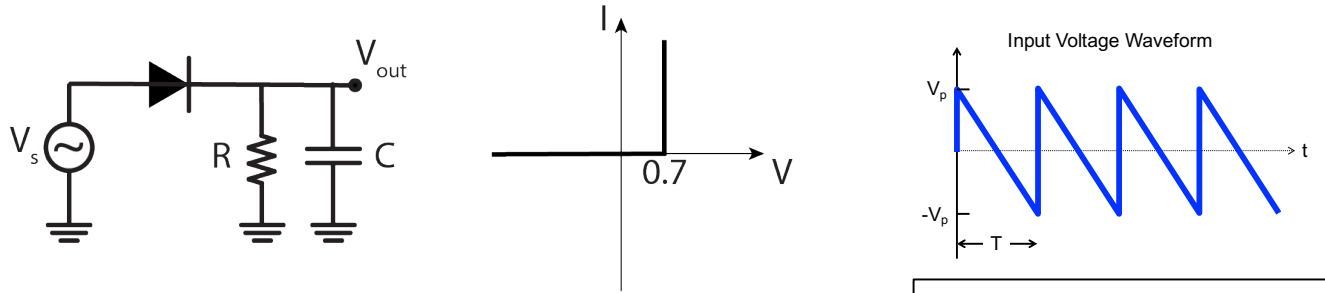- 4) The circuit below is made with an ideal diode with the I-V characteristic given below. The input waveform is shown below. Assume the peak voltage $V_p > 3V$.



- Explain how the circuit works.
- Assume $R = \infty$, draw the output waveform on the right.
- Now consider a finite resistance value R such that $e^{-\frac{T}{RC}} = \frac{1}{2}$, where T is the period of the input waveform. Draw the qualitative output waveform on the right.
- What is the maximum and minimum output voltages in c)? Express your answers in V_p .

