
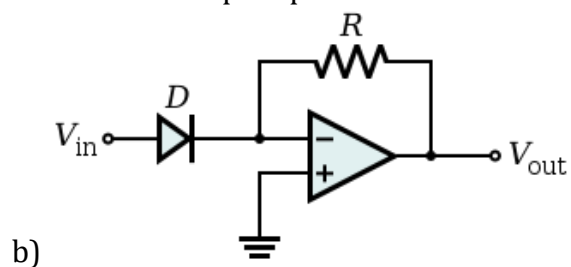


HW#4


(Submit to bCourses by 11 pm on 2/22)

- 1) A semiconductor is doped with As with an exponential profile:
 $N_D(x) = N_0 e^{-\frac{x}{d}}$ for $x > 0$, where $N_0 = 10^{18} \text{ cm}^{-3}$ and $d = 1 \mu\text{m}$.
 - a) Derive the analytical expression of the electrical field in the region $x > 0$.
 - b) Find the magnitude of the electrical field at $x = 1 \mu\text{m}$.
 - c) What is the direction of the electric field?
 - d) What is the direction of drift current? What is the direction of the diffusion current?

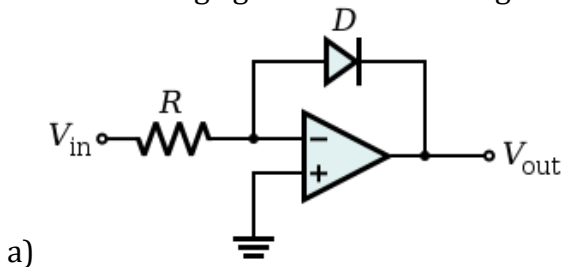- 2) Find the voltage gain of the following circuits. Treat the Op amp as ideal.



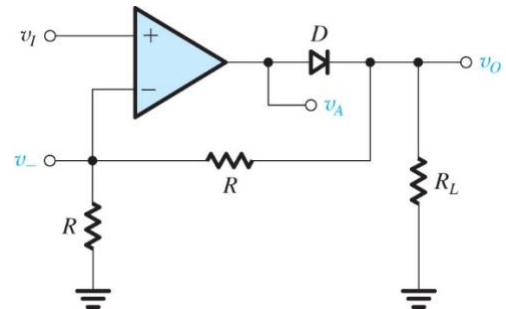- 3) The op amp in the precision rectifier circuit show below is ideal with output saturation levels of +/- 13V. Assume that when the conducting the diode exhibits a constant voltage drop of 0.7V. Find v_- , v_o , and v_A for:



- a) $v_I = +1V$
- b) $v_I = +3V$
- c) $v_I = -1V$
- d) $v_I = -3V$
- e) Find the average output voltage obtained with v_I is a symmetrical square wave of 1kHz frequency, 5V amplitude and zero average.

- 4) For the circuit below, both diodes are identical. Find the value of R for which $V = 50 \text{ mV}$.

