

HW#8

(Submit to bCourses by 11:59 pm on 4/21, Sunday)


- 1) The circuit shown on the right is a common source amplifier with a diode-connected NMOS load, Q_2 . Using $i_{D1} = i_{D2}$, show that for the range of v_I over which Q_1 is operating in saturation, that is, for

$$V_{t1} \leq v_I \leq v_o + V_{t1}$$


the output voltage will be given by

$$v_o = V_{DD} - V_t + \sqrt{\frac{(W/L)_1}{(W/L)_2}} V_t - \sqrt{\frac{(W/L)_1}{(W/L)_2}} v_I$$

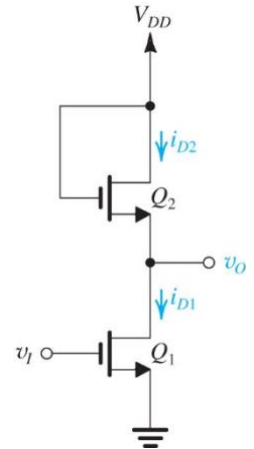
where we have assumed $V_{t1} = V_{t2} = V_t$. Thus the circuit functions as a linear amplifier, even for large input signals. For $(W/L)_1 = (50 \text{ } \mu\text{m} / 0.5 \text{ } \mu\text{m})$, and $(W/L)_2 = (5 \text{ } \mu\text{m} / 0.5 \text{ } \mu\text{m})$, find the voltage gain.



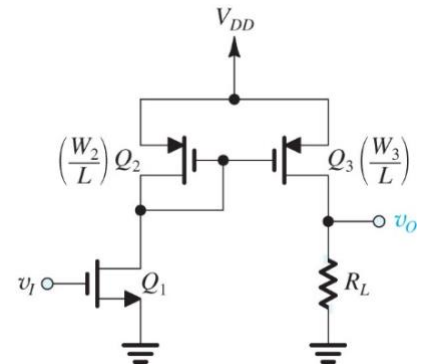- 2) The circuit here is an amplifier using a current mirror Q_2 - Q_3 . Here Q_1 is a common source amplifier fed with $v_I = V_{GS} + v_i$, where V_{GS} is the gate-to-source bias voltage of Q_1 and v_i is a small signal to be amplified. Find the output voltage v_o and the voltage gain v_o/v_i . Also find the small-signal resistance of the diode-connected transistor Q_2 in terms of g_{m2} , and the total resistance between the drain of Q_1 and ground. What is the voltage gain of the CS amplifier Q_1 ? Neglect all r_o 's.



- 3) The amplifier here is formed by cascading two common-source stages. Assuming that $V_{tn} = |V_{tp}|$ and that the biasing current sources have output resistance equal to those of Q_1 and Q_2 , find an expression for the overall voltage gain in terms of g_m and r_o of Q_1 and Q_2 . If Q_1 and Q_2 are to be operated with equal overdrive voltages, $|V_{OV}|$, find the required value of $|V_{OV}|$ if $\lambda = 0.2V^{-1}$ and the required gain is 400 V/V.

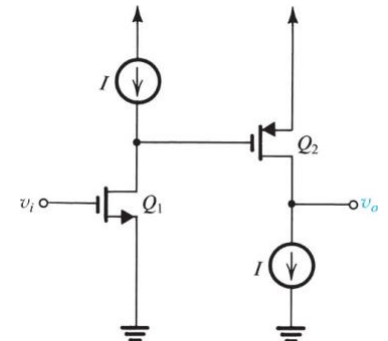

- 4) In this common-gate amplifier, Q_2 and Q_3 are matched, $k'_n(W/L)_n = k'_p(W/L)_p = 4 \text{ mA/V}^2$, and all transistors have $|V_t| = 0.8V$ and $\lambda = 0.05 \text{ V}^{-1}$. The v_{sig} is a small signal with no dc component.

- Ignore λ , find the dc drain current of Q_1 and the required value of V_{BIAS} .
- Find the values of g_m and r_o of all transistors.
- Find the value of R_{in} .
- Find the value of R_{out} .
- Calculate the voltage gain v_o/v_i and v_o/v_{sig} .
- How large can v_{sig} be (peak-to-peak) while maintaining saturation mode operation for Q_1 and Q_2 ?

