
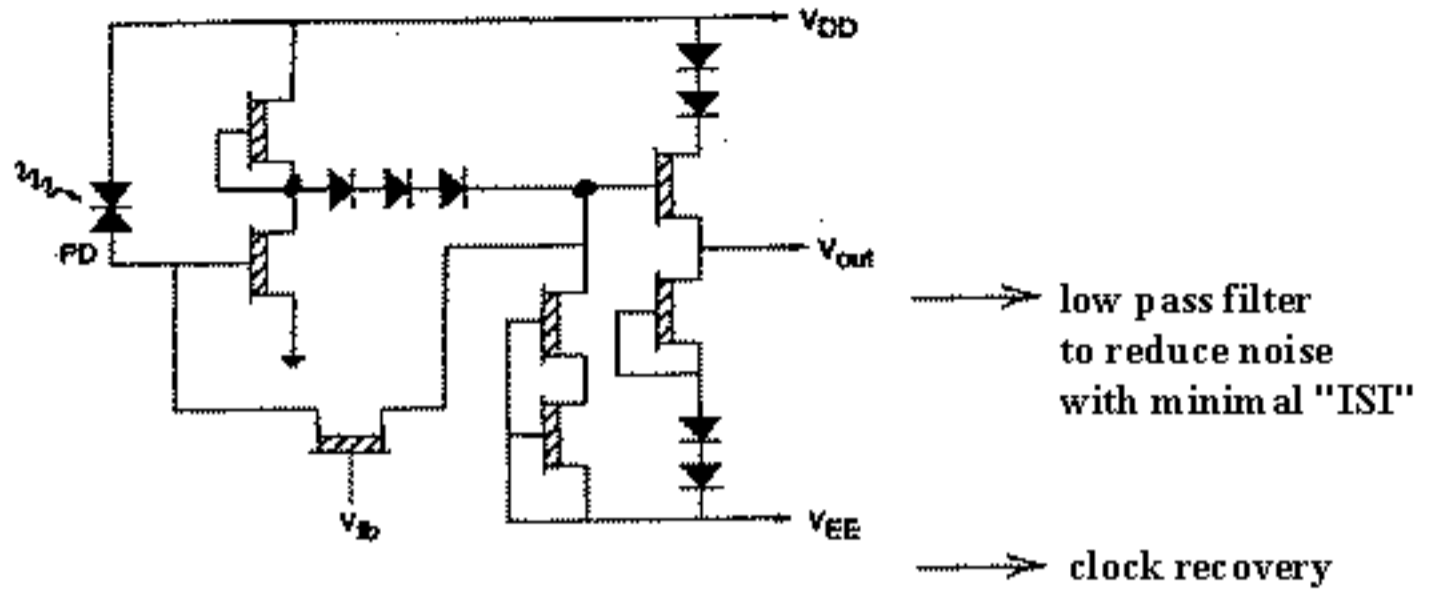

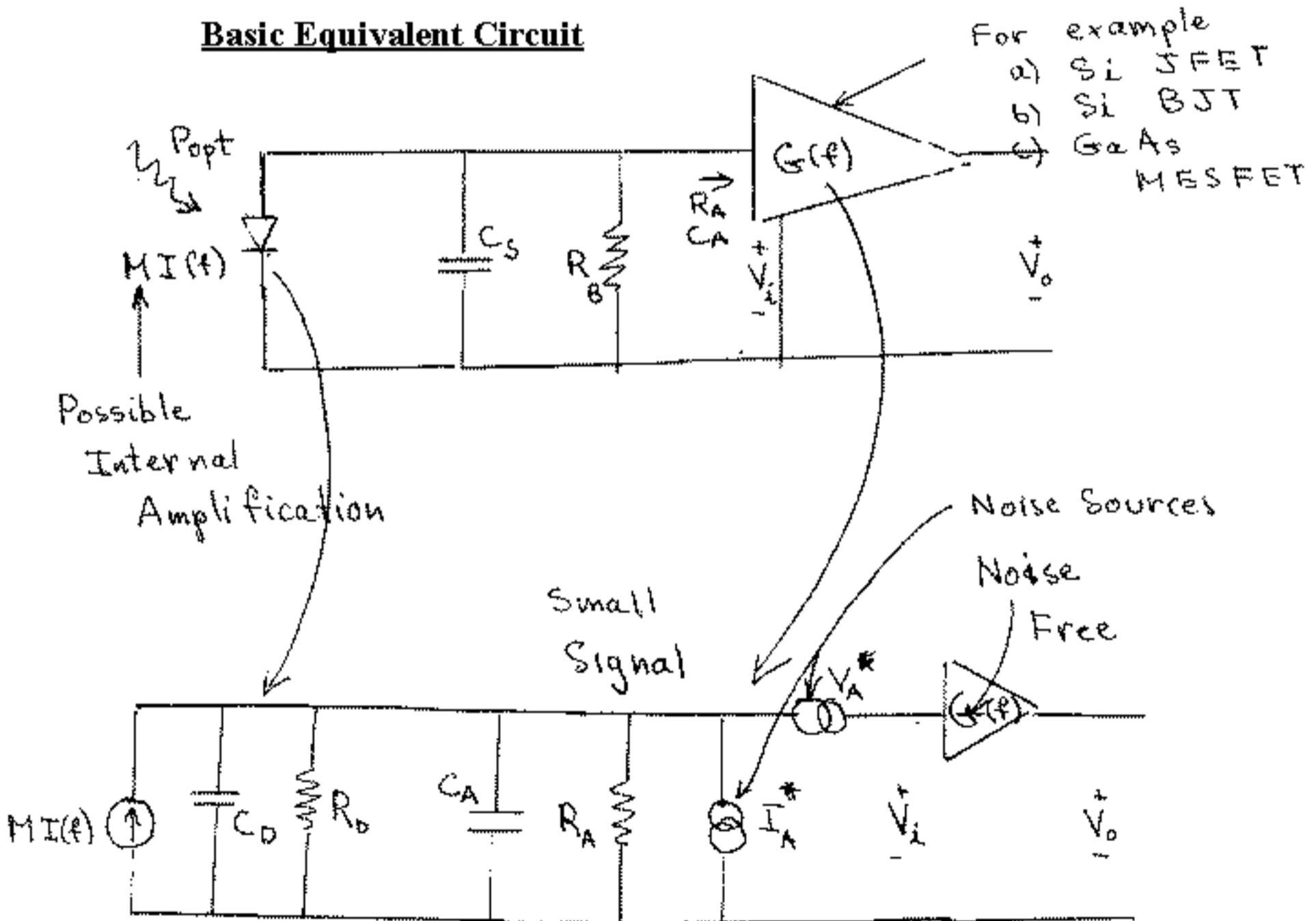
### Example Receiver S/N Ratio Calculation




### Basic Equivalent Circuit



Reference on Noise:  
*Noise in Receiving System*  
 Raoul Pettai, Wiley (1984)

### Example Small Signal Analysis

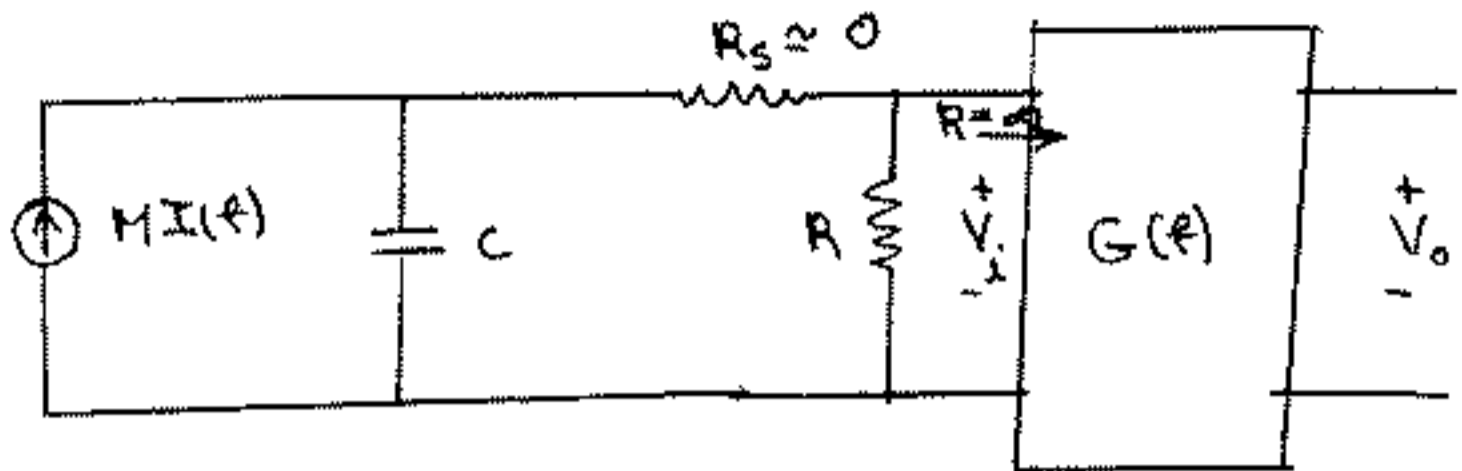

$$\frac{1}{R} = \frac{1}{R_A} + \frac{1}{R_D} + \frac{1}{R_B}$$

$$C = C_D + C_S + C_A$$

↑  
stray

$$V_i = \frac{R M I(f)}{1 + j 2\pi f C R}$$

$$V_o = G(f) V_i = \frac{G(f) R M I(f)}{1 + j 2\pi f C R}$$

For "Equalized" Amplifier  $G(f) = G_0 (1 + j 2\pi f R C)$   
 and

a) Output is independent of frequency

$$V_o = G_0 M R I$$

b)  $\frac{V_o}{I(f)}$  has the same functional relationship as a transimpedance amplifier


Various Noise Sources

$$(I_{sh}^*)^2 = \Delta f (2eI \cdot M^2 F) \text{ --- Photodiode Shot Noise}$$

current ↑  
 amplification factor ↑  
 Excess Noise Due to M

$$(I_{th}^*)^2 = \Delta f \left( \frac{4kT}{R} \right) = 4kT \left( \frac{1}{R_A} + \frac{1}{R_B} + \frac{G_D}{R_D} \right) \Delta f$$

Equivalent Noise Circuit:

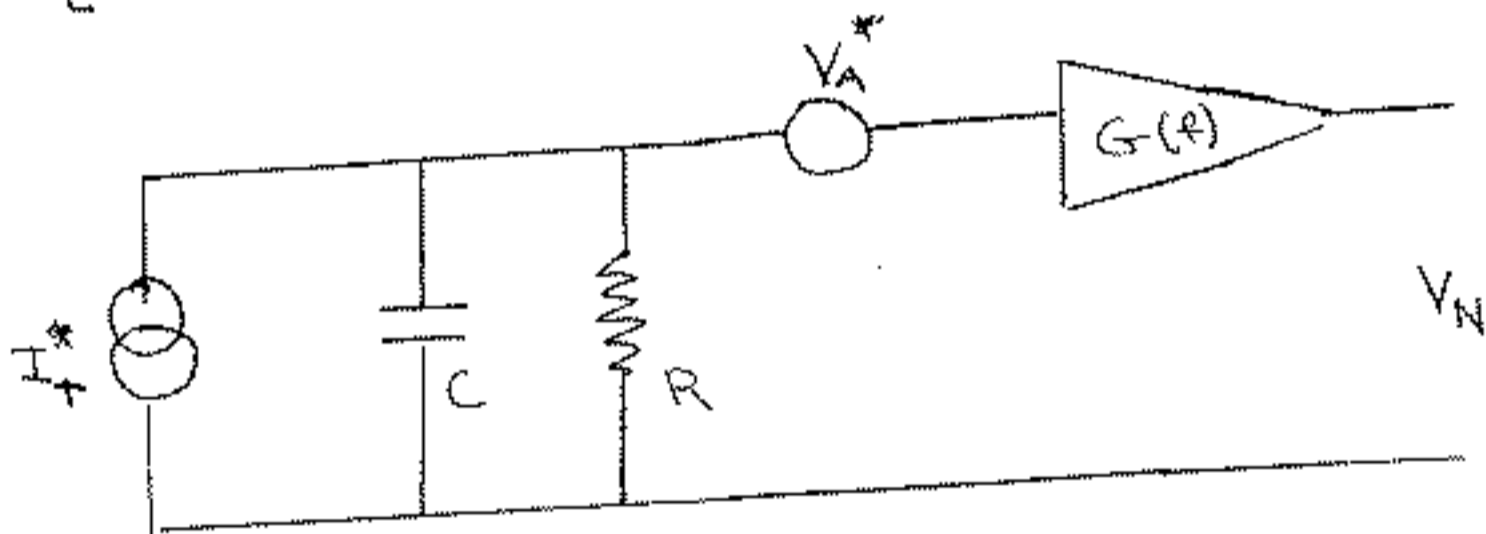

$$(I_T^*)^2 = (I_{sh}^*)^2 + (I_{th}^*)^2 + (I_A^*)^2$$

$$C = C_S + C_A + C_D$$

$$\frac{1}{R} = \frac{1}{R_D} + \frac{1}{R_A} + \frac{1}{R_B}$$

$$V_N^2 = G_0^2 \int_{0 \rightarrow \Delta f} |G(f)|^2 (V_A^*)^2 df + \int_{0 \rightarrow \Delta f} \frac{G^2(f) R^2 (I_T^*)^2}{|1 + j2\pi fCR|^2} df$$

(over the bandwidth)

$$V_N^2 = G_o^2 \int_0^{\Delta f} [1 + 4\pi^2 f^2 C^2 R^2] (V_A^*)^2 + R^2 (I_T^*)^2 df$$

Thus

$$\frac{V_o}{V_N} = \frac{G_o M I R}{[(\Delta f + \frac{4\pi^2}{3} (\Delta f)^3 C^2 R^2) (V_A^*)^2 + \Delta f R^2 (I_T^*)^2]^{\frac{1}{2}}}$$

$$= K = \frac{I}{\sqrt{\Delta f} \left[ \frac{(V_A^*)^2}{M^2} \left( \frac{1}{R^2} + \frac{4\pi^2}{3} (\Delta f)^2 C^2 \right) + 2e I F + \frac{4kT}{M^2 R} + \frac{(I_T^*)^2}{M^2} \right]^{\frac{1}{2}}}$$

(a)

(b)

(c)

(d)

(e)

Notes:

- 1)  $\frac{S}{N}$  increases with M until shot noise dominates
- 2) Increasing R excellent as long as (a) & (d) significant. If R too large equalization is needed to assure band-width
- 3) Shot Noise causes K to be signal dependent
- 4) At high frequencies (b) dominates (increases as  $C^2$  - thus important to minimize C)
- 5) Assumes noise sources uncorrelated

Given K (12 for BER  $\approx 10^{-9}$ ) can solve for I

$$I^2 - 2pI - q = 0$$

$\swarrow$  (c)  
 $\uparrow$   
 $eFk^2\Delta f$

Solution:

$$K^2\Delta f(I_A^*)^2 + K^2\frac{kT\Delta f}{M^2R} + \frac{K^2\Delta f}{M^2} \left[ \frac{V_A^{*2}}{R^2} \left( 1 + \frac{4\pi^2(\Delta f)^2 C^2 R^2}{3} \right) \right]$$

$\uparrow$  (e)                       $\uparrow$  (d)                       $\uparrow$  (a)                       $\uparrow$  (b)

$$I = p \pm \sqrt{p^2 + q}$$

Relevant sign is + (otherwise noise can  $\rightarrow 0$ )

$$= p \left\{ 1 + \left( 1 + \frac{q}{p^2} \right)^{\frac{1}{2}} \right\}$$

Note:

Minimum

Advantageous to have M to decrease  $q \ll p^2$  (but F increases with M)

$$I = 2p \rightarrow \text{shot noise limit}$$

$$= K^2 2e \Delta f F$$

Example Si-APD

$$\eta = 0.75 \quad R = 0.5 \text{ A/W} \quad F = 6$$

$$B = 2\Delta f = 1 \text{ MHz} \quad K = 12$$

$$I = K^2 e (2\Delta f) F$$

$$= 144 \times 1.6 \times 10^{-19} \times 10^6 \times 6$$

$$= 1.4 \times 10^{-10} \text{ amps}$$

Show that when thermal noise dominates and

$$\Delta f = \frac{1}{2\pi RC}$$

$$M^2 \gg \frac{2\pi kTC}{e^2 F^2 K^2}$$

assures the shot noise limit