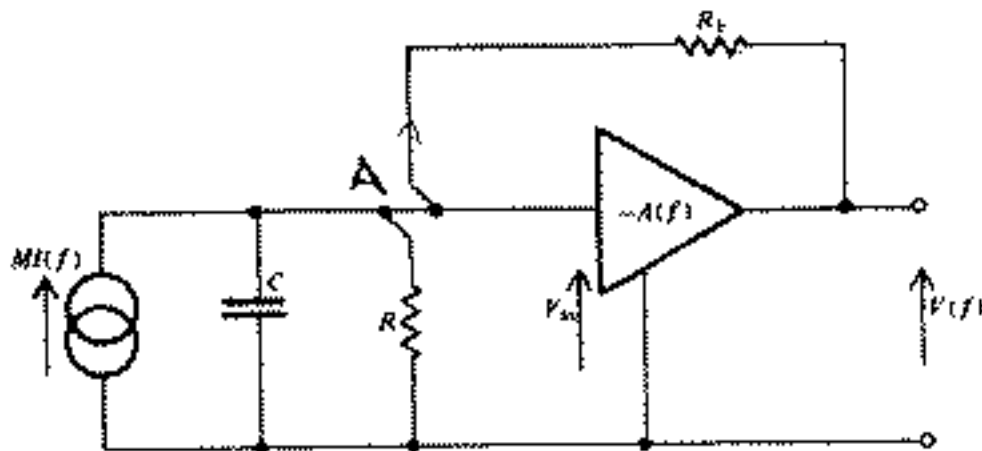


The Transimpedance Amplifier

R and R_f can be large ($-A(f)$ cancels) and good reproducibility, results



$$V_{in} = -V/A$$

$$M I + \frac{V - V_{in}}{R_f} = V_{in} \left(\frac{1}{R} + j 2\pi f C \right) \quad \text{Node Equation at A}$$


$$M I = -V \left(\frac{1}{R_f} + \frac{1}{A R_f} + \frac{1}{A R} + j \frac{2\pi f C}{A} \right)$$

$$V = \frac{-R_f M I}{\left(1 + \frac{1}{A} + \frac{R_f}{A R} + j \frac{2\pi f C R_f}{A} \right)}$$

$$= \frac{-R_f M I}{\left[1 + \frac{j 2\pi f C R_f}{\left(1 + \frac{R_f}{R} + A \right)} \right]}$$

$$V \approx \frac{-R_f M I}{1 + j(2\pi f C R_f)/A} \approx -R_f M I$$

Noise Terms

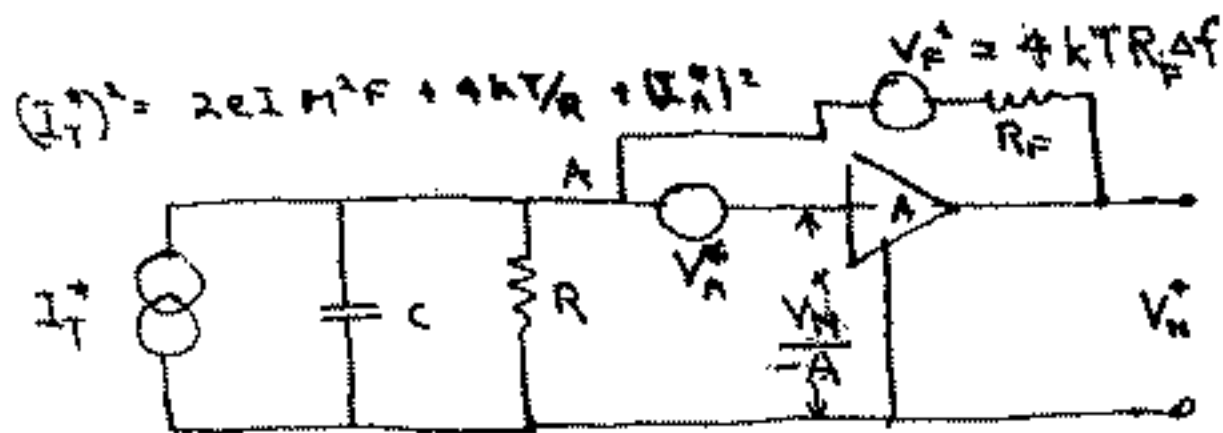

Use Superposition and Node Equation at A

① V_A^* ($I_T^* = V_F^* = 0$)

$A \text{ large} \rightarrow \infty$

$$\left(V_A^* + \frac{V_N^*}{-A} \right) \left(\frac{1}{R} + j2\pi f C \right) = \left(V_N^* - \left(V_A^* + \frac{V_N^*}{-A} \right) \right) \frac{1}{R_F}$$

$A \text{ large} \rightarrow \infty$

$$V_N^* = V_A^* R_F \left(\frac{1}{R_F} + \frac{1}{R} + j2\pi f C \right) / \left(1 + \frac{1}{A} + \frac{R_F}{AR} + j \frac{2\pi f C R_F}{A} \right)$$

For A large

$$V_N^* = V_A^* \left(1 + \frac{R_F}{R} + j2\pi f C R_F \right)$$

② I_T^* ($V_F^* = V_A^* = 0$)

$$\left(V_N^* - \frac{V_N^*}{-A} \right) \frac{1}{R_F} + I_T^* = \frac{V_N^*}{(-A)} \left(\frac{1}{R} + j2\pi f C \right) \quad \text{Eq. (2)}$$

$$V_N^* \left(\frac{1}{R_F} + \frac{1}{AR_F} + \frac{1}{AR} + j \frac{2\pi f C}{A} \right) = -I_T^*$$

For A large from Eq. (2)

$$V_N^* = -R_F I_T^*$$

③ $V_F^* = V_A^* + V_N(-A) \approx V_F^*$
 ($V_A^* = I_T^* = 0$)

Total Noise

$$(V_N^*)^2 = \int (V_A^*)^2 \left(\left(1 + \frac{R_F}{R}\right)^2 + 4\pi^2 f^2 C^2 R_F^2 \right) + R_F^2 (I_T^*)^2 + (V_F^*)^2 df$$

$$(V_N^*)^2 = \int_0^{\Delta f} (V_N^*)^2 df$$

$$V_N = \left[(V_A^*)^2 \left\{ \left(1 + \frac{R_F}{R}\right)^2 + \frac{4\pi^2}{3} (\Delta f)^2 C^2 R_F^2 \right\} + R_F^2 (I_T^*)^2 + 4kTR_F \right]^{1/2} (\Delta f)^{1/2}$$

$$2eIM^2F + \frac{4kT}{R} + (I_A^*)^2$$

$$K = \left| \frac{V}{V_N} \right| = \frac{I}{\left[\frac{(V_A^*)^2}{M^2} \left\{ \left(\frac{1}{R} + \frac{1}{R_F}\right)^2 + \frac{4\pi^2}{3} C^2 (\Delta f)^2 \right\} + 2eIF + \frac{4kT}{M^2} \left(\frac{1}{R} + \frac{1}{R_F}\right) + \frac{(I_A^*)^2}{M^2} \right]^{1/2} (\Delta f)^{1/2}}$$

(a) (b) (c) (d) (e)

Same as previously with $\frac{1}{R}$ replaced by $\frac{1}{R} + \frac{1}{R_F}$

Note: No equalization

Example APD $C = 3 \text{ pF}$, $R = 4 \text{ k}\Omega$, $R_F = 10 \text{ k}\Omega$
 Si Bipolar Transistor Input $V_A^* = 2 \text{ nV}/\sqrt{\text{Hz}}$
 $\lambda = 1.3 \mu\text{m}$ $I_A^* = 2 \text{ pA}/\sqrt{\text{Hz}}$

| | p-i-n $M=1, F=1$ | APD $M=20, F=10$ |
|---|--|---|
| Term (a) | $6.25 \times 10^{-26} \text{ [A}^2/\text{Hz]}$ | $1.8 \times 10^{-28} \text{ [A}^2/\text{Hz]}$ |
| Term (b) | $2.3 \times 10^{-24} \text{ [A}^2/\text{Hz]}$ | $5.8 \times 10^{-27} \text{ [A}^2/\text{Hz]}$ |
| Term (d) | $2.1 \times 10^{-24} \text{ [A}^2/\text{Hz]}$ | $5.2 \times 10^{-27} \text{ [A}^2/\text{Hz]}$ |
| Term (e) | $4.0 \times 10^{-24} \text{ [A}^2/\text{Hz]}$ | $1.0 \times 10^{-26} \text{ [A}^2/\text{Hz]}$ |
| Total, (a) + (b) + (d) + (e) = (A) | $8.5 \times 10^{-24} \text{ [A}^2/\text{Hz]}$ | $2.1 \times 10^{-26} \text{ [A}^2/\text{Hz]}$ |
| $\frac{1}{2}(I_{SH})_{ul}^2 = (KeF)^2 \Delta f = (B)$ | $1.2 \times 10^{-28} \text{ [A}^2/\text{Hz]}$ | $7.7 \times 10^{-28} \text{ [A}^2/\text{Hz]}$ |
| $q/p^2 = (A)/(B)$ | 11800 | 0.3 |
| $I_{min} = p[1 + (1 + q/p^2)]$ | 490 nA | 96 nA |
| $(\Phi_{in})_{min}$ (with $\eta = 0.5$) | 1 μW | 200 nW |

Shot Noise Dominates