

PROBLEM SET #10

Issued: Tuesday, Nov. 12th, 2013

Due: Wednesday, Nov. 20th, 2013, 8:00 a.m. in the EE 140/240A homework box

1. An amplifier with a forward gain of A_0 has two coincident poles at ω_p .
 - (a) Calculate the maximum value of A_0 for a 60° phase margin with a closed-loop gain of (i) unity and (ii) 4.
 - (b) Repeat part (a) assuming that you compensated the amplifier such that $\omega_{p1} = \omega_p/50$ and $\omega_{p2} = \omega_p$.

2. A dc amplifier has an open-loop gain of 1000 and two poles: a dominant one at 1MHz and a high-frequency one whose location can be controlled. It is required to connect this amplifier in a negative-feedback loop that provides a dc closed loop gain of 100 and a maximally flat response. Find the required value of feedback factor (i.e., f) and the frequency at which the second pole should be placed.

3. Consider a two-stage two-pole op amp with open-loop transfer function $A(s) = \frac{a_0}{(1+s/\omega_{p1})(1+s/\omega_{p2})}$. Assume that $a_0 = 60\text{dB}$, and ω_{p1} is the dominant pole at the output and located at $2\pi \times 100\text{kHz}$, $G_{m1} = 10\text{mS}$, $G_{m2} = 5\text{mS}$, $R_{out1} = 5\text{k}\Omega$, $R_{out2} = 4\text{k}\Omega$.
 - a. Find the value of ω_{p2} so that a unity gain feedback circuit using this op amp exhibits a 45° phase margin. Sketch the magnitude and phase Bode plots of the op amp's open-loop transfer function.
 - b. Let $\omega_{p2} = 2\pi \times 10\text{MHz}$ for this and all remaining parts of this problem. Find the op-amp's unity-gain frequency and unity-gain phase margin. Sketch the magnitude and phase Bode plots of the op amp's open-loop transfer function.
 - c. Given what you found in part (b), is it safe to put this op amp into unity-gain feedback? Explain why or why not.
 - d. Derive an expression and find numerical value for the needed compensation capacitor C_c that provides a phase margin of 60° in unity gain feedback.
 - e. Derive an expression and find numerical value for the needed compensation capacitor C_c that provides a phase margin of 75° in unity gain feedback.

4. A two-stage op-amp has a compensation capacitor connected between the input and the output of its second stage. Assume that the frequency of its second-pole is 60MHz and that this frequency stays constant with changes in the compensation capacitor. Assume the input stage generates a transconductance of 0.775mA/V, and the second stage provides a voltage gain of 100. What is the required size of the compensation capacitor if the phase margin is to be 55° for the feedback configuration as shown in Fig. PS10.4.

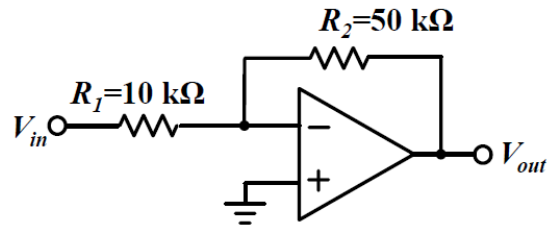


Fig. PS10.4