

**PROBLEM SET #12**

Issued: Tuesday, Dec. 3<sup>rd</sup>, 2013

Due: Wednesday, Dec. 11<sup>th</sup>, 2013, 8:00 a.m. in the EE 140/240A homework box

- Using feedback techniques, determine the input and output impedance and current gain ( $I_{out}/I_{in}$ ) of the circuit in Fig. PS12.1. Leave your answer in terms of variables ( $g_{m1}$ ,  $R_1$ ,  $r_o$ , etc.) and assume  $\gamma = 0$ .

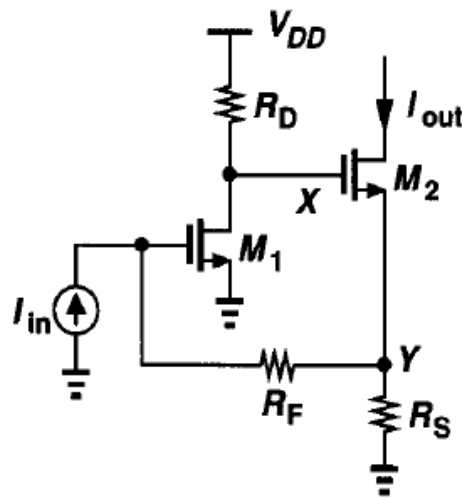


Figure PS12.1

- Consider the circuit in Fig. PS12.2, where  $(W/L)_{1-4} = 50/0.5$ ,  $|I_{D1-4}| = 0.5$  mA,  $V_{in} = 0.7$  V,  $V_{tp} = -0.8$  V,  $k_n' = 134$   $\mu\text{A}/\text{V}^2$ ,  $k_p' = 38$   $\mu\text{A}/\text{V}^2$ ,  $\lambda_n = 0.1$   $\text{V}^{-1}$ ,  $\lambda_p = 0.2$   $\text{V}^{-1}$ , and  $R_2 = 3$  k $\Omega$ .
  - For what range of  $R_1$  are the above currents established while  $M_2$  remains in saturation? What is the corresponding range of  $V_{in}$ ?
  - Calculate the closed-loop gain and output impedance for  $R_1 = 805$   $\Omega$ .

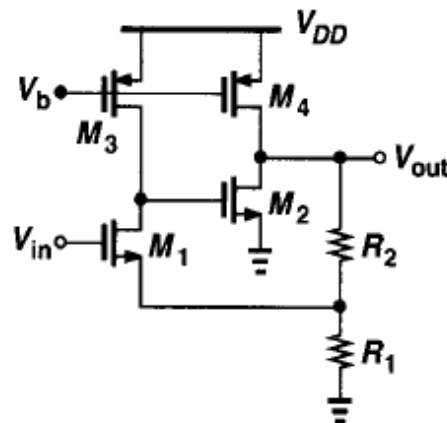


Figure PS12.2

3. A CMOS feedback amplifier is shown in Fig. PS12.3. If the dc input voltage is zero, calculate the overall voltage gain  $v_o/v_i$  and the output resistance assuming the following parameters:

$$\mu_n C_{ox} = 60 \mu\text{A}/\text{V}^2, \mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2, V_{tn} = 0.8 \text{ V},$$

$$V_{tp} = -0.8 \text{ V}, \lambda_n = |\lambda_p| = 0.03 \text{ V}^{-1}, \text{ and } \gamma_n = \gamma_p = 0.$$

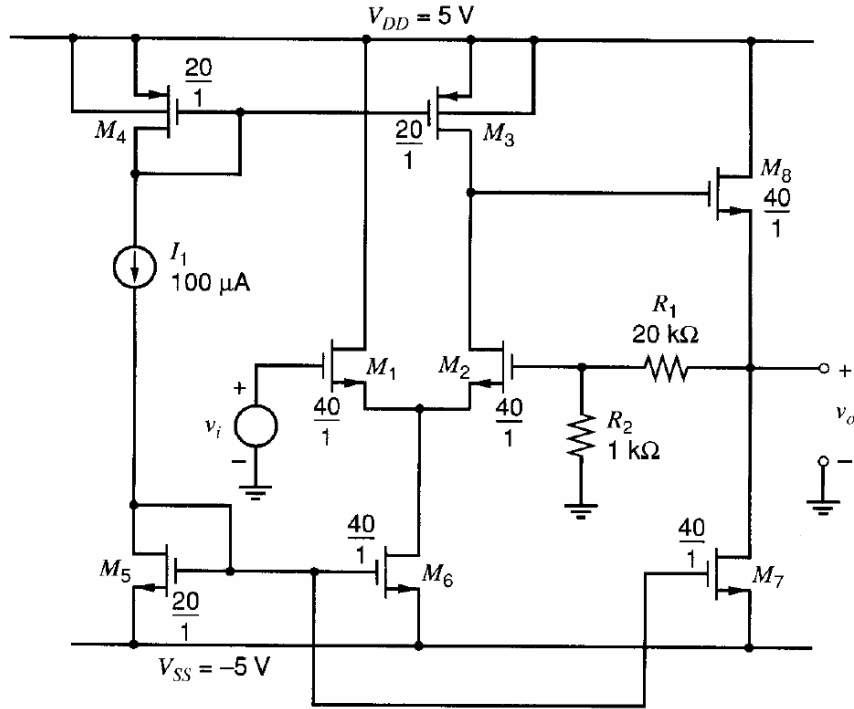


Figure PS12.3