

**PROBLEM SET #8**

Issued: Tuesday, Oct. 22<sup>nd</sup>, 2013

Due: Tuesday, Oct. 29<sup>th</sup>, 2013, 6:00 p.m. in the EE 140/240A homework box

1. Consider the circuit in Fig. PS8.1. Assume the tail current source is a simple current mirror, and the transistors have parameters  $\lambda = 0.1\text{V}^{-1}$  and  $\gamma = 0$ . The transistors are nominally biased so that:

$$I_{D-nom} = 2\text{mA}, g_{mTail} = 20\text{mS}, g_{m1,2} = 10\text{mS}, g_{m3,4,5,6} = 5\text{mS}, g_{m7,8} = 10\text{mS}, |V_{th}| = 0.5\text{V}, V_{DD} = 5\text{V}.$$

- (a) Determine the DC value of input and bias voltages  $V_{B1}$ ,  $V_{B2}$  and  $V_{B3}$  for maximum output swing.
- (b) Calculate the output slew rate when the amplifier is used as a unity-gain circuit and there is 1pF capacitor connected at the output node.
- (c) Find the open-loop voltage gain  $A = V_{out}/V_{in}$  for  $A_{dm}$ ,  $A_{cm}$ ,  $A_{dm-cm}$ , and  $A_{cm-dm}$ .
- (d) Repeat part (c) assuming the amplifier is mismatched such that  $(I_{D-M1,3,5,7} - I_{D-M2,4,6,8})/I_{D-nom} = 2\%$ , and  $(g_{m1,3,5,7} - g_{m2,4,6,8})/g_{m,nom} = 5\%$ .

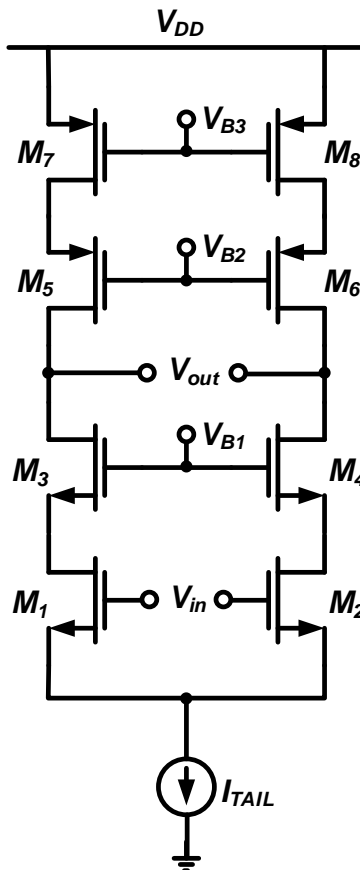


Fig. PS8.1

2. Write an expression for the common-mode input range of the op amp in Fig. PS8.2 in terms of  $V_{DD}$  and  $V_{SS}$ . Assume that the transistors have  $|V_t| = 1$  V, and ignore the body effect. Also assume that the biasing is arranged so that  $|V_{ov}| = 0.2$  V for each transistor except  $M_9$ . Finally, assume that  $M_1$  and  $M_2$  are biased at the edge of saturation by  $M_9$  and  $I_C$ . If the common-mode input range is required to be no less than 0.2V, what is the minimum supply difference,  $V_{DD} - V_{SS}$ ?

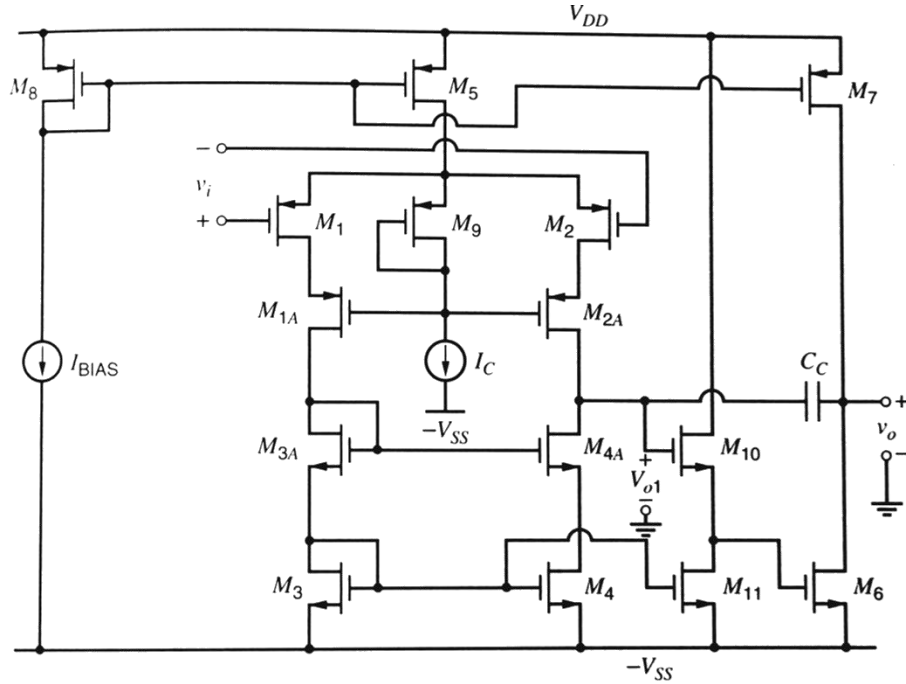


Fig. PS8.2

3. For the circuit in Fig. PS8.3(i):

- Find the transfer function and sketch a Bode plot assuming the amplifier is ideal.
- Find the transfer function and sketch a Bode plots if

$$A(s) = \frac{A_0}{1 + \frac{s}{\omega_p}}$$

For the circuit in Fig. PS8.3(ii):

- If the amplifier offset is  $V_{OS} = 1\text{mV}$ , calculate the value of  $R_f$  such that  $|V_{out}| = 0.5\text{V}$  when no input signal is applied.
- Repeat b) with  $R_f$  included.

$$R = 1\text{k}\Omega, C = 1\text{nF}, A_0 = 105, \omega_p = 10 \text{ rad/s}$$

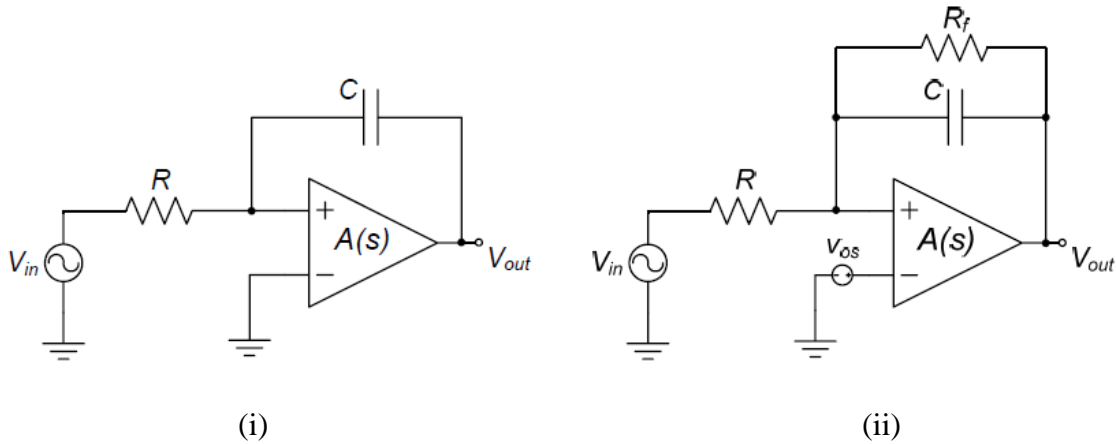


Fig. PS8.2