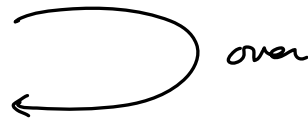


Lecture 10w: Supply & Temperature Independent BiasingLecture 10: Supply & Temperature Indep. Biasing• Announcements:

- ↪ HW#4 due tomorrow at 8 a.m.
- ↪ HW#5 online soon
- ↪ Lab#1 reports are due the week of Oct. 8
 - Turn them in to Yang in your lab section
- ↪ Lab#2 is online
 - This is a hardware lab
 - You must show up to lab for Lab#2
- ↪ Office Hour Change: Yang's Thursday office hours moved to M 2:30-3:30

• Lecture Topics:


- ↪ Supply & Temperature Independent Biasing
- ↪ Output Swing
- ↪ Dynamic Range

• Last Time: Started supply independent biasing

Define: Sensitivity of Y to X

$$S_x^Y = \frac{\frac{\Delta Y}{Y}}{\frac{\Delta X}{X}} = \frac{X}{Y} \frac{\Delta Y}{\Delta X} = \frac{X}{Y} \frac{\partial Y}{\partial X}$$

For supply dependence, we want $S_{V_{CC}}^{I_0} = 0$.

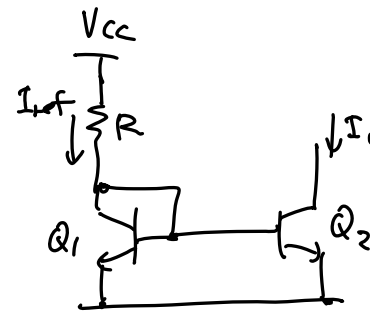Simple Current Source

Neglecting base currents:

$$I_0 = I_{ref} = \frac{V_{CC} - V_{BE(Q1)}}{R}$$

$$I_0 \approx \frac{V_{CC}}{R} \quad [V_{CC} \gg V_{BE(Q1)}]$$

Thus:

$$S_R^{I_0} = \frac{R}{I_0} \frac{\partial I_0}{\partial R} = \frac{R^2}{V_{CC}} \left(-\frac{V_{CC}}{R^2} \right) \Rightarrow S_R^{I_0} = -1$$

$$S_{V_{CC}}^{I_0} = \frac{V_{CC}}{I_0} \frac{\partial I_0}{\partial V_{CC}} = R \left(\frac{1}{R} \right) \Rightarrow S_{V_{CC}}^{I_0} = 1$$

∴ a 10% change in V_{CC} leads to 10% change in I_0 !

terrible!

Widlar Current Source (Any better?)

$(\ln I_{ref} - \ln I_o)$

$V_T \ln \frac{I_{ref}}{I_o} = I_o R_2$

Differentiate w/r to V_{cc} !

$$V_T \left(\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} - \frac{1}{I_o} \frac{\partial I_o}{\partial V_{cc}} \right) = R_2 \frac{\partial I_o}{\partial V_{cc}}$$

math

$$\frac{\partial I_o}{\partial V_{cc}} = \frac{V_T}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \frac{I_o}{(R_2 + \frac{V_T}{I_o})}$$

$S_{V_{cc}}^{I_{ref}} = 1$

$$\therefore S_{V_{cc}}^{I_o} = \frac{V_{cc}}{I_o} \frac{\partial I_o}{\partial V_{cc}} = V_T \frac{\left(\frac{V_{cc}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{cc}} \right)}{I_o R_2 + V_T}$$

$$\Rightarrow S_{V_{cc}}^{I_o} = \left(\frac{1}{1 + \frac{I_o R_2}{V_T}} \right) S_{V_{cc}}^{I_{ref}}$$

Since $I_{ref} = \frac{V_{cc} - V_{BE(sat)}}{R_1} \approx \frac{V_{cc}}{R_1} \Rightarrow S_{V_{cc}}^{I_{ref}} = 1$

$$\therefore S_{V_{cc}}^{I_o} = \frac{1}{1 + \frac{I_o R_2}{V_T}}$$

For $I_{ref} = 1\text{mA}$, $I_o = 10\mu\text{A}$, $R_2 = 11.91\text{k}\Omega$, then
 10% Δ in $V_{cc} \rightarrow 1.37\%$ Δ in I_o
 (better than the simple current source!)

How can we do better?

\rightarrow Use another voltage reference: $\uparrow R \quad V_{ref}$

- ✓ ① $V_{BE} \rightarrow$ base emitter junction voltage
- ② $V_z \rightarrow$ Zener diode
- ③ $V_t \rightarrow$ threshold voltage (MOS)
- ✓ ④ $V_T = \frac{kT}{q} \rightarrow$ thermal voltage
- ✓ ⑤ $E_g \rightarrow$ bandgap

V_{BE}-Referenced Biasing

$I_{ref} = \frac{V_{CC} - 2V_{BE1}}{R_1}$

$I_o: \frac{V_{BE1}}{R_2} = \frac{V_T}{R_2} \ln \frac{I_{ref}}{I_{S1}}$

$\frac{\partial I_o}{\partial V_{CC}} = \frac{V_T}{R_2} \left(\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}} - \frac{1}{I_{S1}} \frac{\partial I_{S1}}{\partial V_{CC}} \right)$

$S_{V_{CC}}^{I_o} = \frac{V_{CC}}{I_o} \frac{\partial I_o}{\partial V_{CC}} = \frac{1}{V_{CC}} \ln \left(\frac{I_{ref}}{I_{S1}} \right)$

Problem: I_{ref} still depends on V_{CC}

$S_{V_{CC}}^{I_{ref}} \approx 1 = \frac{V_{CC}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}}$

$S_{V_{CC}}^{I_o} = \frac{1}{\ln(I_{ref}/I_{S1})} \left[1 - \frac{V_{CC}}{I_{S1}} \frac{\partial I_{S1}}{\partial V_{CC}} \right] = \frac{1}{\ln(I_{ref}/I_{S1})}$

If we can eliminate this "1", then $S_{V_{CC}}^{I_o} = 0$ → need to eliminate this dependence of I_{ref} on V_{CC} !

Solution: Derive I_{ref} independently of V_{CC} .
 use self-biasing

Graphically:

Use start up clock to insure operation

$I_{o1} = \frac{V_T}{R_2} \ln \frac{I_{ref}}{I_{S1}}$

$V_{CE3} = V_{CC} - 2V_{BE1} + \Delta V_{CC}$

$V_{BE3} = V_{BE4} \rightarrow I_o \neq I_{ref}$

$V_{BE3} \approx V_{BE4}$

$I_{ref} \downarrow$ mirror


$V_{BE3} \approx V_{BE4}$

$S_{V_{CC}}^{I_{ref}} \rightarrow S_{V_{CC}}^{I_o} \approx 0$

pretty damn good!


$\frac{kT}{q}$ -Referenced Bias Ckt.

Based on the Widlar current source:

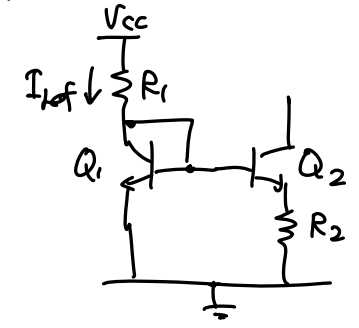

Here, $I_{ref} \neq I_o$.
 ↓
 so sensitive to V_{cc} variations
 ↓
 But can fix this by setting $I_{ref} = I_o$.

Use self-biasing:

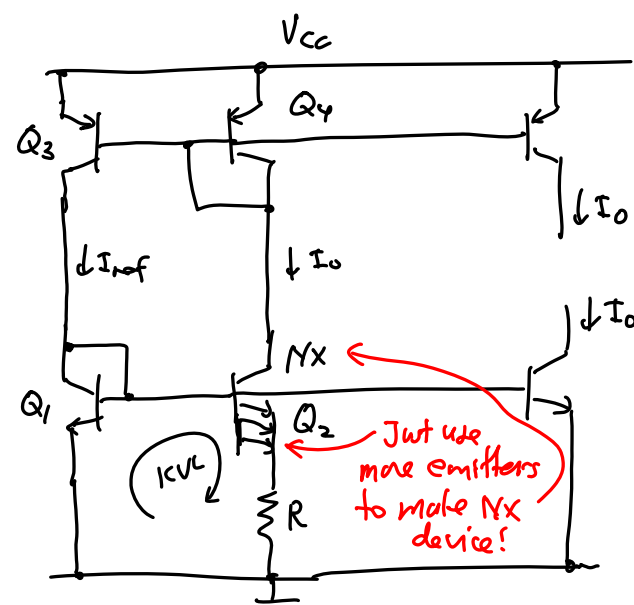


Just use more emitters to make Nx device!

Assuming $I_{r2} = NI_{r1}$:

KVL: $I_o R = V_{BE1} - V_{BE2} = V_T \ln N$ ← at least wr to V_{cc}

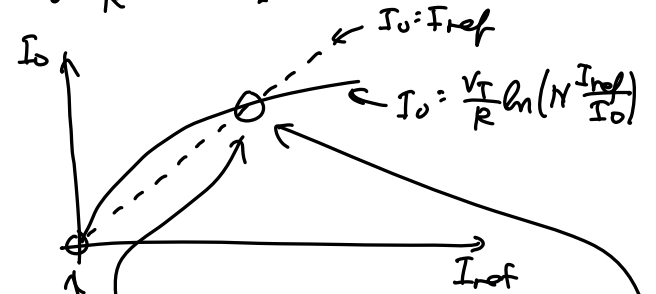$I_o = \frac{V_T}{R} \ln N = \frac{kT}{q} (\text{const.})$



Two possible operating pts.
 ⇒ we startup cktry to guarantee this one

(What we have very small $S_{I_o}^{V_{cc}}$)

$\frac{kT}{q}$ -Reference Temperature Dependence

$$TC_f = \frac{1}{I_o} \frac{\partial I_o}{\partial T} = \ln N \left(\frac{1}{R} \frac{\partial V_T}{\partial T} - \frac{V_T}{R^2} \frac{\partial R}{\partial T} \right) \frac{R}{V_T \ln N}$$

$$\therefore TC_f = \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$= \underbrace{TC_f|_{V_T}}_{3300 \text{ ppm/}^\circ\text{C}} - \underbrace{TC_f|R}_{1800 \text{ ppm/}^\circ\text{C}} \sim 1500 \text{ ppm/}^\circ\text{C}$$

↪ Better than V_{BE} -Ref, but still not zero...
 How can get ↗?

Bandgap Reference

Basic Idea:

$V_{BE} \rightarrow \text{neg. } TC_f$
 $\frac{kT}{q} \rightarrow \text{pos. } TC_f$

➔ Add together to cancel ➔ get net $TC_f = 0!$

0th Order Picture:

$V_{BE} + k\left(\frac{kT}{q}\right)$
 Choose k to get $TC_f = 0$.

What should k be? (0th Order Picture)
 ➔ get ballpark estimate

↻ over

V_{BE}
 V_{60}
 $1.205V$
 $0K$ $300K$
 T
 $\sim -2mV/^\circ C$
 $\sim 700mV$

Bandgap voltage obtained via a linear extrapolation to $0K$. (Not the same as what one usually sees in physics.)


$\frac{kT}{q}$
 $0.1mV/^\circ C$
 $\sim 26mV$
 $0K$ $300K$
 T

V_{60}
 $\sim 1.205V$
 $0K$ $300K$
 T
 $TC_f = 0$
 $TC_f = 0$
 So will only get this @ one temperature
 reality

0th Order → there will actually be some curvature

- 240A folks: read Gray & Meyer
 - ↳ Sections 4.4.2 through 4.4.3
 - ↳ These cover supply and temperature independent biasing, including bandgap references
 - ↳ Can also read Razavi, Chpt. 11, on bandgap references

Output Swing (Headroom)

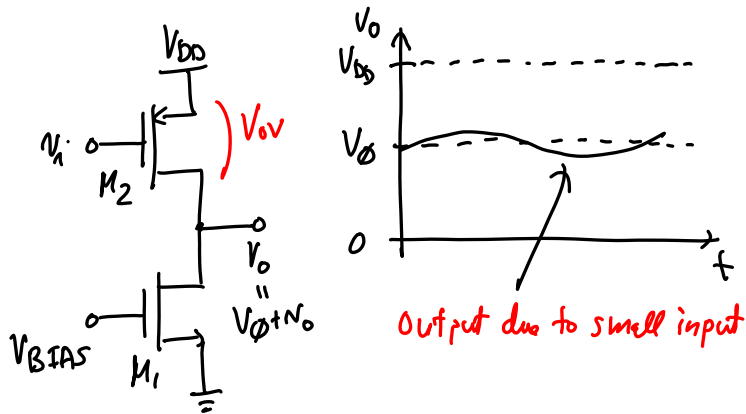

I_D vs. V_{DS} Characteristic:

