

Lecture 12: Current Source Matching

Announcements:


- ↳ Lab#2 online: starts this week
- ↳ HW#6 online soon
- ↳ 240A HW#1A online soon

Lecture Topics:

- ↳ High Swing Current Sources (cont.)
- ↳ Current Source Matching Considerations
- ↳ Op Amp Review

Last Time:

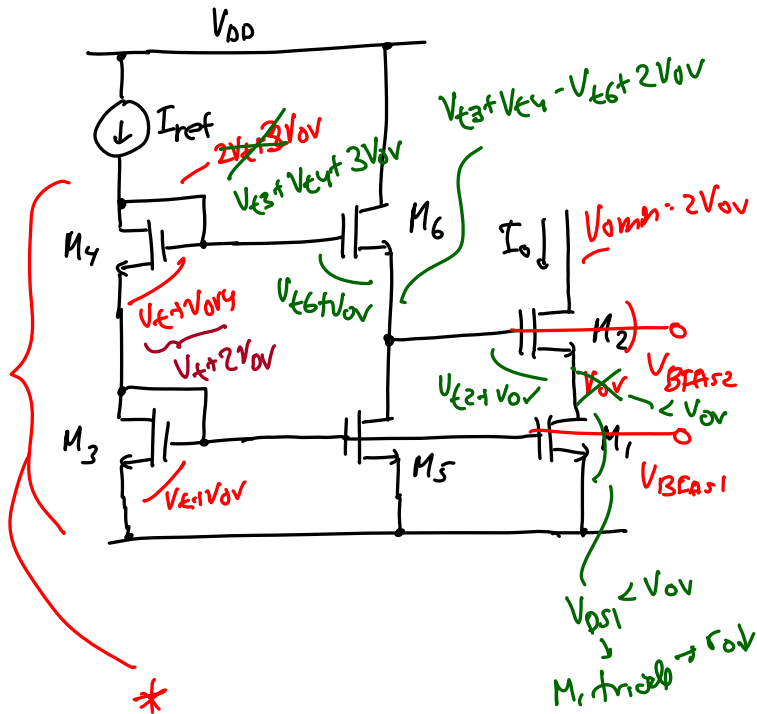Problem: Body effect $M_4, M_6, M_2 \rightarrow$ increases $V_{gs} - V_{t}$'s



$$V_{t4} = V_{t6} \rightarrow \left. \begin{aligned} V_{S4} &= V_t + V_{ov} \\ V_{S6} &= V_t + 2V_{ov} \end{aligned} \right\} V_{t6} > V_{t4}$$

$$V_t = V_{t0} + \gamma(\sqrt{2\alpha_F + V_{S8}} - \sqrt{2\alpha_F}) \rightarrow V_{S8} \uparrow \rightarrow V_t \uparrow$$

Problem if this makes $V_{DS1} < V_{ov}$ ($M_1 \rightarrow$ trouble)

What is this voltage? (V_{D1})

very bad!

$$V_{GS} + V_{t3} - V_{t6} - V_{t2} + V_{ov}$$

$$\underbrace{(V_{t4} - V_{t6})}_{(-)} + \underbrace{(V_{t3} - V_{t2})}_{(-)} + V_{ov} < V_{ov}$$

$V_{D1} < V_{ov}$
 M_1 not saturated!

Solutions:

① Remove $\gamma \rightarrow$ tie the wells M_4, M_6, M_2 to their sources $\rightarrow V_{S8} = 0V$


$$V_t = V_{t0} + \gamma(\sqrt{2\alpha_F + V_{S8}} - \sqrt{2\alpha_F}) = V_{t0}$$

Problem: too much die area consumed when giving these devices their own wells \rightarrow cost \uparrow

② Bias M_4 so that $V_{GS4} \geq V_t + 2V_{ov}$

e.g., $V_{GS4} = V_t + 3V_{ov}$

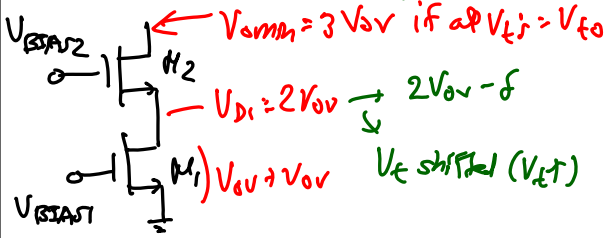$\left(\frac{W}{L}\right)_4 = \frac{1}{9} \left(\frac{W}{L}\right)_3$ ← safety margin against V_t shift



Issues: $I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$

(a)


channel length $\downarrow \rightarrow \lambda \uparrow$
If $V_{DS1} \neq V_{DS3}$

$I_D = \frac{(1 + \lambda V_{DS1})}{(1 + \lambda V_{DS3})} I_{ref} \rightarrow I_D \neq I_{ref}$

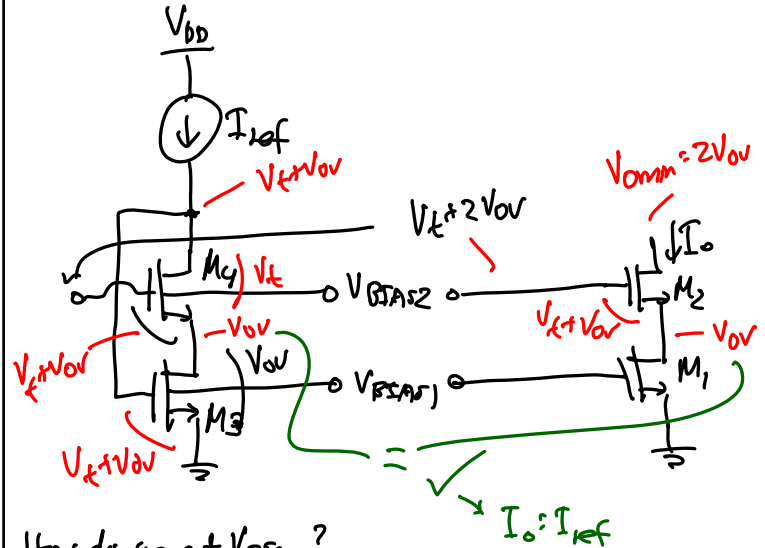
(b) As technology advances, $V_{DD} \downarrow \rightarrow$ losing headroom even for V_{BIAS} generation

this is for much! → Solution

* Solution: Alternate Biasing Scheme for Cascode



How do we get V_{BIAS2} ?

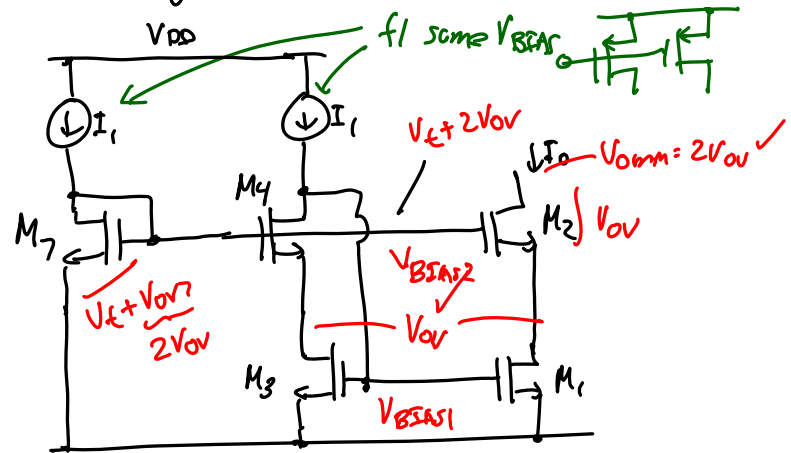

$$I_{D1} = I_{D2}$$


$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (2V_{ov})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{ov})^2$$

$$\left(\frac{W}{L}\right)_1 = \frac{1}{4} \left(\frac{W}{L}\right)_2 = \frac{1}{4} \left(\frac{W}{L}\right)_{ref}$$


rest of Xsistms

Note: Still must worry about Body effect!
defensive design $\rightarrow V_{GS2} > V_t + 2V_{ov}$

Current Source Matching Considerations

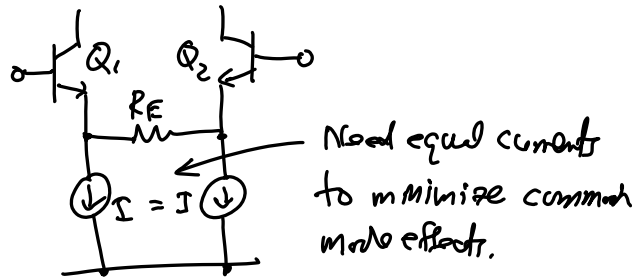

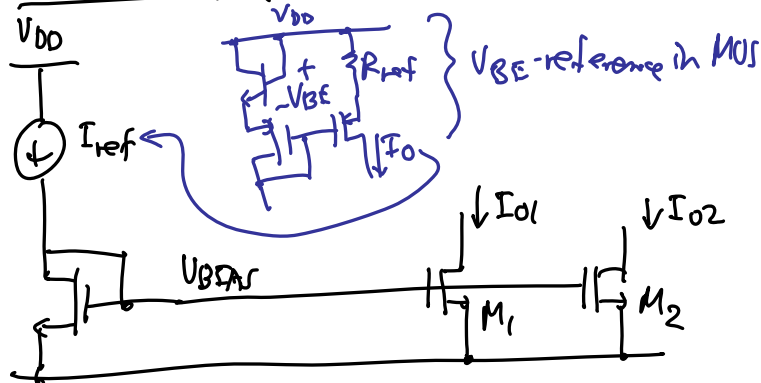Consider matching of simple current sources:



In MOS, we need matched current sources:

$$I_{D1} = I_{D2} \rightarrow I_{01} = I_{02}$$

$$I_{01} = I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{t1})^2$$

$$I_{02} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{t2})^2$$

$I_{01} \neq I_{02}$ if $(W/L)_1 \neq (W/L)_2$ & $V_{t1} \neq V_{t2}$

will always have this due to finite fabrication tolerances!

Need to quantify their impact \rightarrow How much mismatch in I_{01} & I_{02} is caused by

Define average & mismatched quantities,

Average

Mismatch

$$I_0 = \frac{1}{2} [I_{01} + I_{02}]$$

$$\Delta I_0 = I_{01} - I_{02}$$

$$\left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right]$$

$$\Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$$

$$V_t = \frac{1}{2} [V_{t1} + V_{t2}]$$

$$\Delta V_t = V_{t1} - V_{t2}$$

*

*
 $\frac{\Delta I_D}{I_D} \triangleq$ fractional current mismatch

$\frac{\Delta(w/L)}{(w/L)} \triangleq$ " " $\left(\frac{w}{L}\right)$ " "
 $\frac{\Delta V_t}{V_t} \triangleq$ " " V_t " "

Rearranging:

$I_{D1} = I_D + \frac{\Delta I_D}{2} \quad \left(\frac{w}{L}_1 = \left(\frac{w}{L}\right) + \frac{\Delta(w/L)}{2} \right) \quad \left(V_{t1} = V_t + \frac{\Delta V_t}{2} \right)$
 $I_{D2} = I_D - \frac{\Delta I_D}{2} \quad \left(\frac{w}{L}_2 = \left(\frac{w}{L}\right) - \frac{\Delta(w/L)}{2} \right) \quad \left(V_{t2} = V_t - \frac{\Delta V_t}{2} \right)$

Plug these into the current equation:

$I_{D1} = I_D + \frac{\Delta I_D}{2}$
 $= \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right)_1 (V_{GS} - V_{t1})^2$
 $= \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{w}{L}\right) + \frac{\Delta(w/L)}{2} \right] \left[V_{GS} - V_t - \frac{\Delta V_t}{2} \right]^2$
 $= \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{w}{L}\right) + \frac{\Delta(w/L)}{2} \right] \left[V_{OV}^2 - 2V_{OV} \frac{\Delta V_t}{2} + \frac{(\Delta V_t)^2}{4} \right]$
 $= \frac{1}{2} \mu_n C_{ox} \left[\left(\frac{w}{L}\right) V_{OV}^2 + \frac{\Delta(w/L)}{2} V_{OV}^2 - \left(\frac{w}{L}\right) V_{OV} \Delta V_t - \frac{\Delta(w/L)}{2} V_{OV} \Delta V_t \right]$

neg! *neg!*

$= \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right) V_{OV}^2 + \frac{1}{2} \mu_n C_{ox} V_{OV}^2 \left[\frac{\Delta(w/L)}{2} - \frac{(w/L)}{V_{OV}} \Delta V_t \right]$

Factor out (w/L)

$\frac{\Delta I_D}{2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{w}{L}\right) V_{OV}^2 \left[\frac{1}{2} \frac{\Delta(w/L)}{(w/L)} - \frac{\Delta V_t}{V_{OV}} \right]$

$\therefore \frac{\Delta I_D}{I_D} = \frac{\Delta(w/L)}{(w/L)} + \frac{\Delta V_t}{(V_{OV}/2)}$

(-) sign means nothing since ΔV_t could be (-)

Fractional Current Mismatch
 Geometry-Based Component
 Indep. of Bias Pt.
 Dep. on Fab!

$V_{OV} \uparrow \rightarrow$ to minimize this component

With today's cbs: (driven by power savings for digital cbs.)

$V_{OV} \downarrow \rightarrow V_{OV} \downarrow \rightarrow \frac{\Delta I_D}{I_D} \uparrow$ X - Bad!

To combat this: $\left(\frac{w}{L}\right) \uparrow \rightarrow \frac{\Delta(w/L)}{(w/L)} \downarrow \rightarrow \frac{\Delta I_D}{I_D} \downarrow$

cost \uparrow

