

Lecture 13: Op Amps & Emitter Coupled Pair


• **Announcements:**

- ↳ Pre-Lecture materials online
- ↳ HW#6 online
- ↳ HW#1A online soon for 240A folks
- ↳ Midterm will be on the date specified in your syllabus: Thursday, Oct. 31, 9:00-11 a.m. in this room (three weeks away)
- ↳ Question: Does anyone have a class before this one? If not, you might have more time. → we will start at 9 a.m.

• **Lecture Topics:**


- ↳ Op Amp Review
- ↳ Emitter Coupled Pair (ECP)
- ↳ Half Circuits

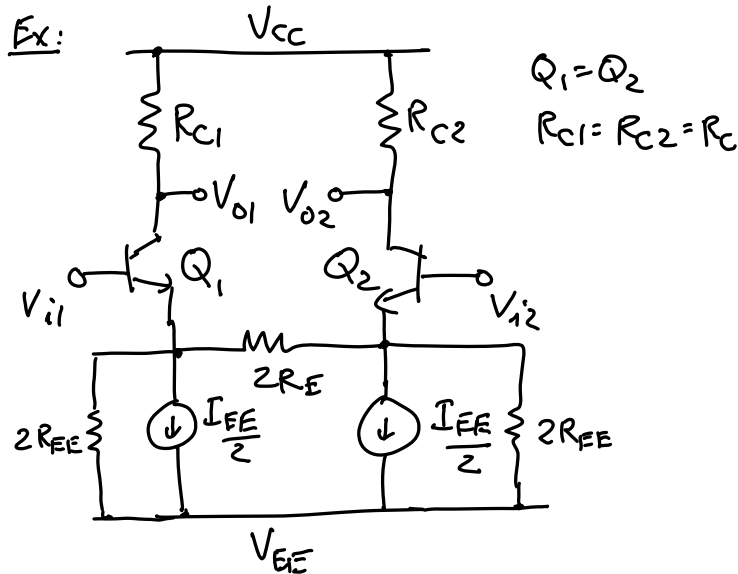• **Last Time:** Started op amp handout; continue this



(1) Find the differential gain (A_{dm})

S.S. Ckt.

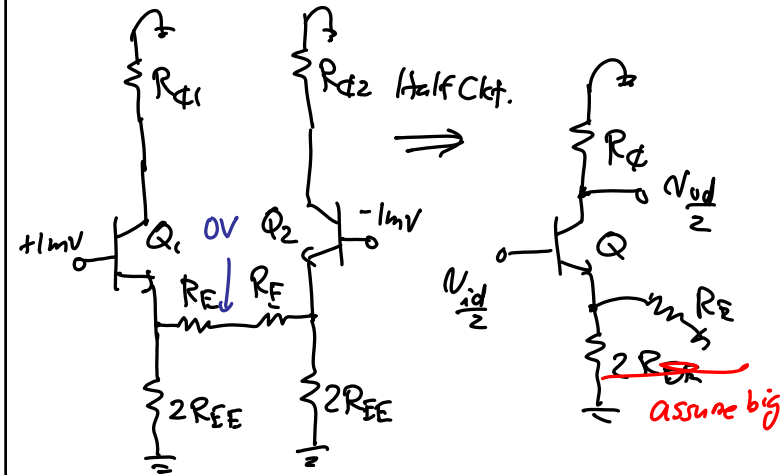

$$\frac{(V_{od}/2)}{(V_{id}/2)} = \frac{-g_m (r_o \parallel (1 + g_m R_E) \parallel R_C)}{1 + g_m R_E}$$

$$A_{dm} = \frac{V_{o1} - V_{o2}}{V_{i1} - V_{i2}} = \frac{V_{od}}{V_{id}}$$