


EE 140

MOS Source-Coupled Pair

CTN

10

MOSFET Source-Coupled Pair

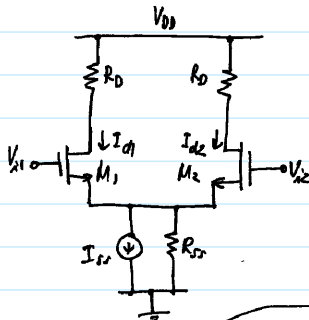

Assume:  $M_1$  &  $M_2$  are identical.

Find  $\Delta I_D = I_{D1} - I_{D2} = f(V_{id})$ .

$\Rightarrow$  approach get  $V_{id} = f(\Delta I_D) \rightarrow$  then invert to get  $\Delta I_D = f(V_{id})$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS1} - V_t)^2 \Rightarrow V_{GS1} = V_t + \sqrt{\frac{2I_{D1}}{k}}$$

$$\therefore V_{id} = V_{GS1} - V_{GS2} = \sqrt{\frac{2I_{D1}}{k}} - \sqrt{\frac{2I_{D2}}{k}}$$

Define:  $\Delta I_D = I_{D1} - I_{D2}$   
 $I_D = \frac{I_{D1} + I_{D2}}{2}$

$$\left. \begin{aligned} I_{D1} &= I_D + \frac{\Delta I_D}{2} \\ I_{D2} &= I_D - \frac{\Delta I_D}{2} \end{aligned} \right\}$$

$$V_{id} = \sqrt{\frac{2(I_D + \frac{\Delta I_D}{2})}{k}} - \sqrt{\frac{2(I_D - \frac{\Delta I_D}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_D + \frac{\Delta I_D}{2} - 2\sqrt{I_D^2 - \left(\frac{\Delta I_D}{2}\right)^2} + I_D - \frac{\Delta I_D}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_D - 2\sqrt{I_D^2 - \left(\frac{\Delta I_D}{2}\right)^2}$$

$\Rightarrow$  Now rearrange to get  $\Delta I_D$  (algebra)

Solve for  $\Delta I_D$ :  $\Delta I_D = \frac{k}{2} V_{id} \left( \frac{2I_{SS}}{k/2} - V_{id}^2 \right)^{1/2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left( \frac{2I_{SS}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_D$

Large signal Equation for Differential Output Current

Valid so long as the devices stay saturated:


$$|V_{id}| \leq \sqrt{\frac{2I_{SS}}{k}} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

$V_{GS}$  for  $I_D = \frac{I_{SS}}{2}$

if true then input devices are both saturated

Thus, to extend the linear input range:

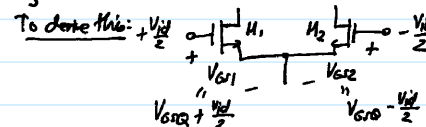- ①  $I_{SS} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ②  $W/L$
- ③  $L \uparrow$



When  $V_{id}/2 \geq V_{GS} - V_t = \Delta V$  then  $M_2$  will cut-off


$\therefore V_{id} \leq 2(V_{GS} - V_t) \rightarrow$  to maintain saturation

$$V_{GS} - V_t = \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_D - \frac{\Delta I_D}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$$

Then plug in  $\Delta I_D$  & solve for  $V_{id}$

EE 140 Diff. Pair w/ Current Mirror Load CTN 11

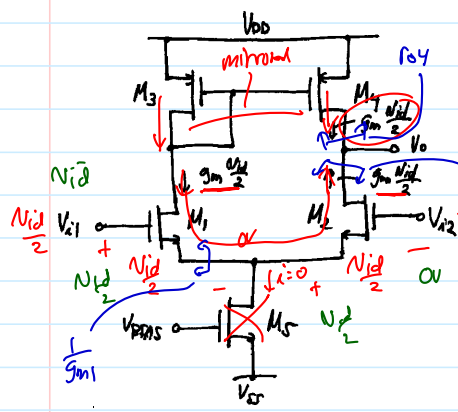MOS Differential Stage w/ Current Mirror Load



$$V_o = \left( \frac{g_{m1}}{2} V_{id} + \frac{g_{m2}}{2} V_{id} \right) R_o = g_m R_o V_{id}$$

$$\Rightarrow \frac{V_o}{V_{id}} = g_m R_o$$

$$R_o = r_{o4} \parallel (2r_{o2})$$


$$r_{o2} \parallel r_{o4}$$

$$r_{o2} (1 + g_{m2} \frac{1}{g_{m1}}) = 2r_{o2}$$

$$\frac{V_o}{V_{id}} = g_m (r_{o2} \parallel r_{o4})$$

*what is R<sub>o</sub>?*  
*From the "writing notes"*  
 $g_m = g_{m1} = g_{m2}$

CMRR-

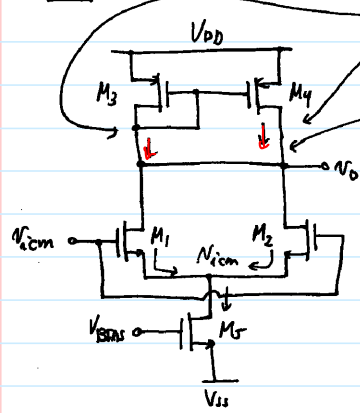

$V_{o3} = V_{o4}$  (they track each other)  
 $\Rightarrow$  Thus, can short the drains of  $M_3$  &  $M_4$

*provided the ckt. is completely symmetrical.*  
*truly symmetric  $\rightarrow$  we can draw a half ckt.*  
*or just combine the two half-ckts. together*

$$A_{cm} = - \frac{2g_{m1,2} \left( \frac{1}{2g_{m3,4}} \right)}{1 + 2g_{m1,2} r_{o5}}$$

$$CMRR = \frac{A_{dm}}{A_{cm}} = g_{m1,2} (r_{o1,2} \parallel r_{o3,4}) (1 + 2g_{m1,2} r_{o5}) \left( \frac{g_{m3,4}}{g_{m1,2}} \right) \rightarrow CMRR = (1 + 2g_{m1,2} r_{o5}) g_{m3,4} (r_{o1,2} \parallel r_{o3,4})$$

*BIG!  $\rightarrow$  Good!*

Thus:

$$CMRR = \frac{A_{dm}}{A_{cm}} = g_{m1,2} (r_{o1,2} \parallel r_{o3,4}) (1 + 2g_{m1,2} r_{o5}) \left( \frac{g_{m3,4}}{g_{m1,2}} \right) \rightarrow CMRR = (1 + 2g_{m1,2} r_{o5}) g_{m3,4} (r_{o1,2} \parallel r_{o3,4})$$

Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep  $M_5$  saturated

$$V_{icm(min)} = CMR^- = V_{S1} + V_{o5} + V_{o5,1,2}$$

$$CMR^- = V_{S1} + \sqrt{\frac{2I_{D5}}{\mu_n C_{ox} (W/L)_5}} + V_{E1,2} + \sqrt{\frac{I_{S1}}{\mu_n C_{ox} (W/L)_{1,2}}}$$


EE 140

Diff. Pair w/ Current Mirror Load

CTN

12

High End - keep  $M_1, M_2$  saturated

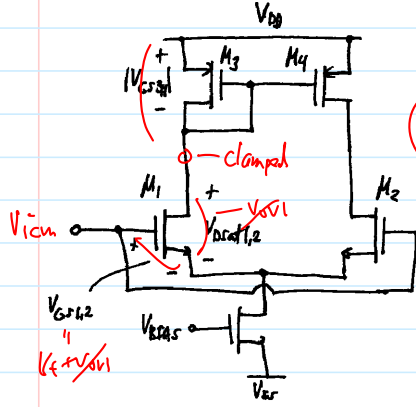

$$V_{icm(max)} = CMR_f = V_{DD} - |V_{GS3,4}| - V_{GS1,2} + V_{GS1,2}$$

$$V_{icm(max)} = CMR_f = V_{DD} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox}(W/L)_{3,4}}} - |V_{GS3,4}| + V_{GS1,2}$$