

Lecture 14: SCP & Current Mirror Load

Announcements:

- ↳ Pre-Lecture materials online
- ↳ HW#1A online for 240A folks; due Friday, Nov. 8 (more than 3 weeks from now)
- ↳ HW#7 online soon
- ↳ Midterm will be on the date specified in your syllabus: Thursday, Oct. 31, 9:00-11 a.m. in this room


??? → now uncertain

Lecture Topics:

- ↳ Emitter Coupled Pair Example
- ↳ Source Coupled Pair
- ↳ Current Mirror Load


Last Time:

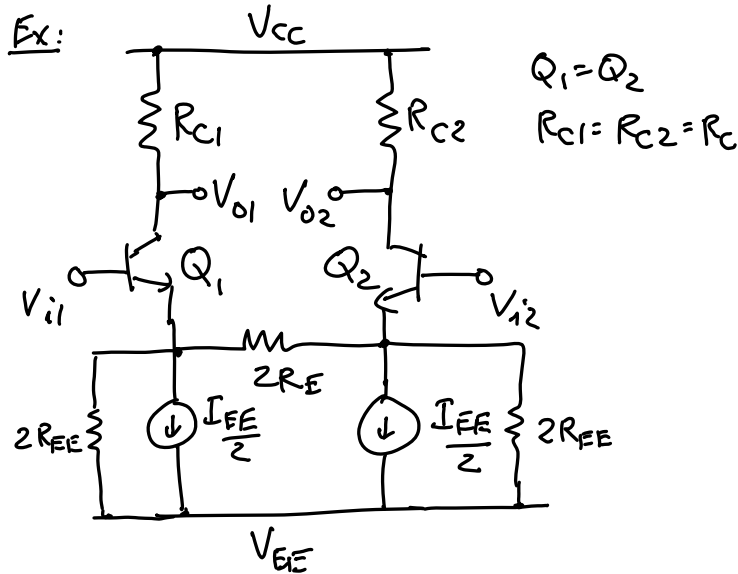- ↳ Going through op amp handout; continue this



(1) Find the differential gain (A_{dm})




S.S. Ckt:

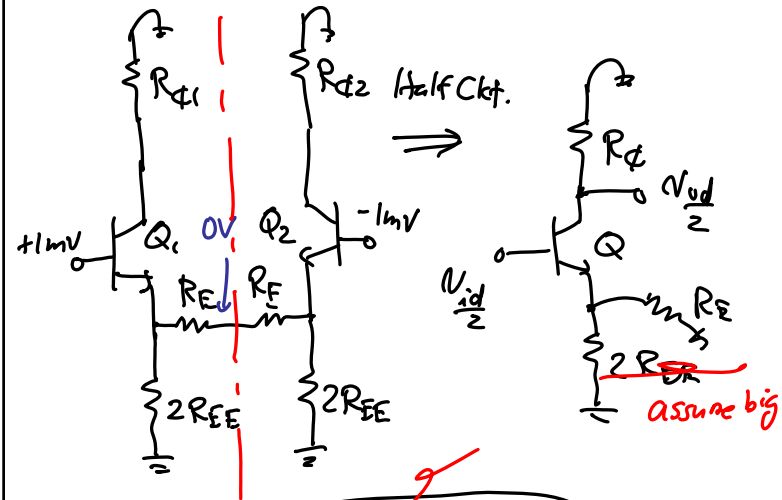

$$\frac{(V_{od}/2)}{(V_{id}/2)} = \frac{g_m (R_C \parallel (1 + g_m R_E))}{1 + g_m R_E}$$

$$A_{dm} = \frac{V_{o1} - V_{o2}}{V_{i1} - V_{i2}} = \frac{V_{od}}{V_{id}}$$

(2) Find the common-mode gain: (A_{cm})

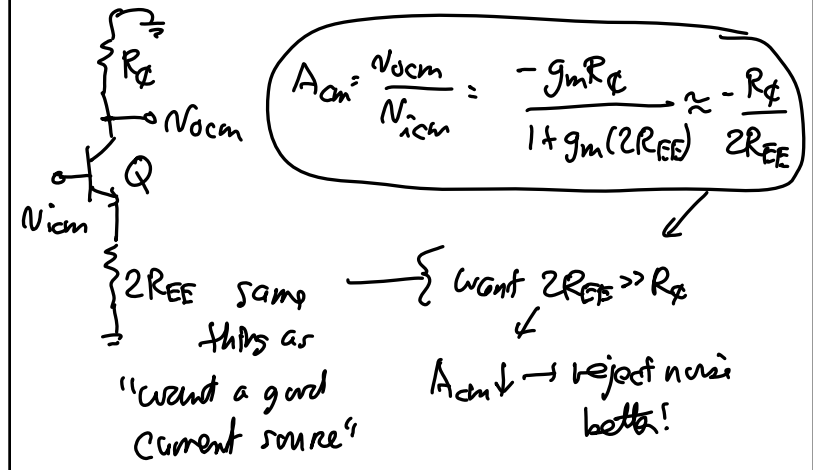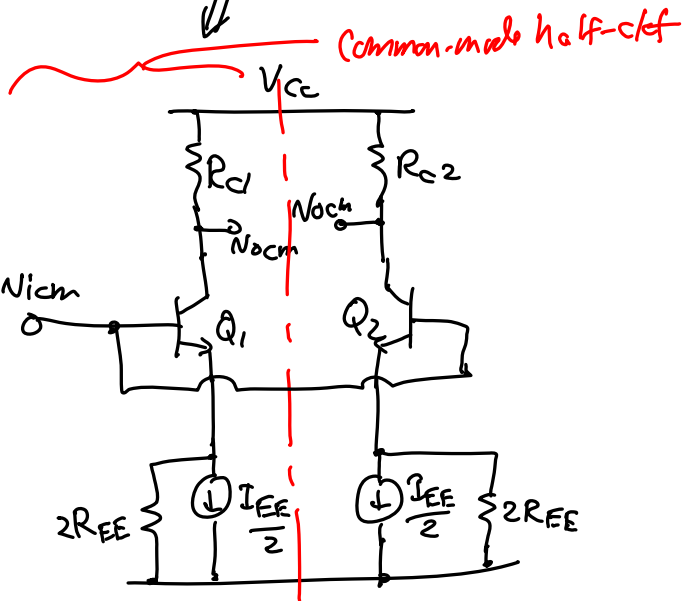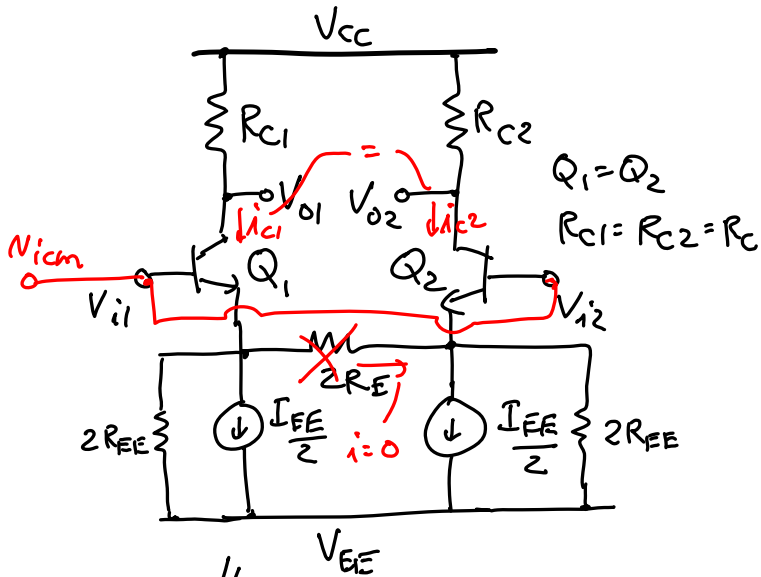

$$A_{cm} = \frac{V_{ocm}}{V_{icm}} = \frac{-g_m R_c}{1 + g_m (2R_{EE})} \approx -\frac{R_c}{2R_{EE}}$$

Want $2R_{EE} \gg R_c$
"Want a good current source"
 $A_{cm} \downarrow \rightarrow$ reject noise better!

If there is a mismatch in the col., e.g., $R_{c1} \neq R_{c2}$, then we can also define:

$$A_{cm-dm} \triangleq \text{Common-mode input to differential-mode output gain} \\ = \frac{V_{od}}{V_{ic}} = \frac{V_{o1} - V_{o2}}{V_{i1}} = \frac{V_{o1} - V_{o2}}{V_{i2}} \quad (\omega / V_{i1} = V_{i2})$$

$$A_{dm-cm} \triangleq \text{differential-mode input to common-mode output gain} \\ = \frac{V_{oc}}{V_{id}} = \frac{V_{oc}}{V_{i1} - V_{i2}} \quad [\omega / V_{oc} = \frac{1}{2}(V_{o1} + V_{o2})]$$

You will be experiencing these in a future trw.

What is R_o ?

Handwritten notes and equations:

- $i_{c2} = \frac{N_x}{2r_{o2}}$
- $i_{c4} = \frac{N_x}{r_{o4}}$
- $i_{ix} = \frac{N_x}{r_{o4}} + \frac{N_x}{2r_{o2}} + \frac{N_x}{2r_{o2}} = \left(\frac{1}{r_{o4}} + \frac{1}{r_{o2}}\right)N_x$
- mirrored (FB)
- $\frac{N_x}{i_{ix}} = R_o = (r_{o2} || r_{o4})$

V_{os} of a Mismatched SCP

Objective: Determine an expression for V_{os} .

Actual Op Amp w/ mismatches

but modeling mismatch via V_{os}

Ideal \rightarrow No mismatches

V_{os} arises due to variations in:

- ① $X_{ratio} = M_1 \cdot M_2 \rightarrow \frac{W}{L} \& V_t$ vary
- ② $R_{01} \neq R_{02} \rightarrow$ cause variations in gain

Definition. $V_{os} = V_{id}$ needed to get $V_{od} = 0V$ in

KVL: $V_{OS} - V_{GS1} + V_{GS2} = 0$

$\therefore V_{OS} = V_{GS1} - V_{GS2}$

$$= V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{OS} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\Delta I_D = I_{D1} - I_{D2} \quad \Delta \left(\frac{W}{L}\right) = \left(\frac{W}{L}\right)_1 - \left(\frac{W}{L}\right)_2$$

$$I_D = \frac{I_{D1} + I_{D2}}{2} \quad \left(\frac{W}{L}\right) = \frac{1}{2} \left[\left(\frac{W}{L}\right)_1 + \left(\frac{W}{L}\right)_2 \right]$$

$$\Delta V_t = V_{t1} - V_{t2} \quad \Delta R_D = R_{D1} - R_{D2}$$

$$V_t = \frac{1}{2}(V_{t1} + V_{t2}) \quad R_D = \frac{1}{2}(R_{D1} + R_{D2})$$

Rearranging:

$$I_{D1} = I_D + \frac{\Delta I_D}{2} \quad \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} \quad V_{t1} = V_t + \frac{\Delta V_t}{2}$$

$$I_{D2} = I_D - \frac{\Delta I_D}{2} \quad \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} \quad V_{t2} = V_t - \frac{\Delta V_t}{2}$$

Substituting into (1): $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta \left(\frac{W}{L}\right) \right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta \left(\frac{W}{L}\right) \right]}}$$

$$\left[V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox}(W/L)}} \right] \cdot \frac{W}{L} \left[1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right]$$

$$= \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

Binomial Theorem:

$$(1+mx)^m \rightarrow 1+mnx$$

$n = \text{small}$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\cancel{1} + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)} - \cancel{1} + \frac{1}{4} \frac{\Delta I_D}{I_D}$$

$$- \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}$$

$$= \Delta V_t + (V_{GS} - V_t) \left(\frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When $V_{id} = V_{os} \rightarrow V_{od} = 0 \therefore I_{D1}R_{D1} = I_{D2}R_{D2}$

↪ mismatch in I_D must be opposite that of R_D

$\therefore \frac{\Delta I_D}{I_D} = - \frac{\Delta R_D}{R_D}$

$$V_{os} = \Delta V_{t} + \frac{1}{2}(V_{GS} - V_{t}) \left\{ - \frac{\Delta R_D}{R_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

Threshold Mismatch
 ↑
 Bias Indep.

Geometric Variations (i.e., layout)
 ↓
 scale c.s. overlap

Again, signs mean nothing as could have

$\frac{\Delta R_D}{R_D} = (-) \quad \& \quad \frac{\Delta(W/L)}{(W/L)} = (-)$

Take the worst case by convention → add everything