

Lecture 15: High Gain Op Amps

• Announcements:

- ↳ Midterm will be on the date specified in your syllabus: Thursday, Oct. 31, 9:00-11 a.m. in this room
- ↳ HW#7 online
- ↳ 240A students should be working on HW#1A, too

• Lecture Topics:

- ↳ Finish offset Voltage (bipolar)
- ↳ Finite Gain BW
- ↳ Effect of FB (a first pass)
- ↳ High Gain Op Amps

• Last Time:


- SCP input offset voltage
- Go through offset voltage handout (skim in lecture, then you should go through it more slowly later)

↻ over

Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$.

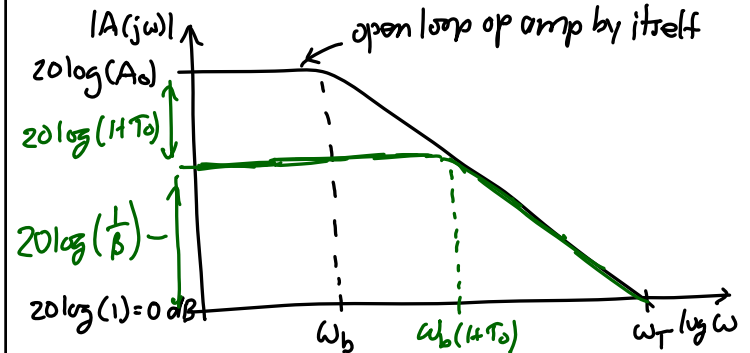In reality, the gain is given by: $A(s) = \frac{A_0}{1 + s/\omega_b}$



$\omega_T \triangleq$ unity gain frequency = freq. @ which $|A(j\omega)| = 1$ (= 0 dB)

At ω_T :

$$|A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_T}{\omega_b}\right)^2}}$$

$$[\omega_T \gg \omega_b] \Rightarrow \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \boxed{\omega_T = A_0 \omega_b}$$

Gain-Bandwidth Product


For $\omega \gg \omega_b$:

$$A(s) \approx \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} = \frac{f_T}{f} \left[\begin{array}{l} \text{Integrate w/ time} \\ \text{Constant } C = \frac{1}{\omega_T} \end{array} \right]$$

The unity gain bandwidth f_T is usually specified on op amp data sheets. Knowing f_T , one can easily determine the op amp gain at a given frequency f .

Frequency Response of Closed Loop Amplifiers

Example. Non-Inverting Amplifier

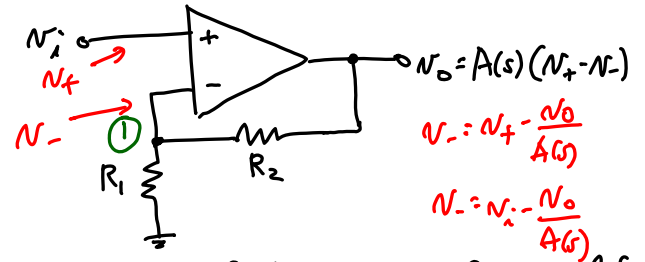

$$V_- = V_+ - \frac{V_o}{A(s)}$$

$$V_- = V_i - \frac{V_o}{A(s)}$$

Find an expression for the gain as a function of frequency.


① Brute force derivation:

$$\text{KCL } \textcircled{1}: \frac{V_o - V_-}{R_2} = \frac{V_-}{R_1} \rightarrow \frac{V_o}{R_2} = V_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\frac{V_o}{R_2} = \left(V_i - \frac{V_o}{A(s)} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{V_o}{V_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$$

$$\left[A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \Rightarrow \frac{V_o}{V_i}(s) = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b} \left(\frac{R_1}{R_1 + R_2} \right)}$$

② More insightful way to do this:

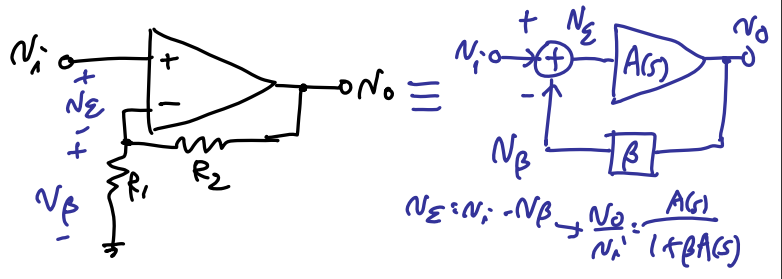


What is \$\beta\$?

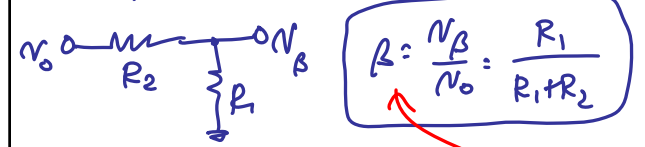

Recall f/ previous FB analysis: feedback factor

$$\frac{V_o}{V_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$
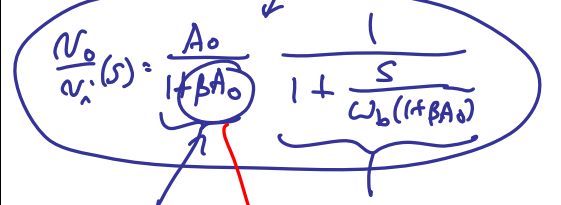
$$\left[A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \rightarrow \frac{V_o}{V_i}(s) = \frac{A_0}{1 + \frac{s}{\omega_b} \left(1 + \beta \frac{A_0}{1 + \frac{s}{\omega_b}} \right)}$$



closed loop dc gain term

frequency shaping term

If \$A_0 \to \infty\$, or if \$\beta A_0 \gg 1 \Rightarrow\$ dc gain = \$\frac{1}{\beta}\$

\$T_0 = \beta A_0 \hat{=} \$ "loop gain" @ \$\omega=0\$ (i.e., @ dc)

Plug in \$\beta\$: [for \$\beta A_0 \gg 1\$]

$$\frac{V_o}{V_i}(s) \cong \frac{1}{\beta} \frac{1}{1 + \frac{s}{\omega_b \beta A_0}} = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{\omega_b A_0} \left(\frac{R_1}{R_1 + R_2} \right)}$$

Observations:


- ① Closed loop DC gain = $\frac{A_o}{1+\beta A_o} = \frac{A_o}{1+T_o} \approx \frac{A_o}{T_o}$
 i.e., the closed loop gain is reduced from the open loop gain by $1+T_o \rightarrow$ show this on graph [$T_o \gg 1$]
- ② Alternatively, closed loop DC gain $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta}$ [$T_o \gg 1$]
- ③ ω_{-3dB} has increased from $\omega_b \rightarrow \omega_b(1+A_o\beta) = \omega_b(1+T_o)$
 To draw the Bode plot, just find the dc gain, draw a horizontal line across, then follow the open loop response after running into it!
- ④ Gain-BW Product = $\frac{A_o}{1+\beta A_o} \omega_b(1+\beta A_o) = A_o \omega_b = \omega_T$
 \therefore the Gain-BW product remains the same for the open & closed loop FB cases!

High Gain Op Amps

How can we increase gain?

- ① Cascode
- ② Cascode Amplifier

Telescopic Op Amp w/ Single-Ended Output

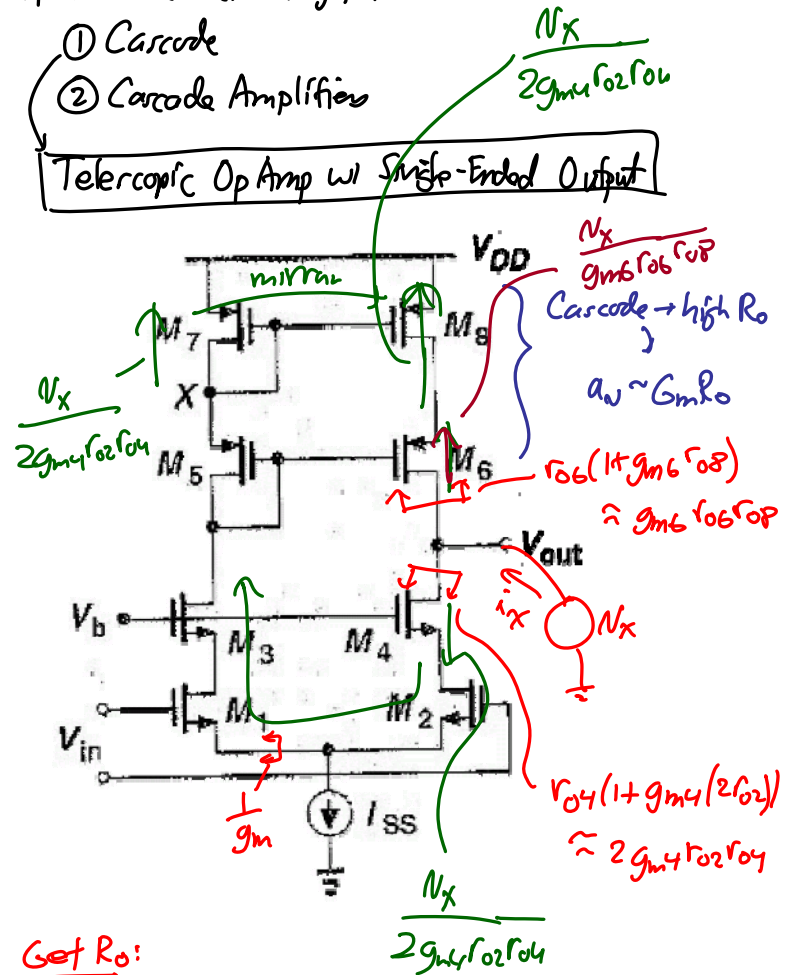

Get R_o :

$$i_{ix} = \frac{N_x}{g_{m6} r_{o6} r_{oP}} + \frac{N_x}{2g_{m4} r_{o2} r_{o4}} + \frac{N_x}{2g_{m4} r_{o2} r_{o4}}$$

$$R_o = \frac{V_x}{i_x} = (g_{m6} r_{o6} r_{o8}) \parallel (g_{m4} r_{o2} r_{o4})$$

$$= (g_{m6} r_{op}^2) \parallel (g_{m4} r_{on}^2)$$

Get Gm!

$$i_o = g_m \frac{V_{in}}{2} + g_m \frac{V_{in}}{2} \Rightarrow G_m = \frac{i_o}{V_{in}} = g_m$$

$$\therefore \text{Gain} \cdot A_v = g_{mN} \left[(g_{mN} r_{on}^2) \parallel (g_{mP} r_{op}^2) \right]$$

$$\text{gain will be } \underline{\underline{BIG!}}$$

Freq. Response:

$$\omega_H = \frac{1}{R_o C_L}$$

Problem/Issues:

① Limited output swing:

$$V_{omax} = V_{DD} - |V_{E7}| - |V_{ov7}| - |V_{E5}| - |V_{ov5}| + |V_{E6}| + |V_{ov6}| - |V_{ov6}|$$

$$V_{omin} = V_{ovSS} + V_{ov2} + V_{ov4}$$

$$V_{swing} = V_{omax} - V_{omin}$$

Problem: Not so large!

