

Lecture 16: High Gain Op Amps II

Announcements:

- ↪ Midterm will be on the date specified in your syllabus: Thursday, Oct. 31, 9:00-11 a.m. in this room
- ↪ HW#7 due tomorrow at 8 a.m.
- ↪ HW#8 online
 - due next Tuesday, 5 p.m., so we can get solutions up
- ↪ 240A students should be working on HW#1A, too

Lecture Topics:



- ↪ Telescopic Op Amp in Feedback
- ↪ Lab#2 Hints
- ↪ Compensation (a 1st pass)
- ↪ Slew Rate (a 1st pass)

Last Time:

- Telescopic op amps

over

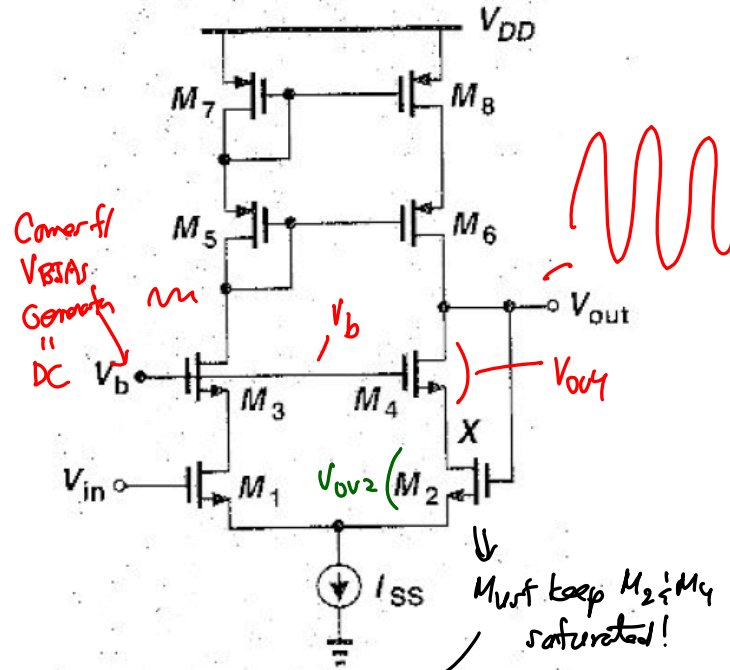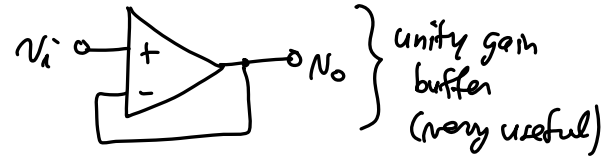Problem 2: Difficult to tie the Input to output!



M4: Need $V_{out} \geq V_b - V_{GS4} + V_{OV4} = V_b - V_{t4} - V_{OV4} + V_{OV4}$

$\therefore V_{out} \geq V_b - V_{t4} \leftarrow V_{omn}$

M2: Need $V_{out} \leq V_x - V_{OV2} + V_{t2} + V_{OV2}$

$V_{out} \leq V_b - V_{t4} - V_{OV4} + V_{t2} \approx V_b - V_{OV4} \leftarrow V_{omx}$
 $V_{t2} \approx V_{t4}$

V_b
 $V_{out_{max}}$
 $V_{t4} \sim 0.8V$
 $V_{out_{min}} = V_b - V_{t4}$
 $\sim 0.6V$
 permissible range of output voltage
 & very small \rightarrow major problem!

Problem ③:

$|A|$
 ω_{p1}
 ω_{p2}
 $\log \omega$
 want this large
 because this won't be so large

Low freq. non-dominant pole associated w/ the "mirror" node \rightarrow hurt stability in FB ckt.

\downarrow

Sols: fully differential, fully balanced op amp

Another Soln: 2-stage op amp

\hookrightarrow over

Classic 2-Stage Op Amp

V_{DD}
 V_{SS}
 $M_1, M_2, M_3, M_4, M_5, M_6, M_7$
 C_c
 v_o

Gain:

1st stage: $A_{N1} = \frac{V_{o1}}{v_i} = -g_{m2}(r_{o2} || r_{o4})$



2nd stage: $A_{N2} = \frac{V_o}{v_{o1}} = -g_{m6}(r_{o6} || r_{o7})$

$A_N = A_{N1} A_{N2} = g_{m2}(r_{o2} || r_{o4}) g_{m6}(r_{o6} || r_{o7})$

Output Swing: $V_{oswing} = V_{DD} - V_{SS} - |V_{ovs1}| - |V_{ov7}|$

Dominant Pole:


$\omega_{p1} = \omega_{H1} = \frac{1}{(r_{o2} || r_{o4})(1 + g_{m6}(r_{o6} || r_{o7}))C_c}$
 Miller Effect

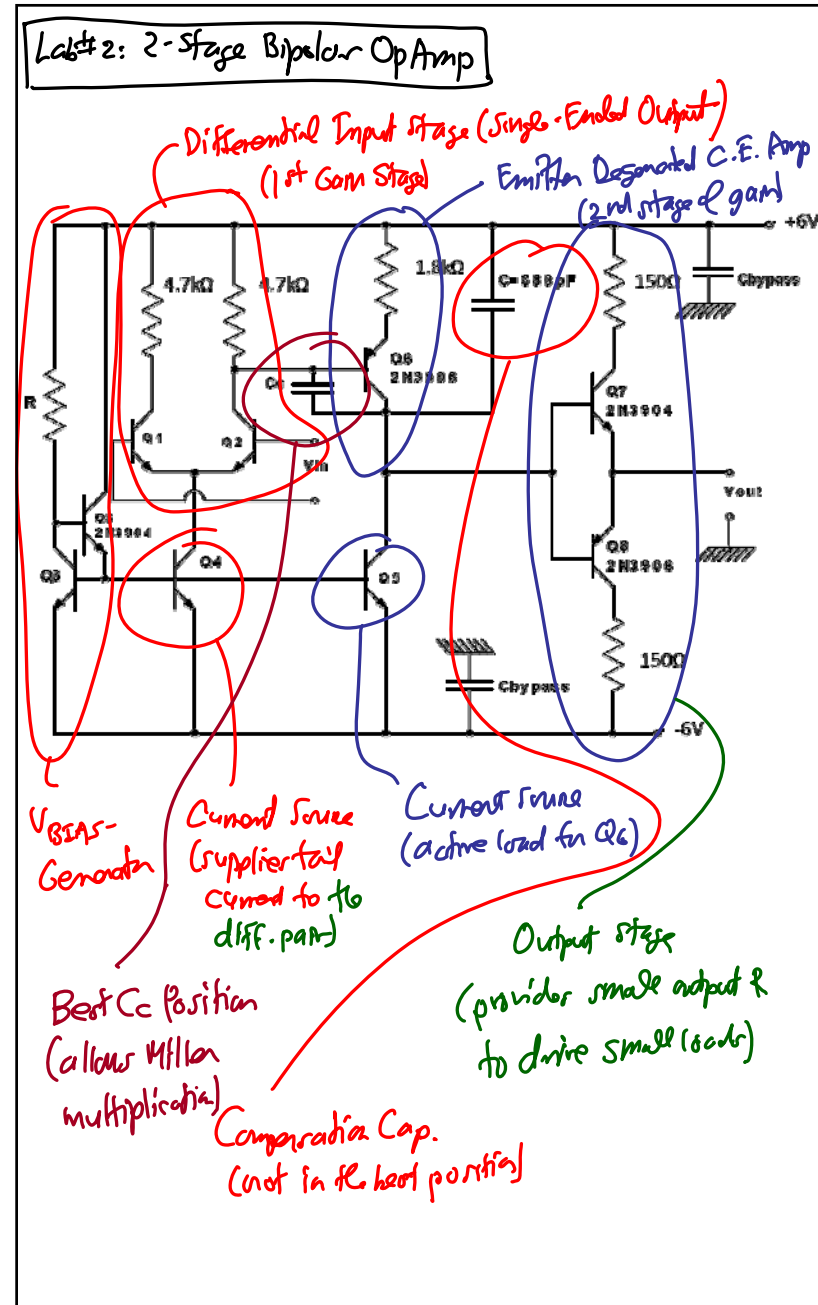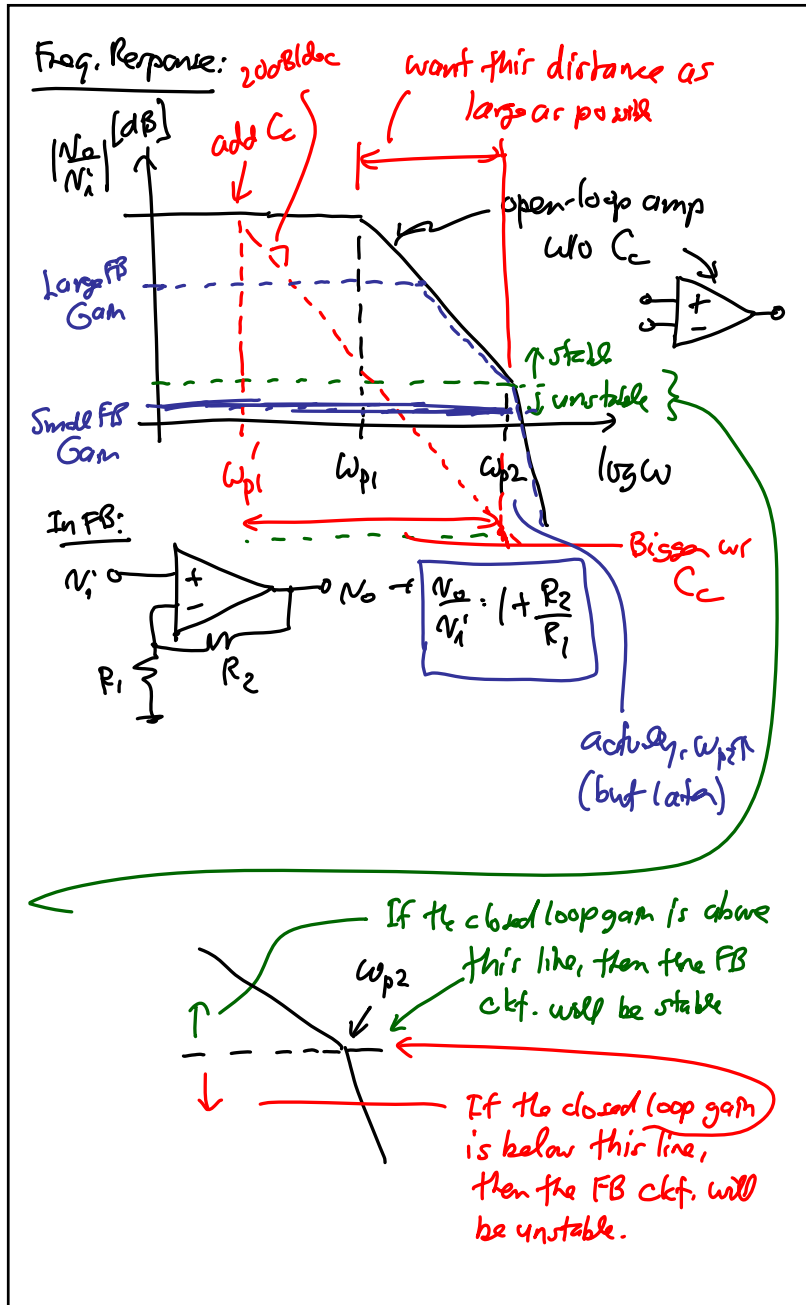

Remarks.


- ① You analyze this in Lab#2.
- ② Usually, the resistively-loaded diff. pair is replaced w/ an active current mirror load for more gain.
- ③ R_{E6} raises the input R of Q_6 (of the 2nd gain stage), plus helps w/ biasing.
- ④ Same comment as ③ for the output stage.
- ⑤ Output stage needed when driving a resistive load

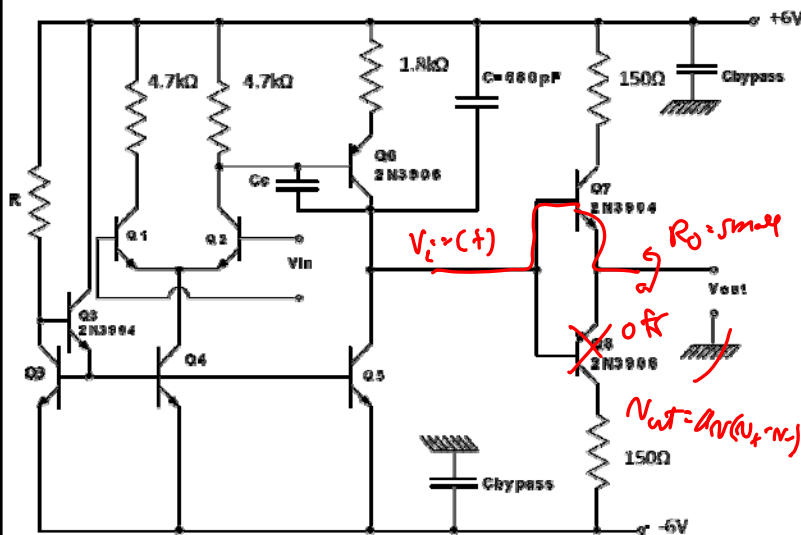↳ often the case for bipolar
↳ not often the case for MOS, where a capacitive load C_L is often more relevant → MOS op amps often don't need output stages!




How Do we Use Op Amps?

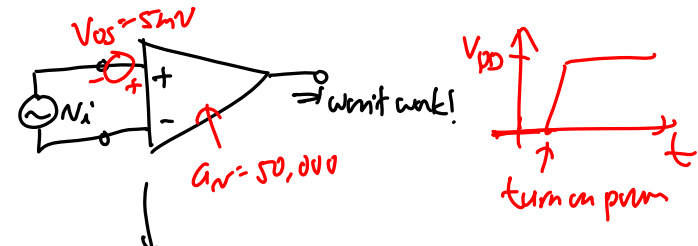(to answer a question regarding how we set V_o to a specific DC value)



Soln: feedback

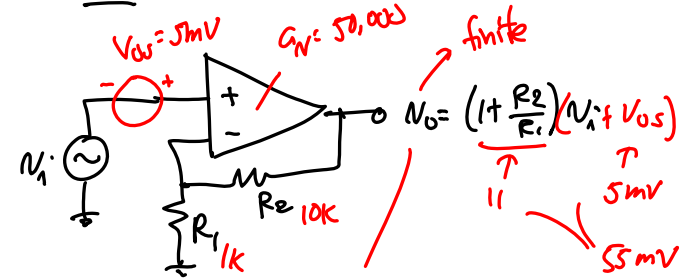

$$V_o = \left(1 + \frac{R_2}{R_1}\right) (N_i + V_{os})$$

\downarrow \uparrow \downarrow \uparrow
 ∞ 0 $5mV$ $5mV$

$= A_v (v_+ - v_-)$
 \downarrow \uparrow
 ∞ 0 ⇒ these must be the case for $v_o = \text{finite}$

- So basically, one can use feedback to set the output voltage of the op amp to a well-defined value
- When you're given a problem that says "assume $V_o = 1V$ ", then this is actually often achieved by just hooking the circuit into a feedback loop that sets this voltage

Comparison for Your Lab #2

Compensation Cap.

Replace w/ C_c to give the same freq. response.

- In your lab, determine the pole generated when $C=680pF$ is present, then remove C and insert a C_c of value that generates the same pole
- These capacitors are compensating the op amp - moving its first and second poles apart to insure stability over a larger range of closed loop gains
- We will learn more about this in much more detail a few weeks from now

Steady State

Using Laplace Xform Theory:

$$\frac{V_o}{V_i}(s) = \frac{1}{1 + \frac{s}{\omega_1}} = \frac{1}{1 + s\tau_1}$$

single (dominant) pole

$$V_i(s) = \frac{V_A}{s}$$

$$V_o(s) = \frac{V_A}{s(1 + s\tau_1)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_1}}$$

↑ Inverse Laplace Xform

$$V_o(t) = V_A(1 - e^{-t/\tau_1}) \leftarrow \text{expected response}$$

$\left| \frac{V_o}{V_i} \right| [dB]$

open loop op amp

0dB

ω_1

$\log \omega$

Theoretical Expectation

Reality Why?

