

Lecture 17: Slew Rate & Output Stages

• **Announcements:**

- ↳ Midterm Thursday, Oct. 31, 9:00-11 a.m. in this room
- ↳ Midterm info sheet online
- ↳ Solutions to past EE140/240A exams also passed out in class
- ↳ Solutions to all HW's through HW#7 online (except 1A)
- ↳ Solution to HW#8 will be emailed on Tuesday, shortly after it's due at 6 p.m. (it will also be online within a day)
- ↳ Discussion sections turn into office hours next week
- ↳ Review Session on Tuesday evening, probably 5-7 p.m., in a room TBD

• **Lecture Topics:**



- ↳ Midterm Info Sheet
- ↳ Finish 1st Pass Slew Rate
- ↳ Output Stages

• **Last Time:**

- Started slew rate



Slew Rate

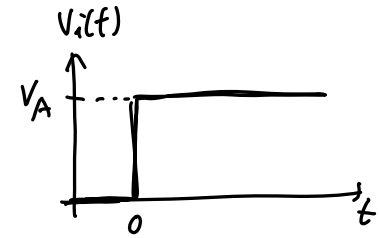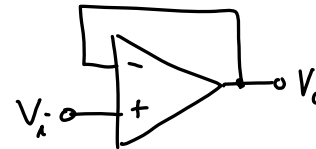

Using Laplace Xform Theory:

$$\frac{V_o}{V_i}(s) = \frac{1}{1 + \frac{s}{\omega_1}} = \frac{1}{1 + s\tau_1}$$

↳ single (dominant) pole



$$V_i(s) = \frac{V_A}{s}$$

$$V_o(s) = \frac{V_A}{s(1 + s\tau_1)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_1}}$$


↳ Inverse Laplace Xform

$$V_o(t) = V_A(1 - e^{-t/\tau_1}) \leftarrow \text{expected response}$$


$\left| \frac{V_o}{V_i} \right| \text{ [dB]}$

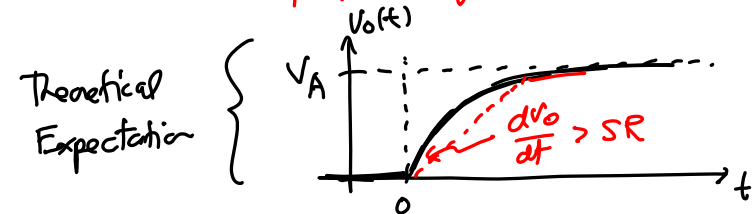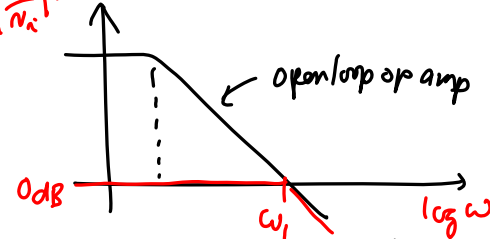



Reality Why?

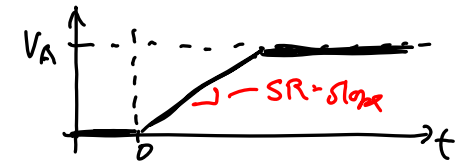

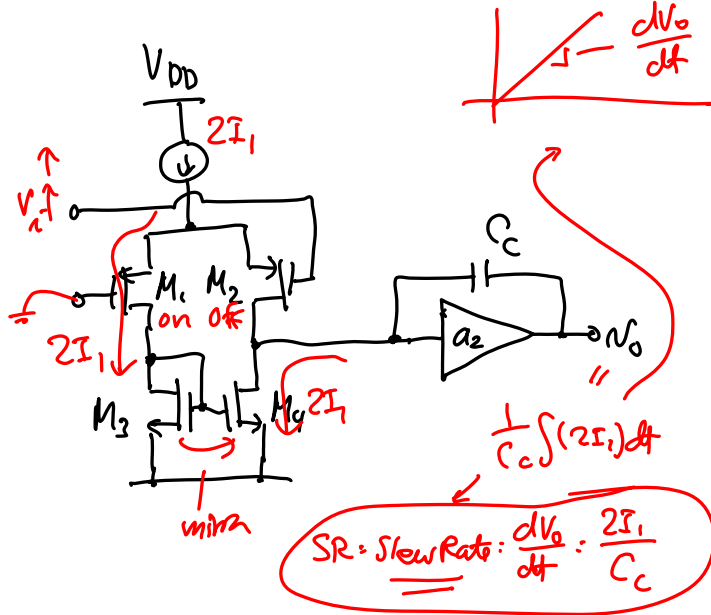Reason: 1st & 2nd stages of op amp cannot source enough current to mimic the slope (or speed) of a fast rising theoretical output waveform



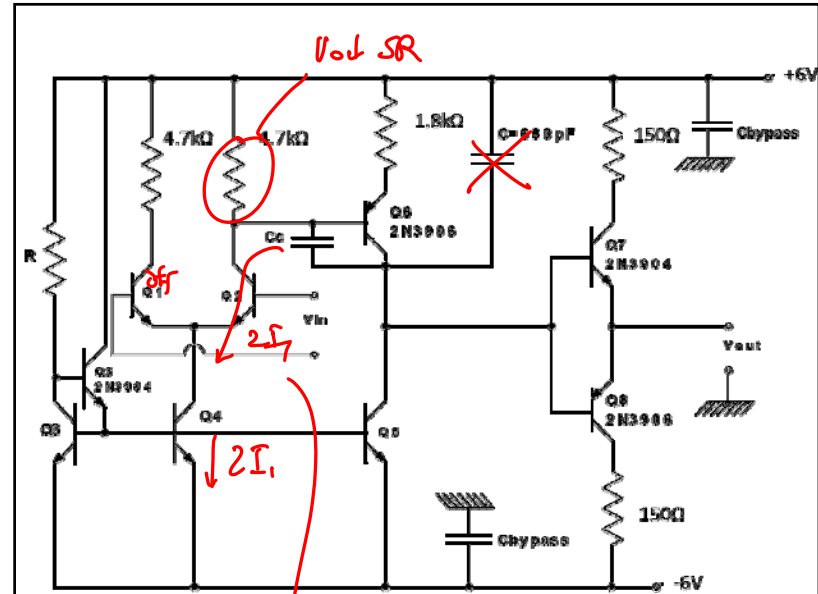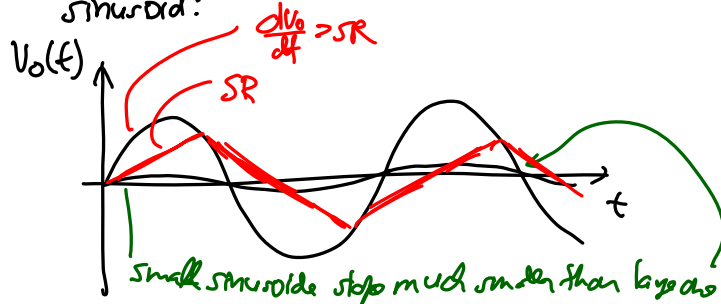
Ex. Apply a very fast (i.e., high freq., large amplitude) sinusoid:



These are (1)-going
& (-) going s/r's.

Determine V_{out} SR

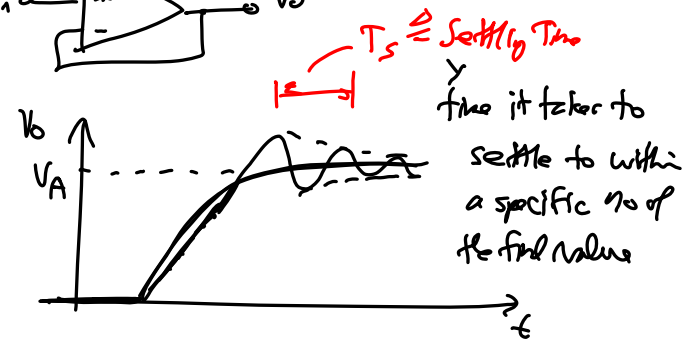Settling Time → determined by stability & slew



Output Stages


- Class A (Emitter or Source Follower)
- Class B
- Class AB (we'll do this one later)

Purpose: Drive loads


- ① Deliver power w/ small distortion.
- ② Minimize output impedance \rightarrow so that the amplifier gain is insensitive to the load.

Desirable Attributes:

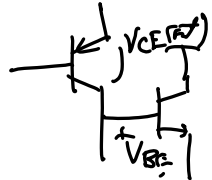- ① High R_{in} ; Low R_{out} .
- ② low quiescent power.
- ③ Minimal effect on the amplifier freq. response.
- ④ Should be able to handle large input/output swings. (i.e., V_i may be $> V_T$, invalidating small-signal approximations)



Emitter Follower (Class A)

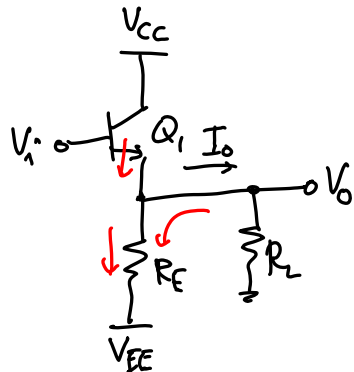

Two main cases: $V_o > 0$

- ① $I_o > 0$: I_o comes fr Q_1
 \Rightarrow adequate I_o can be delivered so long as Q_1 stays forward-active


② $I_o < 0$: ($V_o < 0$)

I_o must be sunk through R_E to V_{EE} .

$$I_o = \frac{V_o - V_{EE}}{R_E} \Rightarrow \text{issue: } I_o = f(V_o)$$

\hookrightarrow | I_{q1} or V_{o1} \rightarrow Problem!

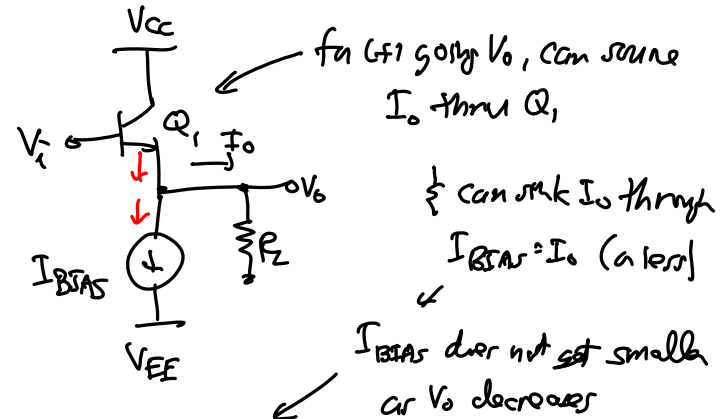
Solution: Replace R_E w/ a current source:



$I_{BIAS} = I_o$ (at least)
 \hookrightarrow I_{BIAS} does not get smaller as V_o decreases

\therefore can maintain drive power as V_o Δ 's!

Actual Implementation:

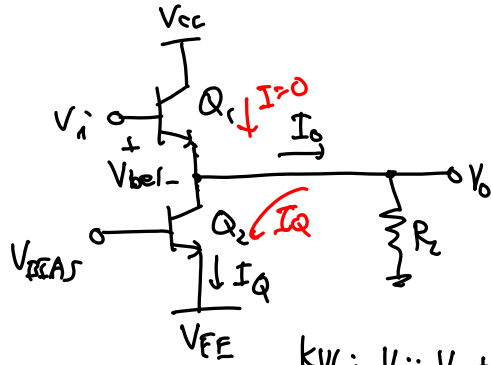


KVL: $V_{i1} = V_o + V_{be1} \approx V_o + V_{BE1}$

More Accurate:

$V_{be1} \neq \text{const.} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$ (Q_1 in F.A.R.)

$I_{C1} = I_Q + I_o = I_Q + \frac{V_o}{R_L}$

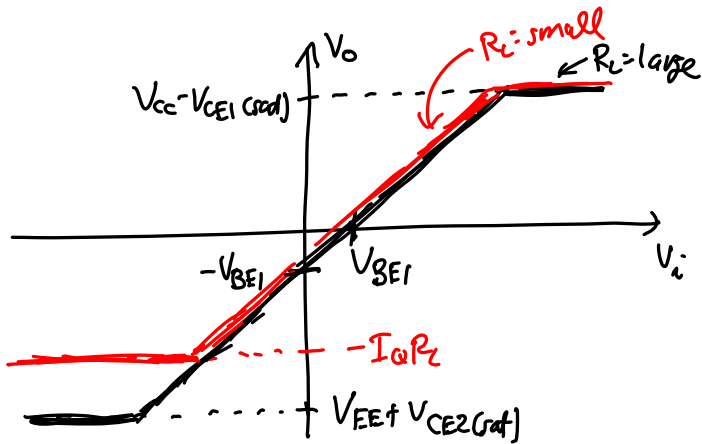$\therefore V_{i1} = V_o + V_T \ln\left(\frac{I_Q + V_o/R_L}{I_{S1}}\right)$ \rightarrow for large power



Two Cases: (depending on the size of R_L)

Case 1: $R_L = \text{large} \rightarrow I_o \text{ small} \rightarrow I_o < I_{C1}$

$\Rightarrow I_o$ not Δ 'ing much $\rightarrow I_{C1}$ not Δ 'ing much

For $V_{i1} = \text{large and } (+)$: Q_1 must source $I_o + I_Q$

$V_o = V_{i1} - V_{BE1}$

@ some pt., Q_1 saturates as $V_o \uparrow$

\rightarrow Get $V_{omax} = V_{CC} - V_{CE1(sat)}$

$\rightarrow V_{i1} = V_{CC} - V_{CE1(sat)} + V_{BE1} > V_{CC}$
0.2V 0.7V \rightarrow

For $V_{i1} = \text{large and } (-)$: V_o follow V_{i1} until Q_2 saturates

$V_{omin} = V_{EE} + V_{CE2(sat)}$

$\rightarrow V_{i1} = V_o + V_{BE1} = V_{EE} + V_{CE2(sat)} + V_{BE1}$

Case 2: $R_L = \text{small} \rightarrow$ thru, I_o can be large!

For $V_{i1} = (+)$ and large: Q_1 can source as much current as needed until it saturates or it fries

For $V_{i1} = (-)$ and large: $V_o = I_o R_L \rightarrow \text{min } V_o = -I_Q R_L$

$\Rightarrow Q_1$ cut-off ($I_{C1} = 0$) \rightarrow further decrease in V_{i1}
 $\Rightarrow V_o$ clamps @ $-I_Q R_L$ yields no ΔV_o


If must drive $R_L = \text{small} \rightarrow$ need large I_Q

Problem: too much power consumption

$P_Q = (V_{CC} - V_{EE}) I_Q \rightarrow$ DC quiescent power consumption

If want large output swing w/ small $R_L \rightarrow$ must consume power!

Solution: **Class B Output Stage**


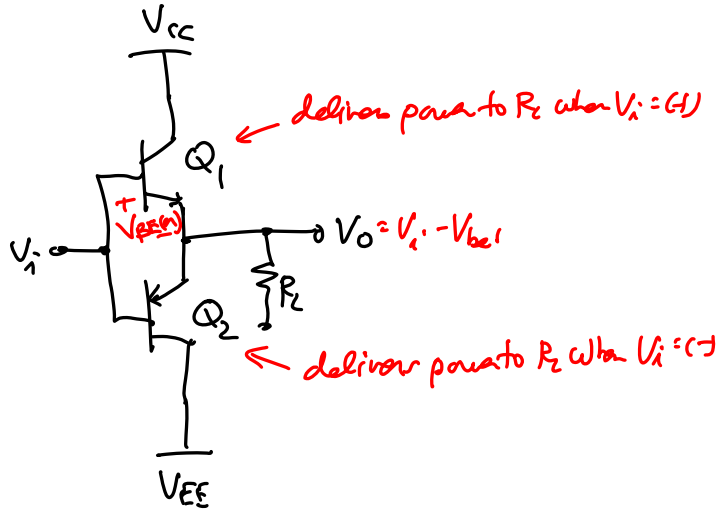


Operation: $Q_1 \text{ \& } Q_2$ are cut-off

$|V_i| < V_{BE(on)} \rightarrow I_{E1} = I_{E2} = 0 \rightarrow V_o = 0V$


$V_{CC} > (V_i) > V_{BE(on)} \rightarrow V_o \cong V_i - V_{BE(on)}$

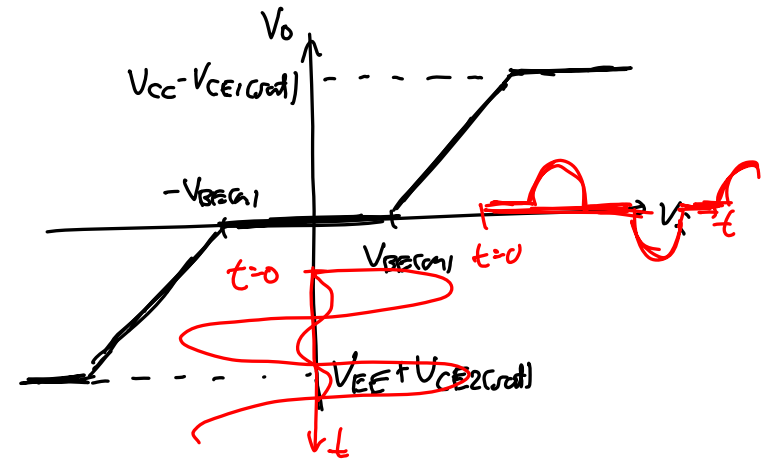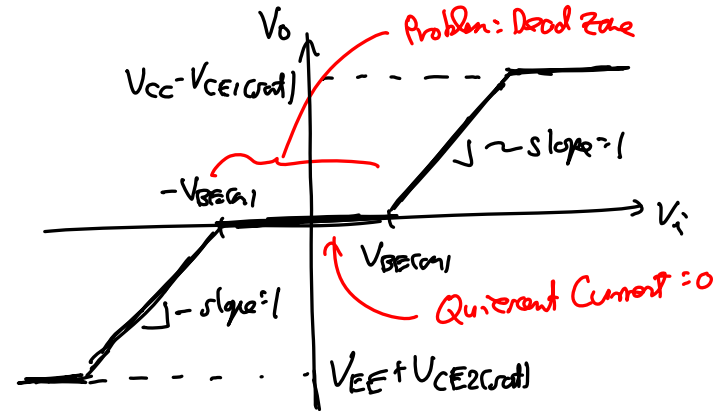$V_{omax} = V_{CC} - V_{CE1(sat)}, V_{omin} = V_{EE} + V_{CE2(sat)}$



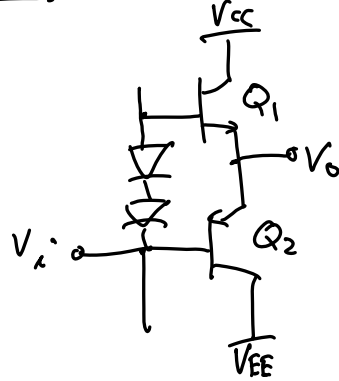Problem: Distorted output due to the dead zone.

Solution: Class AB clst. → use diodes to supply enough voltage to keep Q_1 & Q_2 on



⇒ you will see this on a future HW