

Lecture 1: Admin & Overview


- **Announcements:**
- **EE 140/240A: Analog Integrated Circuits**
- **Instructor:** Prof. Clark T.-C. Nguyen
- -----
- **Go though**
 - ↳ **Course information sheet**
 - ↳ **Syllabus**
 - ↳ **Grading Information and Policy**
- **Hand out class account sheets**
- **About Me:**
- **Education:** Ph.D., University of California at Berkeley, 1994
- **1995:** joined the faculty of the Dept. of EECS at the University of Michigan
- **2006:** (came back) joined the faculty of the Dept. of EECS at UC Berkeley
- **Research:** microelectromechanical systems (MEMS) that employ transistor-level circuit design
- **Teaching:** (at the UofM) mainly transistor circuit design courses; (UC Berkeley) 140, 143, 240A, 243, 245
- **2001:** founded Discera, the first company to commercialize vibrating RF MEMS technology
- **Mid-2002 to 2005:** DARPA MEMS program manager
 - ↳ ran 10 different MEMS-based programs
 - ↳ **topics:** power generation, chip-scale atomic clock, gas analyzers, nuclear power sources, navigation-grade gyros, on-chip cooling, micro environmental control
- -----

- For the course website, just google ee140
 - ↳ The website is already up and running
- This course will be screencast
 - ↳ EE 140 screencast previously, so you can actually view previous year lectures, too
 - ↳ If you miss a lecture ...
 - ↳ Can view lectures at either <http://itunes.berkeley.edu/> or <http://www.youtube.com/ucberkeley>
 - ↳ **Warning:** It's a very bad idea not to come to lecture in person
 - ↳ People who think they will watch the videos, often don't get time to do so
- This course now "contains" EE 240A
 - ↳ EE 240A same as 140, but with additional material for graduate students, mainly MEng
 - ↳ Additional homework problems
 - ↳ Additional project specs or a different project altogether
- **Office Hour Changes?:**
- Discussion sections start next week
 - ↳ Need to change the M 3-4 discussion
 - ↳ Can we do M 5-6? F 4-5 possible
- -----
- **Lecture Topics:**
 - ↳ **Review**
 - Op Amp Examples
 - Ideal Op Amps
 - Non-Ideal Op Amps
- -----

- Look at op amp usage examples using prepared pages

Review of Ideal Op Amps

Ideal Op Amp:

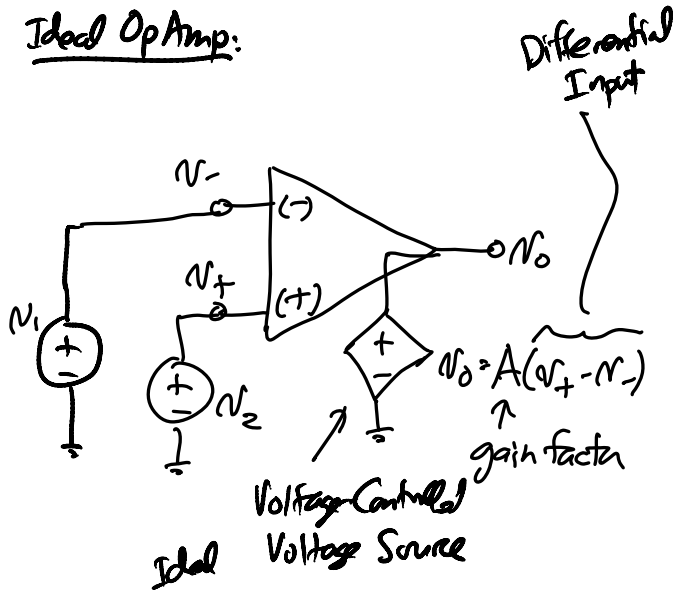


Properties of Op Amps:

- $A = \infty \rightarrow V_+ = V_-$ (provided there is neg. FB!)
- $R_o = 0 \Omega$
- $R_i = \infty \rightarrow i_+ = i_- = 0$
- Infinite BW


$$V_o = A(V_+ - V_-)$$

↑ ↑ ↓
finite ∞ 0

Inverting Amplifier (Example)

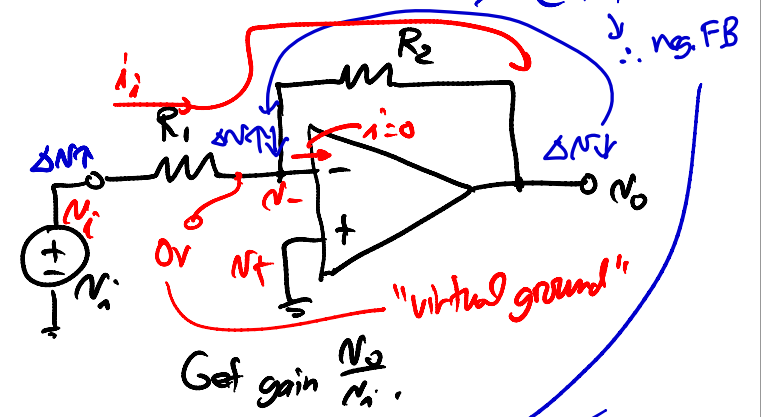

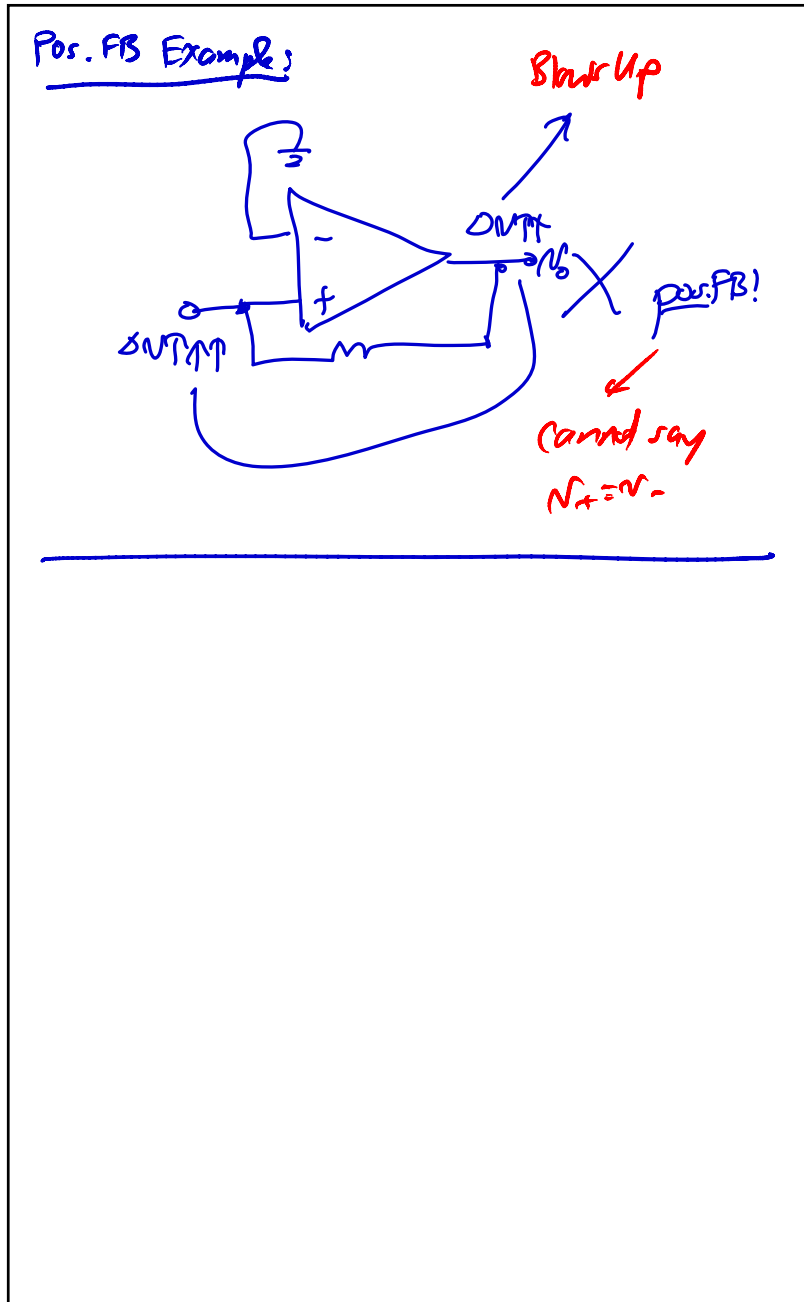- Verify that we have neg. FB
- so $V_o = \text{finite} \rightarrow V_+ = V_-$
 $i_- = \frac{V_i - 0}{R_i} = \frac{V_i}{R_i}$ $V_o = 0 - i_- R_f$
 $V_o = -\left(\frac{V_i}{R_i}\right) R_f \rightarrow \frac{V_o}{V_i} = -\frac{R_f}{R_i}$



- Non-Ideal Op Amps:
- Actual op amps, of course, are not ideal; rather, they ...
 - ↔ Have finite gain, A_o
 - ↔ Have finite bandwidth, BW
 - ↔ Have finite input resistance, R_i
 - ↔ Have finite input capacitance, C_i
 - ↔ Have finite output resistance, R_o
 - ↔ Generates noise
 - ↔ Have input bias currents (because R_i is not infinite)
 - ↔ Have input offset currents and voltages
 - ↔ Have finite slew rate
 - ↔ Have finite output swing
- All of the above can be temperature dependent!
- A major objective of this class is understand what gives rise to the above non-idealities and to teach design strategies to get around them

- Then, start going through the Device Modeling Handout, on BJT modeling