
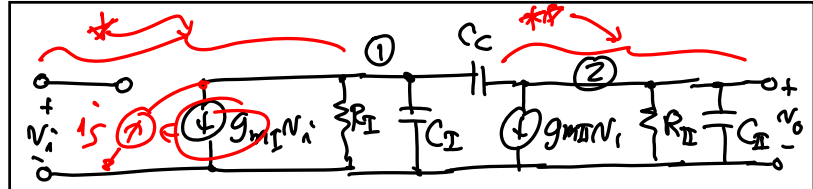


Lecture 21: CMOS Op Amp Compensation

- Announcements:
- Design Project Checkpoint:
 - ↳ Due Tuesday, Nov. 19, 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (except MOS R's)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
- HW#9 due tomorrow at 8 a.m.
- HW#10 online soon
- Lecture Topics:
 - ↳ Practical CMOS Op Amp Compensation
 - ↳ Review of Pole-Zero Plots
 - ↳ Nulling the RHP Zero

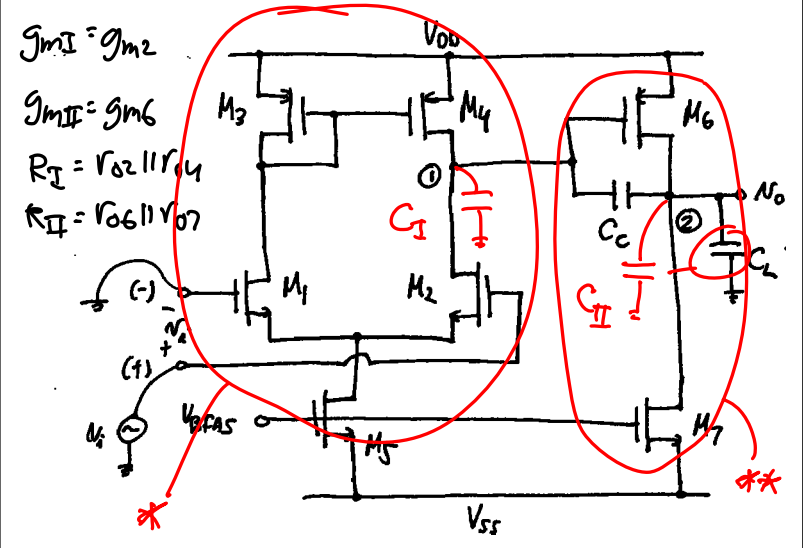--- Last Time: CMOS 2-Stage Op Amp Compensation



KCL①: $i_s = \frac{V_i}{R_I} + sC_{I}V_i + (V_i - V_o)sC_c$

KCL②: $g_{mII}V_i + \frac{V_o}{R_{II}} + sC_{II}V_o + (V_o - V_i)sC_c = 0$

$\frac{V_o}{i_s} = \frac{(g_{mII} - sC_c)R_I R_{II} \leftarrow N(s)}{1 + s[(C_{II} + C_c)R_{II} + (C_I + C_c)R_I + g_{mII}R_I R_{II} C_c] + s^2 R_I R_{II} (C_I C_{II} + C_c C_I + C_c C_{II})}$

$\frac{V_o}{i_s}(s) = \frac{N(s)}{D(s)} \rightarrow$ This Xfer fun has 2 poles & one zero.

The zero: $N(s) = 0 \rightarrow z = \frac{g_{mII}}{C_c}$ $\leftarrow (+) \hat{=} \text{real}$
 $z = s$ \uparrow
 RHP in the complex plane

The Poles:
 $D(s) = (1 - \frac{s}{p_1})(1 - \frac{s}{p_2}) = 1 - s(\frac{1}{p_1} + \frac{1}{p_2}) + \frac{s^2}{p_1 p_2}$
 $[p_2 \gg p_1] \rightarrow \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$ $\leftarrow \text{complex}$
 \uparrow
 i.e., there is a dominant pole

Thus:

$$P_1 = \frac{1}{(C_I + C_C)R_{II} + (C_I + C_C)R_I + g_{mII}R_I R_{II} C_C}$$

as $C_C \uparrow \rightarrow |P_1| \downarrow$ (pole-splitting) ↑ Miller multiplied term \Rightarrow offset

$$P_1 \approx -\frac{1}{g_{mII}R_I R_{II} C_C}$$

For the 2nd pole:


$$P_2 = \frac{1}{R_I R_{II} (C_I C_{II} + C_C C_I + C_C C_{II})}$$

$$P_2 = -\frac{g_{mII} C_C}{C_I C_{II} + C_C C_I + C_C C_{II}} \rightarrow P_2 \approx -\frac{g_{mII}}{C_I + C_{II}}$$

as $C_C \uparrow \rightarrow |P_2| \uparrow$ $C_C \rightarrow \infty$

ω_2 by Inspection When $C_C = \text{big}$, @ high freq. (around ω_2), it becomes a short


M6 becomes "diode-connected"

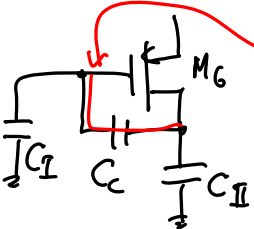

$$\omega_2 = \frac{1}{C} = \frac{1}{\left(\frac{1}{g_{m6}}\right)(C_I + C_{II})} = \frac{g_{mII}}{C_I + C_{II}} \checkmark$$

$= g_{mII}$

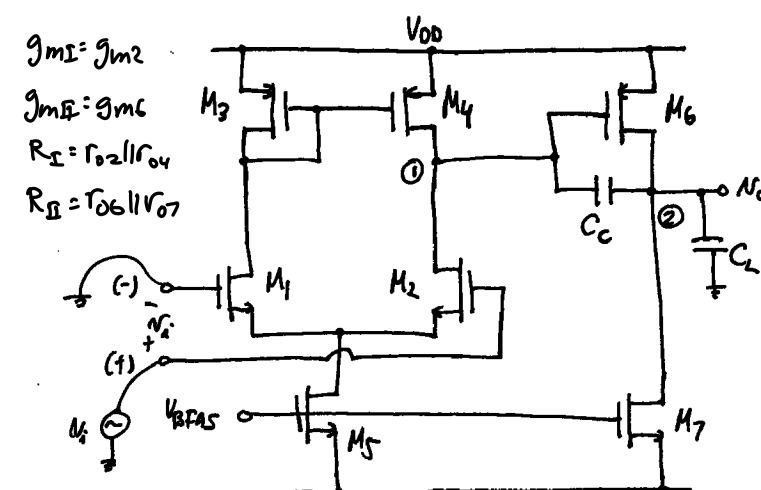CMOS 2-Stage Op Amp Compensation (Summary)



$g_{mI} = g_{m2}$
 $g_{mII} = g_{m6}$
 $R_I = r_{o2} || r_{o4}$
 $R_{II} = r_{o6} || r_{o7}$

From our previous analysis:

$$P_1 = -\frac{1}{g_{mII} R_I R_{II} C_C} \quad [C_C \gg C_I \text{ or } C_{II}] \quad [C_L \gg C_I]$$

$$P_2 = -\frac{g_{mII} C_C}{C_I C_{II} + C_C (C_I + C_{II})} \approx -\frac{g_{mII}}{C_I + C_{II}} \approx -\frac{g_{m6}}{C_L}$$


$z = +\frac{g_{mII}}{C_C} \leftarrow$ RHP zero (this will cause problems)

Remarks.

- ① Note that as $C_C \uparrow \rightarrow |P_1| \downarrow$
- ② As $C_C \uparrow \rightarrow |P_2| \uparrow \rightarrow |P_2| = \frac{g_{mII}}{C_I + C_{II}}$ } pole-splitting
- ③ With $C_C = 0$ (i.e., before compensation)

$$P_1 = -\frac{1}{R_I C_I} \quad P_2 = -\frac{1}{R_{II} C_{II}}$$

④ On a pole/zero diagram

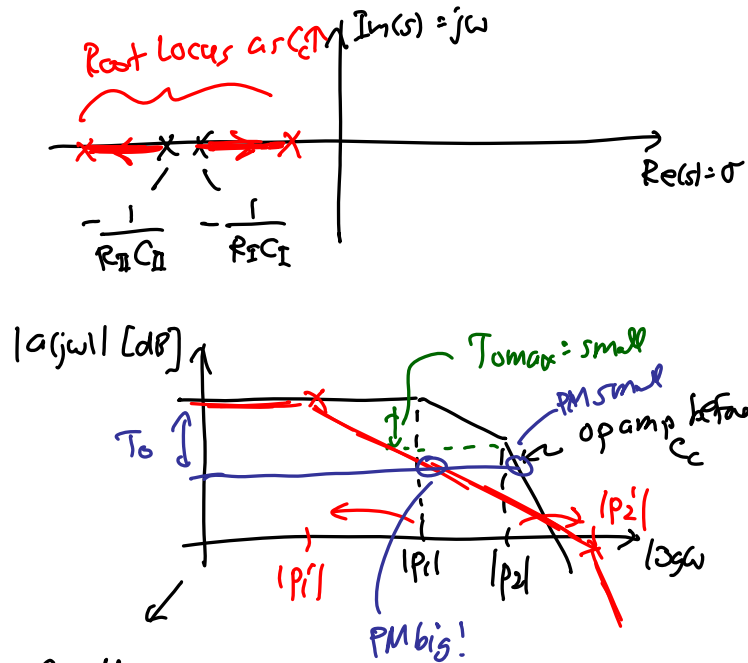


Great!

But what about the RHP zero?

- Now, go through the handouts:
 - Review of Pole/Zero Plots
 - RHP Zero
- These give a general picture of how a RHP zero can hurt stability (but a LHP plane zero can really help)

Where Does the RHP Zero come from?

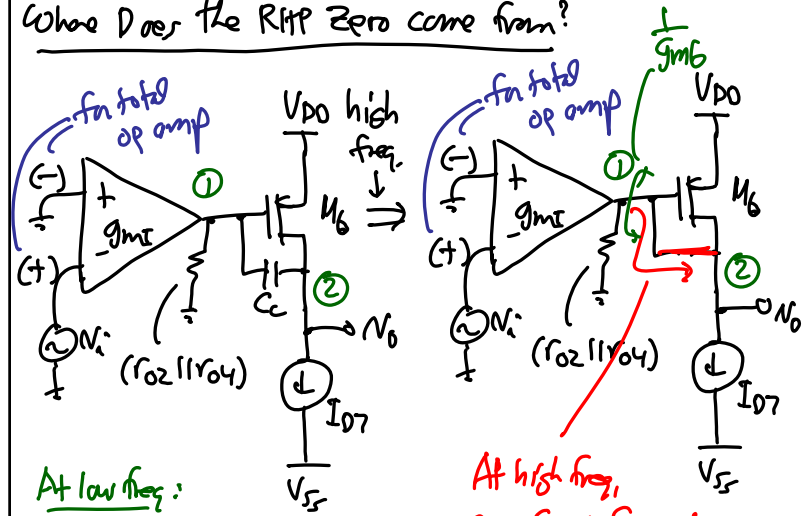

At low freq:

$$\frac{N_o}{N_i} = -g_{m6}(r_{o2} || r_{o4})$$

$$\text{total gain} = \frac{N_o}{N_i} \cdot \frac{N_o}{N_o} = (-) \cdot (-)$$



At high freq, get feed-forward path

$$\frac{N_o}{N_i} = -\frac{g_{m1}}{g_{m6}}$$

creates the RHP zero

$$\text{total gain} = (-)$$

180° phase shift!

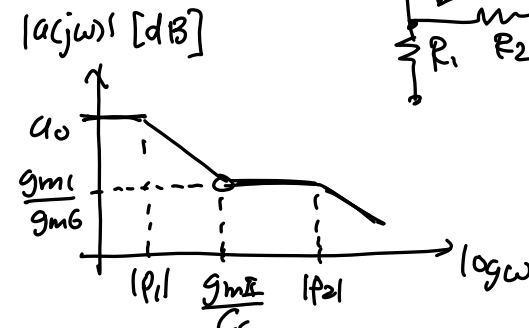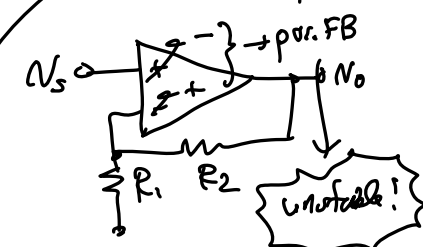


Observation.

Miller effect compensation requires FB path.


↳ BUT: The feedforward path (that creates the zero) is not needed!

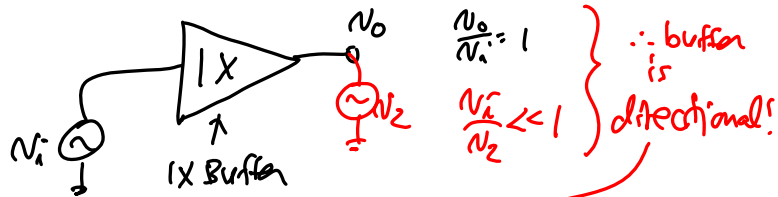- Solution:
- ① Kill the feedforward path
 - ② Keep the feedback path



↳ Solution: Put a 1X buffer in series w/ C_c to prevent feedforward, but allow FB!

The Ckt:

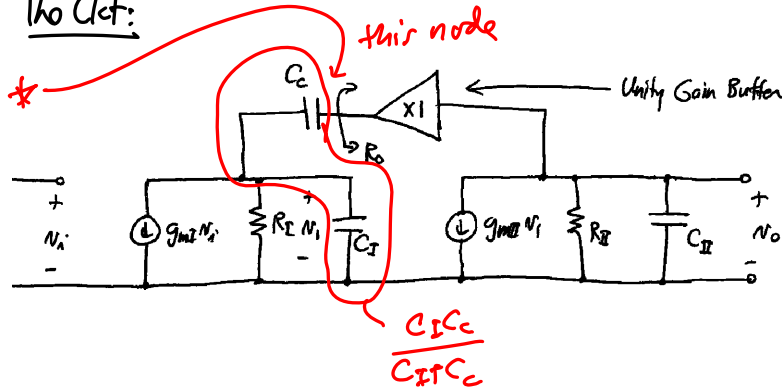

Apply KCL:

$$P_1 \approx -\frac{1}{g_{mII} R_I R_{II} C_c} \quad (\text{same as before})$$

$$P_2 \approx -\frac{g_{mII} C_c}{C_{II}(C_I + C_c)} \approx -\frac{g_{mII}}{C_{II}}$$

$[C_c \gg C_I]$

$$P_3 \approx -\frac{1}{R_o(C_I C_c / (C_I + C_c))} \approx -\frac{1}{R_o C_I} \quad \text{comes from } \star$$

series combination of C_I & C_c

$$Z \approx -\frac{1}{R_o C_c} \leftarrow \text{LHP zero! } \text{Good!}$$

Remarks:

- ① An additional pole $P_3 = -\frac{1}{R_o C_I}$ has been created! But since R_o is small (for a buffer) and C_I is small, P_3 is at a very high freq. \rightarrow contributes very little phase @ ω_{ulg} , where $|T(j\omega)| = 1$.
- ② A LHP zero now emerges, $Z_I = -\frac{1}{R_o C_c}$.

\uparrow
This helps stability as discussed before.
(by contributing (+) phase shift \rightarrow PMN)