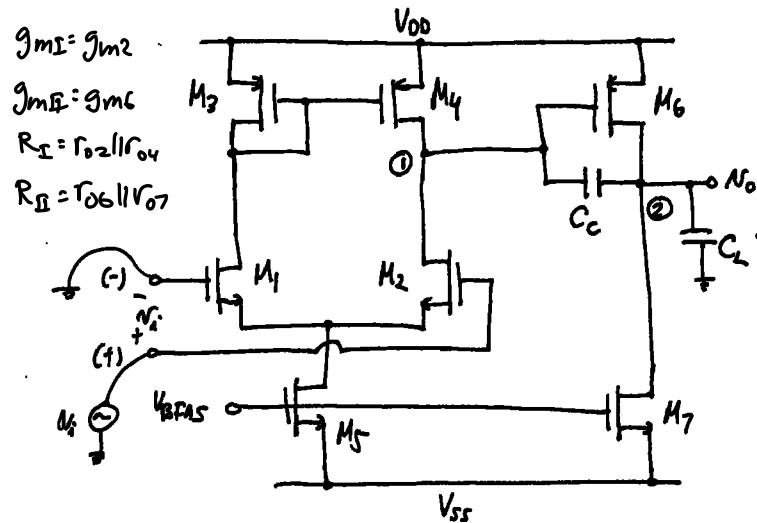


Lecture 22: RHP Zero

- Announcements:
- Design Project Checkpoint:
 - ↳ Due Tuesday, Nov. 19, 11:59 p.m.
 - ↳ Send to your TA a spice file for your op amp design that simulates correctly, i.e., that reaches a stable bias point where all transistors are saturated (except MOS R's)
 - ↳ It doesn't need to meet the project specs, but it should simulate correctly
- HW#10 online, due next Wednesday @ 8 a.m.
- Lecture Topics:
 - ↳ Nulling the RHP Zero

Last Time:

CMOS 2-Stage Op Amp Compensation (Summary)




From our previous analysis:

$$p_1 = -\frac{1}{g_{mI} R_I R_{II} C_c} \quad [C_c \gg C_{I1} \text{ or } C_{I2}] \quad [C_c \gg C_I]$$

$$p_2 = -\frac{g_{mII} C_c}{C_I C_{II} + C_c(C_I + C_{II})} \approx -\frac{g_{mII}}{C_I + C_{II}} \approx -\frac{g_{m6}}{C_I}$$

$$z = +\frac{g_{mI}}{C_c} \leftarrow \text{RHP zero (this will cause problems)}$$

Where Does the RHP Zero come from?

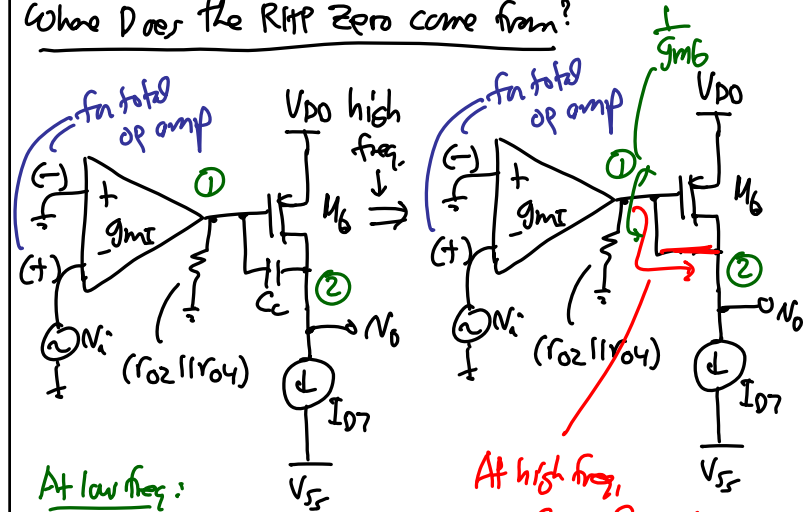

At low freq:

$$\frac{N_0}{N_1} = -g_{m6}(r_{o6} || r_{o7})$$

$$\text{total gain} = \frac{N_0}{N_1} \cdot \frac{N_0}{N_0} = (-) \cdot (-) = (+)$$

At high freq,
get feed-forward path

$$\frac{N_0}{N_1} = -\frac{g_{mI}}{g_{m6}} \leftarrow \text{creates the RHP zero}$$


$$\text{total gain} = (-) \leftarrow 180^\circ \text{ phase shift!}$$

Observation.

Miller effect compensation requires FB path.


↳ BUT: The feedforward path (that creates the zero) is not needed!

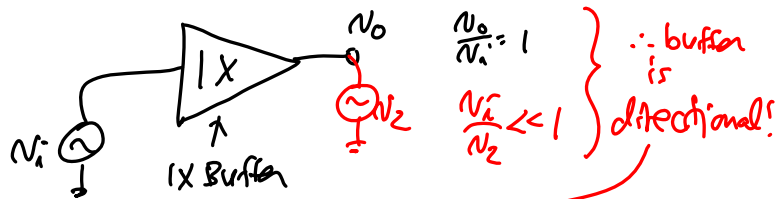- Solution:
- ① Kill the feedforward path
 - ② Keep the feedback path



↳ Solution: Put a 1X buffer in series w/ C_c to prevent feedforward, but allow FB!

The Ckt:

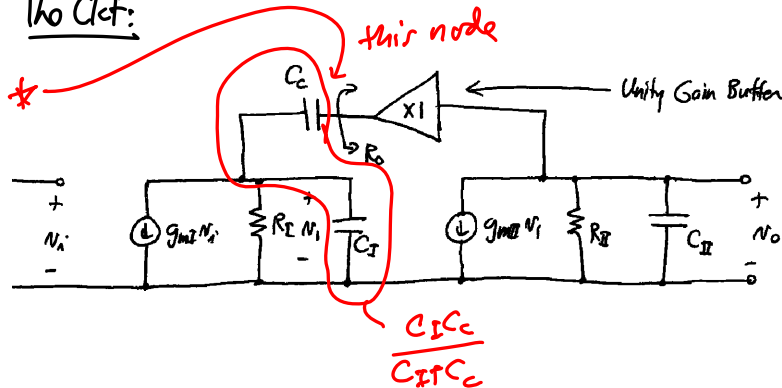

Apply KCL:

$$P_1 \approx -\frac{1}{g_{mII} R_I R_{II} C_c} \quad (\text{same as before})$$

$$P_2 \approx -\frac{g_{mII} C_c}{C_{II}(C_I + C_c)} \approx -\frac{g_{mII}}{C_{II}}$$

$[C_c \gg C_I]$

$$P_3 \approx -\frac{1}{R_o(C_I C_c / (C_I + C_c))} \approx -\frac{1}{R_o C_I} \quad \text{comes from } \star$$

series combination of C_I & C_c

$$Z \approx -\frac{1}{R_o C_c} \leftarrow \text{LHP zero! } \text{Good!}$$


Remarks:

① An additional pole $P_3 = -\frac{1}{R_o C_I}$ has been created! But since R_o is small (for a buffer) and C_I is small, P_3 is at a very high freq. → contributes very little phase @ ω_{ulg} , where $|T(j\omega)| = 1$.

② A LHP zero now emerges, $Z_I = -\frac{1}{R_o C_c}$.

↑
This helps stability as discussed before.
(by contributing (+) phase shift → PMN)

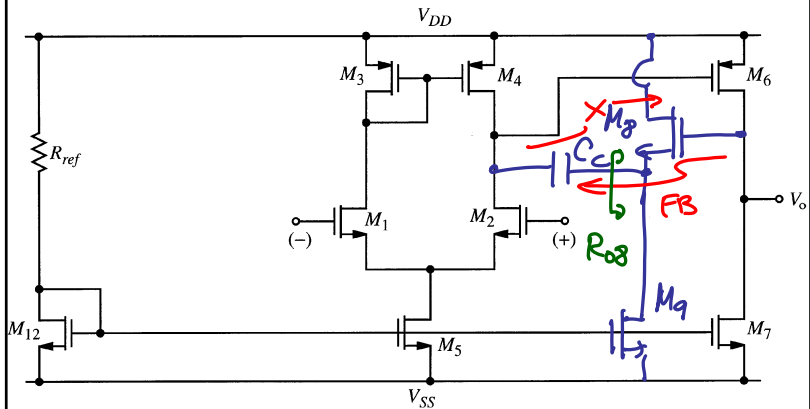
Actual Implementation of Buffer-Based Zero Cancellation



$R_{os} \approx \frac{1}{g_{m8}} = \frac{1}{\sqrt{2\mu_n C_{ox} (\frac{W}{L})_p I_{Dp}}}$ → Want this sufficiently small to drive $|p_3| \uparrow$
 ↑ increase I_{Dp} , or increase $(\frac{W}{L})_p$
 ↓ Problems: more power ↓ more area ↓ cost!

Solution: Better technique!

Nulling Resistor in Series w/ C_c

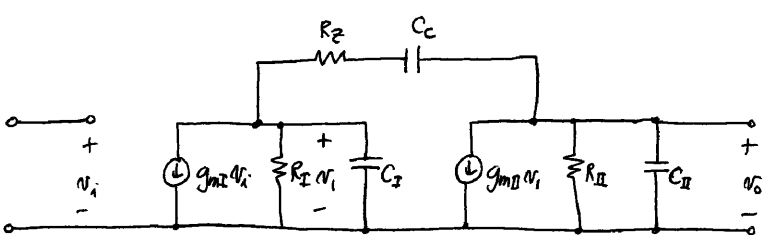

Doing KCL:

$$p_1 = -\frac{1}{g_{m1} R_I R_{II} C_c}$$

$$p_2 \approx \frac{-g_{mII} C_c}{C_I C_{II} + C_c (C_I + C_{II})} \approx -\frac{g_{mII}}{C_{II}}$$

} same as before

$$p_3 = -\frac{1}{R_2 C_I} \leftarrow \text{pole due to } R_2$$

$$z_1 = \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_2 \right)} \leftarrow \text{relocated zero (function of } R_2)$$

Note: The position of the zero depends upon the value of the "nulling resistor" R_2

If $R_2 < \frac{1}{g_{mII}}$ then z_1 is in the RHP

If $R_2 > \frac{1}{g_{mII}}$ then " " LHP!

↳ This is great! → can convert the zero to a LHP one!

can even stick the zero on top of a pole to eliminate it!

$$H(s) = \dots \frac{(s - z_1)}{(s - p_1)}$$

if $z_1 = p_1$

The Root Locus:

When everything starts before R_2

add $R_2 \uparrow$

$R_2 = \frac{1}{g_{mII}}$

$R_2 < \frac{1}{g_{mII}}$

$-\infty$ $+\infty$

Zero Placement Strategies

① Eliminate $z_1 \rightarrow$ move it to ∞ :

$$z_1 = \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_2 \right)} \rightarrow \infty \text{ when } R_2 = \frac{1}{g_{mII}} \text{ Load Cap.}$$

After doing this: $p_3 \approx -\frac{g_{mII}}{C_I}$ $p_2 \approx -\frac{g_{mII}}{C_{II}}$

Usually $C_{II} \gg C_I$, so these poles are far apart... but be careful

This is good, but we can do better:

② Eliminate p_3 by placing z_1 on top of it:

$$z_1 = p_3 \Rightarrow \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_2 \right)} = -\frac{1}{R_2 C_I}$$

$$R_2 = \frac{1}{g_{mII} \left(1 - \frac{C_I}{C_c} \right)}$$

After this: ① p_3 gone; p_1 & p_2 left

② Now, can place w/lt @ p_2 and really get PM: 45° (w/o worrying about the influence of p_3)



But can still do better


③ Eliminate p_2 by placing z_1 on top of it:

$\Rightarrow p_3$ becomes the "new" p_2 ! (higher f; higher T_{max})

$$z_1 = p_2 \Rightarrow \frac{1}{C_c \left(\frac{1}{g_{mII}} - R_2 \right)} = -\frac{g_{mII}}{C_{II}}$$
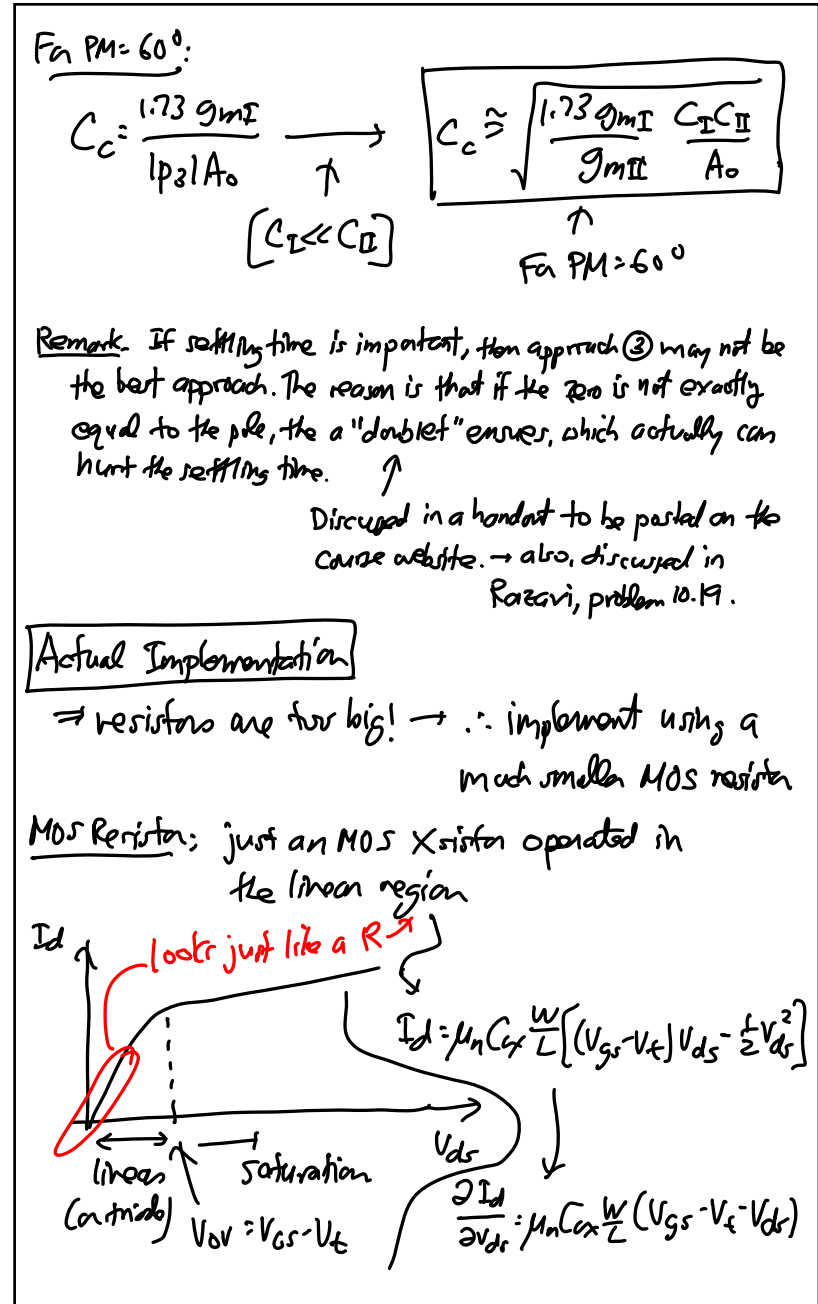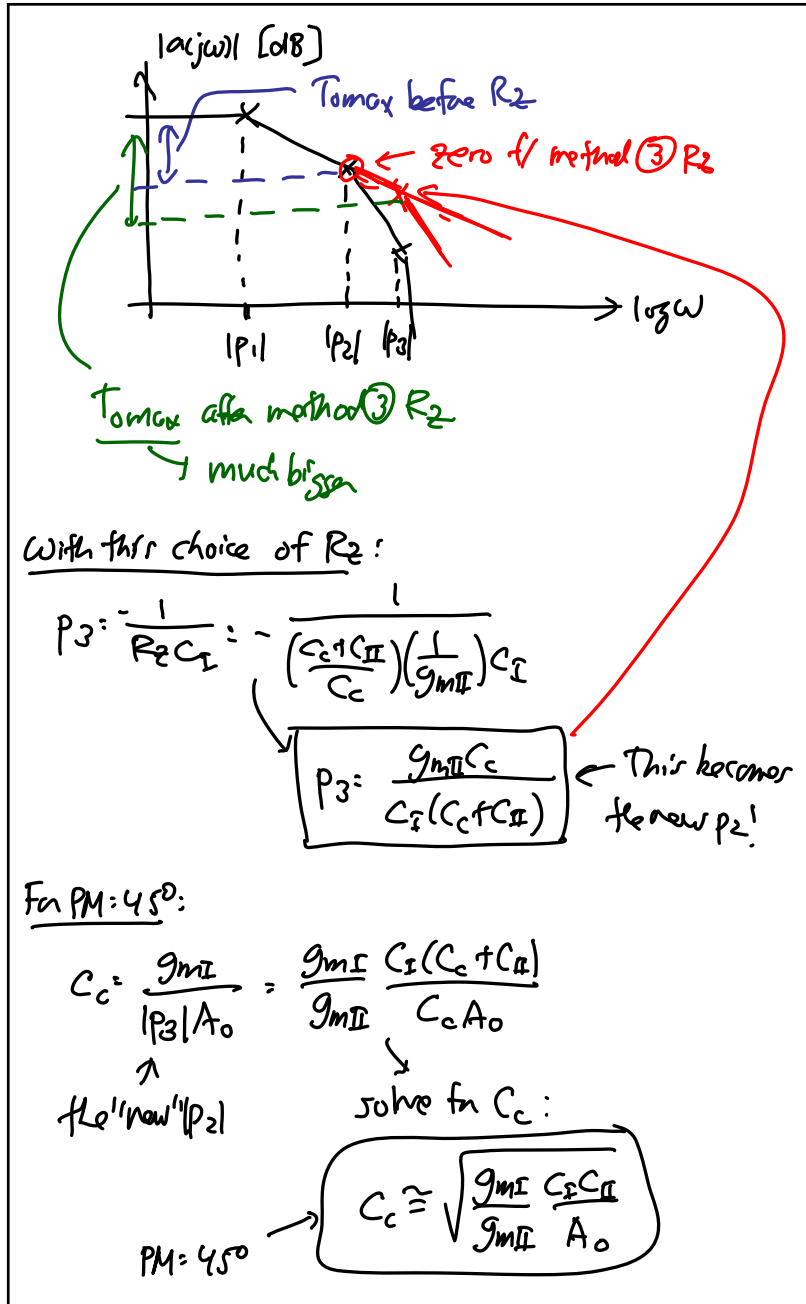
$$R_2 = \left(\frac{C_c + C_{II}}{C_c} \right) \left(\frac{1}{g_{mII}} \right) = \frac{1}{g_{mII}} \left(1 + \frac{C_{II}}{C_c} \right)$$



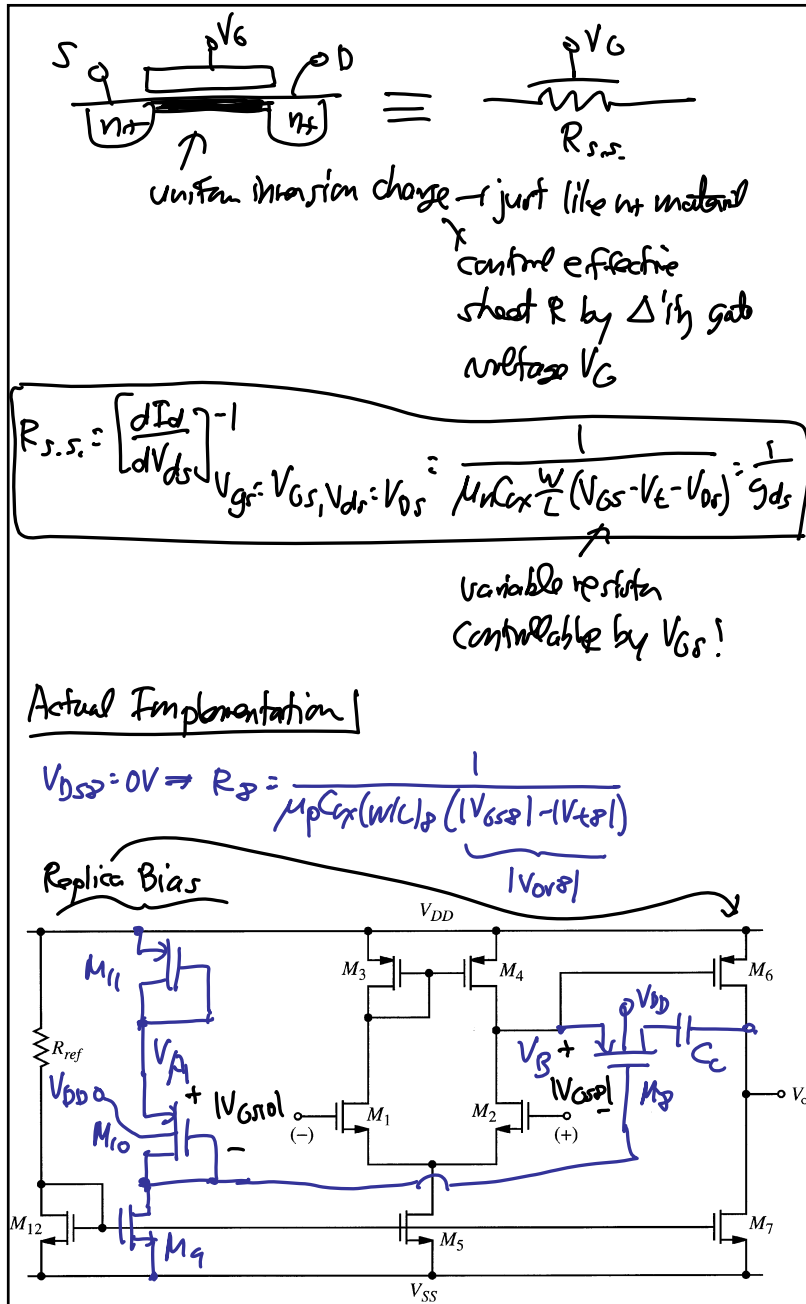

Design:

Need $V_A = V_B \rightarrow |V_{GS11}| = |V_{GS6}|$, know $|V_{t11}| = |V_{t6}|$

$$\sqrt{\frac{2I_{D11}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{11}}} = \sqrt{\frac{2I_{D6}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_6}}$$

$$\left(\frac{W}{L}\right)_{11} = \left(\frac{W}{L}\right)_6 \frac{I_{D11}}{I_{D6}} = \left(\frac{W}{L}\right)_6 \frac{I_{D10}}{I_{D6}}$$

Also need $|V_{GS10}| = |V_{GS8}|$

Because $V_A = V_B \rightarrow V_{S10} = V_{S8} \rightarrow |V_{t10}| = |V_{t8}|$

$$\therefore |V_{GS10}| = |V_{GS8}| = \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{10}}}$$

Thus:

$$R_B = \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_B \sqrt{\frac{2I_{D10}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{10}}}} = \frac{\sqrt{\mu_p C_{ox} (W/L)_{10}}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_B \sqrt{2I_{D10}}}$$