

Lecture 24: PSRR & Feedback I

- Announcements:
- HW#11 due Nov. 27 @ 8 a.m.
- No homework over Thanksgiving
- Pre-Lecture for Settling Time online
- Lecture Topics:
  - ↳ Settling Time (finish)
  - ↳ Power Supply Rejection Ratio (PSRR)
  - ↳ Start Feedback

• Last Time: going thru Settling Time Handout

Settling Time

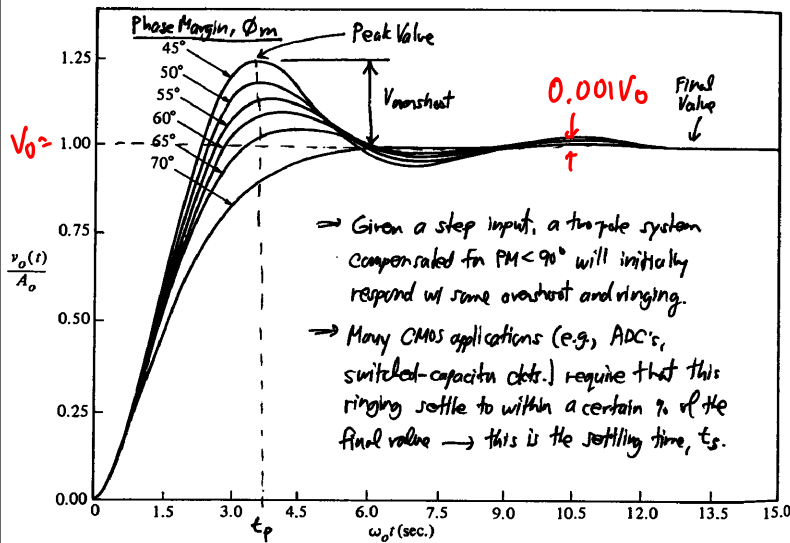



Figure 8.2-3 Response of second-order system with various phase margins.

Obtain Expressions for:

- ①  $V_{overshoot}$
  - ② Settling Time,  $T_s$
- } as functions of phase margin,  $\Phi_m$


Power Supply Rejection Ratio (PSRR)

In today's mixed-signal ckt:

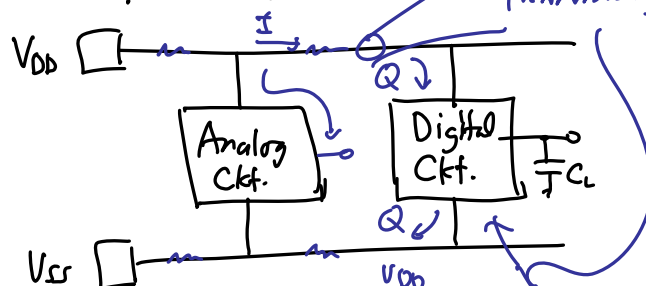

But for analog ckt, supply noise can be a big issue!  
 noise not much of a problem for the digital ckt.

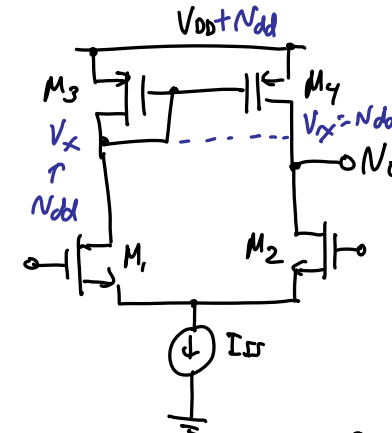Ex. CMOS Differential Input Stage w/ Current Mirror Load



$N_0 / V_{DD} \approx 1 \Rightarrow$  supply noise directly seen @ output!


For this example,  $PSRR \approx \frac{g_{m2}(r_{o2} || r_{o4})}{1} = g_{m2}(r_{o2} || r_{o4})$

Lecture 24w: Power Supply Rejection Ratio (PSRR) & Feedback I

Definition. Power Supply Rejection Ratio (PSRR)

$$PSRR \triangleq \frac{\text{Gain w/ Input to Output}}{\text{Gain w/ Supply to Output}} = \frac{A_{v}(V_{dd}=0)}{A_{dd}(V_i=0)}$$

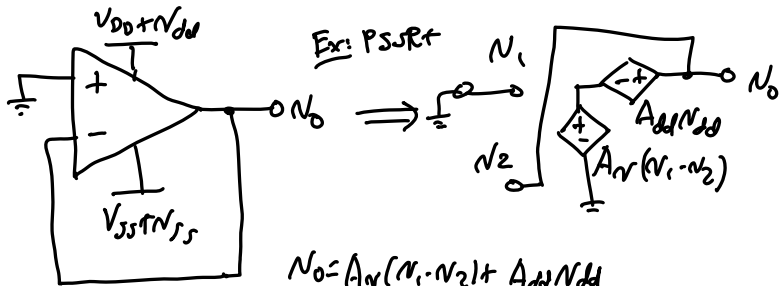For more complicated ckt's., much more work is req'd.  
 ↳ to make it easier, use a unity gain configuration  
 ↳ can also get  $PSRR = f(\omega)$



$$N_o = A_v(N_i, N_z) + A_{dd}N_{dd}$$


$$N_o(1 + A_v) = A_{dd}N_{dd} \rightarrow \frac{N_o}{N_{dd}} = \frac{A_{dd}}{1 + A_v} = \frac{1}{\frac{A_v}{A_{dd}}} \approx \frac{1}{PSRR}$$

$$\frac{1}{PSRR} = \frac{N_o}{N_{dd}} \rightarrow PSRR = \frac{N_{dd}}{N_o}$$

Just find this X for fun to get PSRR  
 when the op amp is hooked in unity gain!

Two-Stage Op Amp PSRR

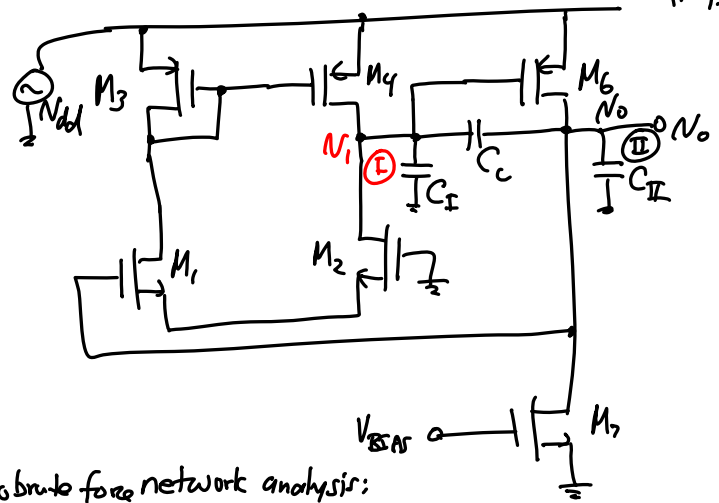Want  $PSRR^+ = f(\omega)$   
 ↑  
 freq.



Do brute force network analysis:

$$KCL \textcircled{1}: G_I N_{dd} = (G_I + sC_c + sC_f)N_i - (g_{m1} + sC_c)N_o$$

$$KCC \textcircled{2}: (g_{m1} + g_{ds6})N_{dd} = (g_{m1} - sC_c)N_i + (G_{II} + sC_c + sC_{II})N_o$$

$$\left\{ \begin{aligned} G_I &= g_{ds1} + g_{ds4} = g_{ds2} + g_{ds4} \\ G_{II} &= g_{ds6} + g_{ds7} \\ g_{m1} &= g_{m1} = g_{m2} \\ g_{m0} &= g_{m6} \end{aligned} \right.$$

$g_{ds} = \frac{1}{r_o}$   
 ↑  
 for saturated device.

Get:

$$\left. \frac{N_{dd}}{N_o} \right|_{\text{closed-loop}} = \frac{N(s)}{D(s)} = \frac{\text{polynomial}}{\text{polynomial}}$$

↳ then use:  $N(s) = 1 + \left(\frac{s}{z_1} + \frac{s}{z_2}\right) + \frac{s^2}{z_1 z_2} \approx 1 + \frac{s}{z_1} + \frac{s^2}{z_1 z_2}$

Lecture 24w: Power Supply Rejection Ratio (PSRR) & Feedback I

$$PSRR^+ = A_{No}^+ \left[ \frac{(1 + \frac{s}{GB})(1 + \frac{s}{|P_{z1}|})}{(1 + \frac{s}{GB/A_{No}^+})} \right]$$

where  $GB = \text{Gain BW Product} = \frac{g_{mI}}{C_c}$

$$A_{No}^+ = \text{DC PSRR}^+ = \frac{g_{mI} g_{mII}}{G_I g_{ds6}}$$

$$|P_{z1}| = \frac{g_{mII}}{C_{II}} \quad \omega_p^+ = \frac{GB}{A_{No}^+}$$

To maximize PSRR<sup>+</sup>: (@dc) decrease  $g_{ds6}$ , raise  $g_{mII}$

$$PSRR^- = A_{No}^- \left[ \frac{(1 + \frac{s}{GB})(1 + \frac{s}{|P_{z1}|})}{(1 + \frac{s}{\omega_p^-})} \right]$$

where  $A_{No}^- = \frac{g_{mI} g_{mII}}{G_I g_{ds7}}$

$$GB = \frac{g_{mI}}{C_c} \quad \omega_p^- = \frac{G_I}{C_c + C_I} \approx \frac{G_I}{C_c}$$

$$|P_{z1}| = \frac{g_{mII}}{C_{II}}$$

To maximize PSRR<sup>-</sup>:  
 ① decrease  $g_{ds7}$   
 ② increase  $g_{mII} = g_{m6}$

Remarks.

① Since often  $g_{ds7} < g_{ds6} \rightarrow$  often  $PSRR^- > PSRR^+$  (@dc)

②  $\frac{\omega_p^-}{\omega_p^+} = \frac{G_I/C_c}{g_{mI} C_c} = \frac{g_{mII}}{g_{ds6}} \rightarrow$  that's quite large  
 $\therefore \omega_p^- \gg \omega_p^+$


Thus, for an NMOS input op amp, PSRR<sup>-</sup> is often better than PSRR<sup>+</sup>.  $\rightarrow$  in design, need to worry more about PSRR<sup>+</sup>!

③ Some methods for ~~reducing~~ <sup>maximizing</sup> PSRR:

- (i) Use buffer-based zero-cancellation in the compensation loop.
- (ii) Use cascode circuitry, or balanced circuit topologies.
- (iii) Supply-independent biasing.
- (iv) Design strategies to minimize parasitic capacitive feedthrough.

Feedback


$\Rightarrow$  we know this:

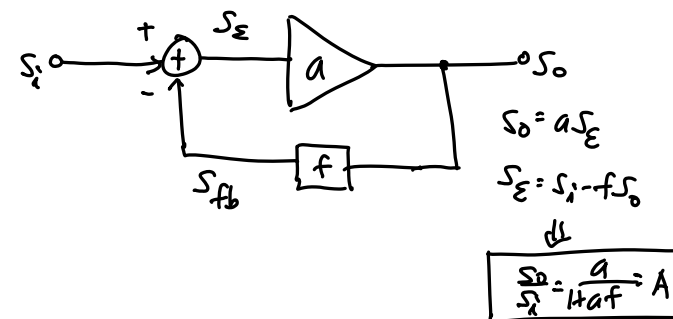


Benefits of Negative FB

- ① Stabilizes the gain of the amp against parameter changes & active device variations
- ② Modifies  $R_i$  and  $R_o$  → basically improves their values according to the type of amplifier implemented  
 e.g., voltage amp:  $R_i$ : large,  $R_o$ : small

@ input:

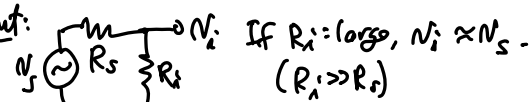

@ output:

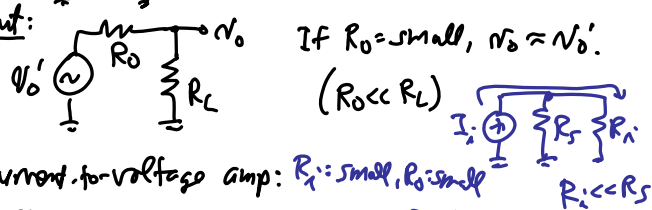

current-to-voltage amp:  $R_i$ : small,  $R_o$ : small

voltage-to-current amp:  $R_i$ : large,  $R_o$ : large

current-to-current amp:  $R_i$ : small,  $R_o$ : large

- ③ Reduces distortion; improves linearity.
- ④ Increases bandwidth (w-3dB).

Disadvantages of Neg. FB

- ① Gain is reduced → reduction factor ~ equal to the amount of gain stabilization, distortion reduction, etc...

Solution: Add more stages of gain → but this adds cost & power...

- ② Feedback causes stability problems (if not compensated properly)

Gain Sensitivity Reduction Via FB

$$A = \frac{a}{1+af} \rightarrow \frac{dA}{da} = \frac{(1+af) - af}{(1+af)^2} = \frac{1}{(1+af)^2} \rightarrow \text{small}$$

usually of this

For a  $\Delta$  in op amp gain:  $\Delta a$


$$\frac{\Delta A}{A} = \frac{1}{(1+af)^2} \rightarrow \Delta A = \frac{\Delta a}{(1+af)^2}$$

much smaller than  $\Delta a$

... and the fractional change:

$$\frac{\Delta A}{A} = \frac{1+af}{a} \frac{\Delta a}{(1+af)^2} \Rightarrow \frac{\Delta A}{A} = \frac{\Delta a}{a(1+af)}$$

Distortion Reduction via FB

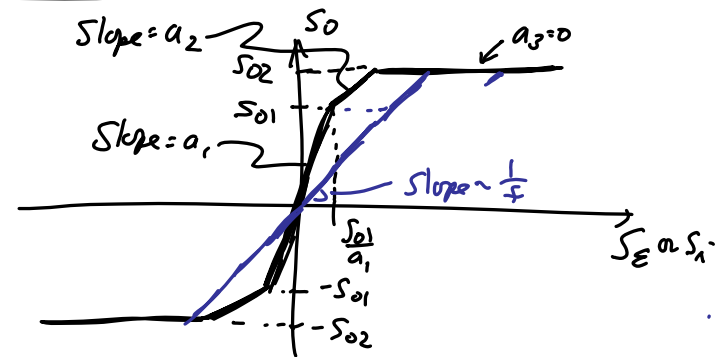


Near, close to loop: for  $a_1$ : large  $\approx 20k$

$$0 < S_0 < S_{01}: A_1 = \frac{a_1}{1+a_1f} \approx \frac{1}{f}$$

$$S_{01} < S_0 < S_{02}: A_2 = \frac{a_2}{1+a_2f} \approx \frac{1}{f}$$

still linear over larger range!

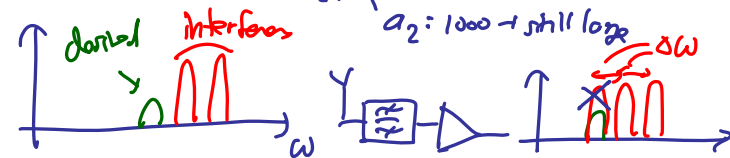


"Inspection" Analysis of FB Ckcts.

↓ starts with...

Identification of FB Connection Types

Series Connection - FB network part in series w/ amplifier part

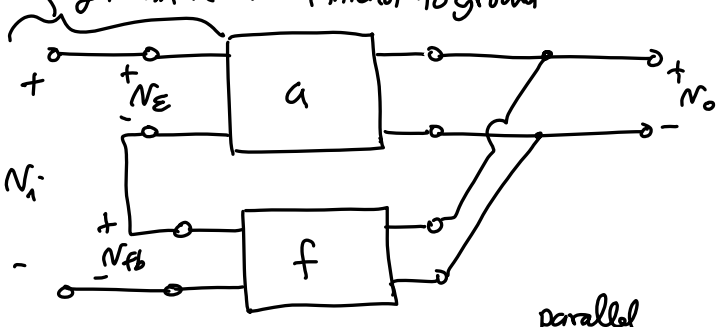↳ must go thru both the FB part & the amplifier part to get from the node of interest to ground



Shunt Connection - FB network part in shunt w/ amplifier part

↳ can get from the node of interest to ground via either FB network part or the amplifier part

over