

Lecture 25: Feedback Z


- Announcements:
- HW#11 due tomorrow @ 8 a.m.
- No homework over Thanksgiving
- Pre-Lecture Feedback Loading Handout online
- Lecture Topics:
  - ↳ Recognizing Feedback Configurations
  - ↳ Effect of FB on  $Z_i$  and  $Z_o$
  - ↳ Feedback Loading

• Last Time: started inspection analysis of FB

Identification of FB Connection Types

Series Connection - FB network part in series w/ amplifier part



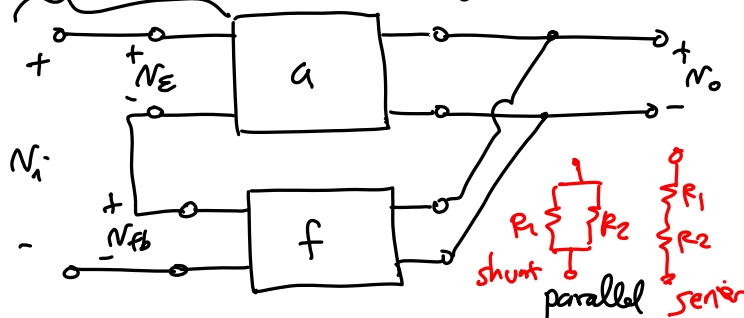
↳ must go thru both the FB part & the amplifier part to get from the node of interest to ground





Shunt Connection - FB network part in shunt w/ amplifier part

↳ can get from the node of interest to ground via either FB network part or the amplifier part

Example.

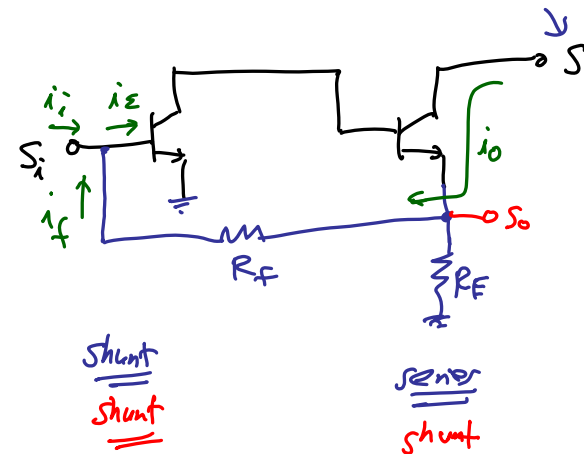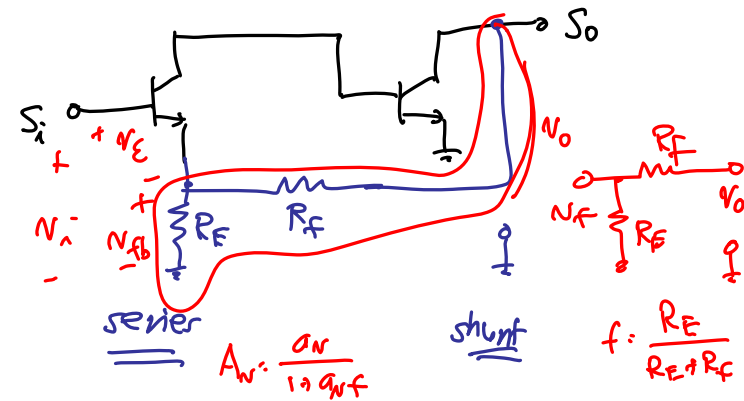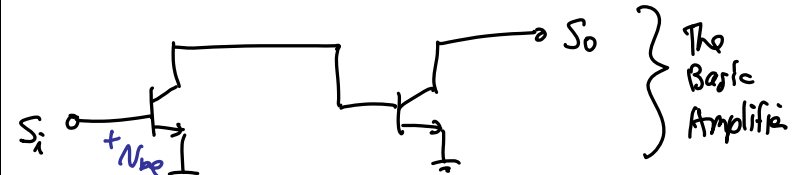


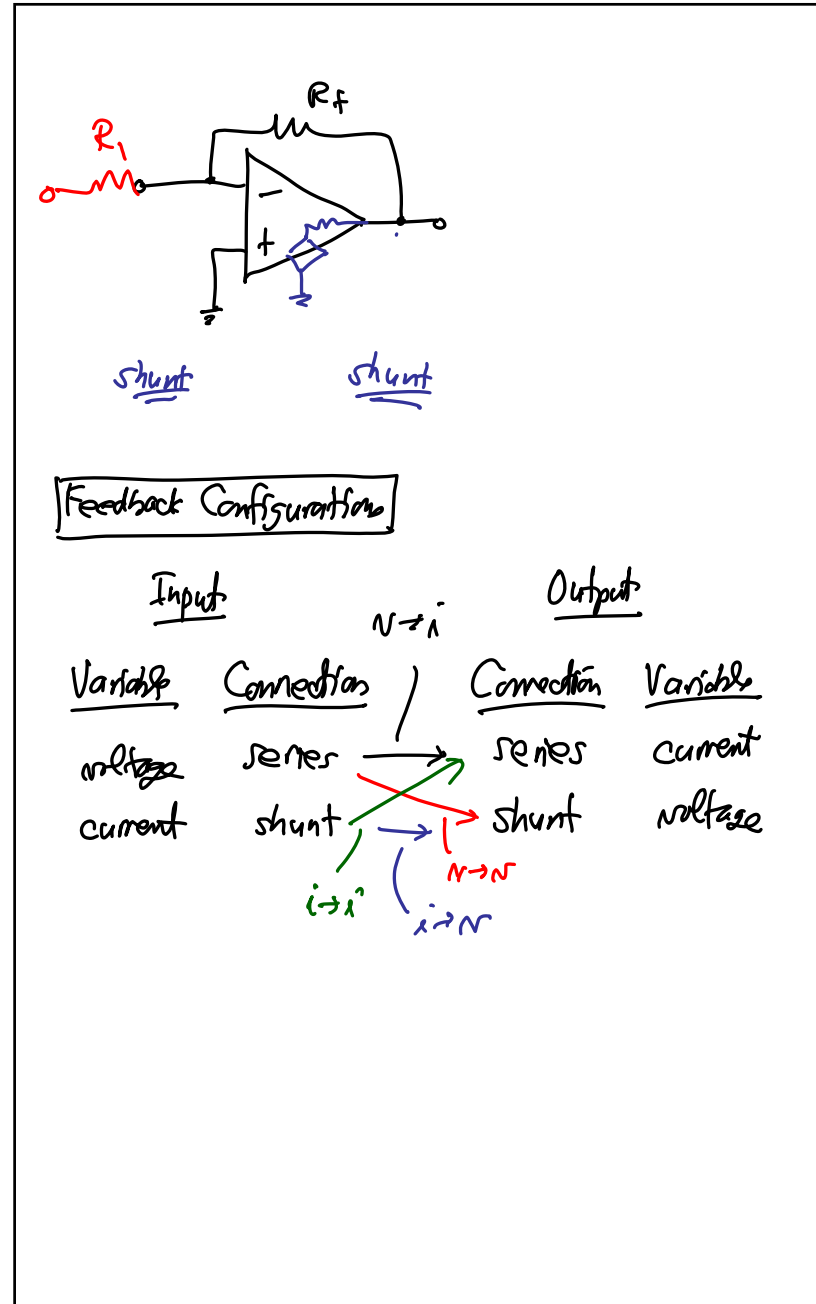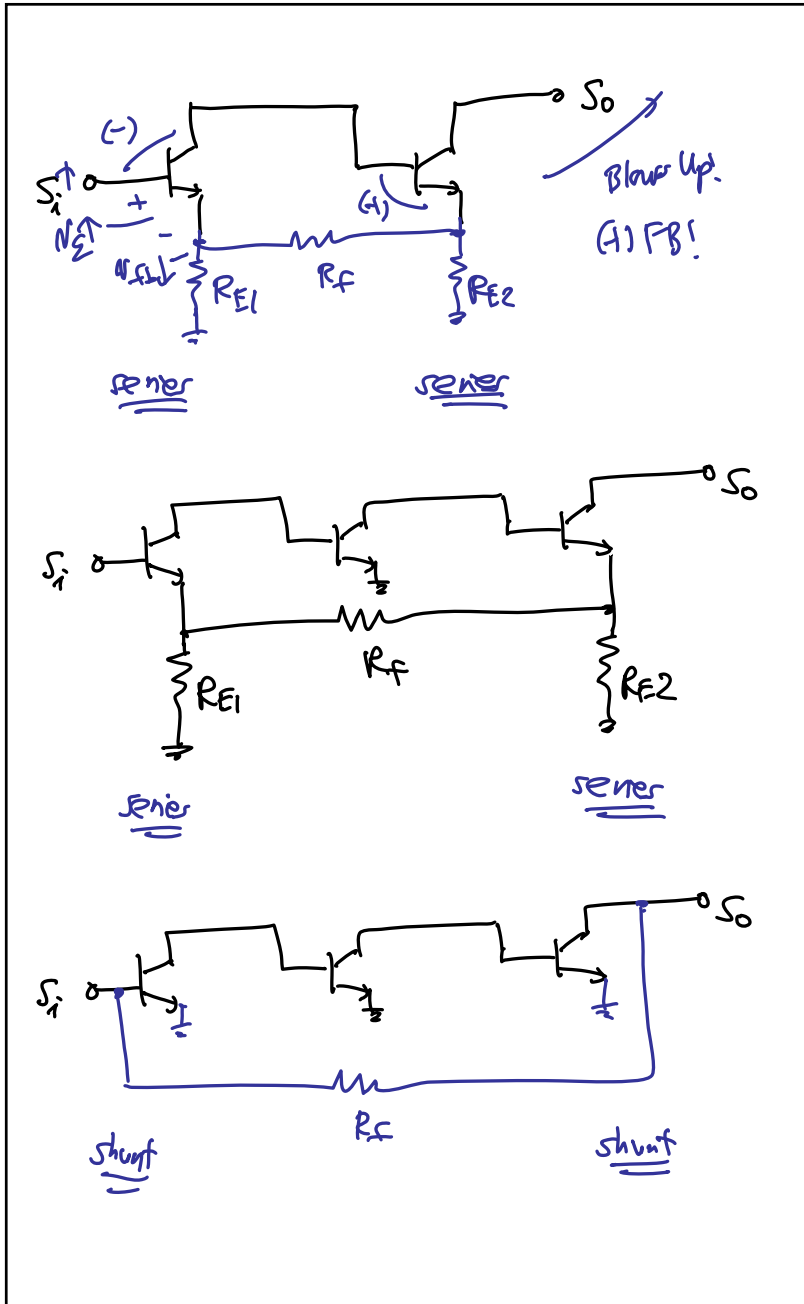

Effect of FB on  $Z_i$  &  $Z_o$

Ex. Series-Shunt FB

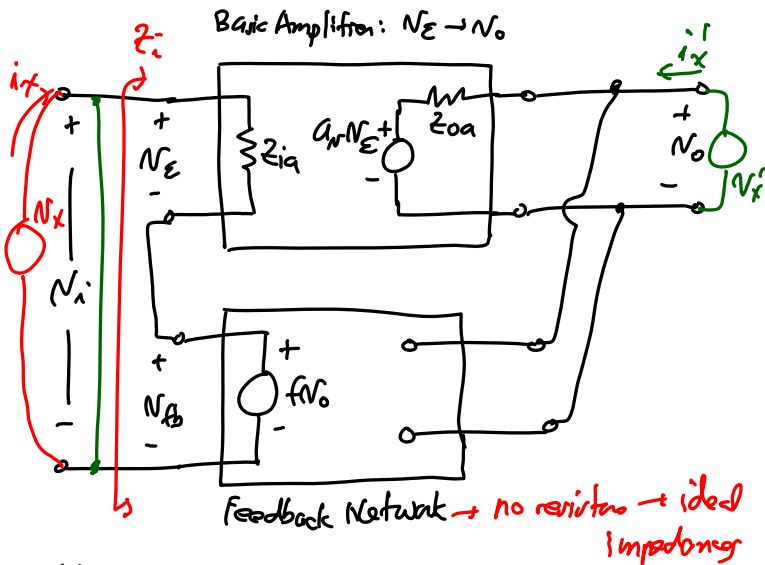Assumption: FB network has ideal impedances  
i.e., it does not load the basic amplifier



Find the T.F.:

$$\left. \begin{aligned} N_E &= N_x - N_{FB} \\ N_o &= a_v N_E \\ N_{FB} &= f v_o \end{aligned} \right\} \begin{aligned} N_o &= a_v (N_x - f v_o) \\ \Rightarrow \frac{N_o}{N_x} &= \frac{a_v}{1 + a_v f} \end{aligned} \quad \checkmark$$

(as expected)

Find  $Z_i = \frac{N_x}{i_x}$ :

$$\begin{aligned} N_x &= N_E + N_{fb} \\ &= N_E + f v_o = N_E + a_v f N_E = N_E (1 + a_v f) \end{aligned}$$

$$i_x = \frac{N_E}{Z_{ia}}$$

$$Z_i = \frac{N_x}{i_x} = \frac{N_E (1 + a_v f)}{\frac{N_E}{Z_{ia}}} = Z_{ia} (1 + a_v f) = Z_i$$

closed loop input impedance

original open-loop impedance of op amp

When we series connection @ input

Closed-loop input impedance raised by  $(1 + a_v f)$ !

If  $Z_i \uparrow \rightarrow$  better voltage amplifier!

Find  $z_o = \frac{N_x'}{i_x'}$ : (w/ input-shorted)

$$N_\Sigma + N_{FB} = 0 = N_\Sigma + fN_x' + N_\Sigma \cdot -fN_x'$$

$$i_x' = \frac{N_x' - a_v N_\Sigma}{z_{oa}} = \frac{N_x' - a_v f N_x'}{z_{oa}}$$

orig. amplifier open-loop output impedance

$$\frac{N_x'}{i_x'} = \frac{z_{oa}}{1 + a_v f} = z_o$$

closed-loop output impedance  $z_o$  lowered by a factor  $(1 + a_v f)$

loop gain

Again, mack for a better voltage amplifier!

Overall series-shunt FB improves the impedance characteristics of a  $v \rightarrow v$  amplifier!  
 $z_i \uparrow, z_o \downarrow$  due to FB

Ex. Shunt-Series FB

$\Rightarrow$  Again, assume the FB network does not load the amplifier

Basic Amplifier:  $i_\Sigma \rightarrow i_o$

Feedback Network:  $i_o \rightarrow i_{FB}$

shunt series

Find the T.F.:

$$\left. \begin{aligned} i_o &= a_v i_\Sigma \\ i_\Sigma &= i_x - i_{FB} = i_x - f i_o \end{aligned} \right\} \frac{i_o}{i_x} = \frac{a_v}{1 + a_v f}$$

Open loop  $i \rightarrow i$  gain

loop gain

similar to the  $v \rightarrow v$  case, except now  $i \rightarrow i$

Find  $z_i := \frac{V_x}{i_x}$

open-loop input impedance

$$\frac{V_x}{i_x} = \frac{z_{io}}{1 + a_i f} = z_i$$

loop gain

⇒ Again, a shunt connection reduces impedance by a factor

of  $(1 + a_i f)$ !  
 expect a  $i$  input!

Find  $z_o := \frac{V_x}{i_x}$

$$\frac{V_x}{i_x} = z_{oc}(1 + a_i f) = z_o$$

↳ series connection raises the impedance by a factor  $(1 + a_i f)$ !

Summary: shunt-series makes for a better  $i \rightarrow i$  amplifier!

Summary:

$T = \text{loop gain}$

① series connection:  $z \rightarrow z(1+T)$

② shunt connection:  $z \rightarrow \frac{z}{(1+T)}$

- Now go through the "Loading from the FB Network" Handout