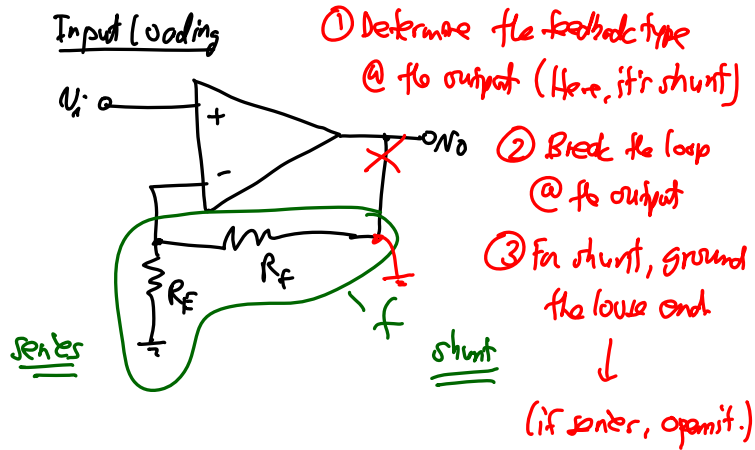


Lecture 27: Feedback Examples


- Announcements:
- HW#12 due Wednesday, 12/11 @ 8 a.m.
- Project (Lab#3) due Friday, 12/13, at 5 p.m. in the 140/240A homework box
  - ↳ Best to be finished with design by next Monday, so you have plenty of time to write the report
  - ↳ Make sure the report is good, since it is what is graded in the end
- Handed out old final exams
- Lecture Topics:
  - ↳ Feedback By Inspection Example
  - ↳ Final Exam Info
  - ↳ Course Wrap Up

-----  
 • Last Time:

To determine loading by FB:




Output Loading:

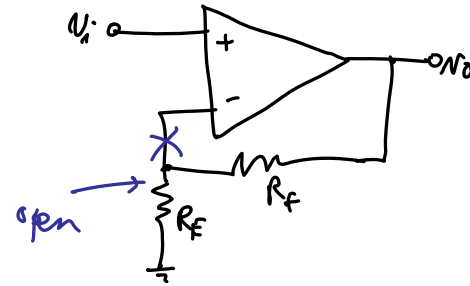

- ① Determine the feedback type @ input. (Here, it's series.)
- ② Break the loop @ input.
- ③ For series, open the lower end.  
 ↳ (If shunt, short it)

Example. Transresistance Amplifier

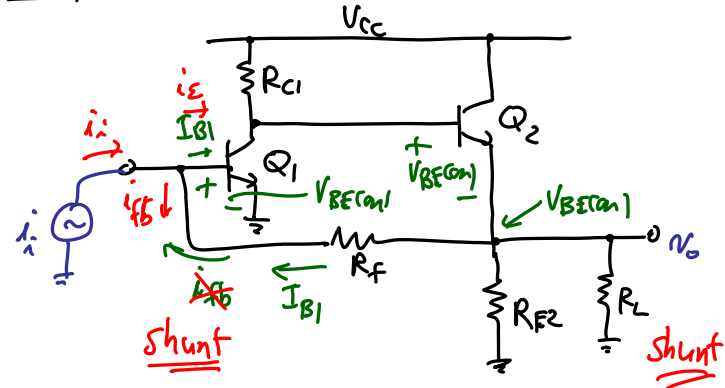

① Determine type of FB → determine type of gain

② Biasing

Note: Don't do this if  $R_f = \text{large}$ .

$I_{B1} \leftarrow \text{tiny} \approx 0$


$I_{C2} \approx I_{E2} = \frac{V_{BE(on)}}{R_{E2} \parallel R_L}$ ;  $I_{C1} = \frac{V_{CC} - 2V_{BE(on)}}{R_{C1}}$

get  $g_m$ 's,  $r_o$ 's,  $r_{\pi}$ 's, etc.

③ What kind of gain?

shunt-shunt FB →  $i \rightarrow v$  gain  
 $\therefore$  we're looking for  $R_m = \frac{v_o}{i_i} = \frac{r_m}{1 + r_m f}$   
 $i \rightarrow v$  gain of OL w/ FB Loading

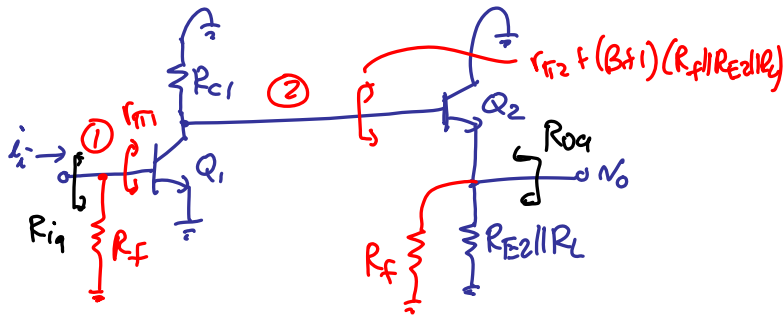④ Determine  $r_m$ : (open loop w/ FB load/ing)



Get  $G_{mi}$

$\frac{v_o}{i_i} \Big|_{\text{OL w/ FB Loading}} = \frac{v_o}{i_i} \cdot \frac{i_i}{v_o} \cdot \frac{v_o}{i_i} = r_m$


$v_o: i_i (r_{\pi1} \parallel R_f) \rightarrow \frac{v_o}{i_i} = (r_{\pi1} \parallel R_f)$

$\frac{v_o}{v_o} = -g_{m1} [R_{C1} \parallel (r_{\pi2} + (\beta+1)(R_f \parallel R_{E2} \parallel R_L))]$

$\frac{v_o}{v_o} \equiv 1$

$r_m = \frac{v_o}{i_i} \Big|_{\text{OL w/ FB Loading}} = -g_{m1} (r_{\pi1} \parallel R_f) [R_{C1} \parallel \dots] = r_m$

Find  $f$ :

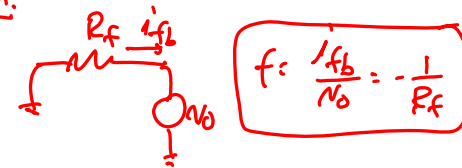

Thus:

$T = r_m f = g_{m1} R_{C1} \left( \frac{r_{\pi1} \parallel R_f}{R_f} \right) \leftarrow \text{loop gain}$

⑤ Finally, get all parameters:


$R_m = \frac{r_m}{1 + r_m f} \approx \frac{1}{f} = -R_f \rightarrow R_m = -R_f$

$$R_i = \frac{R_{in} \text{ w/ FB Loading}}{1 + r_{mf}} = \frac{r_{\pi 1} \parallel R_F}{1 + g_{m1} R_{C1} \left( \frac{r_{\pi 1} \parallel R_F}{R_F} \right)} = R_i$$

$$R_o = \frac{R_{out} \text{ w/ FB Loading}}{1 + r_{mf}} = \frac{\frac{r_{\pi 2} + R_{C1}}{\beta + 1} \parallel R_{E2} \parallel R_F \parallel R_L}{1 + g_{m1} R_{C1} \left( \frac{r_{\pi 1} \parallel R_F}{R_F} \right)} = R_o$$


Find  $\omega_{-3dB}$ :

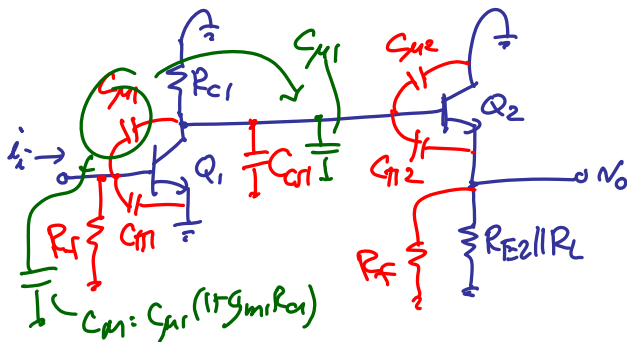- ① Find the  $\omega_{-3dB}$  of the open-loop amplifier w/ FB loading, i.e., of this:  $\rightarrow$  Use OCTC analysis



- ② Multiply by  $(1+T)$ :
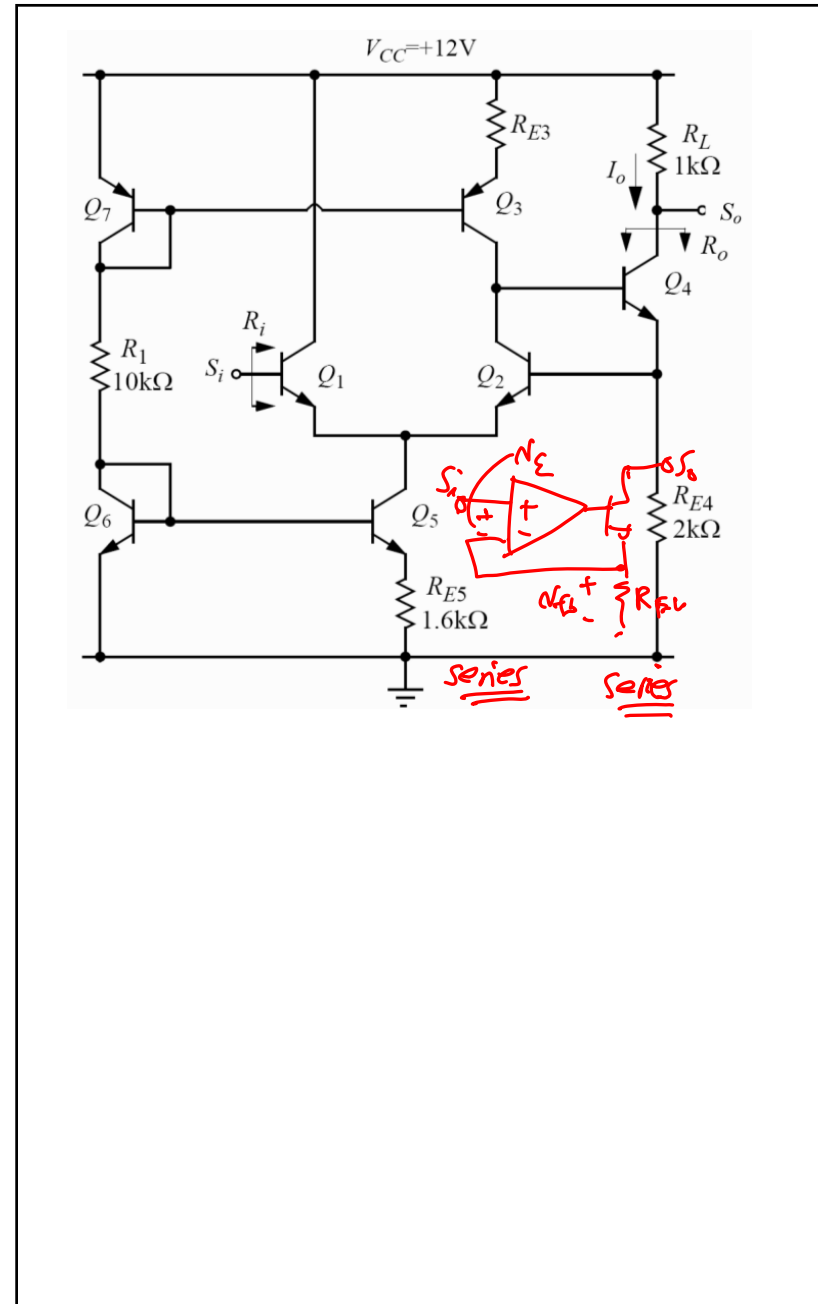
$$\omega_{-3dB} \text{ (closed-loop)} = (1+T) \times \omega_{-3dB} \text{ (OL w/ FB Loading)}$$



- What's next?
- **EE 240B: Advanced Analog Integrated Circuits**
- Analysis and optimized design of integrated analog systems and building blocks. Specific topics include operational and wide-band amplifiers, gain-bandwidth and power considerations, analysis of noise in integrated circuits, low noise design, feedback, precision passive elements, analog switches, comparators, CMOS voltage references, non-idealities such as matching and supply/IO/substrate coupling. The course will include a significant design project applying the techniques taught in class to implement the analog front-end of a high-speed serial link.
- **EE 142/242A: Integrated Ckts for Communication**
- Analysis and design of electronic circuits for communication systems, with an emphasis on integrated circuits for wireless communication systems. Analysis of noise and distortion in amplifiers with application to radio receiver design. Power amplifier design with application to wireless radio transmitters. Radio-frequency mixers, oscillators, phase-locked loops, modulators, and demodulators.
- **EE 147/247A: Introduction to MEMS**
- Physics, fabrication, and design of micro-electromechanical systems (MEMS). Micro and nanofabrication processes, including silicon surface and bulk micromachining and non-silicon micromachining. Integration strategies and assembly processes. Transduction strategies and mechanical circuits. Electronic position-sensing circuits and electrical and mechanical noise. CAD for MEMS.

- One more thing: (since many of you might be near graduation)
- The MAS-IC program
  - ↪ An internet-based Masters in Integrated Circuits from the UC Berkeley Dept. of EECS
  - ↪ This course, 240A, was actually offered as a MAS-IC course this semester, using pre-taped lectures from last Spring 2013 (more professionally taped than the ETS taping we did this semester)
  - ↪ If you're interested in getting a Masters Degree while working or otherwise remotely, this is an opportunity
  - ↪ Go to [www.eecs.berkeley.edu/masic](http://www.eecs.berkeley.edu/masic)