


Lecture 2: Device Models I (Bipolar Review)

- Announcements:
- The course website was up and running last week
 - ↳ Just google ee140 to get to it
- Discussion sections
 - ↳ M 4-5 p.m. in 241 Cory
 - ↳ F 4-5 p.m. at a location TBD (this one starts this week)
- HW#1 should be online later today ... due next Wednesday, at 8 a.m., in the 140/240A box on 1st floor (near the TI lab)
- TA office hours held in ~~367~~ ^{Soda Hall} Cory for now
 - ↳ Waiting to hear if the room needs to be changed
 - ↳ Actually, looks like it will be 238 Cory
- Lecture Topics:
- ↳ Review (fast)
- ↳ Bipolar Junction Transistor Modeling
 - Basic Structure & Physics
 - Large Signal Models
 - DC Operating Point
 - Small Signal Models
 - Frequency Shaping Elements
 - Layout
 - Unity Gain Frequency
- Last Time: Reviewed op amps and started into BJT modeling using the module handout
- Continue with the handout



Example | Find the DC operating pt.

⇒ want the I_c 's of all Xistors → g_m, r_o, \dots

Small-signal element

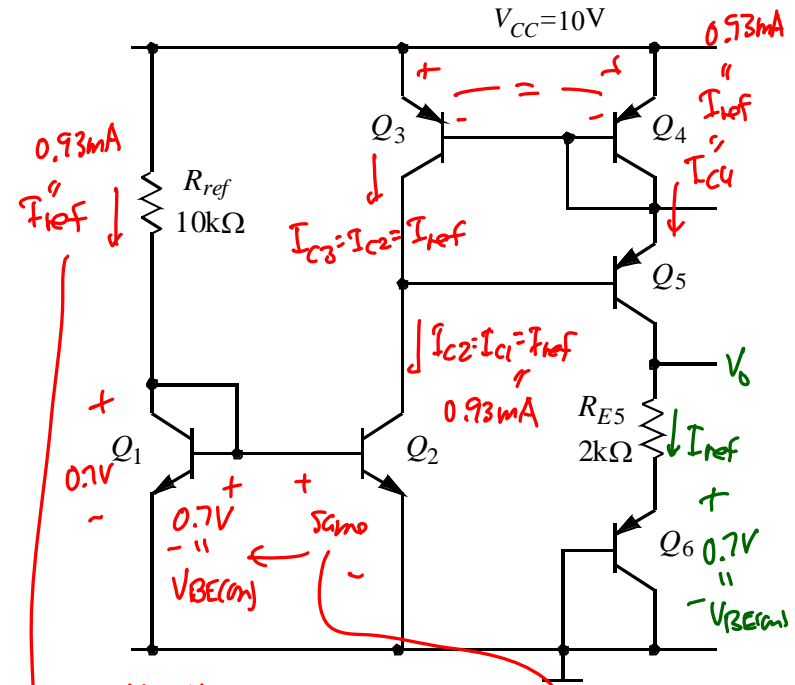
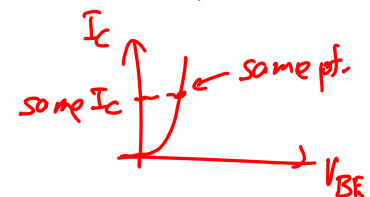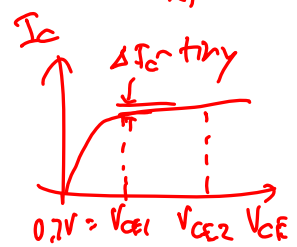
$$I_{ref} = \frac{V_{CC} - V_{BE(on)}}{R_{ref}} = \frac{10 - 0.7}{10k} = 0.93 \text{ mA}$$



$$V_o = V_{BE6(on)} + I_{E5} R_{E5} = 0.7 + (0.93\text{m})(2\text{k}) = 2.56\text{V}$$

For Q_5 to be FA, need:

$$V_o < \underbrace{V_{CC} - V_{BE4(on)} - V_{CE5(sat)}}_{10 - 0.7 - 0.2 = 9.1\text{V}} \quad \checkmark \quad Q_5 \text{ is FA!}$$

What if $R_{E5} > 20\text{k}\Omega$:

$$V_o = 0.7\text{V} + (0.93\text{m})(20\text{k}) = 19.3\text{V} \quad \rightarrow \quad \text{X} \quad Q_5 \text{ is saturated!}$$

$$V_o = V_{CC} - V_{BE4(on)} - V_{CE5(sat)} = 9.1\text{V}$$

$$I_{E5} = \frac{V_o - V_{BE6(on)}}{R_{E5}} = \frac{9.1 - 0.7}{20\text{k}} = \underline{\underline{0.42\text{mA}}}$$