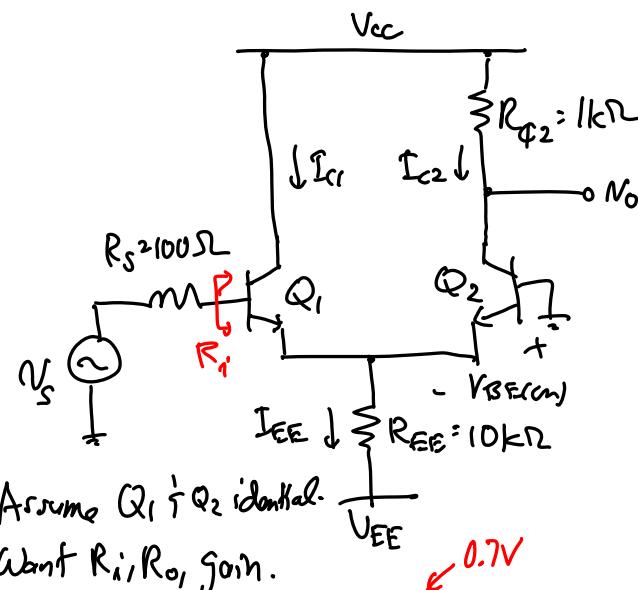


Lecture 5: MOS Inspection Analysis

- Announcements:
- Handed out computer account sheets
- Lecture Topics:
  - ↳ Multi-Tx Amplifier Examples
  - ↳ MOS Inspection Analysis
- -----
- Last Time:
- Multi-TX inspection analysis
- Continue with this

Inspection Analysis of a Multi-Transistor Circ.




Find the DC operating pt.

$$I_{EE} = \frac{-V_{BE(ON)} - V_{EE}}{R_{EE}}$$


$$I_{C1} = I_{C2} = \frac{I_{EE}}{2}$$

$$g_m = g_{mr} = g_{m2}$$

$$r_{in} = r_{T1} = r_{T2}$$

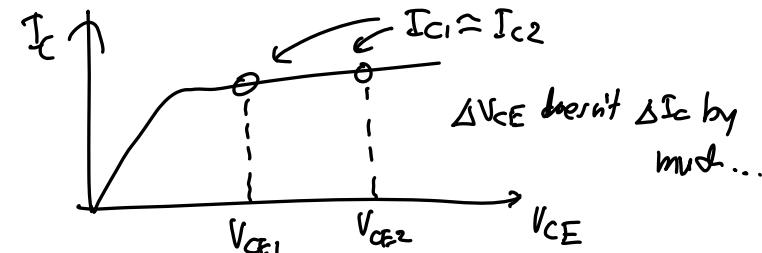

Draw the S.S. Circ:

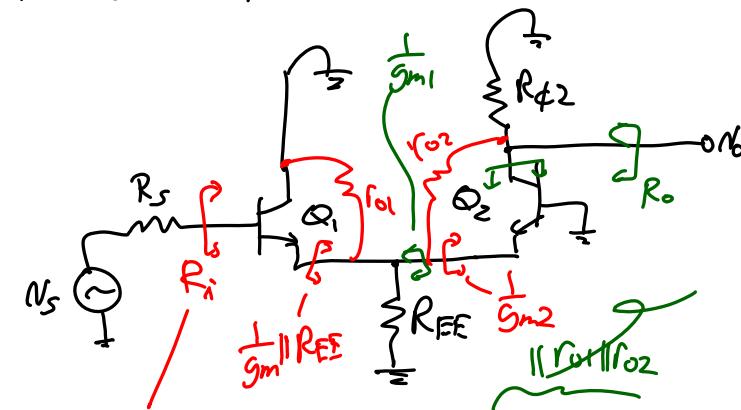

$$R_i = r_{T1} + (\beta + 1)R_E = r_{T1} + (\beta + 1)(R_{EE} \parallel \frac{1}{g_{m2}})$$



$$[R_{EE} \gg \frac{1}{g_{m2}}] \rightarrow R_i \approx r_{T1} + \frac{(\beta + 1)}{g_{m2}}$$

$$R_o = 2r_{o2} \quad \text{assuming } R_s \text{ small}$$

$$R_o = R_{o2} \parallel r_{o2} \left( 1 + \frac{\frac{1}{g_{m2}} \left( \frac{1}{g_{m1}} + \frac{R_s}{\beta + 1} \right)}{1 + \frac{1}{g_{m2}}} \right)$$

$$= R_{o2} \parallel (2r_{o2}) \approx R_{o2}$$

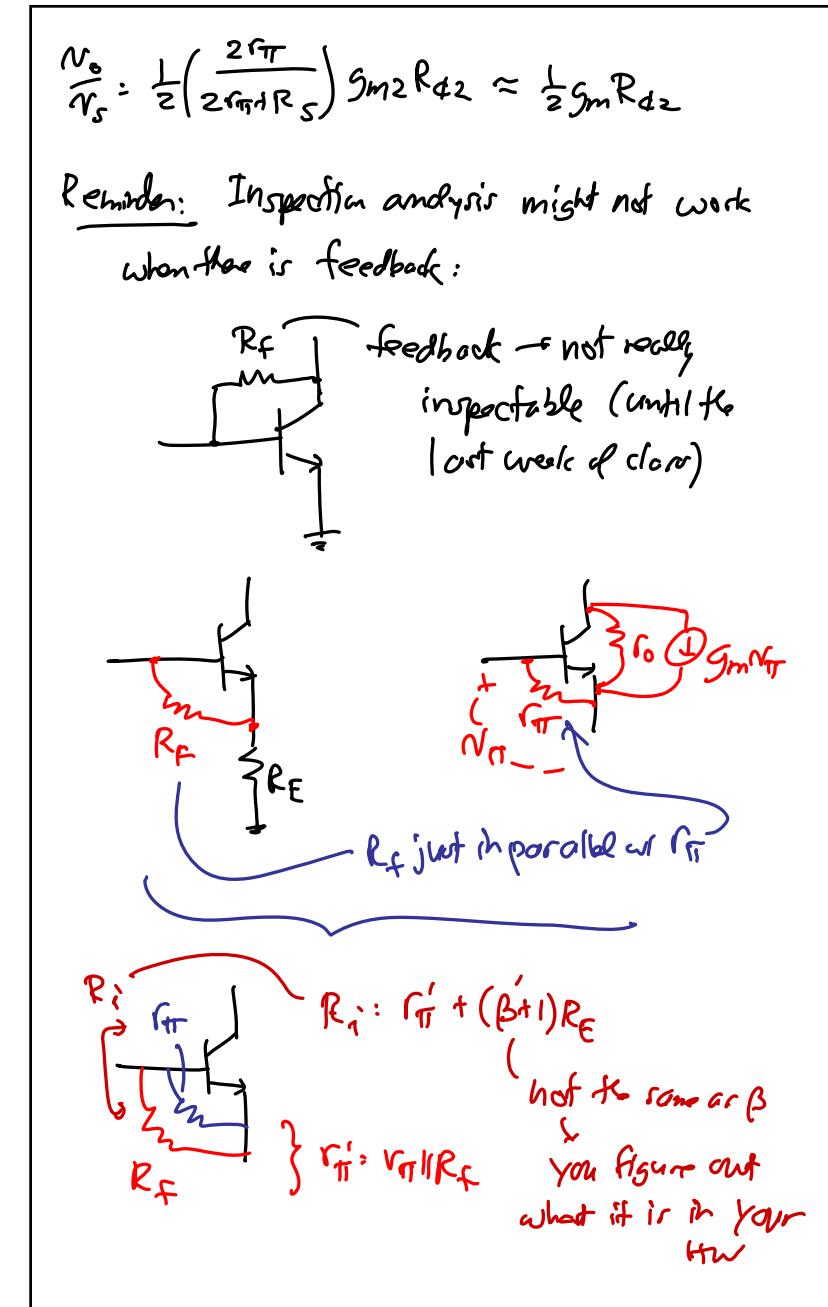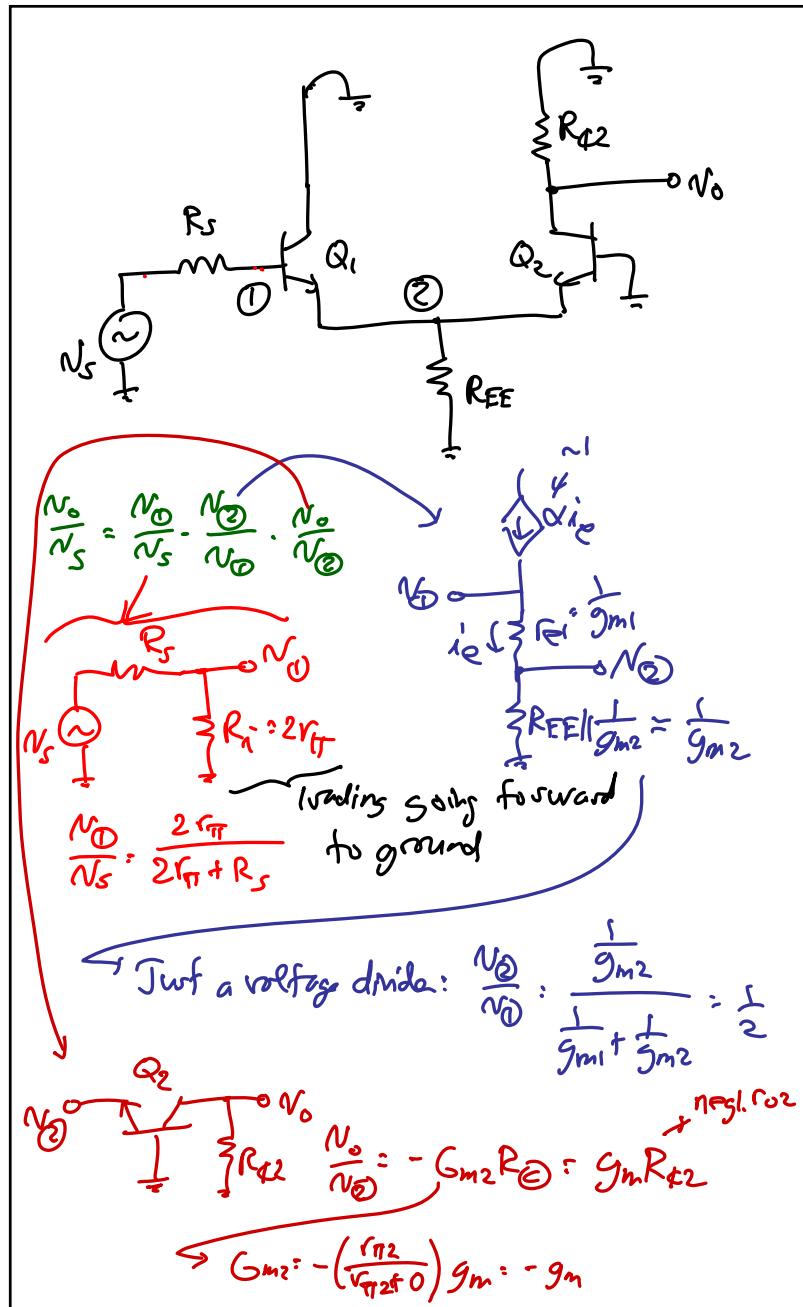
$$50\text{k}\Omega - 10\mu\text{A} \quad [2r_{o2} \gg R_{o2}]$$



## Lecture 5w: MOS Inspection Analysis
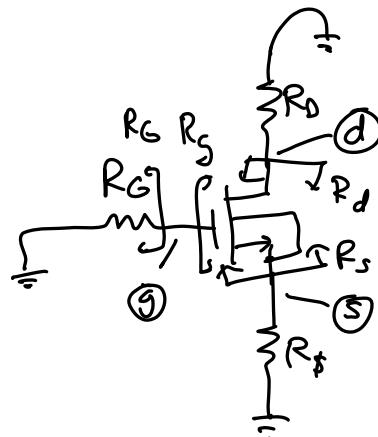
## MOS Xntrn Ckfs.

$\Rightarrow$  for now, ignore Body effect (i.e., ignore  $g_{mb}$ )  
 ↳ use the same inspection formulas as bipolar,  
 but use  $B \rightarrow \infty$ ,  $r_{ff} = \frac{B}{g_m} \rightarrow \infty$



$\Rightarrow$  referring to the bipolar "Inspection Formula" sheet:

Bipolar

$$R_b = \left( \frac{1}{g_m + R_E} \right) (B+1) \xrightarrow{B \rightarrow \infty} R_g = \infty$$

$$R_e = \frac{1}{g_m} + \frac{R_B}{B+1} \xrightarrow{B \rightarrow \infty} R_s = \frac{1}{g_m}$$

$$R_c = r_o \left[ 1 + \frac{g_m R_E}{1 + R_E / r_{ff}} \right] \xrightarrow{r_{ff} \rightarrow \infty} R_d = r_o (1 + g_m R_f)$$

MOS


$$\frac{N_d}{N_g} = -G_m R_D \quad , \quad G_m = \frac{g_m}{1 + g_m R_f}$$

$$\frac{N_d}{N_s} = -G_m R_D \quad , \quad G_m = -g_m$$

$$\frac{N_s}{N_g} = \frac{g_m R_f}{1 + g_m R_f} = \frac{R_f}{g_m + R_f}$$

## MOS Inspection Analysis

Ex. Common-Source Common-Drain Cascade

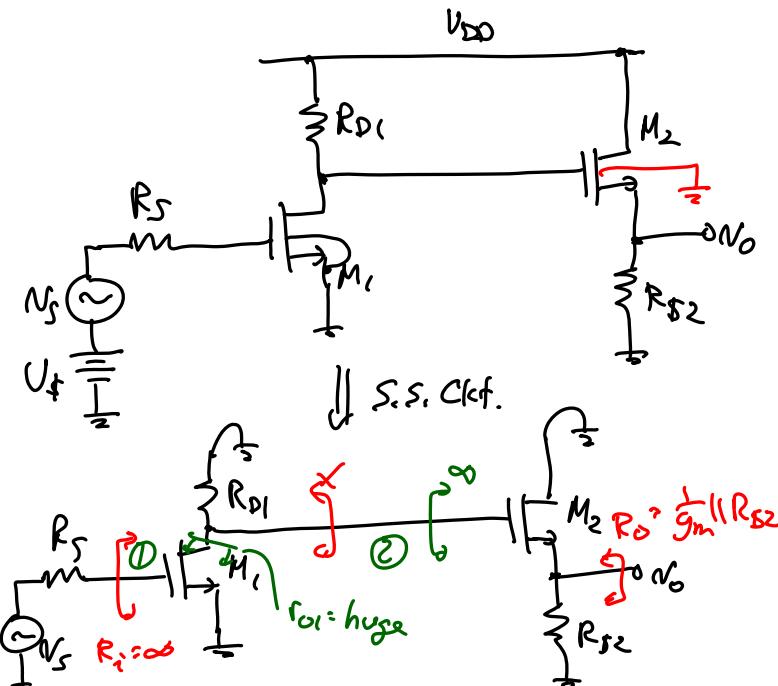

## Lecture 5w: MOS Inspection Analysis


$$\frac{V_o}{V_s} = \frac{N_0}{N_s} \cdot \frac{N_{(2)}}{N_{(1)}} \cdot \frac{N_0}{N_{(2)}}$$

$$= (1) (-g_{mr} R_{D1}) \left( \frac{R_{S2}}{g_{m2} + R_{S2}} \right) = \frac{N_0}{N_s}$$

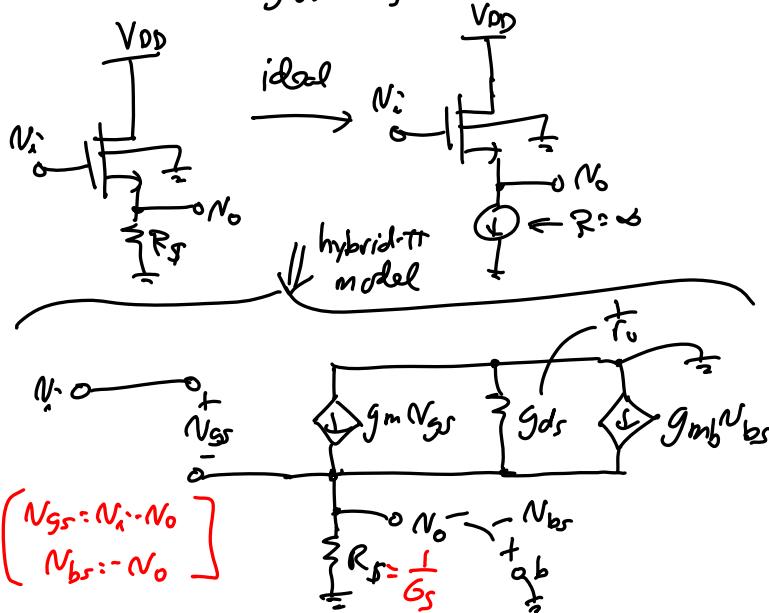Problem, Simulate in SPICE  $\rightarrow$  the gain will be  
 ~90% of what is calculated using  
 the problem is w/  $g_{mb}$  in the source follower

$\Rightarrow$  there is the difference  
 between bipolar & MOS  
 hybrid- $\pi$  models

Source Follower: (w/ substrate  
 grounded)



$$g_m(N_s - N_0) = N_0(g_{ds} + G_f + g_{mb})$$

$$\Rightarrow A_{v1} = \frac{N_0}{N_s} = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_f}$$



$$\left[ \begin{array}{l} R_s \rightarrow \infty \rightarrow G_s = 0 \\ g_{ds} \ll g_m + g_{mb} \end{array} \right]$$

Body factor

$$A_v \approx \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}, \quad \eta = \frac{g_{mb}}{g_m} = \frac{\gamma}{2\sqrt{V_{SB} + 2\phi}}$$


$\neq 1$

To make it '1', do this:

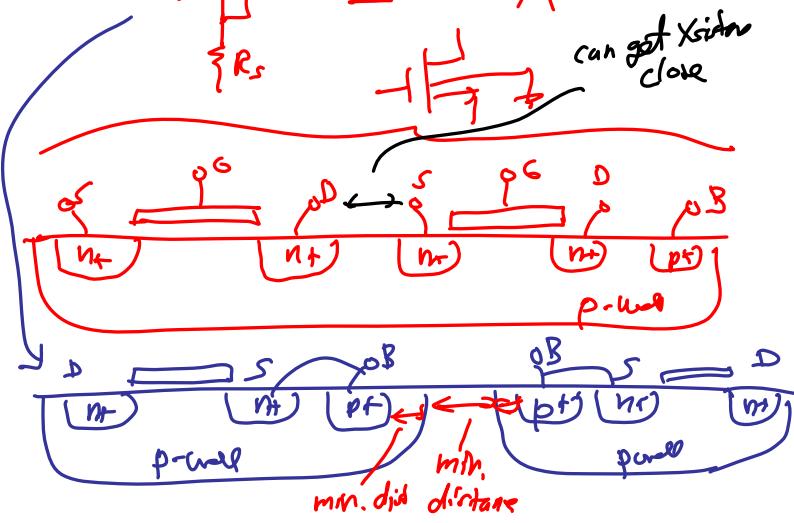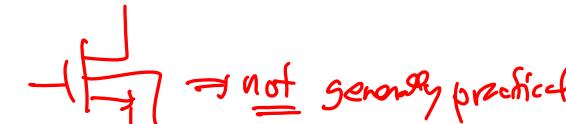

## Lecture 5w: MOS Inspection Analysis

X Need min. distances between wells when transistors have their own wells  $\rightarrow$  takes more chip area  
bad  $\rightarrow$  Cost!

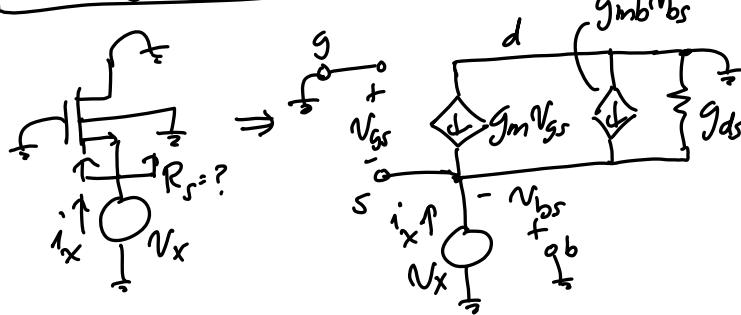Effect of  $g_{mb}$  on Impedance

$$\begin{cases} V_{gs} = -V_x = V_{bs} \\ V_{ds} = -V_x \end{cases}$$

$G_m + g_{mb} + g_{ds}$

$$R_o = \frac{1}{g_{m+g_{mb}} + g_{ds}} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel R_o$$

$\downarrow$


$$[g_{ds} \ll g_{m+g_{mb}}]$$

$$R_o \approx \frac{1}{g_{m+g_{mb}}}$$

$\Rightarrow$  more extensive analysis shows that other inspection formulas change to accommodate a grounded body by replacing "gm" in the denominator w/ "gm+gmb"

$\Rightarrow$  end up w/ the following:
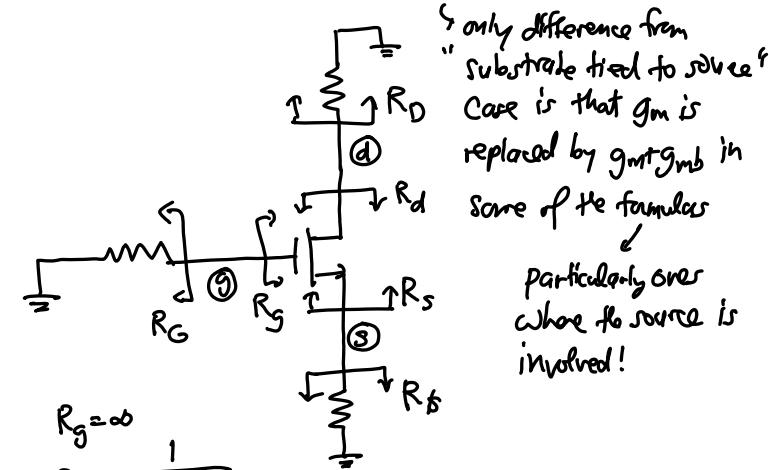
## MOS Inspection Formulas w/ Substrate Grounded



$$R_g = \infty$$

$$R_s = \frac{1}{g_{m+g_{mb}}}$$

$$R_d = R_s [1 + (g_m + g_{mb}) R_b]$$

$$\frac{V_d}{V_g} = -G_m R_d \quad , \quad G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_b}$$

$$\frac{V_d}{V_s} = -G_m R_b \quad , \quad G_m = -(g_m + g_{mb})$$

$$\frac{V_s}{V_g} = \frac{g_m R_b}{1 + (g_m + g_{mb}) R_b}$$

Remark: When the substrate is tied to the source,  $g_{mb} = 0$ .

only difference from "substrate tied to source"  
 Case is that  $g_m$  is replaced by  $g_m + g_{mb}$  in some of the formulas  
 particularly over where the source is involved!