


**Lecture 6: Frequency Response Inspection Analysis**

- Announcements:
- HW#2 due tomorrow at 8 a.m.
- HW#3 now online soon; Lab#1 online
- Lecture Topics:
  - ↳ Amplifier Bode plot
  - ↳ Open Circuit Time Constant (OCTC) Analysis
  - ↳ Frequency Response Inspection Analysis

• Last Time:

**MOS Inspection Analysis**

Ex. Common-Source Common-Drain Cascode

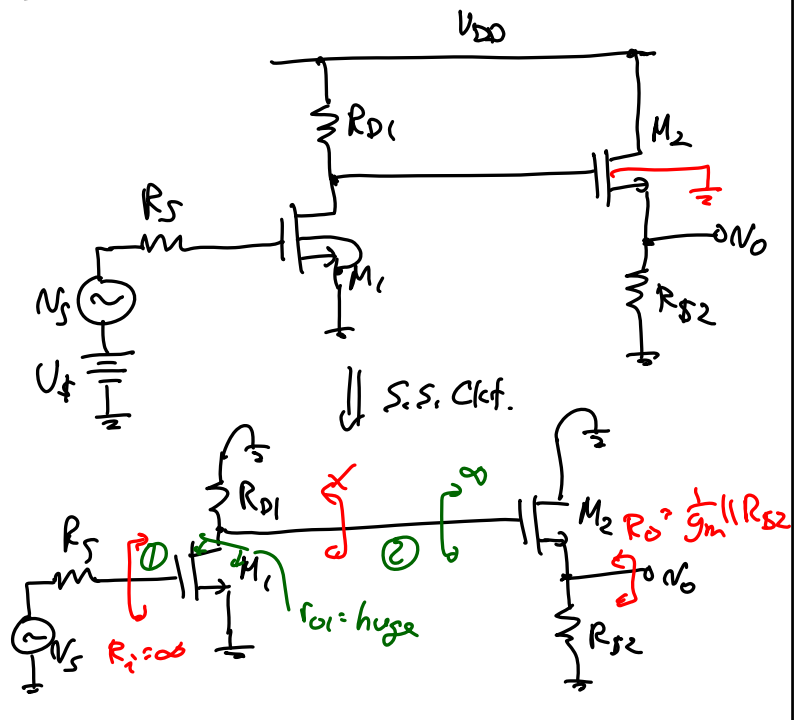


$$\frac{V_o}{V_s} = \frac{V_{D1}}{V_s} \cdot \frac{V_{D2}}{V_{D1}} \cdot \frac{V_o}{V_{D2}}$$

$$= (1) (-g_{m1} R_{D1}) \left( \frac{R_{S2}}{\frac{1}{g_{m2}} + R_{S2}} \right) = \frac{V_o}{V_s}$$

Problem: Simulate in SPICE → the gain will be 80-90% of what is calculated using the problem is w/  $g_{mb}$  in the source follower

this is the difference between bipolar & MOS hybrid-π models

Source Follower: (w/ substrate grounded)

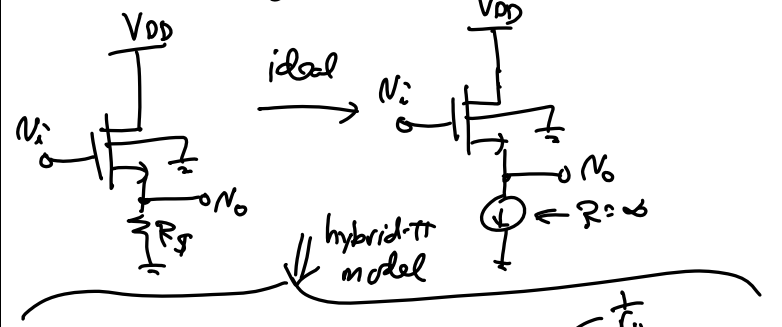

$$\begin{bmatrix} V_{gs} = V_i - V_o \\ V_{bs} = -V_o \end{bmatrix}$$

$$g_m(V_i - V_o) = V_o(g_{ds} + G_f + g_{mb})$$

$$\Rightarrow A_v = \frac{V_o}{V_i} = \frac{g_m}{g_m + g_{mb} + g_{ds} + G_f}$$


$R_s \rightarrow \infty \rightarrow G_f = 0$   
 $g_{ds} \ll g_m + g_{mb}$

Body factor


$$A_v \approx \frac{g_m}{g_m + g_{mb}} = \frac{1}{1 + \eta}, \quad \eta = \frac{g_{mb}}{g_m} = \frac{\gamma}{2\sqrt{V_{GS} - 2\phi_f}}$$

$\neq 1$


To make it '1', do this:

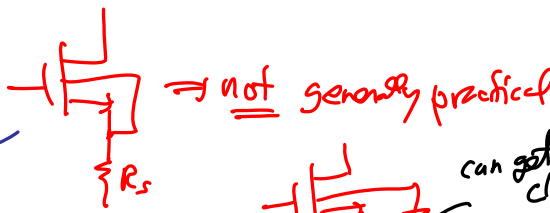

not generally practical



can get Xsistns close

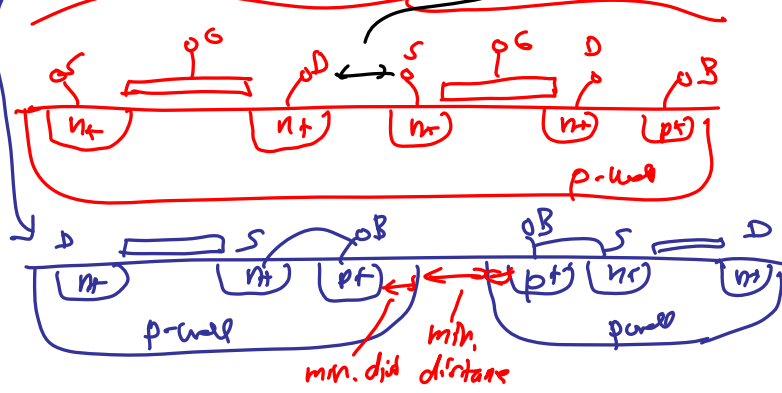


p-well

min. dist. distance

X Need min. distances between wells when Xsistns have their own wells  $\rightarrow$  takes more chip area  $\rightarrow$  Cost!

Effect of  $g_{mb}$  on Impedance

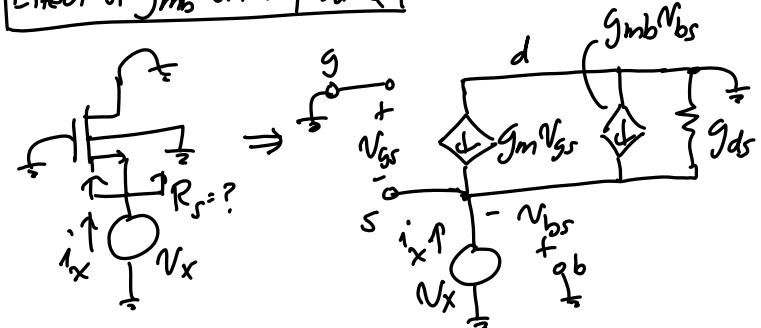

$V_{GS} = -V_X = V_{BS}$   
 $V_{DS} = -V_X$

$$R_o = \frac{1}{g_m + g_{mb} + g_{ds}} = \frac{1}{g_m} \parallel \frac{1}{g_{mb}} \parallel r_o$$

$g_{ds} \ll g_m + g_{mb}$

$$R_o \approx \frac{1}{g_m + g_{mb}}$$

$\Rightarrow$  more extensive analysis shows that other inspection formulas change to accommodate a grounded body by replacing "g<sub>m</sub>" in the denominator w/ "g<sub>m</sub>+g<sub>mb</sub>"

$\Rightarrow$  end up w/ the following:

**MOS Inspection Formulas w/ Substrate Grounded**

only difference from "substrate tied to source" case is that  $g_m$  is replaced by  $g_m + g_{mb}$  in some of the formulas particularly over where the source is involved!

$$R_g = \infty$$

$$R_s = \frac{1}{g_m + g_{mb}}$$

$$R_d = r_o [1 + (g_m + g_{mb}) R_s]$$

$$\frac{N_d}{N_g} = -G_m R_{\text{node}}, \quad G_m = \frac{g_m}{1 + (g_m + g_{mb}) R_s}$$

$$\frac{N_d}{N_s} = -G_m R_{\text{node}}, \quad G_m = -(g_m + g_{mb})$$

$$\frac{N_s}{N_o} = \frac{g_m R_s}{1 + (g_m + g_{mb}) R_s}$$

Remark: When the substrate is tied to the source,  $g_{mb} = 0$ .

**Poles & Zeros  $\rightarrow$  Bode Plots**

Complex variable  $\rightarrow j\omega$

midband gain  $a_0$

$$a(s) = \frac{N_o}{N_i}(s) = \frac{a_0}{(1 + \frac{s}{\omega_{p1}})(1 + \frac{s}{\omega_{p2}}) \dots}$$

3dB down =  $\omega = 3\text{dB}$

20 dB/dec

Distance between  $\omega_{p1}$  &  $\omega_{p2}$  often decides whether or not a PB ckt using is stable or not!

Want this large

0.1|p<sub>1</sub>|, |p<sub>1</sub>|, 10|R<sub>1</sub>|, |p<sub>2</sub>|, 10|p<sub>2</sub>|, 0.1|p<sub>2</sub>|, |p<sub>3</sub>|, 10|p<sub>3</sub>|


0.1|p<sub>1</sub>|, |p<sub>1</sub>|, 10|R<sub>1</sub>|, |p<sub>2</sub>|, 10|p<sub>2</sub>|, 0.1|p<sub>2</sub>|, |p<sub>3</sub>|, 10|p<sub>3</sub>|

-90°, -180°, -270°

Total Phase Response

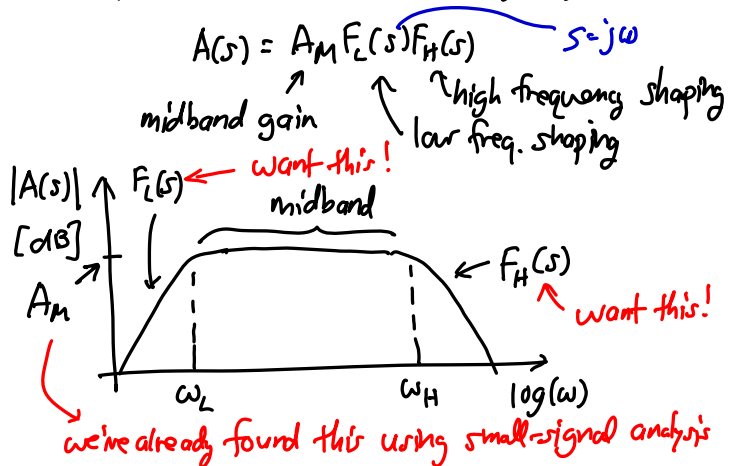**Freq. Response**

Recall that the transfer function of a general amplifier can be expressed as a function of frequency via:



**High Freq. Response Determination Using Open Ckt. Time Constant (OCTC) Analysis**

In general:

$$F_H(s) = \frac{1 + a_1 s + a_2 s^2 + \dots + a_{n_z} s^{n_z}}{1 + b_1 s + b_2 s^2 + \dots + b_{n_p} s^{n_p}}, \quad n_p > n_z$$

$$= \frac{\prod_{j=1}^{n_z} (1 - \frac{s}{z_j})}{\prod_{i=1}^{n_p} (1 - \frac{s}{p_i})} = \frac{\prod_{j=1}^{n_z} (1 + \frac{s}{\omega_{zj}})}{\prod_{i=1}^{n_p} (1 + \frac{s}{\omega_{pi}})}$$

from which:

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \dots + \frac{1}{\omega_{pn_p}} = \sum_{i=1}^{n_p} \frac{1}{\omega_{pi}} = \sum_{k=1}^{n_p} \tau_{pk}$$

$\uparrow$  coeff. of the 1<sup>st</sup> order term

Through network theory, one can prove that: (see Gray & Meyer, Chpt. 7)

$$\sum_{i=1}^{n_p} \tau_{pi} = \sum_j C_j R_{j0} = \sum_j \tau_{j0}$$

where  $C_j$  are capacitors in the H.F. ckt., i.e., small ones  
 $R_{j0} \hat{=}$  driving pt. resistance seen between the terminals of  $C_j$  determined with

- ① all small (< 1nF) capacitors open-circuited
- ② all independent sources eliminated (i.e., short voltage sources, open current sources)
- ③ short all large (coupling/bypass) capacitors (i.e., > 1μf or > 1nF)

In calculating the H.F. response, we use the dominant pole approximation:

(i)  $\omega_{p1} \ll \omega_{p2}, \dots, \omega_{pn_p}$

(ii)  $F_H(s) \cong \frac{1}{1 + \frac{s}{\omega_H}}$

(ii)  $b_1 \cong \frac{1}{\omega_{p1}} \rightarrow \omega_H = \omega_{p1} \cong \frac{1}{b_1} = \frac{1}{\sum_j \tau_{j0}} = \frac{1}{\sum_j C_j R_{j0}}$

When there is no dominant pole, an approximate expression for  $\omega_H$  is:

$$\omega_H \approx \sqrt{\frac{1}{\omega_{p1}^2 + \omega_{p2}^2 + \dots - \omega_{z1}^2 - \omega_{z2}^2 - \dots}}$$

(just FYI)

• Now, go to inspection formula sheet and go over how to use the frequency response parts

Example H.F. Analysis (C.F. Ckt.)  
 ⇒ just start w/ s.s. Ckt. (biasing not shown)

Find  $\tau_{\text{O1}}$ :

$R_{\text{O1}} = R_s \parallel R_B \parallel r_{\pi}$   
 $\tau_{\text{O1}} = C_{\pi} (R_s \parallel R_B \parallel r_{\pi})$

Find  $\tau_{\text{uo}}$ :

$R_{\text{uo}}: \frac{v_x}{i_x} = R_{\text{O1}} + R_{\text{O2}} + g_m R_{\text{O1}} R_{\text{O2}}$   
 $R_{\text{O2}} = (R_s \parallel R_B \parallel r_{\pi}) + r_o \parallel R_f$   
 $+ g_m (R_s \parallel R_B \parallel r_{\pi}) R_f$   
 $\tau_{\text{uo}} = C_{\mu} R_{\text{uo}}$

Find  $\tau_{\text{O2}}$   $\tau_{\text{O2}} = C_{cs} (r_o \parallel R_f) \approx C_{cs} R_f$   
 $[r_o \gg R_f]$

$\omega_H = \frac{1}{\tau_{\text{O1}} + \tau_{\text{uo}} + \tau_{\text{O2}}}$

Now, use Miller's Theorem:

$C_M = (1 - a_v) C_{\mu} = (1 + g_m R_f) C_{\mu}$

$\tau_{\text{O1}} = (R_s \parallel R_B \parallel r_{\pi}) (C_{\pi} + (1 + g_m R_f) C_{\mu})$   
 $\tau_{\text{O2}} = (C_{\mu} + C_{cs}) R_f$

$\omega_H = \frac{1}{\tau_{\text{O1}} + \tau_{\text{O2}}}$

Equal!

**Multistage Ex.**

$\tau_0 = C_{\mu 1} (R_S \parallel (2r_{\pi 1}))$   
 $\tau_{\pi 1} = C_{\pi 1} (r_{\pi 1} \parallel \frac{R_C + \frac{1}{g_{m2}}}{1 + g_{m1}(\frac{1}{g_{m2}})})$   
 $\tau_2 = C_{\pi 2} \left[ \left( \frac{1}{g_{m1}} + \frac{R_S}{\beta + 1} \right) \parallel \frac{1}{g_{m2}} \parallel R_{EE} \right]$   
 $\tau_3 = (C_{c2} + C_{\mu 2}) R_{L2}$

$\omega_H = \frac{1}{\tau_0 + \tau_2 + \tau_3 + \tau_{\pi 1}}$

*assume large* (pointing to  $R_{EE}$ )  
*neg!* (pointing to  $\tau_{\pi 1}$ )

**MOS Two-Stage Amplifier**

$\tau_0 = C_{gs1} (R_S \parallel (2r_{\pi 1}))$   
 $\tau_{\pi 1} = C_{\pi 1} (r_{\pi 1} \parallel \frac{R_C + \frac{1}{g_{m2}}}{1 + g_{m1}(\frac{1}{g_{m2}})})$   
 $\tau_2 = C_{gs2} \left[ \left( \frac{1}{g_{m1}} + \frac{R_S}{\beta + 1} \right) \parallel \frac{1}{g_{m2}} \parallel R_{EE} \right]$   
 $\tau_3 = (C_{c2} + C_{\mu 2}) R_{L2}$

$\omega_H = \frac{1}{\tau_0 + \tau_2 + \tau_3 + \tau_{\pi 1}}$

*assume large* (pointing to  $R_{EE}$ )  
*neg!* (pointing to  $\tau_{\pi 1}$ )