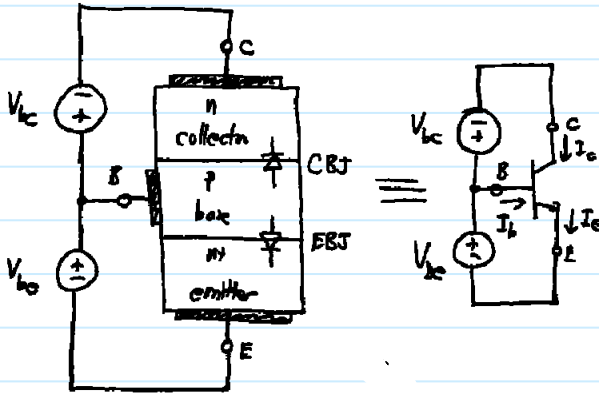



Modeling the Bipolar Junction Transistor (BJT)

⇒ physically, BJTs are just back-to-back pn junctions

npn bipolar Xsistor



ppn bipolar Xsistor

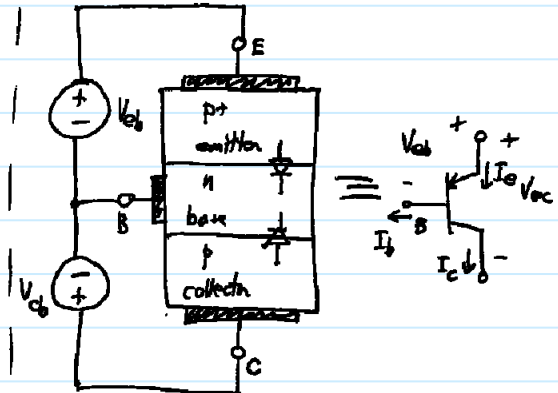


Regions of Bipolar Xsistor Operation

EBJ	CBJ	Mode
R	R	Cut-off (both diodes off)
F	R	Forward Active (widely used in analog amplification ckt)
R	F	Reverse Active
F	F	Saturation

Key: R = reverse-biased, F = forward-biased

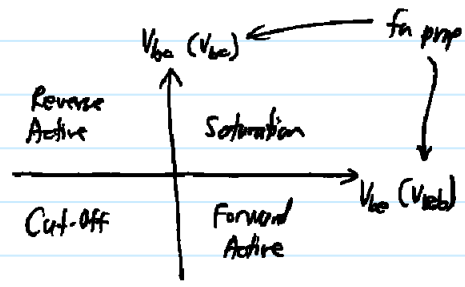
⇒ can also think of this in a convenient graphical sense:
 → for npn (ppn):



① Cut-off Region - (npn transistor)



⇒ both diodes reverse-biased
 ⇒ no current flows:

$I_b = 0, I_c = 0, I_e = 0$

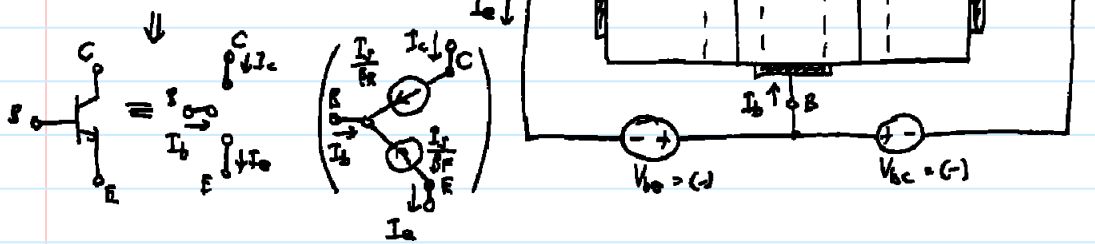

② Forward-Active Region - (npn transistors)

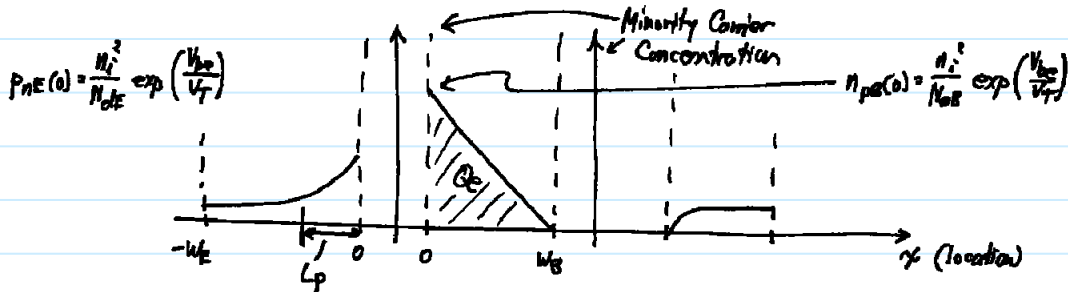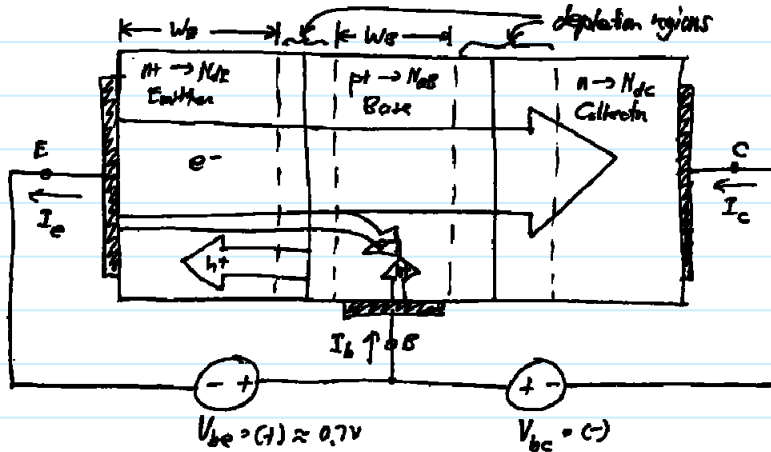⇒ BEJ Forward Biased (i.e., diode on), BCJ Reverse-Biased (i.e., diode off)



Forward biasing of the BEJ generates three current components:

- ① e⁻'s injected from emitter to base: $I_{nB} = -A J_{nB}^{diff}$
 - ② h⁺'s injected from base to emitter: $I_{pE} = A J_{pE}^{diff}$
 - ③ recombination of e⁻'s & h⁺'s in base: I_{rB}
- $I_C = I_{nB} = 0$
 $I_E = I_{nB} + I_{pE} + I_{rB} = ① + ② + ③$
 $I_B = I_{pE} + I_{rB} = ② + ③$

$$I_{nB} = -A J_{nB}^{diff} = -A q D_{nB} \frac{dn_p(x)}{dx} = -q A D_{nB} \frac{[n_{pB}(w_B) - n_{pB}(0)]}{w_B} = \boxed{q A D_{nB} \frac{n_i^2}{N_D w_B} \exp\left(\frac{V_{BE}}{V_T}\right) = ①} *$$

diffusion constant for e⁻'s in B
 slope
 $n_{pB}(w_B) = \frac{n_i^2}{N_D} \exp\left(\frac{V_{BC}}{V_T}\right) \approx 0$
 $n_{pB}(0) = \frac{n_i^2}{N_D} \exp\left(\frac{V_{BE}}{V_T}\right)$
 $I_C = I_{rB} \exp\left(\frac{V_{BE}}{V_T}\right)$

$$I_{pE} = A J_{pE}^{diff} = A q D_{pE} \frac{dp_n(x)}{dx} = q A D_{pE} \frac{[p_n(0) - p_n(-w_E)]}{w_E} = \boxed{q A D_{pE} \frac{n_i^2}{N_A w_E} \exp\left(\frac{V_{BE}}{V_T}\right) = ②} *$$

diffusion constant for h⁺'s in E
 slope
 $p_n(0) = \frac{n_i^2}{N_A} \exp\left(\frac{V_{BE}}{V_T}\right)$
 $p_n(-w_E) \approx 0$
 could also replace by diffusion length, L_p (for h⁺ in n-type material)

minority-carrier charge in base

$$I_{IB} = \frac{Q_E}{\tau_b} = \frac{1}{\tau_b} \left[\frac{1}{2} n_{p0}(0) W_B q A \right] = \frac{1}{2} \frac{n_i^2 W_B q A}{N_B \tau_b} \exp\left(\frac{V_{BE}}{V_T}\right) = \textcircled{3} \quad *$$

minority carrier lifetime in base

Define Forward Current Gain = β_F :

$$\beta_F = \frac{I_C}{I_B} = \frac{\textcircled{1}}{\textcircled{3} + \textcircled{2}} = \frac{\frac{q A D_n n_i^2}{N_B W_B}}{\frac{I_n^2 W_B q A}{2 N_B \tau_b} + \frac{q A D_p n_i^2}{N_{DE} W_E}} = \left[\frac{W_B^2}{2 \tau_b D_n} + \frac{D_p W_B N_A}{D_n W_E N_D} \right]^{-1}$$

N_{DE}
 \uparrow
 L_p
 \uparrow
 N_{DE}

To maximize β_F , want: ① $W_B = \text{small}$

② $N_{DE} \gg N_B$ (this is why emitter is nt) \rightarrow also leads to $D_{pE} \ll D_{nE}$ which we also want

③ $\tau_b = \text{large}$ (base Si must be free of impurities/defects to prevent recombination)

More Complete Expression for β_F :

$$\beta_F = \underbrace{\frac{N_B W_B}{D_n} \frac{D_n}{N_{DE} L_p}}_{\text{Injection Efficiency}} + \underbrace{\frac{1}{2} \left(\frac{W_B}{L_n} \right)^2}_{\text{Volume Recombination}} + \underbrace{s \left(\frac{A_s}{A_E} \right) \left(\frac{W_B}{D_n} \right)}_{\text{Surface Recombination}} + \underbrace{\frac{W_E N_B W_B}{2 D_n \tau_n}}_{\text{Recombination in the BE Depletion Region}} e^{-\frac{V_{BE}}{2V_T}}$$

Significant @ low current levels

Where: s = Surface recombination velocity

D_i = Diffusion constant

n_i = intrinsic carrier concentration

N_i = carrier concentration


A_E = total emitter area

A_s = sidewall emitter area


τ = minority carrier lifetime

L_i = diffusion length ($L_i = \sqrt{D_i \tau}$)

W_B = active base width

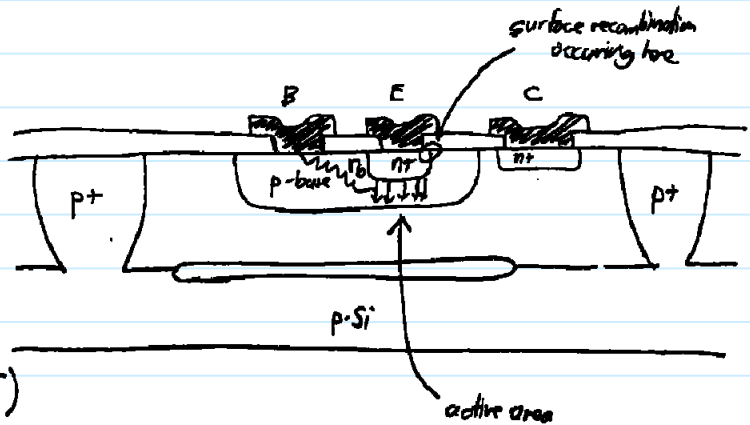

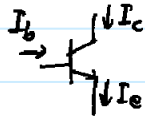So β relates I_b & I_c . To relate I_c & I_e , use KCL:





$$I_e = I_c + I_b = I_c + \frac{I_c}{\beta} = (1 + \frac{1}{\beta}) I_c$$


$$\Rightarrow I_c = (\frac{1}{1 + \frac{1}{\beta}}) I_e = (\frac{\beta}{\beta + 1}) I_e = \alpha I_e, \text{ where } \alpha = \frac{\beta}{\beta + 1} \Rightarrow \beta = \frac{\alpha}{1 - \alpha}$$

Equivalent Large Signal Ckt. Models for Forward-Active BJTs

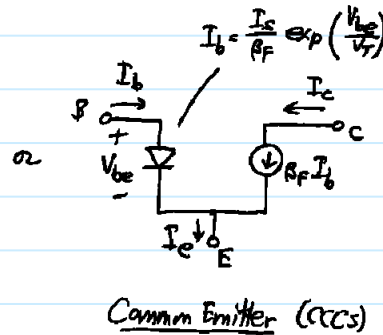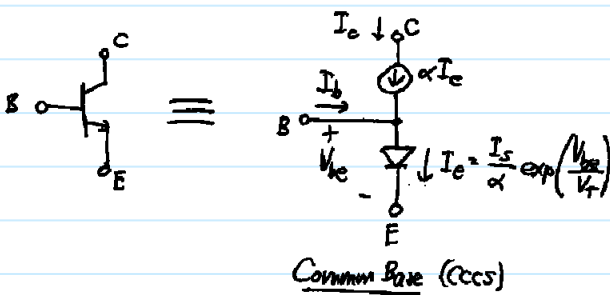
There are several of them. The most useful ones are:



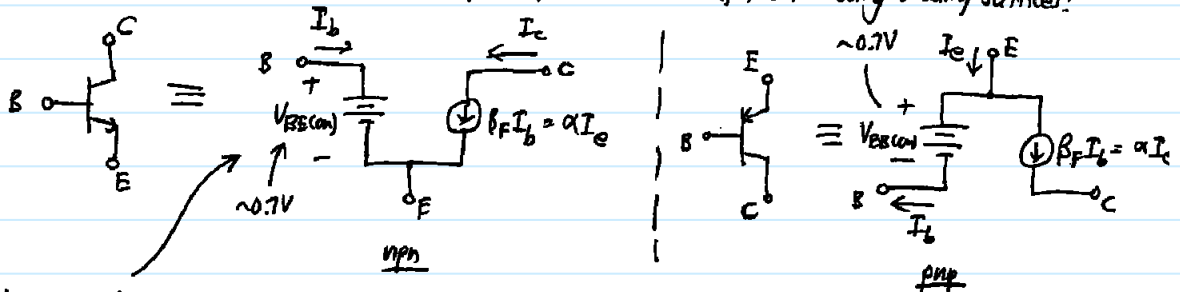But usually one doesn't have to use those complicated models. Rather, the following usually suffices:



Just as in a diode:

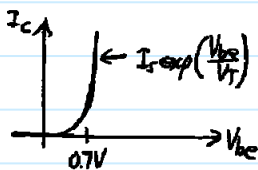

You should already be used to using approximate models like this
 \Rightarrow the more complicated models are a waste of time in comparison

③ Reverse-Active Region -

\Rightarrow very similar to forward-active region except now: BEJ reverse-biased

BCJ forward-biased


\Rightarrow one important difference: $\beta_R \propto \frac{N_{ac} W_B D_B}{N_{ab} W_B D_C}$ \rightarrow since collectn is n -
 $N_{ac} \ll N_{ab} \rightarrow D_B \ll D_C$
 $\therefore \beta_R$ is much smaller than β_F
 \Rightarrow poor device performance

④ Saturation Region-

BEJ forward-biased $\rightarrow V_{BE(sat)} \sim 0.8V$ (higher than 0.7V in saturation)

BCJ forward-biased $\rightarrow V_{BC(sat)} \sim 0.6V$

Result:

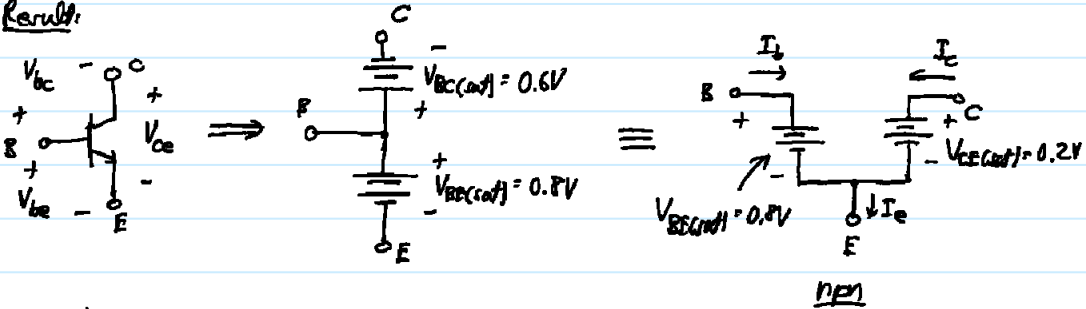

\Rightarrow currents now determined by the attached elements & KCL:



$$I_e = I_b + I_c ; \text{ no longer have } I_b = \frac{I_c}{\beta} \text{ or } I_c = \alpha I_e$$

These no longer apply when BJT is in saturation.

When determining DC operating point:


- Pass $\left\{ \begin{array}{l} \text{① Assume forward-active} \rightarrow \text{check for cut-off (enough } V_{be}?) \\ \text{② Determine } V_{ce} \\ \text{③ If } V_{ce} > V_{ce(sat)} = 0.2V, \text{ then ok (i.e., it's forward-active) ... otherwise, must do the} \\ \text{analysis over assuming saturation.} \end{array} \right.$

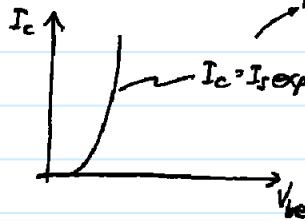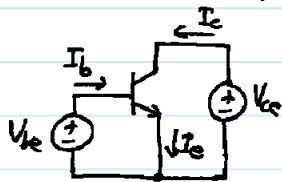IV Characteristics of Bipolar Junction Transistors




nonlinear \rightarrow not easy to work since we can't use linear system theory \rightarrow then need to linearize!
 (a diode-like characteristic) digital str. \rightarrow presence of analog str. \rightarrow small-signal models

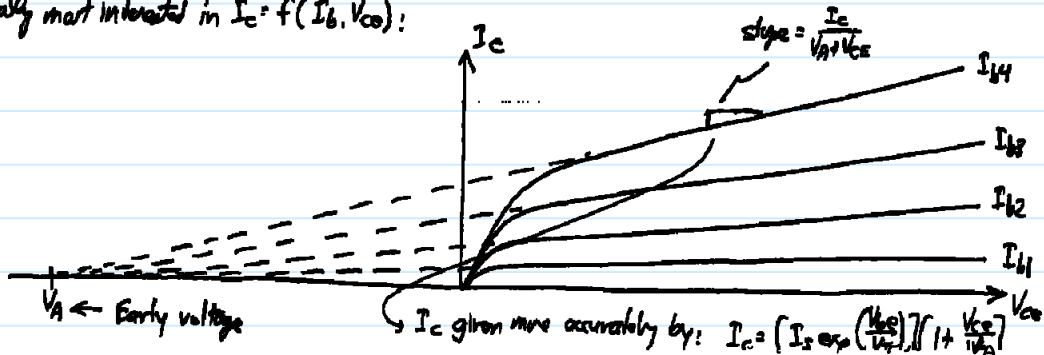\rightarrow really most interested in $I_c = f(I_b, V_{ce})$:



I_c given more accurately by: $I_c = [I_s \exp(\frac{V_{be}}{V_T})] [1 + \frac{V_{ce}}{V_A}]$

What is happening physically?

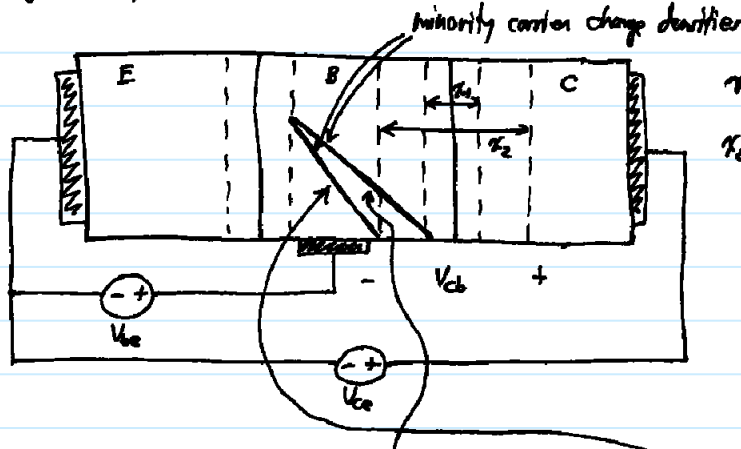

$x_1 \triangleq$ depl. region width for $V_{ce} = V_{ce1}$
 $x_2 \triangleq$ depl. region width for $V_{ce} = V_{ce2} > V_{ce1}$

- ① Case: $V_{ce} = V_{ce1} \rightarrow x_1 \rightarrow I_{c1} \propto$ slope of this curve line
- ② Now, increase $V_{ce1} \rightarrow V_{ce2} \rightarrow V_{cb} \uparrow \rightarrow x_1 \uparrow$ to $x_2 \rightarrow I_{c2} \propto$ slope of this line
 $\therefore I_{c2} > I_{c1}$


Thus, $V_{ce} \uparrow \rightarrow I_c \uparrow$ due to $x_{depl} \uparrow$

Result: $I_c = f(I_b, V_{ce})$ in forward-active!

$$I_c = \left[I_s \exp\left(\frac{V_{be}}{V_T}\right) \right] \left[1 + \frac{V_{ce}}{V_A} \right]$$

← This, V_{ce} , is a more accurate I_c equation.

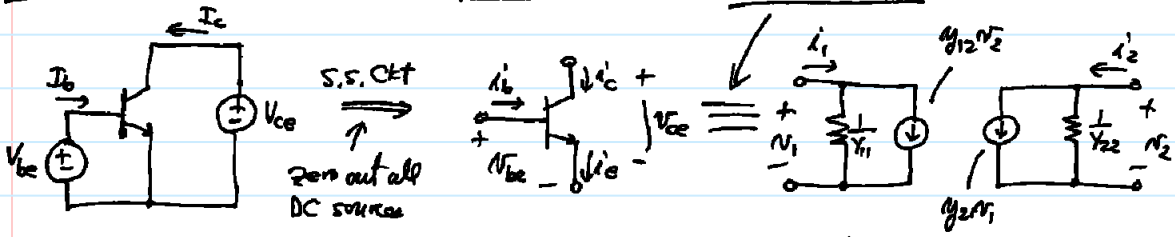Small-Signal Models for Forward-Active Bipolar Xistors




If only interested in the forward direction

$$Y_{11} = \frac{i_1}{n_1} \Big|_{n_2=0} \quad Y_{21} = \frac{i_2}{n_1} \Big|_{n_2=0}$$

$$Y_{12} = \frac{i_1}{n_2} \Big|_{n_1=0} \quad Y_{22} = \frac{i_2}{n_2} \Big|_{n_1=0}$$


Hybrid- π Model

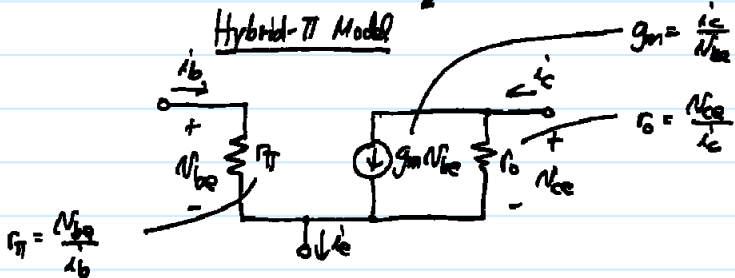

Specified by the bias point.



Determine the S.S. elements

$$g_m = \frac{i_c}{v_{be}} = \left. \frac{\partial I_c}{\partial v_{be}} \right|_{Qpt.} = \frac{\partial}{\partial v_{be}} \left[I_s \exp\left(\frac{v_{be}}{V_T}\right) \right] \Big|_{V_{be} = V_{BE}} = \frac{I_c}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow g_m = \frac{I_c}{V_T}$$

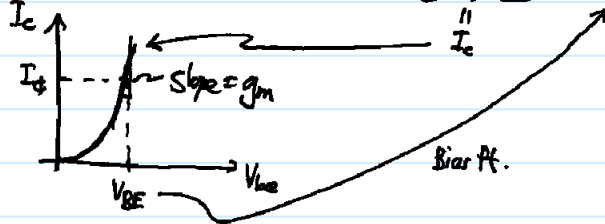

Note: fraction of the DC operating pt.



$$r_{\pi} = \frac{v_{be}}{i_b}$$

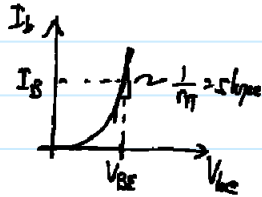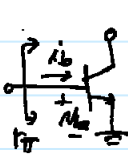

$$r_{\pi} = \frac{v_{be}}{i_b} = \frac{v_{be}}{\frac{i_c}{\beta}} = \frac{\beta}{g_m} = \frac{\beta}{\frac{I_c}{V_T}} = \frac{\beta V_T}{I_c} = \frac{V_T}{I_B}$$

∴ $r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$ Again, fraction of the DC operating pt.

$$r_o = \frac{v_{ce}}{i_c}$$

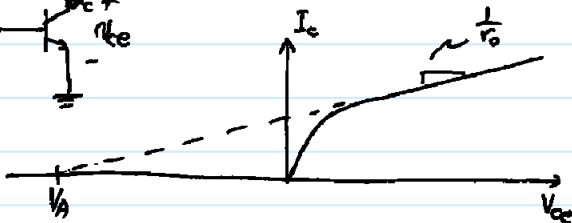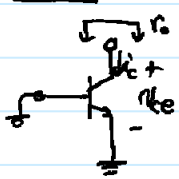

$$r_o = \left. \frac{\partial v_{ce}}{\partial i_c} \right|_{Qpt.} = \left[\left. \frac{\partial I_c}{\partial v_{ce}} \right|_{Qpt.} \right]^{-1}$$

$$= \left[\frac{\partial}{\partial v_{ce}} \left(I_s \exp\left(\frac{v_{be}}{V_T}\right) \left[1 + \frac{v_{ce}}{V_A} \right] \right) \Big|_{V_{be} = V_{BE}} \right]^{-1}$$

$$= \left[\frac{I_s \exp\left(\frac{V_{BE}}{V_T}\right)}{V_A} \right]^{-1} = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$$

$$\therefore r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} \quad [V_A \gg V_{CE}]$$

... and thus, we have the hybrid-π model:



SOURCE: βI_B

$$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B}$$

$$g_m = \frac{I_C}{V_T}$$

$$r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C}$$

SOURCE: V_{AF}

Remarks:

i.e., β, I_B

- g_m is independent of device specifics; depends only on temperature (thru V_T) and biasing I_C
- small-signal model valid for $v_{be} \ll V_T \ll 26\text{mV} @ 300\text{K}$


quite different from MLC as we'll see

What about emitter resistance?

$$r_e = \frac{V_{be}}{i_e} = \frac{V_{be}}{\frac{i_c}{\alpha}} = \frac{\alpha}{g_m} = \frac{\alpha V_T}{I_E} = \frac{V_T}{I_E}$$


$$\Rightarrow r_e = \frac{\alpha}{g_m} \approx \frac{1}{g_m} = \frac{V_T}{I_E}$$

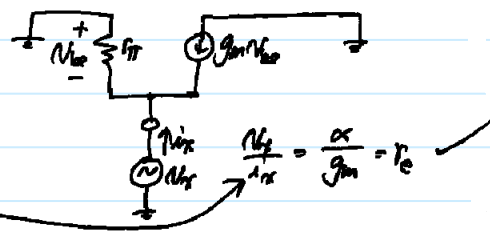Note that although it's not explicitly shown in the hybrid- π model, r_e is present.
 \Rightarrow i.e., if you analyze this, you find that



To explicitly show emitter resistance, use the T-model:

T-Model: (Common Base Model)

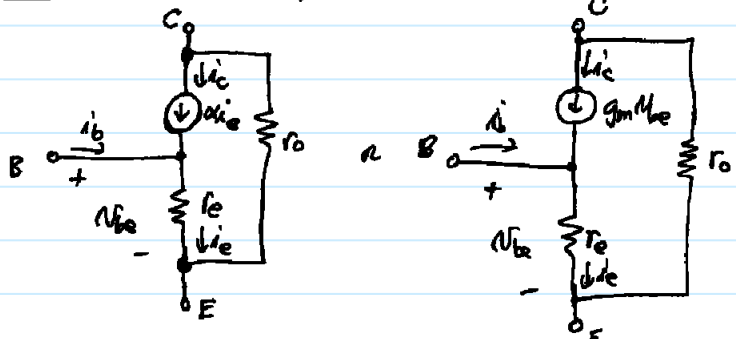

where as before:


$$g_m = \frac{I_E}{V_T}$$

$$r_o = \frac{V_T}{I_E} = \frac{\alpha}{g_m} \approx \frac{1}{g_m}$$


relative

Small-Signal Models for npn Transistors

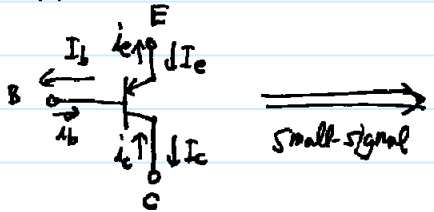
For npn transistors, use the same small-signal models as pnp with no change in polarities!



Hybrid- π Model:

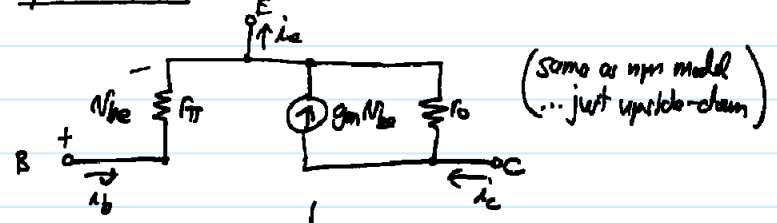


T-Model:

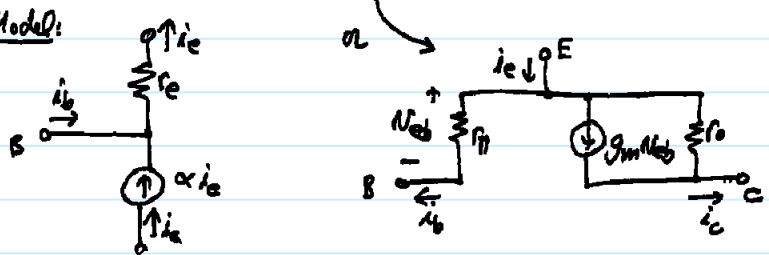


Note that in these S.S. models, the same current directions as used for npn are used too \Rightarrow i.e., no change in S.S. polarities (large-signal directions, however, can be as before)

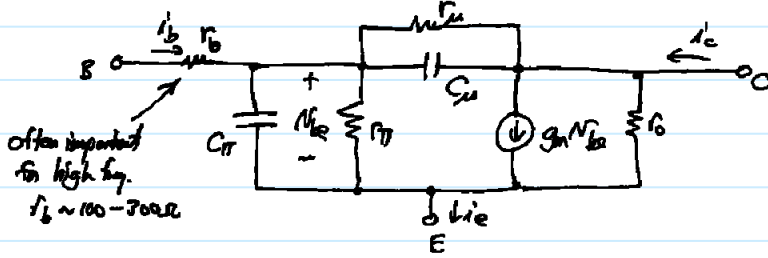More Complete Hybrid- π Model (adding frequency effects & 2nd order effects)



C_{μ} - Base-to-Collector Capacitance

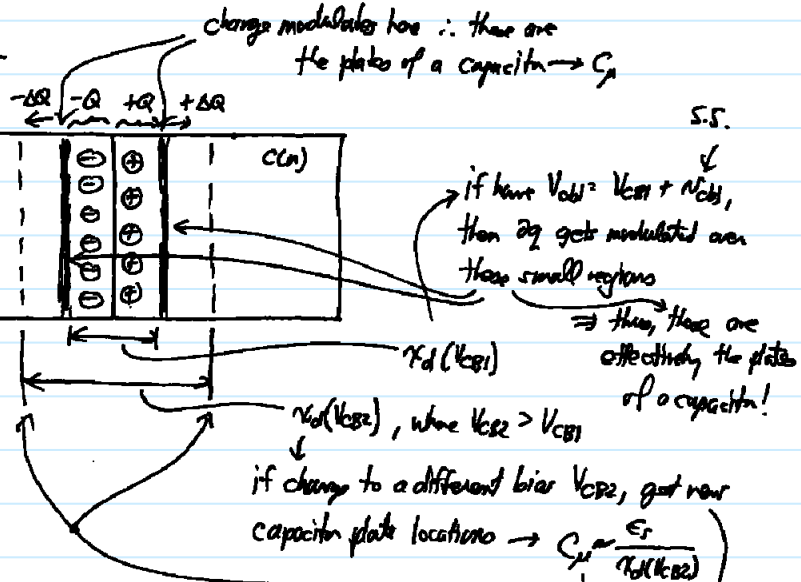

$C_{\mu} = \frac{C_{\mu 0}}{\sqrt{1 + \frac{V_{CB}}{\phi_j}}} = f(V_{CB})$ where $C_{\mu 0}$ = capacitance for $V_{CB} = 0$

ϕ_j = function of the built-in potential between p and n-type semiconductors $= \frac{kT}{q} \ln \left(\frac{N_B N_C}{n_i^2} \right)$

In general: $C_{\mu} = \frac{C_{\mu 0}}{(1 + \frac{V_{CB}}{\phi_j})^m}$, where $m = \frac{1}{2}$ or $\frac{1}{3}$ depending upon how abrupt the junction is

In space: CJC, VBC, NTC

$1.5 \times 10^{10} \text{ cm}^{-3}$

Detailed Derivation: [F12]

$r_d \approx r_a = \left[\frac{2\epsilon (V_b + V_{cb})}{q N_A (1 + \frac{N_b}{N_A})} \right]^{1/2} \rightarrow Q = q N_A r_d = A \left[\frac{2\epsilon q N_A (V_b + V_{cb})}{1 + \frac{N_b}{N_A}} \right]^{1/2}$


$[N_A \ll N_b]$

$C_j = \frac{dQ}{dV_{cb}} \Big|_{V_{cb}} = \left[\frac{2\epsilon q N_A}{1 + \frac{N_b}{N_A}} \right]^{1/2} \frac{1}{2} A (V_b + V_{cb})^{-1/2} = A \left[\frac{q\epsilon N_A N_b}{2(N_A + N_b)} \right]^{1/2} \frac{1}{\sqrt{V_b + V_{cb}}} = C_j |_{V_{cb}}$


$C_j = \frac{\epsilon_s A}{r_d(V_{cb})}$

C_{π} - Base-to-Emitter Capacitance

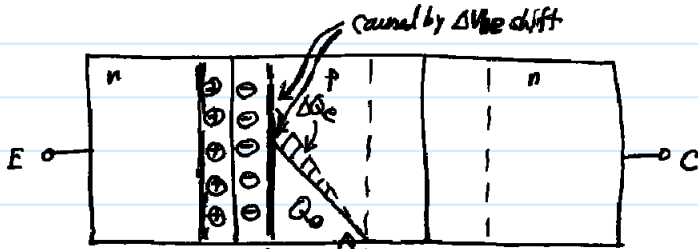Two components comprise C_{π} : ① Junction capacitance, C_{je}
 ② Diffusion capacitance, C_b



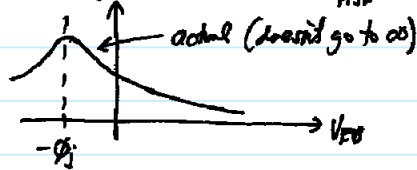Plot of a junction capacitance:
 $C_{je} = \frac{C_{je0}}{(1 + \frac{V_{BE}}{\phi_0})^m}$
 In STICE: CJE, VJE, MJE
 Note: ϕ_0 is the built-in potential, m is the grading coefficient.



Diffusion capacitance: (or Base Charging Capacitance)
 ⇒ can define a base transit time:

$$\tau_F = \frac{Q_e}{I_c} = \frac{x_B^2}{2D_n}$$

think of I_c as the rate of xfer of charge through the base

$$Q_e = \tau_F I_c$$

$$\Delta Q_e = \tau_F \Delta I_c$$

Switch to J.C. parameters (variables):

$$Q_e = C_b M_{e0} \rightarrow C_b = \frac{Q_e}{V_{be}} = \tau_F \frac{I_c}{V_{be}} = \tau_F g_m = \tau_F \frac{I_c}{V_T} = C_b$$


∴ $C_b \propto I_c$

Remember to say the fn
 STM use this!

$$C_{\pi} = C_b + C_{je}$$

$$C_{\pi} = \tau_F g_m + \frac{C_{je0}}{(1 + \frac{V_{BE}}{\phi_0})^m}$$

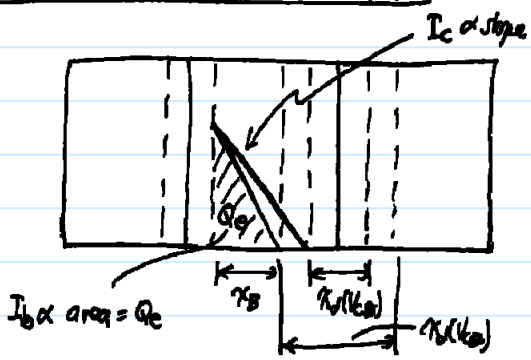
Collector-to-Base Feedback Resistor, r_{μ}




Remember, recombination base current $I_{rs} = \frac{Q_e}{\tau_b}$!

∴ $N_{ce} \uparrow \rightarrow x_B \downarrow \rightarrow Q_e \downarrow \rightarrow I_b \downarrow$
 $\rightarrow I_c \uparrow$ (due to Early effect)

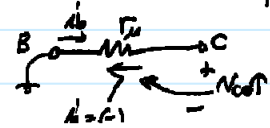$N_{ce} \uparrow \rightarrow I_b \downarrow$ can be modeled by an r_{μ} connected G-to-B



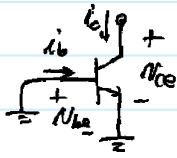

\Rightarrow here, $N_{be} = 0 \rightarrow N_{be} = N_{cb}$

$$\therefore \frac{i_c}{N_{be}} = \frac{1}{r_o} = \frac{i_c}{N_{cb}} = \frac{\beta i_b}{N_{cb}} \rightarrow \frac{N_{cb}}{i_b} = \beta r_o = r_{\mu}$$

$r_{\mu} = r_o$
 assuming all of i_b is recombination current

In general, base recombination current is only part of the total base current and is the only component dependent on $V_{bc} \Rightarrow$ thus,

$r_{\mu} > \beta_0 r_o \rightarrow r_{\mu} = 2-10 \beta_0 r_o$

label pop \uparrow npn $\rightarrow I_b$ is 10% recomb. where base recomb. more significant

Complete Forward Active BJT S.S. Model (including parasitics)

\Rightarrow Actual integrated BJT:

should draw this on the board


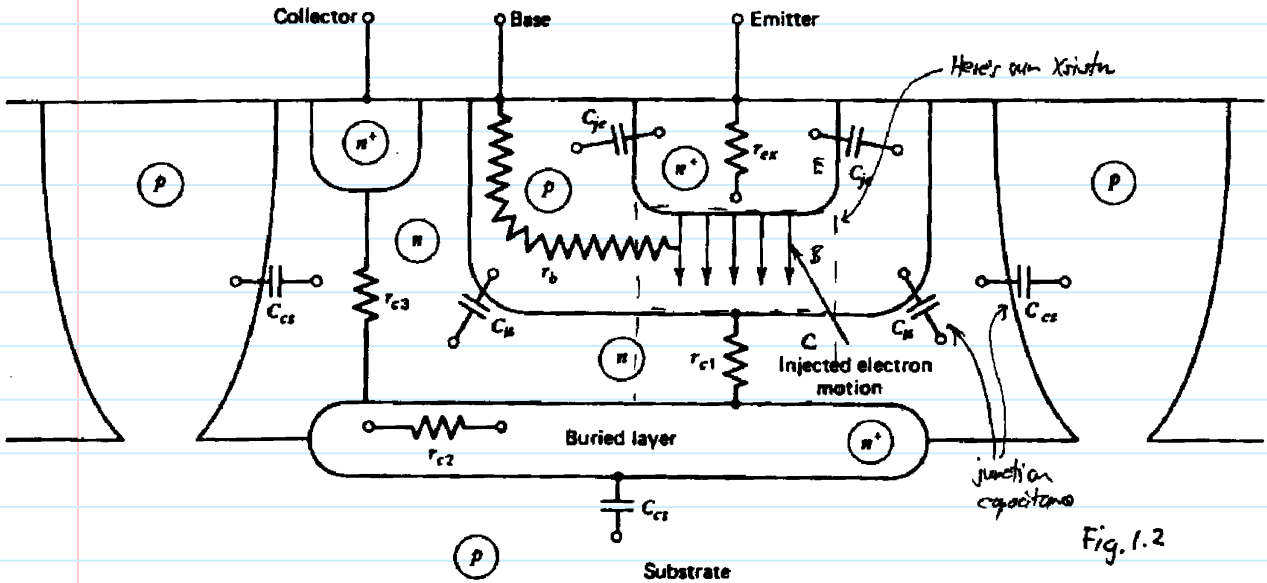


Fig. 1.2

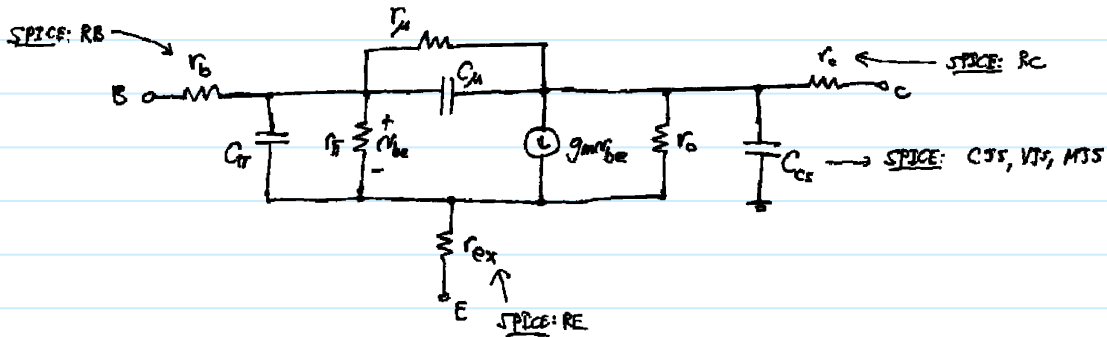


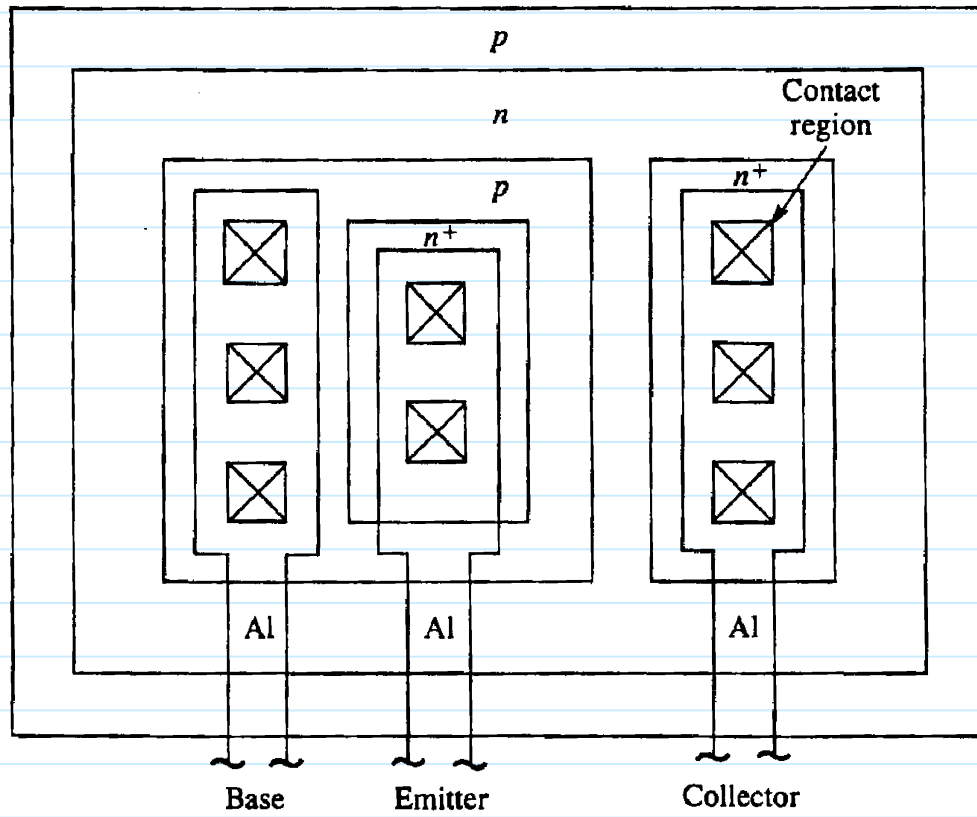
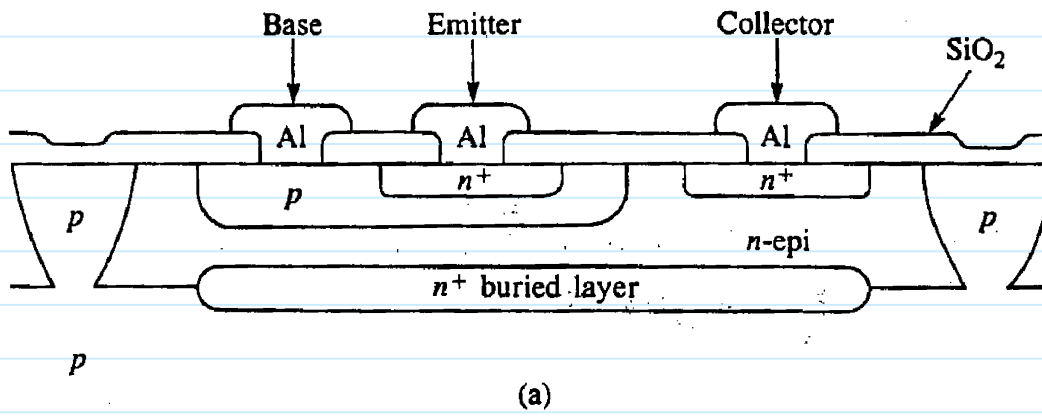


Fig. 1.1

f_T (unity gain freq. for β)

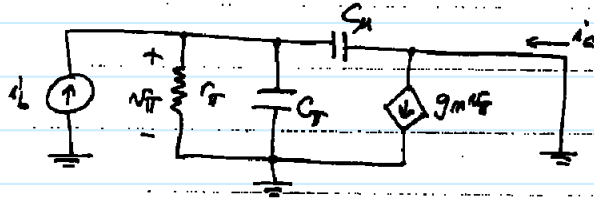Find $\beta(j\omega)$: (β as a function of freq.)



Find $\frac{i_c}{i_b} |_{\omega \rightarrow 0}$:

$$v_{\pi} = i_b \left(r_{\pi} \parallel \frac{1}{sC_{\pi}} \parallel \frac{1}{sC_{\mu}} \right)$$

$$[g_m \gg sC_{\mu}]$$

$$i_c = g_m v_{\pi} - sC_{\mu} v_{\pi} = (g_m - sC_{\mu}) v_{\pi} \approx g_m v_{\pi}$$

$$i_c = g_m \left(r_{\pi} \parallel \frac{1}{sC_{\pi}} \parallel \frac{1}{sC_{\mu}} \right) i_b$$


$$\frac{i_c}{i_b} = \frac{g_m}{\frac{1}{r_{\pi}} + s(C_{\pi} + C_{\mu})} = \frac{g_m r_{\pi}}{1 + s r_{\pi} (C_{\pi} + C_{\mu})} = \frac{\beta_0}{1 + \frac{j\omega}{\omega_p}} \quad \left[\beta_0 = g_m r_{\pi} \right]$$

(low freq. β)

$$\beta(j\omega) = \frac{\beta_0}{1 + \frac{j\omega}{\omega_p}}$$

$$\omega_p = \frac{1}{r_{\pi} (C_{\pi} + C_{\mu})}$$

Plot $|\beta(j\omega)|$: (Bode plot)

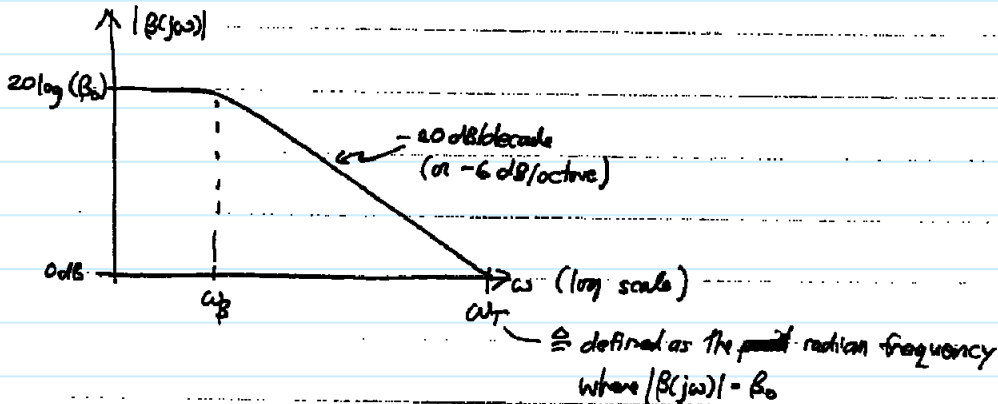

For ω large: (i.e. ω close to ω_T)

$$|\beta(j\omega)| \approx \frac{\beta_0}{\omega r_{\pi} (C_{\pi} + C_{\mu})} = 1 \rightarrow$$

$$\omega_T = \frac{g_m}{C_{\pi} + C_{\mu}}$$

$\Rightarrow f_T = \frac{\omega_T}{2\pi}$ is a figure of merit for the frequency performance of a transistor.


Also, note that $\omega_T = \beta_0 \omega_p$

$$C_{\pi} = \frac{g_m}{\omega_T} - C_{\mu}$$


$f_T = 100 \text{ MHz} \rightarrow 15 \text{ GHz}$ for bipolar Xistors.

MOS Transistor

Physical Structure & Device Symbols -


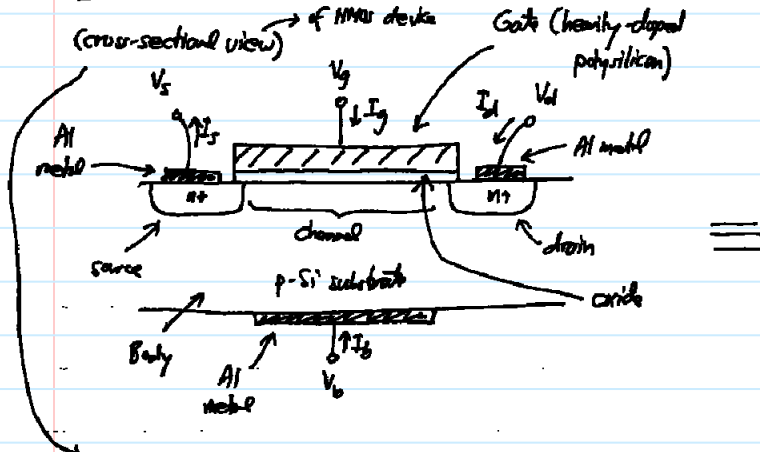


NMOS Transistor Device Symbols

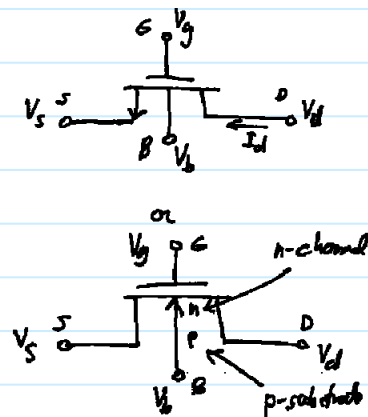


But first start w/ a perspective view: (this also defines dimensions)
 use the micrograph on next page → pg. 16a

IV Characteristics (NMOS)

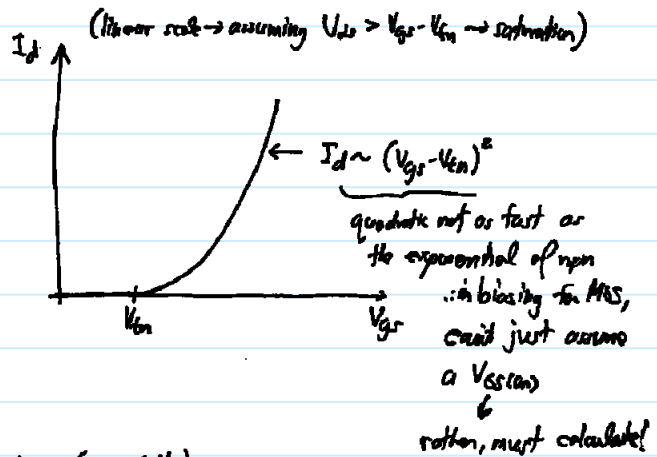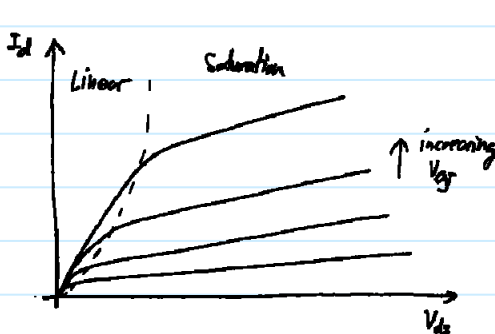

NMOS Transistor Mathematical Model

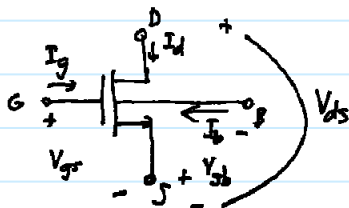

① Cut-off Region: ($V_{gs} \leq V_{th}$)

$I_g = I_s = 0 ; I_d = 0$

② Linear (or Triode) Region: ($V_{gs} - V_{th} \geq V_{ds} \geq 0$)

$I_g = I_s = 0 ; I_d = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th} - \frac{V_{ds}}{2}) V_{ds}$

Body Factor → $\gamma = \frac{1}{C_{ox}} \sqrt{2q \epsilon_s N_{sub}}$ ← substrate doping conc
 permittivity in Si

$= k_n (V_{gs} - V_{th} - \frac{V_{ds}}{2}) V_{ds}$

General:

$k_n = k_n' \frac{W}{L} = \mu_n C_{ox} \frac{W}{L}$

$I_g = I_s = 0$ for all regions (at least for dc)

$V_{th} = f(V_{sb}) = V_{th0} + \gamma (\sqrt{|V_{th0} + V_{sb}|} - \sqrt{|V_{th0}|})$


③ Saturation Region: ($V_{ds} \geq V_{gs} - V_{th} \geq 0$)

$I_g = I_s = 0 ; I_d = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$


$= \frac{1}{2} k_n (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$

$\mu_n \hat{=} e^-$ mobility in the channel

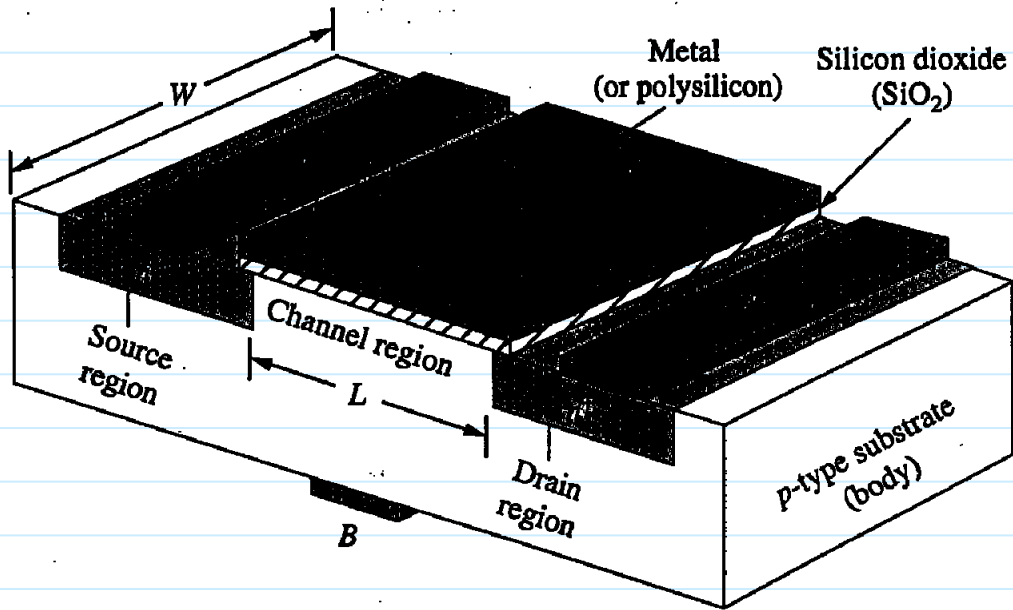$C_{ox} \hat{=} \text{oxide capacitance per unit area}$



(a)

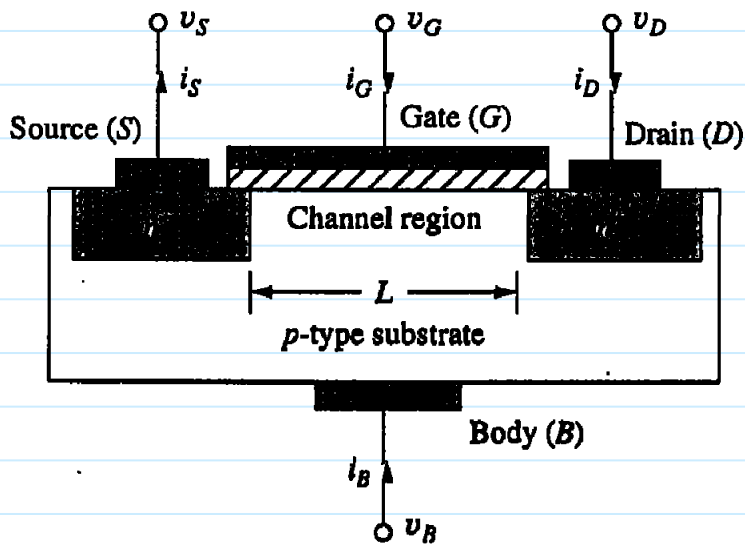


(b)



(c)

Fig. 2.1

PMOS Kirin Mathematical Model

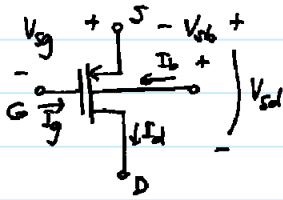

① Cut-off Region: ($V_{SG} \leq -V_{tp}$) or ($|V_{GS}| \geq |V_{tp}|$)

$$I_{SD} = 0$$

② Linear (or Triode) Region: ($V_{SG} + V_{tp} \geq V_{SD} \geq 0$; or ($|V_{GS}| - |V_{tp}| \geq |V_{DS}| \geq 0$)

$$I_{SD} = k_p \left(V_{SG} + V_{tp} - \frac{V_{SD}}{2} \right) V_{SD} = \mu_p C_{ox} \frac{W}{L} \left(V_{SG} + V_{tp} - \frac{V_{SD}}{2} \right) V_{SD}$$

$$= \mu_p C_{ox} \frac{W}{L} \left(|V_{GS}| - |V_{tp}| - \frac{|V_{DS}|}{2} \right) |V_{DS}|$$

For all regions:

$$k_p = k_p' \frac{W}{L} = \mu_p C_{ox} \frac{W}{L}$$

$I_G = 0$ and $I_B = 0$ (at dc)

$$V_{tp} = V_{to} - \gamma \left(\sqrt{|V_{BS}| + \phi_f} - \sqrt{2\phi_f} \right)$$

③ Saturation Region: ($V_{SD} \geq V_{SG} + V_{tp} \geq 0$; $|V_{DS}| \geq |V_{GS}| - |V_{tp}| \geq 0$)

$$I_{SD} = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} + V_{tp})^2 (1 + \lambda V_{SD}) = \frac{1}{2} k_p (V_{SG} + V_{tp})^2 (1 + \lambda V_{SD})$$

$$= \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{tp}|)^2 (1 + \lambda |V_{DS}|)$$

$\mu_p \hat{=}$ h^+ mobility in the channel

$C_{ox} \hat{=}$ gate oxide capacitance per unit area

Threshold Voltage

$$V_t = \phi_{ms} - \psi_s - \frac{Q_B}{C_{ox}} - \frac{Q_{ss}}{C_{ox}}$$

, where ϕ_{ms} = work function difference [in V] between gate material and bulk Si

ψ_s = surface potential in the Si @ onset of strong inversion

= $2\phi_f$ for uniformly doped substrate ($\phi_f \sim 0.3$ V)

Q_{ss} = oxide charge per unit area at the oxide-Si interface [C/cm^2]

Q_B = charge stored per unit area in the depletion region (at onset of inversion)

$$\Rightarrow |Q_B| = \sqrt{2q\epsilon_s N_B (2|\phi_f| + |V_{SB}|)} \quad [C/cm^2]$$

\uparrow conc. in bulk \uparrow reverse bias

C_{ox} = gate oxide capacitance per unit area [F/cm^2]

Care: $V_{S13} = 0 \Rightarrow V_t(V_{SB} = 0) = V_{t0} = \phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_{B0}}{C_{ox}}$, where

Then:

$$V_t = \phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_B}{C_{ox}}$$

$$Q_{B0} = \sqrt{2q\epsilon_{si}N_B(2|\phi_f| + |V_{SB}|)}$$

$$= \phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_{B0}}{C_{ox}} - \frac{Q_B - Q_{B0}}{C_{ox}}$$


$$\underbrace{\phi_{ms} - 2\phi_f - \frac{Q_{ss}}{C_{ox}} - \frac{Q_{B0}}{C_{ox}}}_{V_{t0}}$$

$$V_t = V_{t0} - \gamma(\sqrt{2|\phi_f| + |V_{SB}|} - \sqrt{2|\phi_f|}), \quad \gamma = \frac{1}{C_{ox}}\sqrt{2q\epsilon_{si}N_B}$$

Signs in the V_t Equation:

Parameter	NMOS	PMOS
Substrate	p-type	n-type
ϕ_{ms} : metal gate	-	-
n+ Si gate	-	-
p+ Si gate	+	+
ϕ_f	-	+
Q_{B0} (or Q_B)	-	+
Q_{ss}	+	+
γ	-	+
C_{ox}	+	+

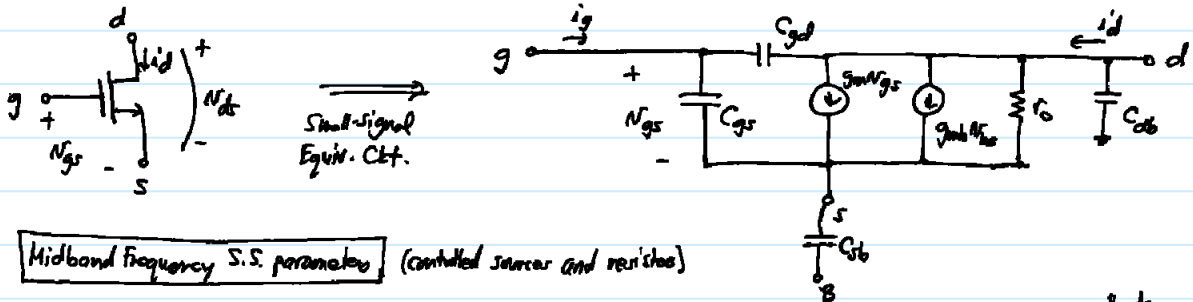MOS Small-Signal Model (for NMOS) ^{in saturation}



Midband Frequency S.S. parameters (controlled source and resistors)

Transconductance, g_m :

$$g_m = \frac{\partial I_d}{\partial V_{gs}} \Big|_{Q_{pt}} = \frac{\partial}{\partial V_{gs}} \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 \right) \Big|_{Q_{pt}} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn}) \Big|_{Q_{pt}} = \mu_n C_{ox} \frac{W}{L} I_D$$

$$\therefore g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn}) = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$g_{mb} = \frac{\partial I_d}{\partial V_{bs}} = - \frac{\partial I_d}{\partial V_{cb}} \Big|_{Q_{pt}} = - \left(\frac{\partial I_d}{\partial V_{tn}} \cdot \frac{\partial V_{tn}}{\partial V_{cb}} \right) \Big|_{Q_{pt}}$$

$$\left[I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 \rightarrow (V_{gs} - V_{tn}) = \sqrt{\frac{2 I_D}{\mu_n C_{ox} \frac{W}{L}}} \right]$$

$$\frac{\partial I_d}{\partial V_{tn}} \Big|_{Q_{pt}} = - \frac{\partial I_d}{\partial V_{gs}} \Big|_{Q_{pt}} = -g_m \quad ; \quad \frac{\partial V_{tn}}{\partial V_{cb}} \Big|_{Q_{pt}} = \frac{\partial}{\partial V_{cb}} \left[V_{t0} + \gamma \left(\sqrt{V_{cb} + 2\phi_{fn}} - \sqrt{2\phi_{fn}} \right) \right] \Big|_{Q_{pt}} = \frac{\gamma}{2\sqrt{V_{cb} + 2\phi_{fn}}} \approx \eta$$

$$\therefore g_{mb} = \eta g_m$$

often neglected!

Note: $V_{SB} \uparrow \rightarrow V_T \uparrow \rightarrow \eta \downarrow \rightarrow I_D \downarrow$

g_{mb} is minimized by maximizing λ !
 V_{SB}

Output Resistance, r_o : ($= \frac{1}{g_{ds}}$)

$$\Rightarrow \text{output conductance} = g_{ds} = \frac{\partial I_d}{\partial V_{ds}} \Big|_{Q_{pt}} = \frac{\partial}{\partial V_{ds}} \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{tn})^2 (1 + \lambda V_{ds}) \right) \Big|_{Q_{pt}}$$

$$= \lambda I_{Dsat} = \frac{\lambda I_D}{1 + \lambda V_{ds}} \approx \lambda I_D = g_{ds}$$

$[1 \gg \lambda V_{ds}]$

if V_{ds} is very large

$$r_o = g_{ds}^{-1} = \frac{1}{\lambda I_D} = \frac{1}{\lambda} + \frac{V_{ds}}{I_D}$$

High Frequency S.S. Parameters (capacitors)

(cross-sectional view)

C_{gs} = gate-to-source overlap capacitance

C_g = gate capacitance = $W L C_{ox}$

C_{gdd} = gate-to-drain overlap capacitance


Sidegate thin man bottom area cap.

Bottom Area C_{sb}


bulk (P)

shielded-out depletion capacitance, C_{db} when inversion layer present

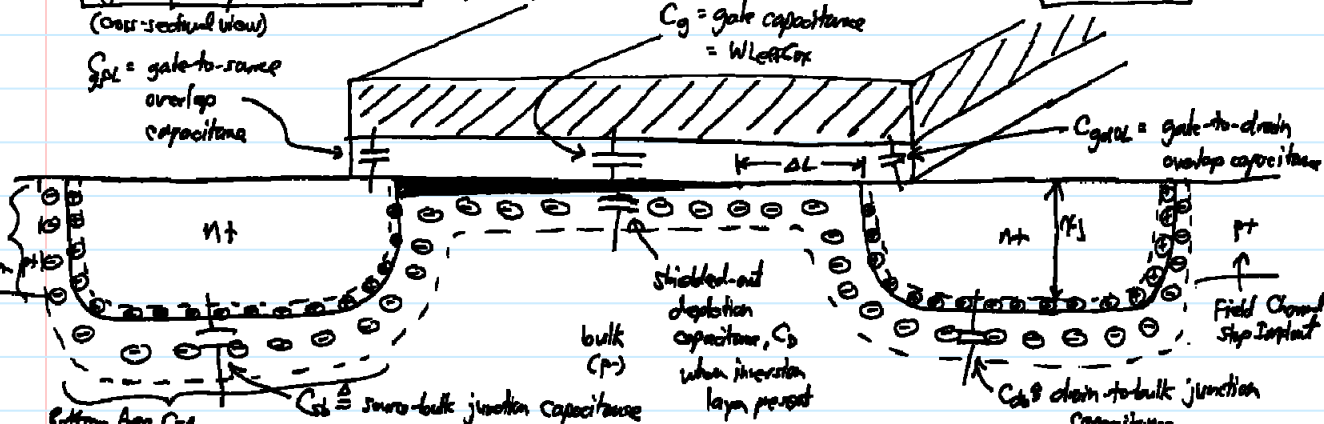Field Effect Stop Implant
 C_{db} drain-to-bulk junction capacitance




(layout view)

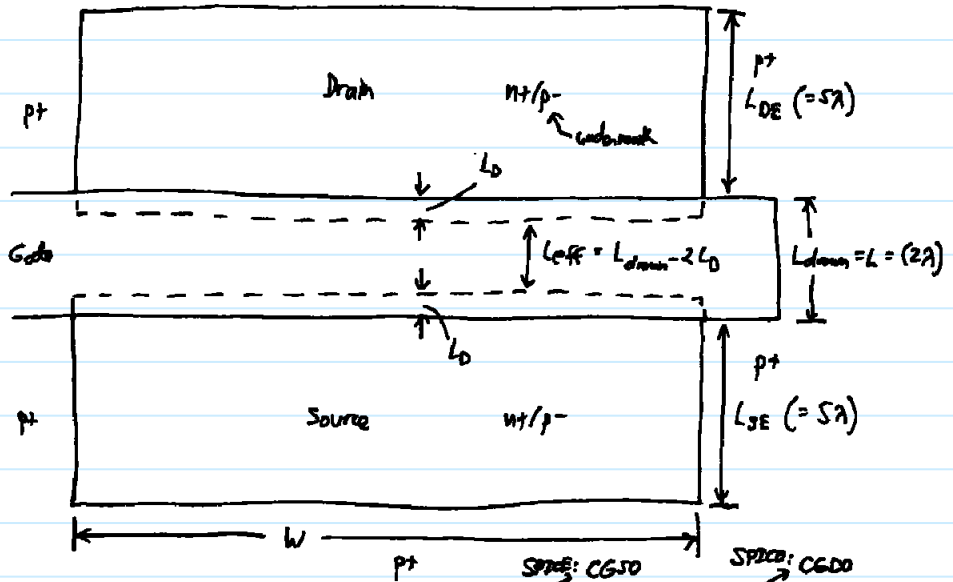

(still considering saturation region)

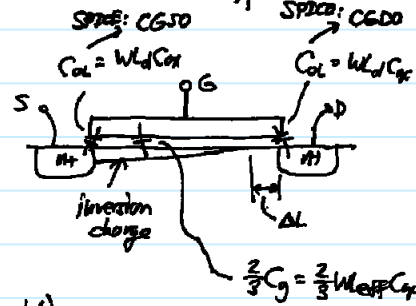In saturation, the inversion charge is not present near the drain:



Gate-to-Source Capacitor, C_{gs}:

$$C_{gs} = C_{ol} + \frac{2}{3} W L_{eff} C_{ox} \quad (\text{inversion charge integrated})$$

$$\frac{2}{3} C_g = \frac{2}{3} W L_{eff} C_{ox}$$

obtained by integrating the charge over the gate length

Gate-to-Drain Capacitor, C_{gd}:

$$C_{gd} = C_{ol} \quad (\text{no inversion charge near the drain in saturation})$$

Source/Drain Junction Capacitance, C_{sb} & C_{db}: (must include these in SPICE simulations!)

⇒ these are depletion capacitance associated with the drain-to-bulk and source-to-bulk pn junctions

⇒ bottom-side capacitance per unit area is different from that at sidewalls due to higher doping at the sidewalls

(there is higher doping in the field areas to prevent channels from forming under interconnect wires)

⇒ take drain capacitance as an example:


$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DS}}{V_0}}}, \quad C_{db0} \triangleq \text{depletion capacitance with } V_{DS} = 0V$$

$$\left(\frac{q \epsilon_s N_A N_D}{2(N_A + N_D)} \right)^{1/2}$$

SPICE: CJ

$$C_{j0} = \sqrt{\frac{q \epsilon_s N_A N_D}{2(N_A + N_D)}} \rightarrow \left(\frac{q \epsilon_s N_A N_D}{2(N_A + N_D)} \right)^{1/2}$$

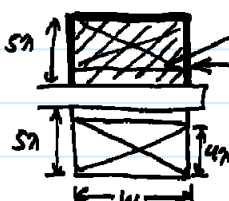depl. cap. per unit area @ bottom-side w/ V_{DS} = 0V



$$= (\text{junction bottom-side area}) C_{j0} + (\text{junction outside perimeter}) C_{jsw}$$

$$= W(s_n) C_{j0} + (w + 2(s_n)) C_{jsw}$$

depletion cap. along sidewalls per unit length for V_{DS} = 0V

$$C_{jsw} = \left(\frac{q \epsilon_s N_A N_D}{2(N_A + N_D)} \right)^{1/2} \times x_j$$

channel stops implant clearing level

s_n junction depth