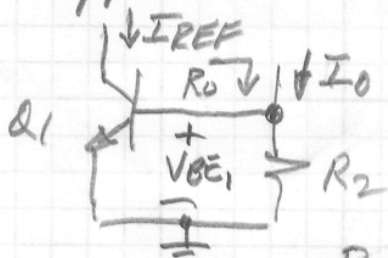


• V_{BE} Bias current source

- let's develop this from the beginning. The obvious approach is to place a V_{BE} across a Resistor:




• Neglecting base current,
 $I_0 = \frac{V_{BE1}}{R_2}$; note: no direct V_{CC} dependence.

But, this circuit has serious problems.

Among several, I₀ is a poor current source because R₀ = r_{π2} || R₂ is not large.

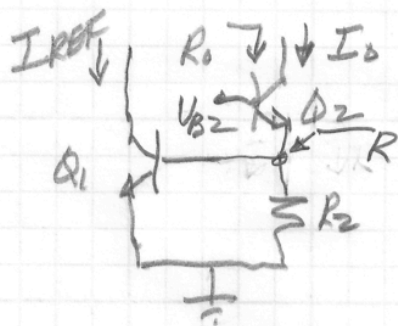- Fix this problem by adding Q₂ as shown:



With β = ∞, I_{C2} = I_{E2} = $\frac{V_{BE1}}{R_2} = I_0$

This circuit is better in two ways:


(i) We can use transistors to do

something with I₀ (e.g., mirrors)

(ii) Much higher R₀ = $\left[1 + \frac{(g_{m2} r_{o2}) R}{1 + g_{\pi} R} \right] r_{o2}$

≈ $\frac{g_{m2} r_{o2} R}{1 + g_{\pi} R}$ where R = R₂ || r_{π1}

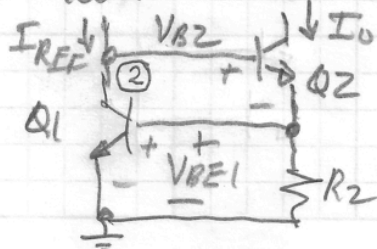- But, now we need to find a convenient bias point, V_{B2}, for the base voltage of Q₂. Grab a point that looks convenient:



(i) DC voltage at ② not established until base of Q₂ connected.

(ii) Source of base current for Q₂

Thus, V_{B2} = V_{BE1} + V_{BE2} ≈ 1.4V

• Now, let's find $\int_{V_{CC}}^{I_0}$: (neglect base currents)

$$I_{ref} = \frac{V_{CC} - 2V_{BE(ON)}}{R_1} \approx \frac{V_{CC}}{R_1} ; \therefore \frac{\partial I_{ref}}{\partial V_{CC}} = \frac{1}{R_1}$$

$$I_0 = \frac{V_{BE1}}{R_2} = \frac{V_T}{R_2} \ln \frac{I_{ref}}{I_{S1}} = \frac{V_T}{R_2} (\ln I_{ref} - \ln I_{S1})$$

$$\frac{\partial I_0}{\partial V_{CC}} = \frac{V_T}{R_2} \left[\frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}} - \frac{1}{I_{S1}} \frac{\partial I_{S1}}{\partial V_{CC}} \right]$$

$$\int_{V_{CC}}^{I_0} = \frac{V_{CC}}{I_0} \frac{\partial I_0}{\partial V_{CC}} = \frac{V_T}{I_0 R_2} \left[\frac{V_{CC}}{I_{ref}} \frac{\partial I_{ref}}{\partial V_{CC}} - \frac{V_{CC}}{I_{S1}} \frac{\partial I_{S1}}{\partial V_{CC}} \right]$$


$$= \frac{V_T}{I_0 R_2} \left[\underbrace{\int_{V_{CC}}^{I_{ref}}}_1 - \underbrace{\int_{V_{CC}}^{I_{S1}}}_0 \right] \approx \frac{V_T}{V_{BE(ON)}} \leftarrow$$

Note: $\int_{V_{CC}}^{I_0}$ is small (≈ 0.035) but how to make it smaller (ideally, = 0)?

Observation: Non-zero $\int_{V_{CC}}^{I_0}$ comes from $\int_{V_{CC}}^{I_{ref}} = 1$.


Solution: Find another current to replace $I_{REF} \approx V_{CC}/R_1$ that is much less sensitive to V_{CC} variations; i.e., we want a new I_{REF} with $\int_{V_{CC}}^{I_{REF}} \approx 0$. We have that current already, I_0 .

• Use self-biasing technique:

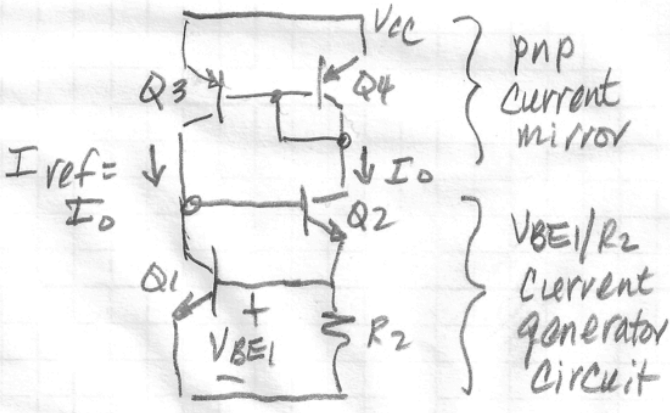

- Solutions:
 - i) Graphical
 - ii) Analytical

• Consider a graphical solution:

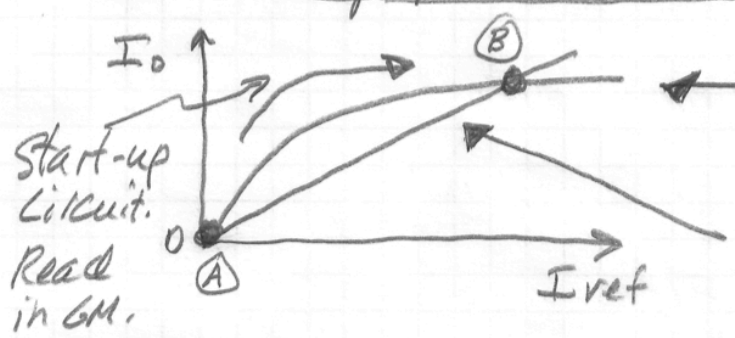

• Bottom half of circuit: VBE generator:

$$I_o \approx \frac{V_{BE1}}{R_2} = \frac{V_T \ln \frac{I_{ref}}{I_{S1}}}{R_2}$$

• Top half of circuit: pnp current mirror



$$I_o = I_{ref}$$

• Two possible stable solutions:

Ⓐ Zero current solution. In a practical circuit, avoid Ⓐ by including a start-up circuit.

Once current is flowing, circuit operation moves to Ⓑ as desired. $\int_{V_{cc}}^{I_o} = 0$ ignoring V_A Effects.

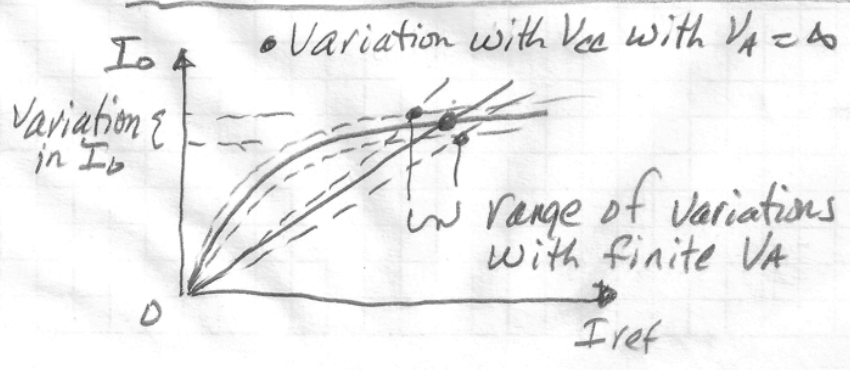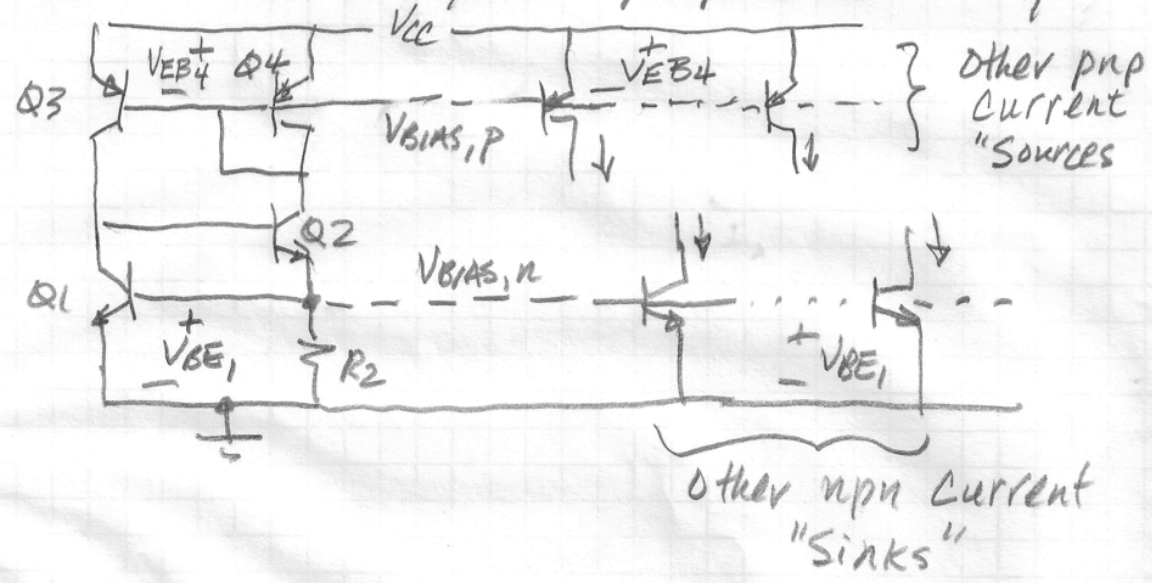We now have a general purpose current generator:




• Let's gain some insight using simple negative feedback

Thus, $\Delta V_2 = \frac{R_{O2} \Delta V_{CC}}{R_{O2} + R_{O4}}$ note: $R_{O4} = \frac{1}{g_{m4} + g_{o4}} \approx \frac{1}{g_{m4}}$
 (Diode-connected device)
 $\approx \frac{g_{m1} r_{O1} R_O \Delta V_{CC}}{g_{m1} r_{O1} R_O + \frac{1}{g_{m4}}} \approx \frac{g_{m1} g_{m4} r_{O1} R_O \Delta V_{CC}}{1 + g_{m1} g_{m4} r_{O1} R_O} \approx \Delta V_{CC}$

and $\Delta V_1 = \frac{R_{O1}}{R_{O1} + R_{O3}} \approx \frac{1}{\frac{1}{g_{m1}} + r_{O3}} = \frac{1}{1 + g_{m1} r_{O3}} \approx \frac{\Delta V_{CC}}{g_{m1} r_{O3}}$
 (Small voltage change at ①)


• Key point: look at accuracy of pnp current mirror versus ΔV_{CC} perturbations:

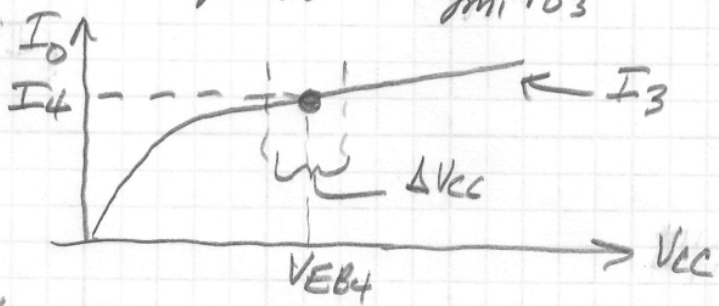$\Delta V_{EC4} = \Delta V_{CC} - \Delta V_2 = \underline{\underline{0}}$
 $\Delta V_{EC3} = \Delta V_{CC} - \frac{\Delta V_{CC}}{g_{m1} r_{O3}} = \frac{(g_{m1} r_{O3} - 1) \Delta V_{CC}}{g_{m1} r_{O3}} \approx \underline{\underline{\Delta V_{CC}}}$



Some change in $I_4 = I_{ref}$ due to Early effect.

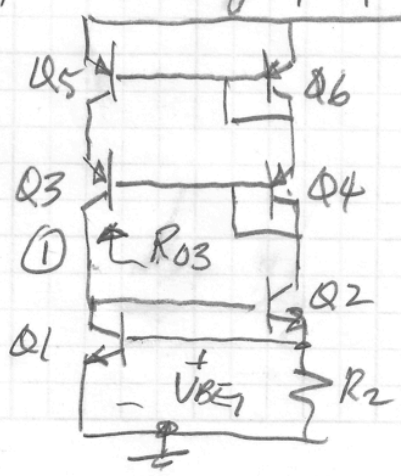• Improve using pnp cascode current mirror



• $R_{O3} \gg r_{O3}$ so $\Delta V_1 \approx 0$
 • But $R_{O3} \approx g_{m3} r_{O3} r_{O5}$
 So $\Delta I_{ref} = \frac{\Delta V_{CC}}{g_{m3} r_{O3} r_{O5}}$
 is very small so $\frac{\partial I_{ref}}{\partial V_{CC}} \approx 0!$

AMPAD

$I_D \approx 0$!!! What about temperature sensitivity?

• Define Fractional Temperature Coefficient:

$$TCF = \frac{1}{I_D} \frac{\partial I_D}{\partial T} \quad \text{where } I_D = \frac{V_{BE1}}{R_2}$$

$$= \frac{R_2}{V_{BE1}} \frac{\partial}{\partial T} \left(\frac{V_{BE1}}{R_2} \right) = \frac{R_2}{V_{BE1}} \left(\frac{1}{R_2} \frac{\partial V_{BE1}}{\partial T} + \frac{V_{BE1}}{R_2^2} \frac{\partial R_2}{\partial T} \right)$$

$$\therefore TCF = \underbrace{\frac{1}{V_{BE1}} \frac{\partial V_{BE1}}{\partial T}}_{TCF|V_{BE1}} - \underbrace{\frac{1}{R_2} \frac{\partial R_2}{\partial T}}_{TCF|R_2}$$

Can we cancel?

• Typical TCF Values:

• Diffused R's $\sim 1000 - 1500$ ppm/ $^{\circ}C$
 (Note: $1000 \text{ ppm} = \frac{1000}{1,000,000} = 0.1\%$)

parts per million

• Polysilicon R's ~ 500 ppm/ $^{\circ}C$

• $V_{BE} \sim -3300$ ppm/ $^{\circ}C$

• So, back to our V_{BE1}/R_2 reference:

$$TCF = TCF|V_{BE1} - TCF|R_2$$

$$\approx -3300 \text{ ppm}/^{\circ}C - 1000 \text{ ppm}/^{\circ}C = -4300 \text{ ppm}/^{\circ}C$$

(i) Commercial Temperature Range = $0 - 70^{\circ}C$


$\Rightarrow \sim 30\%$ Variation in I_D

(ii) Military Temperature Range = -55 to $125^{\circ}C$

$\Rightarrow \sim 77\%$ Variation in I_D

AMPAD

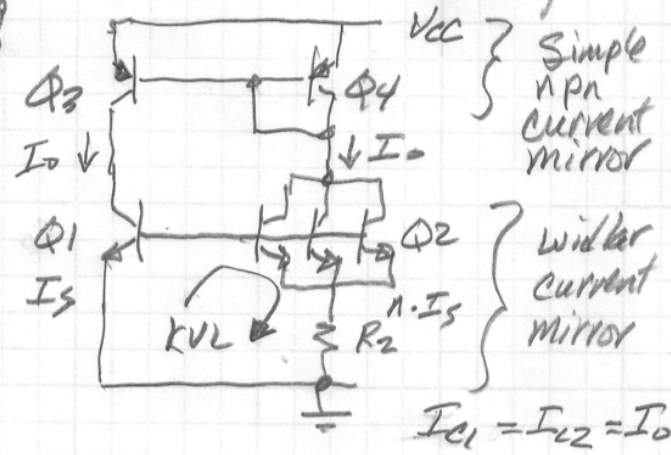- Consider a current generator with a positive TCF.
- $\frac{RT}{q}$ - based bias current generator (self-biased):



KVL loop:
 $I_0 = \frac{V_{BE1} - V_{BE2}}{R_2}$
 $I_0 = \frac{\Delta V_{BE}}{R_2}$

$I_0 = \frac{V_T \ln \frac{I_{S2}}{I_{S1}}}{R_2}$

(Example) = $\frac{V_T \ln(N)}{R_2}$
 (For $N=3$) = $\frac{1.10 \frac{kT}{q}}{R_2}$
 $\therefore kT/q$ reference

$TCF = \frac{1}{I_0} \frac{\partial I_0}{\partial T}$

= $\frac{R_2}{V_T \ln(N)} \frac{\partial}{\partial T} \left(\frac{V_T}{R_2} \ln(N) \right)$



= $\frac{R_2}{V_T \ln(N)} \cdot \ln(N) \left[\frac{1}{R_2} \frac{\partial V_T}{\partial T} - \frac{V_T}{R_2^2} \frac{\partial R_2}{\partial T} \right]$

= $\frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R_2} \frac{\partial R_2}{\partial T} \approx +3300 \text{ ppm/}^\circ\text{C} - 1000 \text{ ppm/}^\circ\text{C} = +2300 \text{ ppm/}^\circ\text{C}$

- Better than $\frac{V_{BE1}}{R_2}$ reference but $\neq 0$

Solution: Silicon Bandgap Reference

Conceptual:

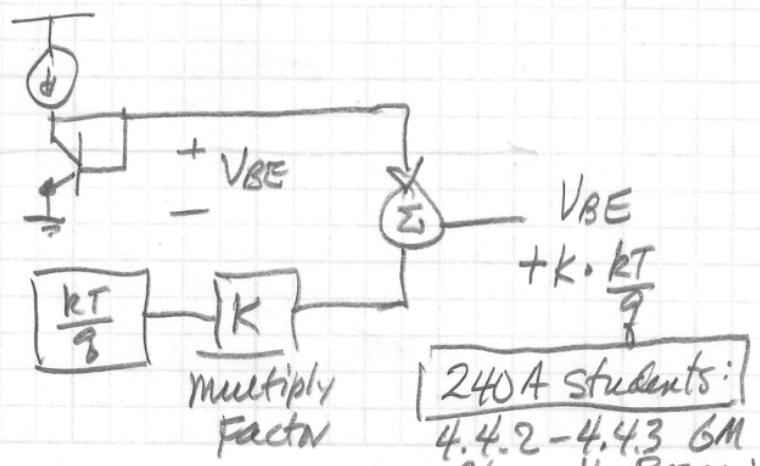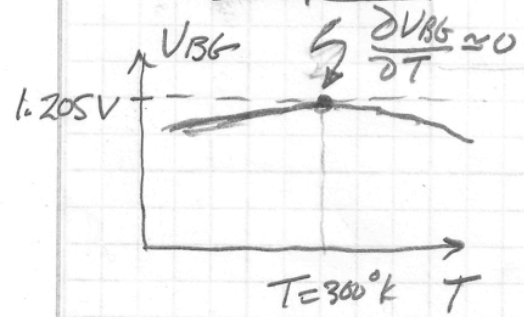

240A students:
 4.4.2 - 4.4.3 GM
 Chap. 11 Razavi

AMPAD