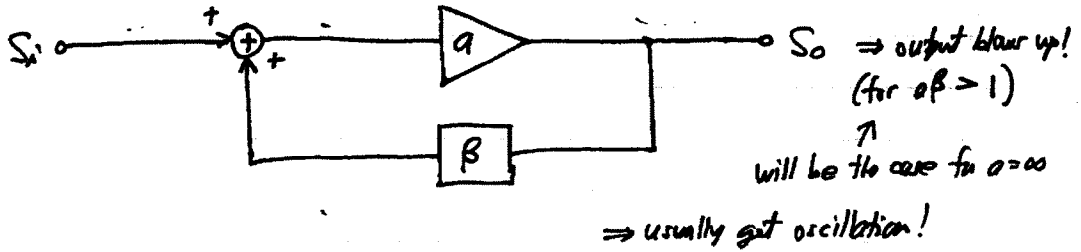


Contrast w/ **Positive Feedback**


These pages courtesy of C. Nguyen  
EE 140/240A Fa 2013



Thus, for a bounded, controllable function, need negative FB around an op amp.

**Op Amp Ckts.**

Example. Inverting Amplifier

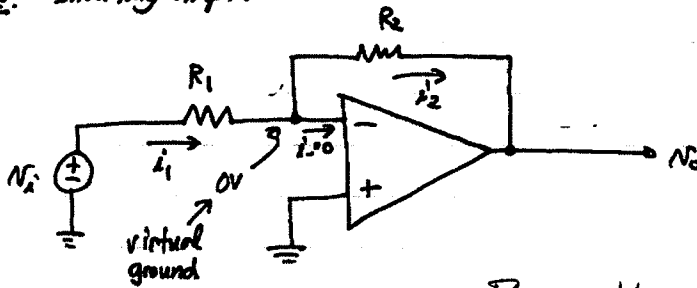

Break the loop and inject test signal.

① Verify that there is negative FB.

②  $\therefore N_o = \text{finite} \rightarrow N_+ = N_- \rightarrow$  node attached to (-) terminal is virtual ground


③  $i_- = 0 \therefore i_1 = i_2$

$$i_1 = \frac{N_i - 0}{R_1} = \frac{N_i}{R_1} = i_2 \Rightarrow N_o = -\left(\frac{N_i}{R_1}\right)R_2 = -\frac{R_2}{R_1}N_i \therefore \boxed{\frac{N_o}{N_i} = -\frac{R_2}{R_1}}$$

1a Analyze to find  $V^+$  input voltage.

Note: Gain dependent only on  $R_1$  &  $R_2$  (external components), not on the op amp gain.

Example.

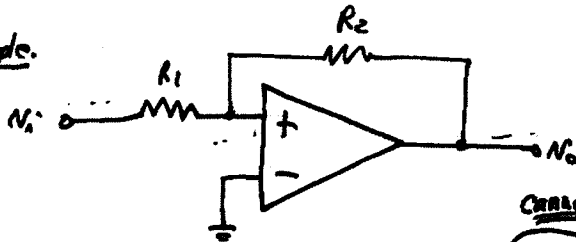

① Verify that there is neg. FB X

Cannot analyze using ideal op amp method!

$\therefore N_o \neq \text{finite}, N_+ \neq N_- \Rightarrow$  this ckt. will "rail out"


$N_o = L^+$  or  $L^-$  depending on initial cond.

$N_+ = (+) \rightarrow L^+$   
 $N_+ = (-) \rightarrow L^-$

How does one make an op amp? (It turns out, you already know!)


⇒ Basic Needed Attributes:

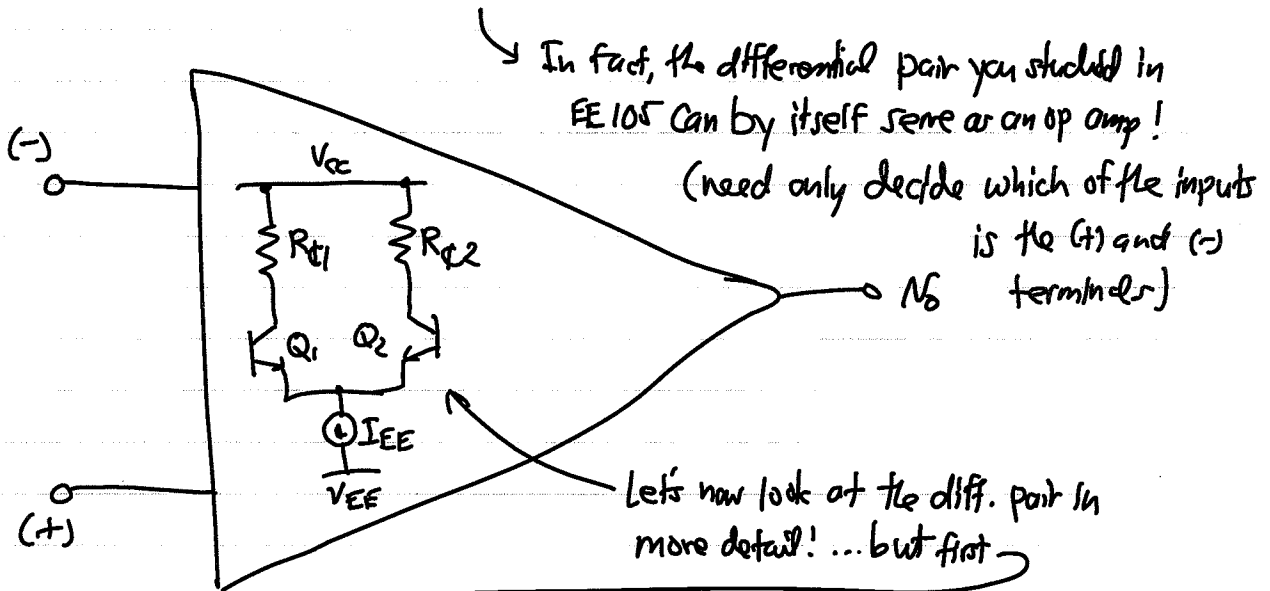- ① Gain (voltage gain).
- ② Two inputs, (+) and (-).
- ③ One output equal to the difference of the inputs multiplied by some gain.




Why have 2 inputs?

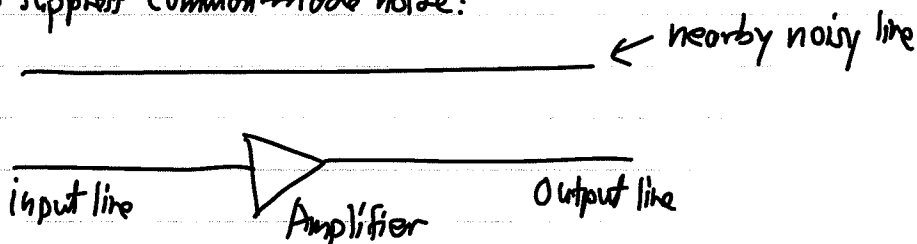
- ① To get a virtual short for op amp dets.
- ② To suppress common-mode noise:



Can avoid this w a differential input:

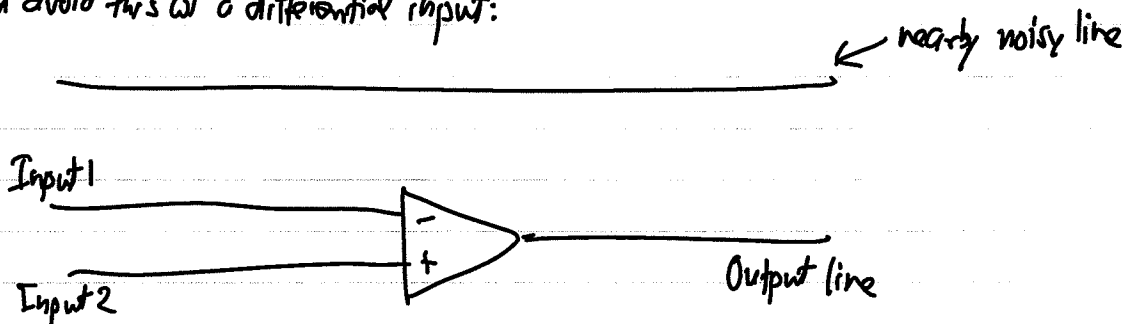

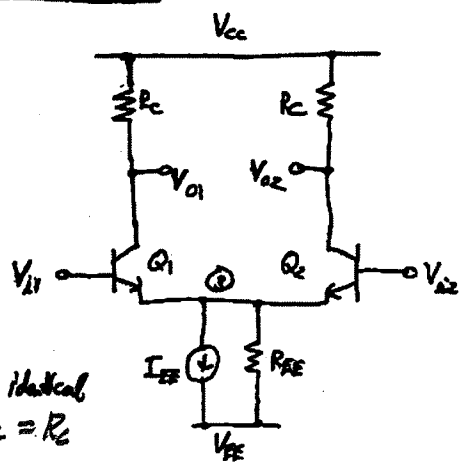**Differential Pair (Emitter-Coupled Pair)**



Assume  
Q1 + Q2 identical  
R\_C1 = R\_C2 = R\_C

Purpose: Amplify the difference between two signals regardless of their common-mode DC values (or their common-mode values in general)

Definition:  
 $V_{id} = V_{i1} - V_{i2}$  (differential input)  
 $V_{icm} = \frac{V_{i1} + V_{i2}}{2}$  (common-mode input)

$$\Rightarrow \begin{cases} V_{o1} = V_{icm} + \frac{V_{id}}{2} \\ V_{o2} = V_{icm} - \frac{V_{id}}{2} \end{cases}$$

Differential Gain =  $A_d = \frac{V_{o1} - V_{o2}}{V_{id}} = \frac{V_{id}}{V_{id}}$

(want this to be large for this differential amplification)

Common-Mode Gain =  $A_{cm} = \frac{V_{o1}}{V_{icm}} \approx \frac{V_{o2}}{V_{icm}}$

(want this to be small so that the amp rejects common-mode signals)

Common-Mode Rejection Ratio =  $CMRR = \frac{A_{dm}}{A_{cm}}$

(should be very high to favor the differential mode and reject the common-mode)

⇒ we also want a high Common-Mode Input Range to reject DC input offsets

⇒ Note: No need for bypass capacitors (large) to the inputs or outputs → can just use direct coupling!

**Biasing & Large Signal Common-Mode Behavior**

Case:  $R_{EE} = \infty$  → ideal current source biasing →  $I_{E1} = I_{E2} = \frac{I_{EE}}{2}$  →  $V_{O1} = V_{O2} \Rightarrow V_{id} = 0$



If  $V_{icm} \uparrow \rightarrow V_{O1} \uparrow$ , but current draw from  $I_{EE}$  stays constant ∴  $I_{E1}$  &  $I_{E2}$  stay constant → bias pt. doesn't change  
 $g_m = \frac{1}{2} \frac{I_{EE}}{V_T}$

Case:  $R_{EE} = \text{finite}$  →  $V_{O1} = V_{i1} - V_{BE(on)}$


If  $V_{icm} \uparrow \rightarrow V_{O1} \uparrow \rightarrow I_{E1} = I_{EE} \uparrow$  (current draw =  $I_{EE} + \frac{V_{O2}}{R_{EE}}$ )

⇒ In general,  $R_{EE}$  will be large, so this component won't be large, and the bias pt. won't Δ much

Input Common-Mode Range:

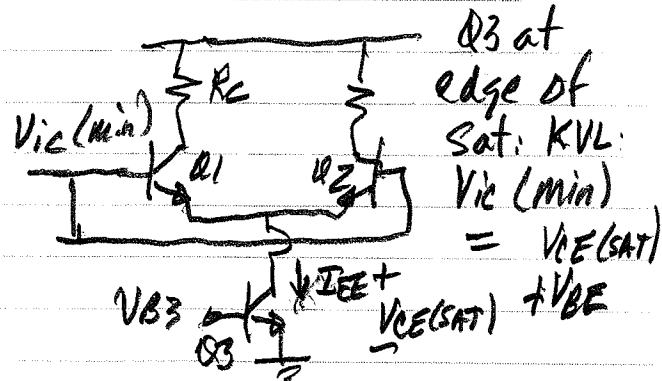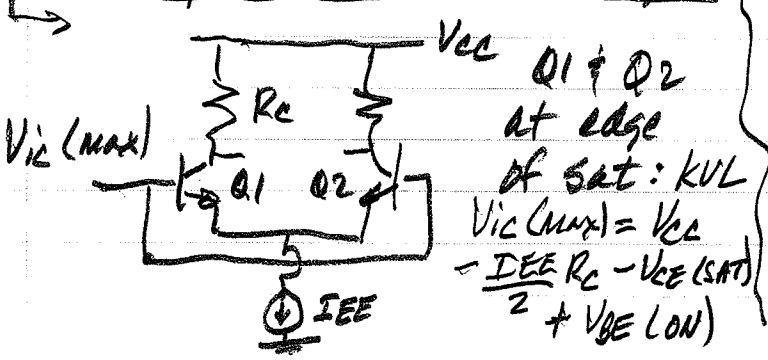

Small-Signal Analysis of Diff. Pair

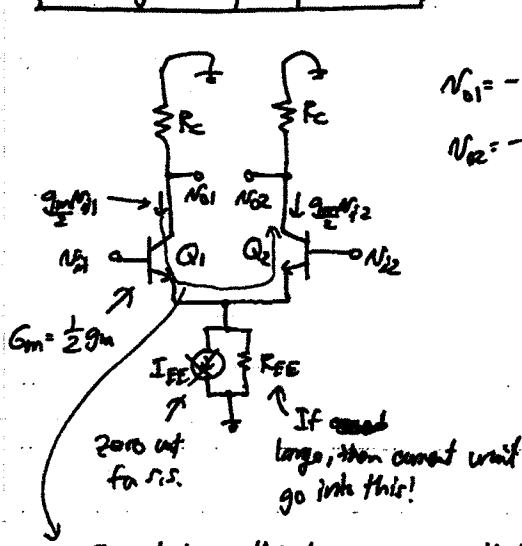


$$\begin{aligned}
 N_{01} &= -\frac{1}{2} g_m N_{i1} R_c + \frac{1}{2} g_m N_{i2} R_c \\
 N_{02} &= -\frac{1}{2} g_m N_{i2} R_c + \frac{1}{2} g_m N_{i1} R_c
 \end{aligned}$$

$N_{01} - N_{02} = -g_m R_c (N_{i1} - N_{i2})$   
 $N_{01} = \frac{1}{2} g_m R_c (N_{i1} - N_{i2})$   
 $N_{02} = +\frac{1}{2} g_m R_c (N_{i1} - N_{i2})$   
 $\therefore N_{od} = N_{01} - N_{02} = -g_m R_c (N_{i1} - N_{i2})$

$\therefore \frac{N_{od}}{N_{id}} = A_{dm} = -g_m R_c$

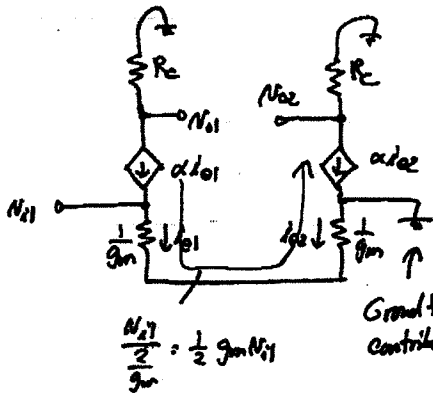⇒ Easiest to see this happening using the T-model: (for those who must see the model ckt.)




↳ This time also get the  $\frac{N_{01} - N_{02}}{N_{i1}}$  gain!

$$\begin{aligned}
 N_{01} &= -\frac{1}{2} g_m R_c N_{i1} \\
 N_{02} &= +\frac{1}{2} g_m R_c N_{i1}
 \end{aligned}$$

$N_{01} - N_{02} = -g_m R_c N_{i1}$   
 $\therefore \frac{N_{od}}{N_{i1}} = -g_m R_c$   
 $\frac{N_{02}}{N_{i1}} = \frac{1}{2} g_m R_c$   
 $\frac{N_{01}}{N_{i1}} = -\frac{1}{2} g_m R_c$

Diff. Mode Analysis

Assume a ckt. w/ only diff. input:

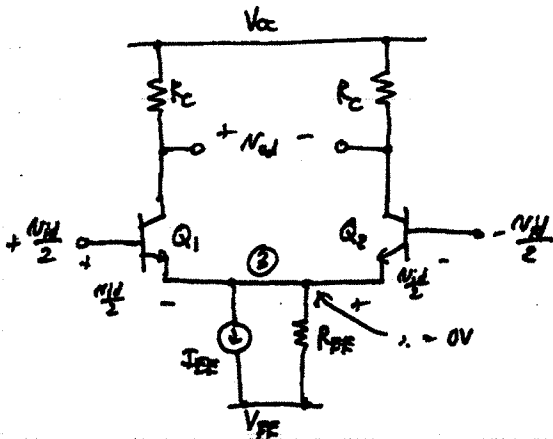

Total current thru  $I_{EE} = \text{const.}$


- $V_E = \text{const.}$  as input changes
- ③ act as an incremental ground! →  $V_{\text{circled 3}} = 0V$  (always!)

∴ we can ground ③, and then have

a **Differential Half Ckt.**

Note: Can really only make this for a purely symmetrical ckt.!

Differential Half Ckt.

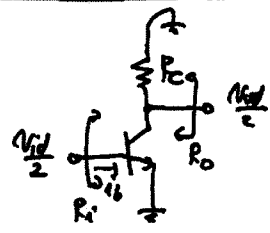


By inspection:  $\frac{v_{out}/2}{v_{in}/2} = \frac{v_{out}}{v_{in}} = A_{dm} = -g_m R_C$

$\frac{v_{out}/2}{i_b} = r_{\pi} \rightarrow R_{id} = \frac{v_{out}}{i_b} = 2r_{\pi} = R_{id}$

$\frac{v_{out}/2}{i_o} = r_o \parallel R_C \rightarrow R_{od} = \frac{v_{out}}{i_o} = 2(r_o \parallel R_C) \approx 2R_C = R_{od}$


S.S. params. determined w/  $I_C = \frac{I_{EE}}{2}$

First define

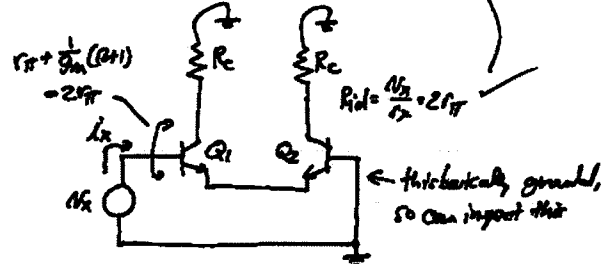

Common-Mode Analysis

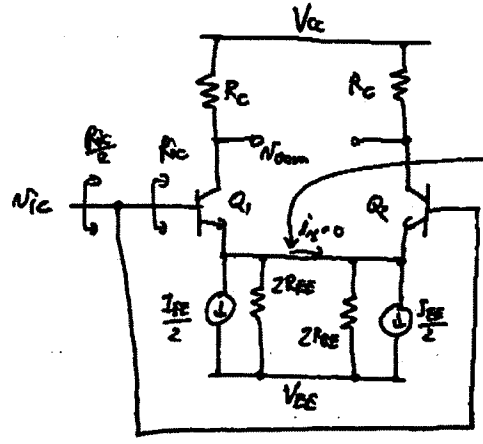
Assume a pure CM input  $\rightarrow$  tie inputs together



By symmetry,  $i_x = 0 \Rightarrow$  thus, totally have the equivalent of an open ckt. base

$\therefore \Rightarrow$  can split the ckt. into CM half-ckts.!

S.S. CM Half-Ckt.

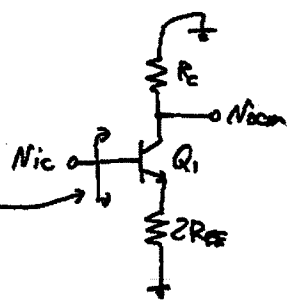

$R_{ic} = r_{\pi} + (\beta+1)(2R_{EE})$   
@ each input


$A_{cm} = \frac{v_{out,cm}}{v_{ic}} = -\frac{g_m R_C}{1 + g_m(2R_{EE})} \approx -\frac{R_C}{2R_{EE}}$

Want small for large CMRR  $\therefore$  want  $R_{EE} \rightarrow$  large!

Common-Mode Rejection Ratio =  $CMRR = \frac{A_{dm}}{A_{cm}} = \frac{-g_m R_C}{-\frac{g_m R_C}{1 + g_m(2R_{EE})}} \Rightarrow CMRR = 1 + 2g_m R_{EE}$

Having looked at S.S. parameters, we now turn to large signal performance. Here, we'll be particularly interested in the linear range of the ECP.

Large Signal ECP Performance

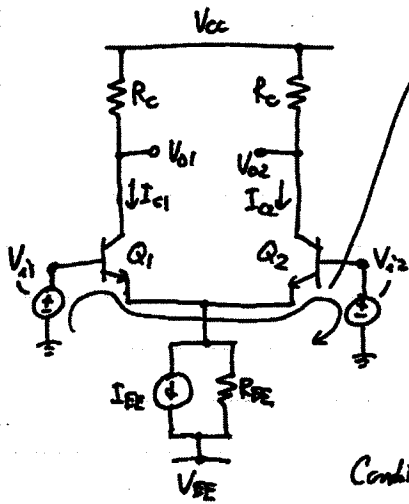

Find  $I_{C1}$  &  $I_{C2}$ :

EVL:  $V_{i1} - V_{be1} + V_{be2} - V_{i2} = 0$

$I_{C1} = I_{S1} \exp\left(\frac{V_{be1}}{V_T}\right) \rightarrow V_{be1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right), V_{be2} = V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right)$

$V_{i1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) - V_{i2} = 0 \rightarrow \ln \frac{I_{C1}}{I_{C2}} = \frac{V_{i1} - V_{i2}}{V_T} = \frac{V_{id}}{V_T}$

$\frac{I_{C1}}{I_{C2}} = \exp\left(\frac{V_{id}}{V_T}\right) \quad (1)$

$I_{EE} = I_{C1} + I_{C2} = \alpha (I_{C1} + I_{C2}) \quad (2)$

Combine (1) & (2) to get:

$I_{C1} = \frac{\alpha I_{EE}}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)}, I_{C2} = \frac{\alpha I_{EE}}{1 + \exp\left(\frac{V_{id}}{V_T}\right)} \quad (3)$

Find  $V_{od}$ :

$V_{01} = V_{CC} - I_{C1} R_C$   
 $V_{02} = V_{CC} - I_{C2} R_C$

$V_{od} = V_{01} - V_{02} = (I_{C2} - I_{C1}) R_C$  using (3)

$= \alpha I_{EE} R_C \left\{ \frac{1}{1 + \exp\left(\frac{V_{id}}{V_T}\right)} - \frac{1}{1 + \exp\left(-\frac{V_{id}}{V_T}\right)} \right\}$   
 $\times \frac{\exp\left(-\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right)} \quad \times \frac{\exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(\frac{V_{id}}{2V_T}\right)}$

$= \alpha I_{EE} R_C \left\{ \frac{\exp\left(-\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right) + \exp\left(\frac{V_{id}}{2V_T}\right)} - \frac{\exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(\frac{V_{id}}{2V_T}\right) + \exp\left(-\frac{V_{id}}{2V_T}\right)} \right\}$


$= \alpha I_{EE} R_C \left\{ \frac{\exp\left(-\frac{V_{id}}{2V_T}\right) - \exp\left(\frac{V_{id}}{2V_T}\right)}{\exp\left(-\frac{V_{id}}{2V_T}\right) + \exp\left(\frac{V_{id}}{2V_T}\right)} \right\} = \alpha I_{EE} R_C \frac{\sinh\left(-\frac{V_{id}}{2V_T}\right)}{\cosh\left(-\frac{V_{id}}{2V_T}\right)}$

$\left. \begin{aligned} \sinh u &= \frac{1}{2}(e^u - e^{-u}) \\ \cosh u &= \frac{1}{2}(e^u + e^{-u}) \end{aligned} \right\} u = -\frac{V_{id}}{2V_T}$

$\therefore V_{od} = \alpha I_{EE} R_C \tanh\left(-\frac{V_{id}}{2V_T}\right)$

From our knowledge of the Taylor series for  $\tanh x \approx x - \frac{x^3}{3} + \frac{2x^5}{15} - \dots$


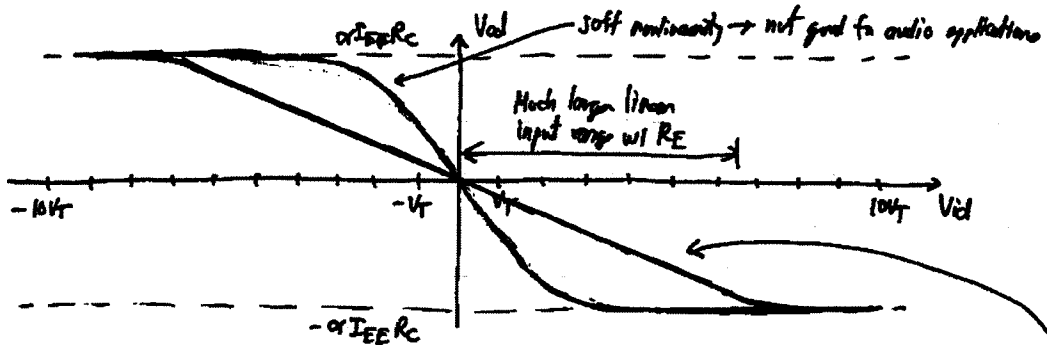
this is fairly linear for small  $V_{id}$ , but gets nonlinear abruptly when  $V_{id}$  approaches a threshold value!



In the above curve, the  $\frac{V_{out}}{V_{in}}$  X for function is really only linear for  $V_{in} < V_t \rightarrow$  beyond  $V_t$ , start to enter the nonlinear realm of curve  $\rightarrow$  causes signal distortion: eg, phone breaking up, television static

To linearize: add emitter degeneration (same trick as used before for single Xrista amplifiers)

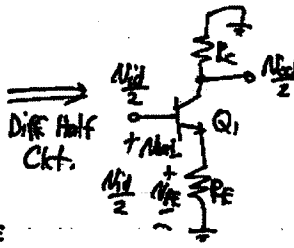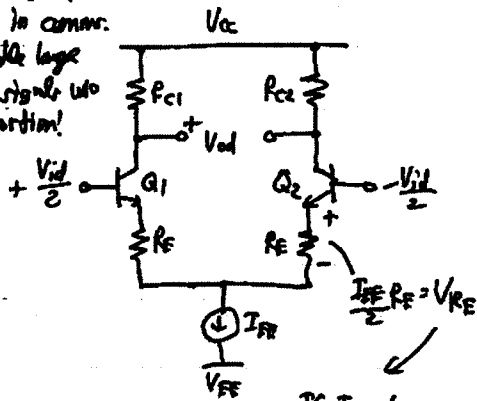Needed in common to handle large input signals w/o distortion!





$$A_{dm} = -\frac{g_m R_c}{1 + g_m R_E}$$

$\Rightarrow$  s.s. gain reduced, but the linear range is increased

If  $I_{EE}$  is large, then this can find large supply voltage


$\frac{N_{vid}}{2} = N_{v_{be1}} + N_{V_{RE}}$   
This can still be  $N_{v_{be1}} < V_t$  if this absorbs some of the input voltage!

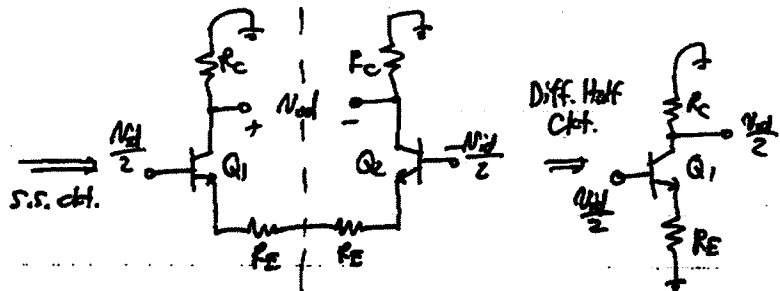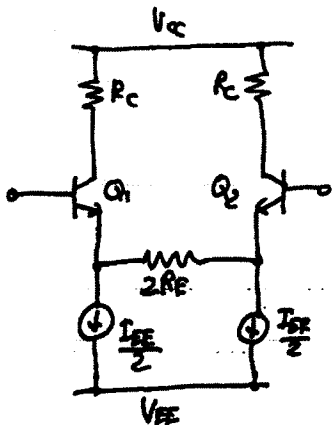Alternative Biasing Technique if Need Large DC Current:-



Some J.S. performance v/o the need to drop a DC voltage across  $R_E \rightarrow$  get both  
Can use lower  $V_{CC}$  &  $V_{EE}$ .

MOSFET Source-Coupled Pair

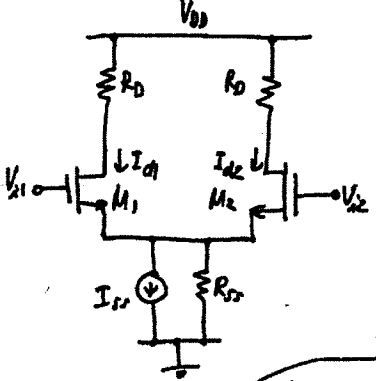

Assume:  $M_1$  &  $M_2$  are identical.

Find  $\Delta I_d = I_{d1} - I_{d2} = f(V_{id})$ .

$\Rightarrow$  approach: get  $V_{id} = f(\Delta I_d) \rightarrow$  then invert to get  $\Delta I_d = f(V_{id})$

$$I_{d1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{gs1} - V_t)^2 \Rightarrow V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k}}$$

$$\therefore V_{id} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_{d1}}{k}} - \sqrt{\frac{2I_{d2}}{k}}$$

Define:

$$\left. \begin{aligned} \Delta I_d &= I_{d1} - I_{d2} \\ I_d &= \frac{I_{d1} + I_{d2}}{2} \end{aligned} \right\} \begin{aligned} I_{d1} &= I_d + \frac{\Delta I_d}{2} \\ I_{d2} &= I_d - \frac{\Delta I_d}{2} \end{aligned}$$

$$V_{id} = \sqrt{\frac{2(I_d + \frac{\Delta I_d}{2})}{k}} - \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_d + \frac{\Delta I_d}{2} - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2} + I_d - \frac{\Delta I_d}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_d - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2}$$

$\Rightarrow$  now rearrange to get  $\Delta I_d$  (algebra)

Solve for  $\Delta I_d$ :

$$\Delta I_d = \frac{k}{2} V_{id} \left( \frac{2I_{ss}}{k/2} - V_{id}^2 \right)^{1/2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left( \frac{2I_{ss}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_d$$

Large Signal Equation for Differential Output Current


Valid so long as the devices stay saturated:

$$|V_{id}| \leq \sqrt{\frac{2I_{ss}}{k}} = \sqrt{\frac{2I_{ss}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

if true then input devices are both saturated

Thus, to extend the linear input range:

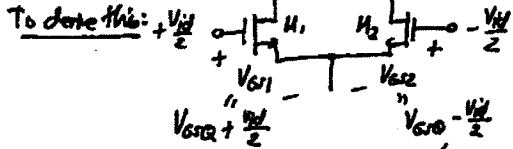- ①  $I_{ss} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ②  $W/L$
- ③  $L \uparrow$



When  $V_{id} \geq V_{GS} - V_t = \Delta V$  then  $M_2$  will cut-off

$\therefore V_{id} \leq 2(V_{GS} - V_t) \rightarrow$  to maintain saturation

$$V_{GS} - V_t = \sqrt{\frac{2I_{d2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$$

then plug in  $\Delta I_d$  & solve for  $V_{id}$



