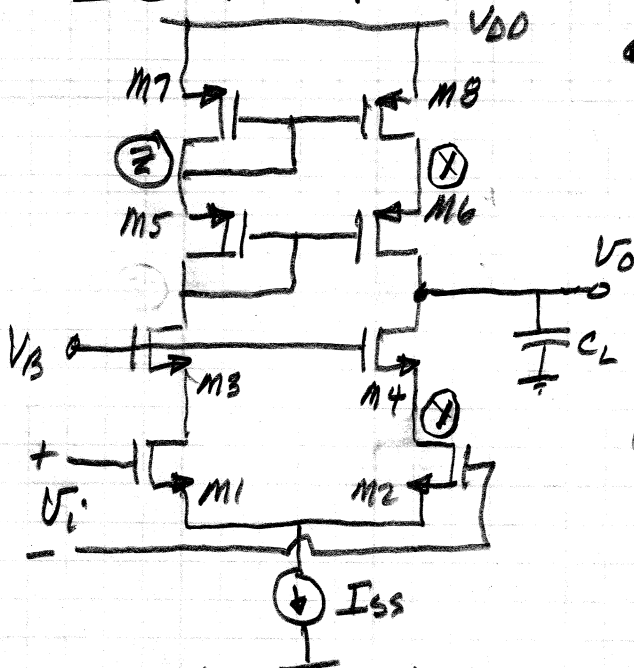


• Telescopic Opamp (cont.):



• Problems with this opamp:

(i) limited output swing

$$V_o(\max) = V_{\otimes} - |V_{ov6}|$$

$$= |V_{DD} - |V_{T7}| - |V_{ov7}| - |V_{ov6}|$$


with $|V_{T5}| = |V_{T6}|$ & $|V_{ov5}| = |V_{ov6}|$

(ii) $V_o(\min) = V_{\oplus} + V_{ov4}$

$$= V_B - V_{T4}$$

with V_B fixed from generator.

• Very limited input common-mode Range:

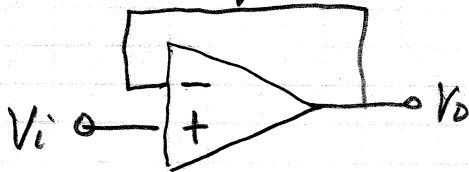

unity-gain follower

$$V_{ic} = \frac{V^+ + V^-}{2} = V_i$$

(i) $V_{ic}(\min) = V_B - V_{T4}$


(ii) $V_{ic}(\max) = V_B - V_{ov4}$

with $V_{T2} = V_{T4}$.

$$CMR_i \equiv \text{input CM range} = V_{ic}(\max) - V_{ic}(\min) = |V_{T4} - V_{ov4}|$$

Very low $CMR_i \rightarrow$ Telescopic opamp not suitable unity-gain buffers or for high dynamic range.

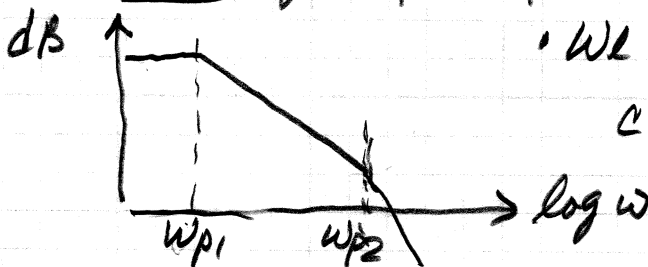• Poor frequency response due to non-dominant pole:



• We want $\frac{\omega_{p2}}{\omega_{p1}}$ large for closed-loop stability


Dominant pole = $\omega_{p1} \approx \frac{1}{R_o C_o} \approx \frac{1}{g_m r_o^2 C_L}$ (Equal $g_m, r_o, etc.$)

First non-dominant pole = ω_{p2} (Probably at \ominus because of high capacitance there)

$$\omega_{p2} \approx \frac{g_m7}{C_{ox} [(W/L)_7 + (W/L)_8]}$$

\therefore Low-frequency non-dominant pole, ω_{p2} , due to current mirror node.

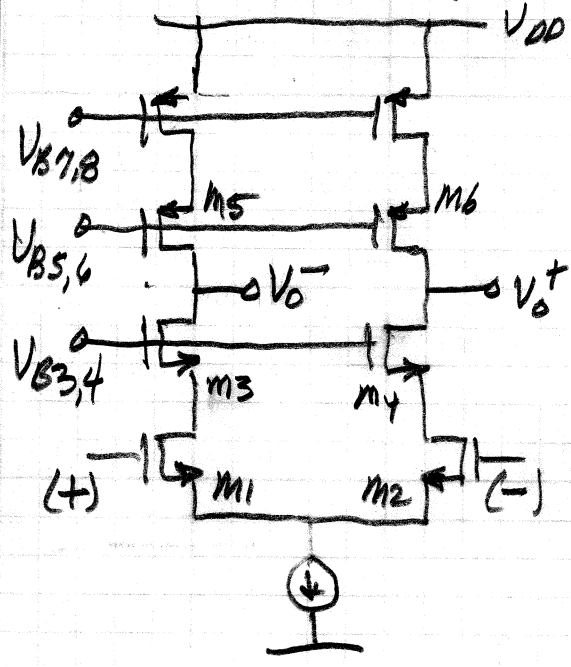
One Solution: Fully-differential (at both input and output):



- 6 dB increase in Dynamic Range
- Improved CMRR and PSRR
- ω_{p2} at higher frequency (i.e., no mirror node). Thus, better closed-loop stability.
- But, CM Feedback circuit needed to set DC voltages at the output nodes.

Another solution: Two-stage CMOS Opamp

AMPAD™

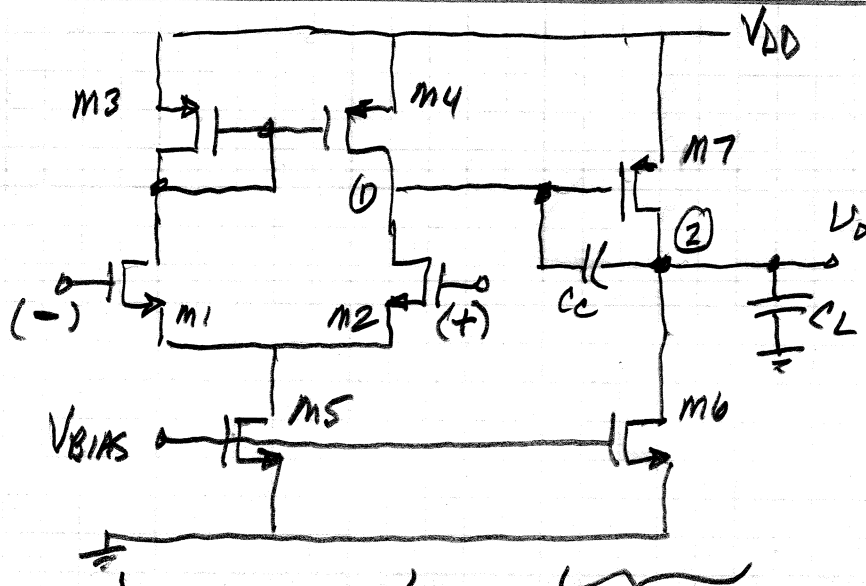

- Two stages connected in cascade.
- $C_c \equiv$ Miller-multiplied frequency compensation capacitor

Input Differential Stage with NMOS tail current source

PMOS common-source second stage with NMOS current source load.


- Determine (+) and (-) input terminals
- Determine DC bias conditions (Assume $V_o(DC) = \frac{V_{DD}}{2}$) (Feedback will set DC voltage at V_o)

Gain: Stage 1: $a_{v1} = \frac{V_{\text{O1}}}{V_i} = \frac{-g_{m1}}{g_{o2} + g_{o4}}$

Stage 2: $a_{v2} = \frac{V_o}{V_{\text{O1}}} = \frac{-g_{m7}}{g_{o6} + g_{o7}}$


Overall gain = $a_v = a_{v1} \cdot a_{v2} = \frac{g_{m1}}{g_{o2} + g_{o4}} \cdot \frac{g_{m7}}{g_{o6} + g_{o7}}$

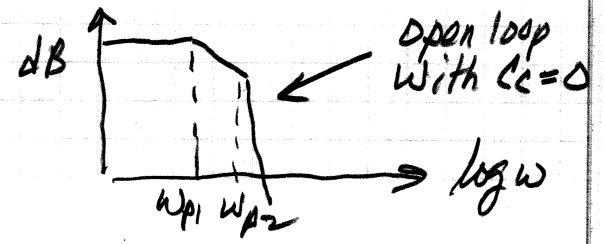Note: $R_{o1} \approx R_o$ so $\omega_{p1} \approx \omega_{p2}$ without C_c . We want an approximate one-pole response out to ω_T for stability reasons. The addition of C_c helps achieve this.



Now, add C_c compensation capacitor:

Miller Effect:

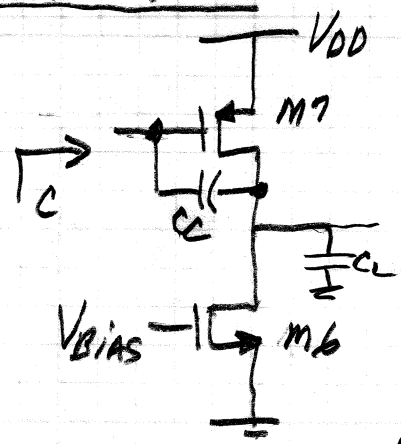

$$C = C_c (1 - a_{v2})$$

$$= C_c \left(1 + \frac{g_{m7}}{g_{o6} + g_{o7}} \right)$$


$$C \approx \frac{g_{m7}}{g_{o6} + g_{o7}} C_c$$

(e.g. $C = 100 C_c$)


- Huge savings in area of C_c using Miller Effect.
- ∴ Dominant pole = ω_{p1}

$$\omega_{p1} = \frac{1}{g_{o2} + g_{o4}} \cdot \frac{g_{m7} C_c}{g_{o6} + g_{o7}}$$

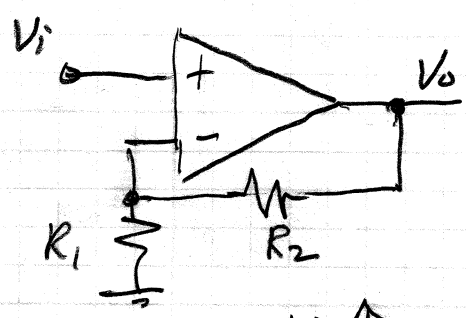• Typical closed-loop configuration: (negative FB)



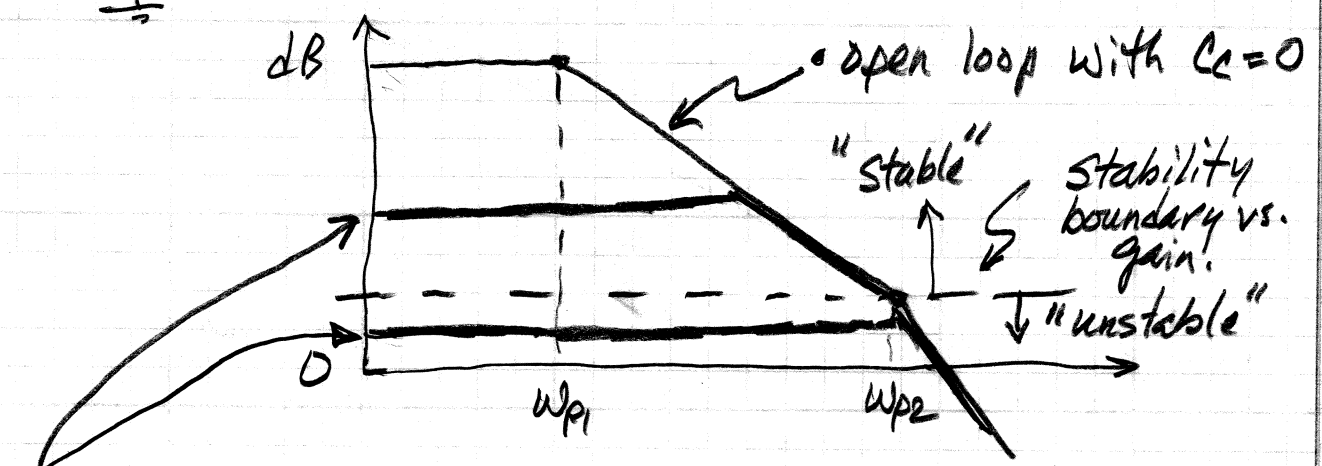
$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1} = \text{closed-loop gain}$$




- Case 1: $1 + R_2/R_1$ large (Easily stable)
- Case 2: $1 + R_2/R_1$ small ("unstable")

AMPAD

Now, add C_c :

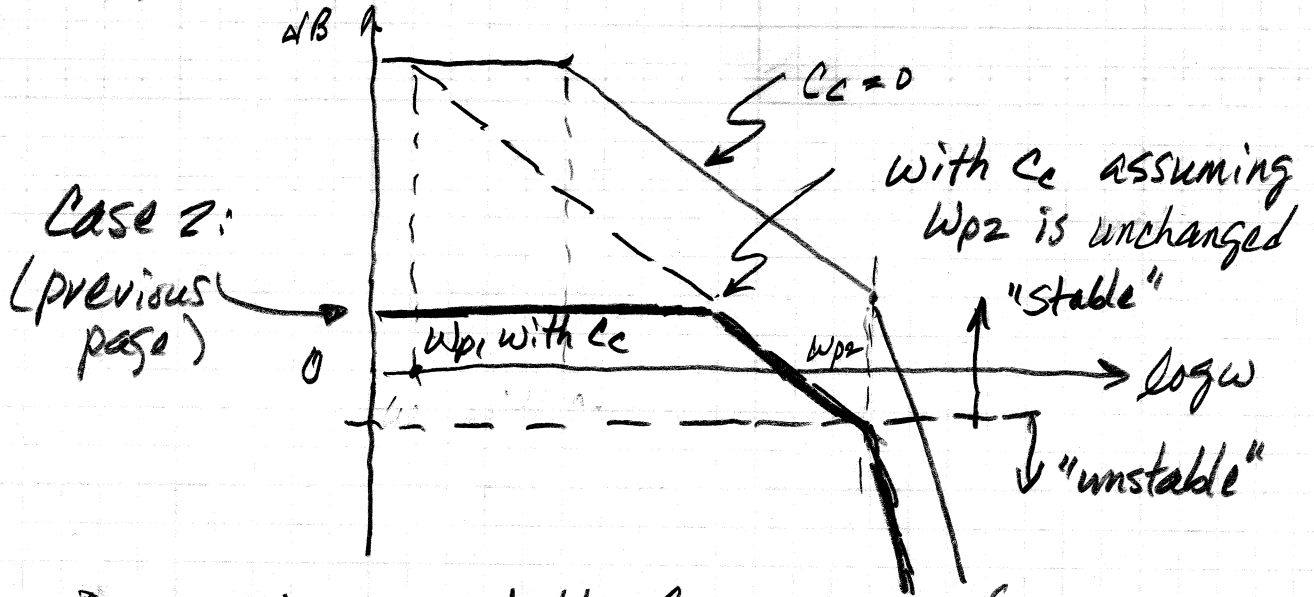

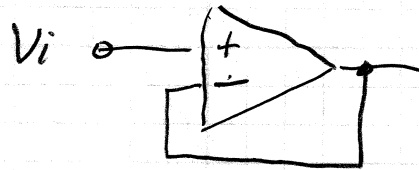
- Opamp is now stable for values of $A_v \geq 1$
- From this, we see that unity-gain is worst-case for closed-loop stability.




• Worst-case FB circuit for stability

In reality, ω_{p2} moves to a higher frequency!

Intuition:

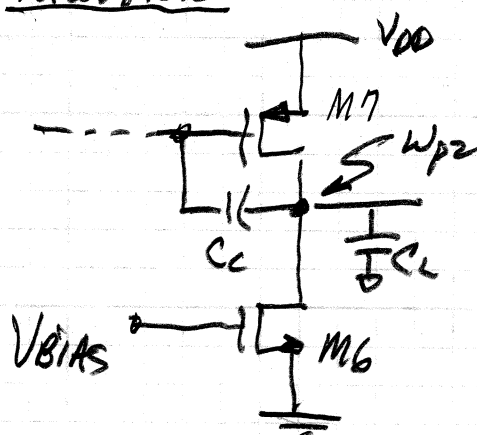

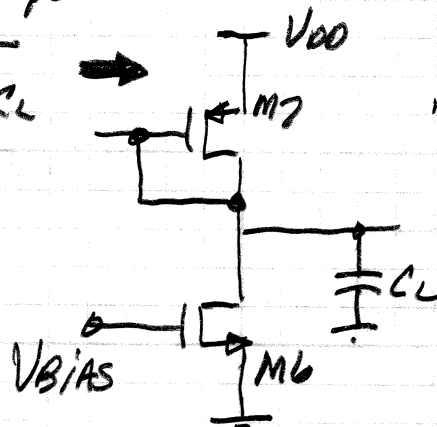• At high frequencies, assume C_c becomes a short circuit:



M_7 is now "diode connected"

$$\omega_{p2} \approx \frac{g_{m7} + g_{o6}}{C_L}$$

$$\omega_{p2} \approx \frac{g_{m7}}{C_L}$$

∴ Very good closed-loop

Stability with pole-splitting Miller compensation!!