
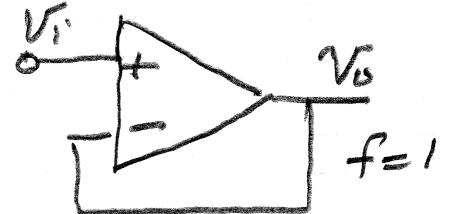


An aside: Frequency / time response of a two-pole system
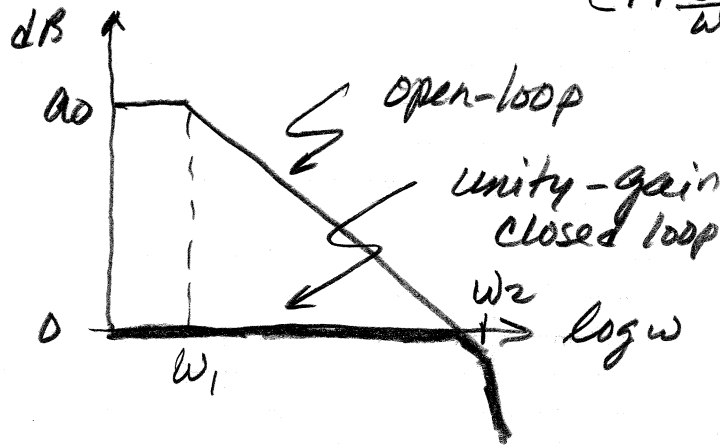
$$a(s) = \text{open-loop gain} = \frac{a_0}{(1 + \frac{s}{\omega_1})(1 + \frac{s}{\omega_2})}$$



Worst-case for closed-loop stability

$$A(s) = \text{closed-loop gain} = \frac{a(s)}{1 + a(s)} = \frac{A_0}{(s/\omega_0)^2 + 2k(s/\omega_0) + 1}$$


Where $A_0 = \frac{a_0}{a_0 + 1}$

$$\omega_0 = [\omega_1 \omega_2 (1 + a_0)]^{1/2}$$

And $k = \frac{\omega_1 + \omega_2}{2\omega_0}$ with $\beta = \omega_2/\omega_1 \equiv$ pole separation factor

- $k > 1 \rightarrow$ overdamped
- $k = 1 \rightarrow$ critically damped
- $k < 1 \rightarrow$ underdamped

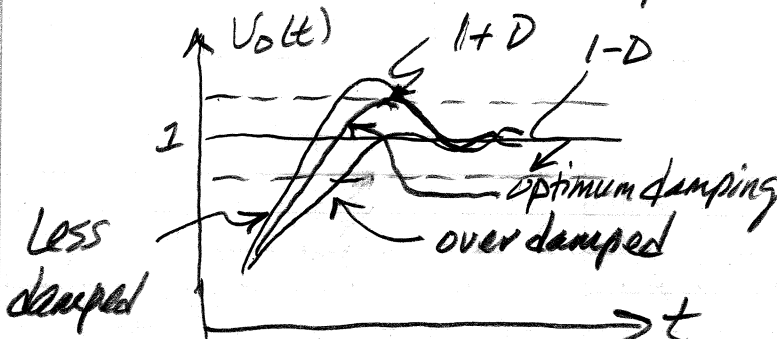
$\beta_0 \equiv$ optimum pole separation factor $\approx \frac{4(1+a_0)}{1 + (\pi/\ln D)^2}$



ϕ_m (MST) \equiv phase margin for minimum settling time

$$= 90^\circ - \tan^{-1} \left[\frac{1 + (\pi/\ln D)^2}{4} \right]$$

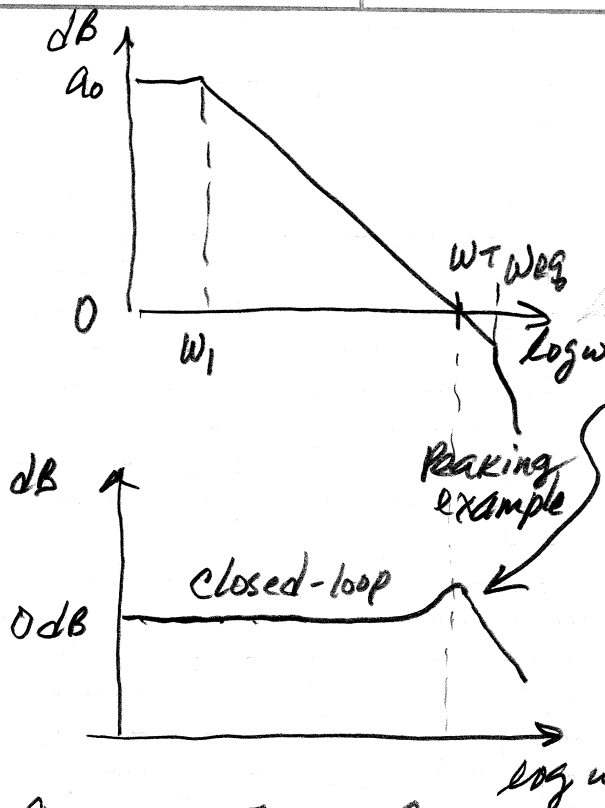• See: Yang & Aulstot, IEEE Trans. Circuits and Systems, March 1990.



• It can be shown that

$$\frac{1}{w_{eg}} = \frac{1}{w_2} + \frac{1}{w_3} + \dots$$

Φ_m	w_T/w_{eg}	Q	Peaking
55°	0.700	0.925	1.08 dB
60°	0.580	0.817	0.72 dB
65°	0.470	0.717	0.40 dB
70°	0.360	0.622	0.12 dB
75°	0.270	0.527	≈ 0 dB

• Canonic Forms for denominator of second-order system:

$$A(s) = \frac{K}{s^2 + \left(\frac{w_0}{Q}\right)s + w_0^2}$$

Where Q = quality factor

w_0 = resonant frequency




$$\text{or } A(s) = \frac{K}{s^2 + 2\zeta w_n s + w_n^2}$$

Where ζ = damping factor

w_n = natural frequency


• Compensation Techniques:

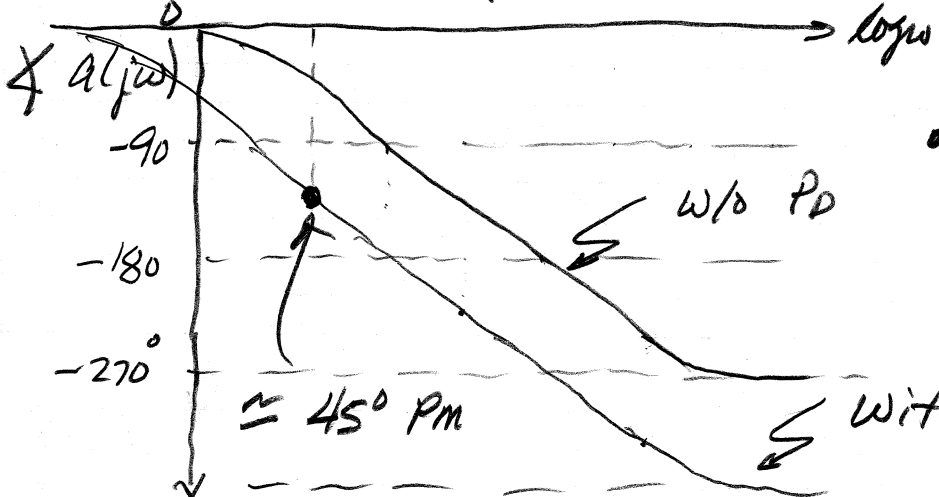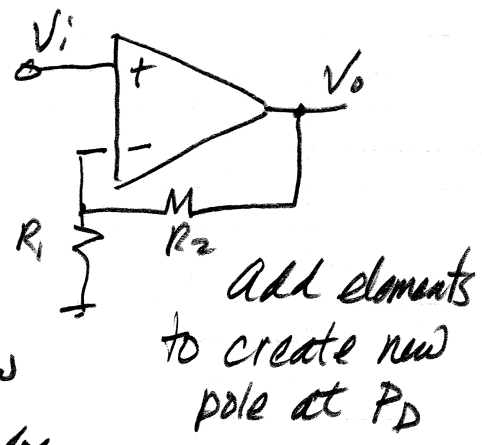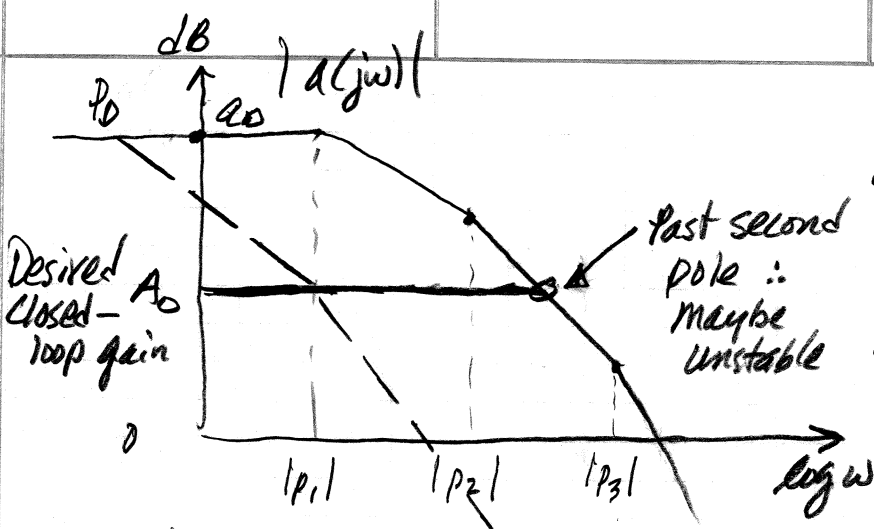- (i) Narrowbanding - Introduce a new dominant pole, P_0 , into the system so that there is sufficient separation between P_0 and P_1 . P_1 becomes second pole. Want $P_1/P_0 = T_{\max}$




• Stable but very much reduced BW

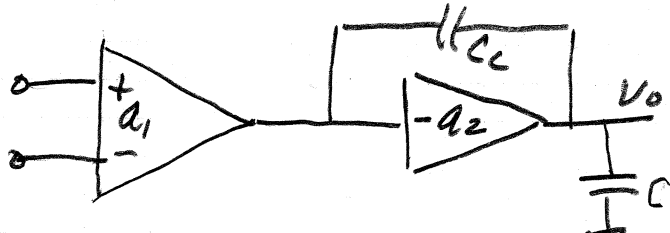(ii) Pole-splitting compensation: Take advantage of Miller multiplication of compensation capacitance



Model:

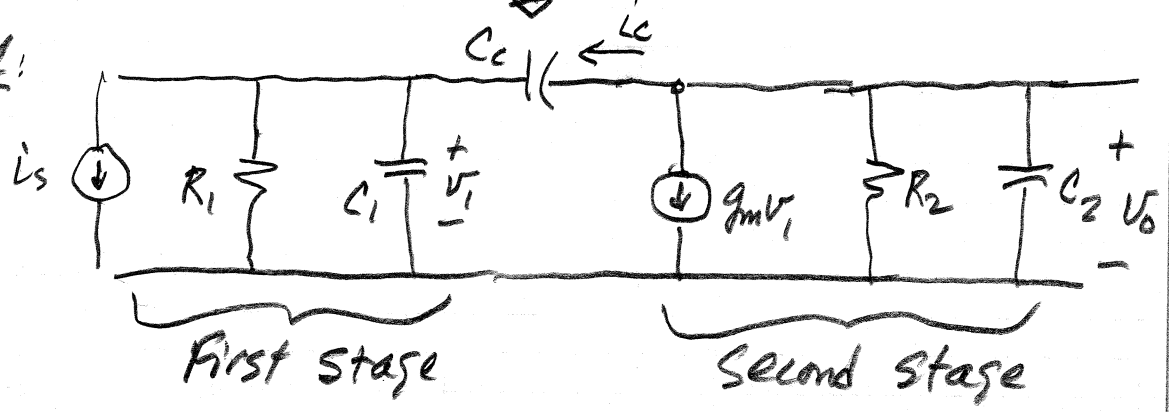

$$\frac{V_o}{i_s} = \frac{(g_m - sC_c) R_1 R_2}{1 + s[(C_2 + C_c) R_2 + (C_1 + C_c) R_1 + g_m R_1 R_2 C_c] + s^2 R_1 R_2 (C_1 C_2 + C_2 C_c + C_1 C_c)}$$

$$z = \text{RHP zero} = \frac{g_m}{C_c}$$

This is a two-pole transfer function:

$D(s) \equiv$ Denominator polynomial

$$= \left(1 - \frac{s}{p_1}\right) \left(1 - \frac{s}{p_2}\right)$$

$$= 1 - s \left(\frac{1}{p_1} + \frac{1}{p_2}\right) + \frac{s^2}{p_1 p_2}$$

Apply a dominant pole approximation: i.e. $p_1 \ll p_2$

$$\therefore D(s) \approx 1 - \frac{s}{p_1} + \frac{s^2}{p_1 p_2}$$

Equating coefficients:


$$p_1 = - \frac{1}{R_1 (C_1 + C_c) + R_2 (C_2 + C_c) + g_m R_1 R_2 C_c}$$

$$\therefore p_1 \approx - \frac{1}{g_m R_2 R_1 C_c} \quad \text{if } g_m R_2 \gg 1 \text{ and } C_c \text{ is large}$$

Now, equate coefficients of s^2 terms:

$$p_2 \approx - \frac{g_m C_c}{C_1 C_2 + C_c (C_1 + C_2)}$$

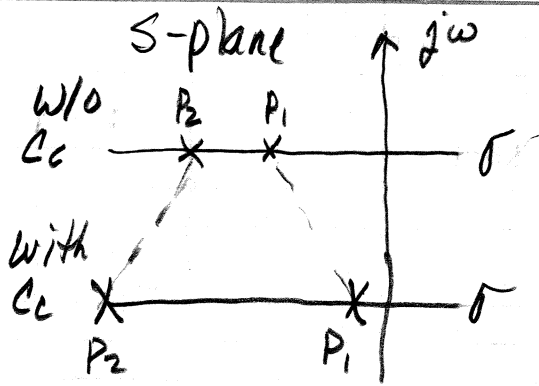- Let's examine relative to p_1 and p_2 before frequency compensation:



$w/o C_c: p_1 = -\frac{1}{R_1 C_1}$
 $w/with C_c: p_1 \approx -\frac{1}{g_m R_2 R_1 C_c}$
 $= -\frac{1}{R_1 C_1} \cdot \frac{1}{g_m R_2} \cdot \left(\frac{C_1}{C_c}\right)$
 Original p_1 Second stage gain
 Both terms typically $\gg 1$


$w/o C_c: p_2 = -\frac{1}{R_2 C_2}$
 $w/with C_c: p_2 \approx -\frac{g_m C_c}{C_1 C_2 + C_c(C_1 + C_2)}$

Let's associate p_2 with the output node: $p_2 = -\frac{1}{R_o C_T}$

Where R_o is output resistance including negative FB around second stage via C_c ; C_T is total capacitance to ground at output.

$R_o = \frac{R_2}{1+T}$ where $T \equiv$ loop gain around stage 2
 $= \frac{R_2}{1+g_m R_2 f} \approx \frac{1}{g_m f}$ with $T = g_m R_2 f \gg 1$

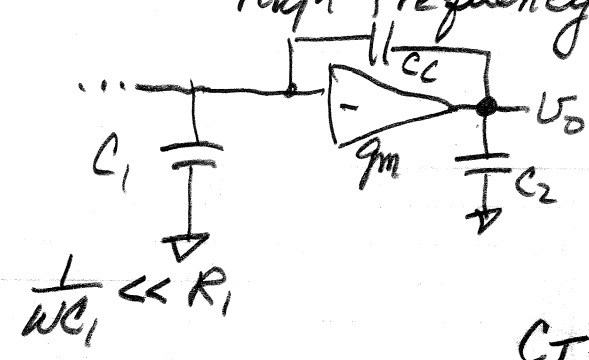Note: p_2 is high frequency so evaluate f at high frequency. Thus, capacitive divider sets f :



$f \approx \frac{C_c}{C_1 + C_c} \cdot R_o \approx \frac{C_1 + C_c}{g_m C_c}$
 $C_T = C_2$ in parallel with $(C_c$ and C_1 in series)
 $C_T = C_2 + \frac{C_1 C_c}{C_1 + C_c} = \frac{C_1 C_2 + C_1 C_c + C_2 C_c}{C_1 + C_c}$

Same result as from p. 142

AMEPAD

Let's rewrite $P_2 = -\frac{1}{R_{OCT}}$ and simplify:

$$P_2 \approx -\frac{g_m C_c}{C_1 + C_c} \cdot \frac{C_1 + C_c}{C_1 C_2 + C_1 C_c + C_2 C_c}$$


But, in practice, $C_c \approx C_2 \gg C_1$ (use layout techniques to minimize C_1)

$$\therefore P_2 \approx -\frac{g_m C_c}{C_1 C_2 + C_1 C_c + C_2 C_c}$$


$$P_2 \approx -\frac{g_m}{C_2}$$

Easy to remember

AMPAD™

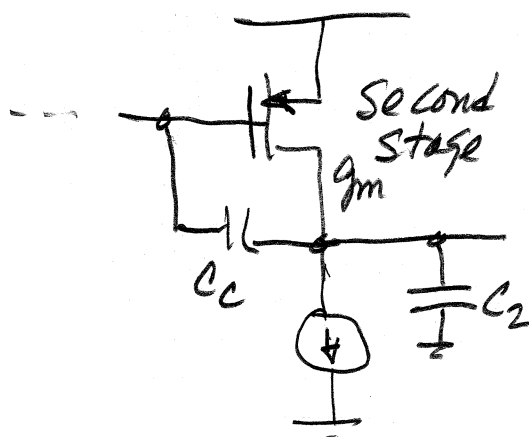

high frequencies

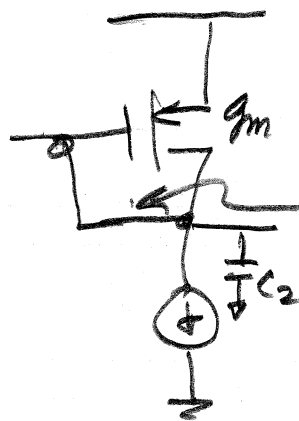

Think of C_c as short circuit so PMOS is diode connected with resistance $= 1/g_m$