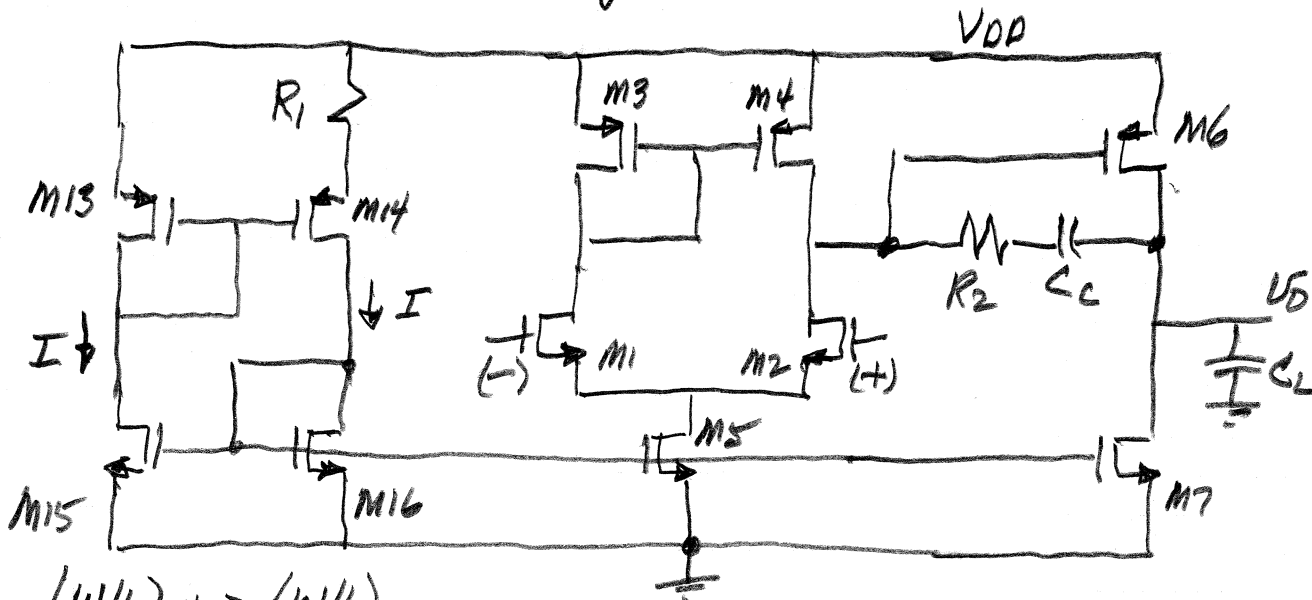


• Some loose ends:  $k'$  generator compensation



$(W/L)_{14} > (W/L)_{13}$

$(W/L)_{15} = (W/L)_{16}$

$\therefore$  all currents =  $I$

KVL neglecting back-gate effects:

$$I = \frac{2}{k_p' R_1^2}$$

$$\frac{1}{\left( \frac{1}{\sqrt{(W/L)_{13}}} - \frac{1}{\sqrt{(W/L)_{14}}} \right)^2}$$

[This is a geometric constant which is insensitive to PVT variations neglecting mismatches]

$$Z_1 = - \frac{1}{R_2 C_{II}}$$

$$P_2 = - \frac{g_{m2}}{C_{II}}$$

Assume  $I_7 = I_6 = KI$

$$\therefore P_2 = - \frac{\sqrt{2k_p'(W/L)_6 I_6}}{C_{II}}$$

$$= - \frac{\sqrt{2k_p'(W/L)_6 KI}}{C_{II}} = - \frac{\sqrt{2k_p'(W/L)_6 K^2}}{k_p' R_1^2 \left( \frac{1}{\sqrt{(W/L)_{13}}} - \frac{1}{\sqrt{(W/L)_{14}}} \right)^2} C_{II}$$


$$= - \frac{2}{R_1 C_{II}} \cdot K_1 \text{ (} K_1 \text{ is another geometric constant)}$$

Finally,  $Z_1 = P_2 \rightarrow \boxed{R_2 = \frac{R_1}{2K_1} \left( \frac{C_{II}}{2I} \right)}$

This is a low-voltage solution.

o Slew-rate in opamps:

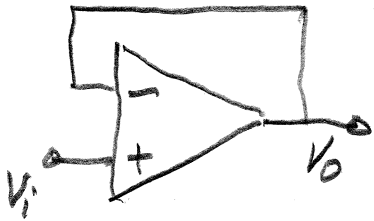Consider a single-pole opamp in unity gain:






$$V_i(s) = \frac{V_A}{s} \text{ (step input)}$$

$$V_o(s) = \frac{V_A}{s(1+s\tau_1)} = \frac{V_A}{s} - \frac{V_A}{s + \frac{1}{\tau_1}}$$


↕ inverse Laplace transform
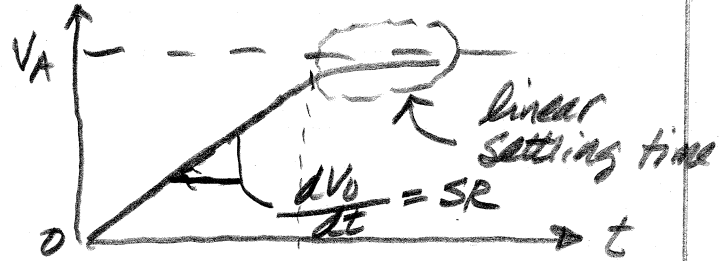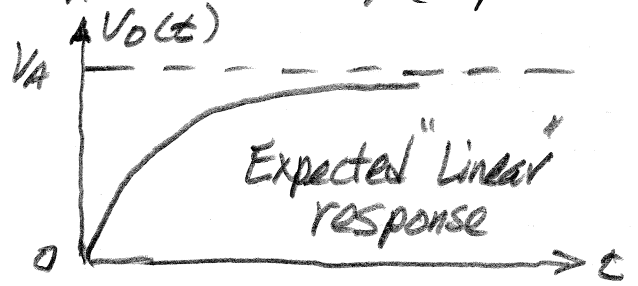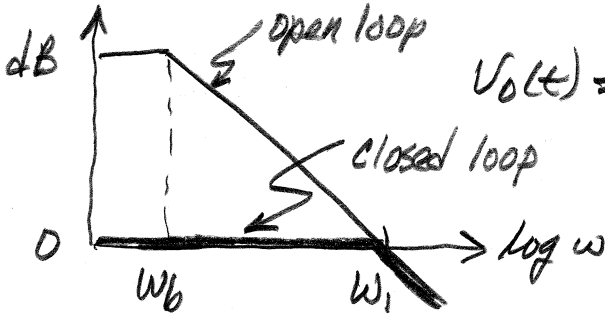
$$V_o(t) = V_A(1 - e^{-t/\tau_1}) \text{ (exponential)}$$



Large-signal non-linear slewing time

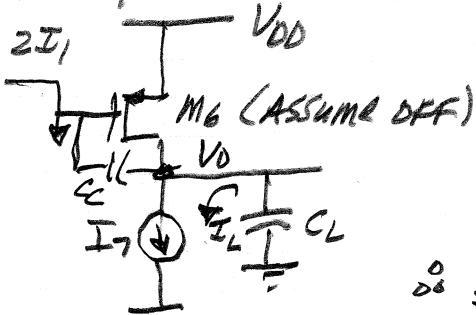\* For two-stage opamp, SR may be limited at output of first stage and/or output of second stage. From before:



KCL at  $V_o$ :  $I_7 = I_L + 2I_1$


$$\therefore I_L = I_7 - 2I_1 = C_L \frac{dV_o}{dt}$$

$$\therefore \frac{I_L}{C_L} = SR_2 \text{ and } \frac{2I_1}{C_c} = SR_1$$

second stage

first stage

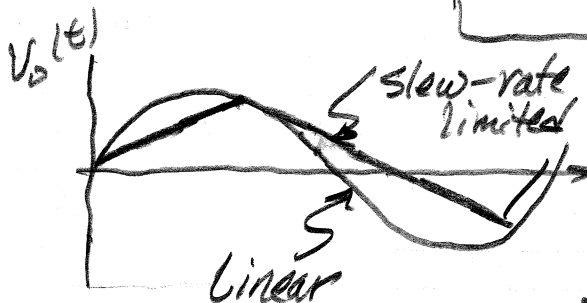For  $SR_1 = SR_2 \rightarrow I_7 = 2I_1 \left( \frac{C_L + C_c}{C_c} \right) \approx 4I_1$



Power Bandwidth

$$V_o(t) = V_p \sin \omega t$$

$$\frac{dV_o}{dt} \Big|_{\max} = \omega V_p = SR \therefore \omega_{\max} = \frac{SR}{V_p}$$

- Consider SR in terms of design variables:

$$SR = \frac{dV_o}{dt} = \frac{I_{XM} (\text{maximum})}{C_L} = \frac{I_{XM}}{G_{MI}} \cdot W_{ULT} A_o$$

$$C_L = \frac{G_{MI}}{W_{ULT} A_o} \quad (W_{ULT} = \omega @ |T(j\omega)| = 1)$$


Many performance parameter dependencies:

To increase SR:

- ① Decrease  $G_{MI}$
- ② Increase  $W_{ULT} \rightarrow$  increase  $p_2$  (limited by max transistor operating freq)
- ③ Use a larger  $A_o$  if possible by the application.

- Best choice is to ① decrease  $G_{MI}$  to increase SR:

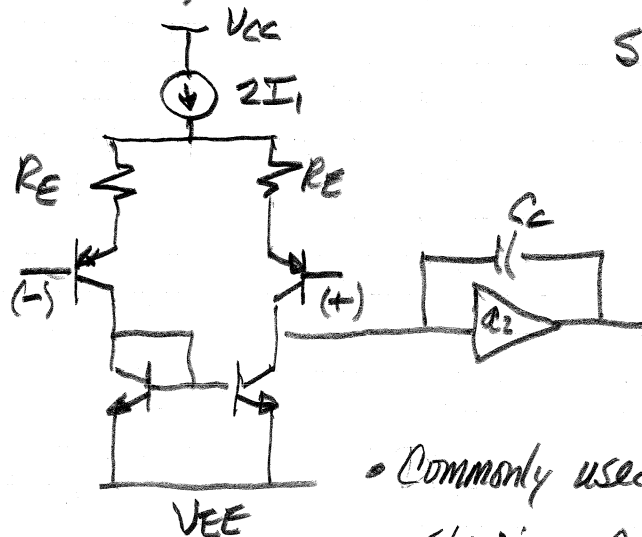(A) Consider BJT design with emitter (or source for mos) degeneration:



$$SR = \frac{2I_T}{G_{MI}} W_{ULT} A_o$$



$$\text{But } G_{MI} \approx \frac{g_{m1}}{1 + g_{m1} R_E}$$

$$SR = 2I_T W_{ULT} A_o \frac{(1 + g_{m1} R_E)}{g_{m1} R_E}$$

Commonly used for fast slewing BJT opamps

- Disadvantages:
- ①  $R_E$  mismatch  $\rightarrow$   $V_{os}$  (must limit  $V_{RE}$  to
  - ②  $R_E \uparrow$  gain  $\downarrow$  (SR-gain tradeoff) limit  $V_{os}$ )
  - ③  $R_E$  contributes thermal noise  $\rightarrow$  must limit size of  $R_E$  to preserve opamp noise performance

(B) JFET input stage in BJT technology:

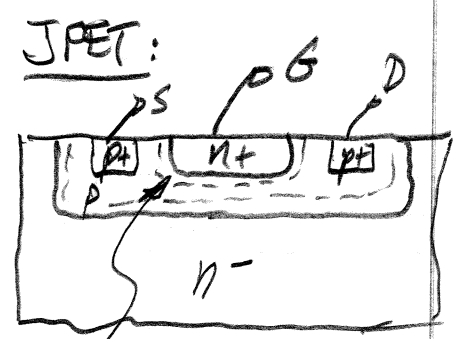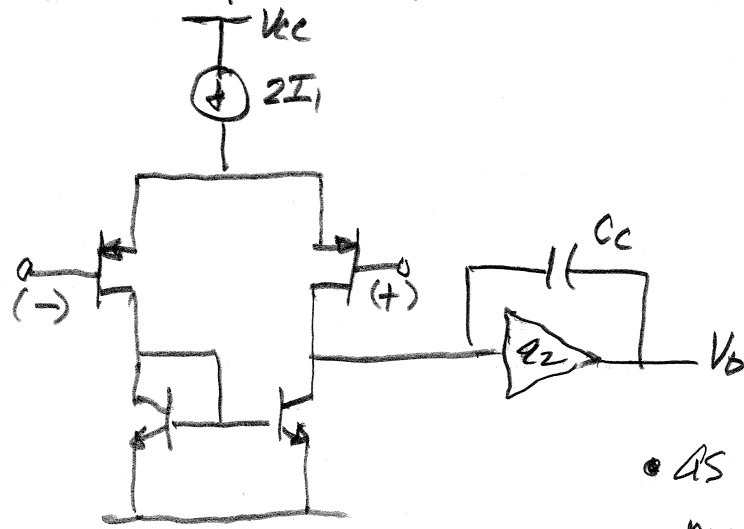

• as  $V_G$  is made more positive, depletion region widens to pinch off the channel region.

For FETs:  $\frac{g_m}{I_D} \approx \frac{2}{(V_{GS} - V_T)} \approx \frac{2}{0.2}$

For BJTs:  $\frac{g_m}{I_C} = \frac{1}{V_T} = \frac{1}{25mV}$


So  $\frac{g_m}{I_C} |_{BJT} \gg \frac{g_m}{I_D} |_{FET}$

∴  $\frac{SR|_{FET}}{SR|_{BJT}} = \frac{\frac{I_D}{g_{mF}} W_{ULT} A_0}{\frac{I_C}{g_{mB}} W_{ULT} A_0} \approx \frac{(V_{GS} - V_T)}{2V_T} \geq 5$

- Limitations:
- ① higher  $V_{OS}$
  - ② Increased voltage noise (but decreased current noise)

AMPAD

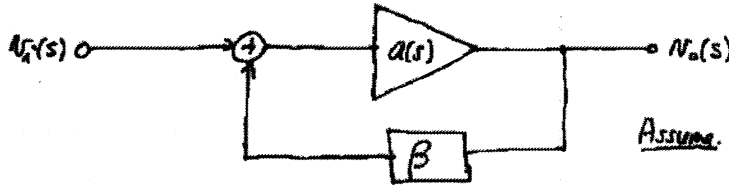Obtain expressions for overshoot ( $V_{overshoot}$ ) and settling time ( $T_s$ ) as functions of phase margin,  $\Phi_m$ :



Assume  $\beta = \text{const. w/ freq.}$

$$A(s) = \frac{N_o(s)}{N_i(s)} = \frac{a(s)}{1+a(s)\beta} \xrightarrow{[\omega_0 = \omega_n]} \frac{A_0 \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2} = \frac{A_0 \omega_0^2}{s^2 + \left(\frac{\omega_0}{Q}\right)s + \omega_0^2}$$

$$a(s) = \frac{a_0}{\left(1 + \frac{s}{\omega_1}\right)\left(1 + \frac{s}{\omega_2}\right)} = \frac{a_0 \omega_1 \omega_2}{(s + \omega_1)(s + \omega_2)}$$

General Laplace Biquad Transfer Functions


where by direct comparison:

Frequency response spectra for various values of  $\zeta$  on next page


$$\begin{cases} \omega_n = \sqrt{\omega_1 \omega_2 (1 + a_0 \beta)} \\ 2\zeta \omega_n = \omega_1 + \omega_2 \rightarrow \zeta = \frac{\omega_1 + \omega_2}{2\omega_n} = \frac{1}{2} \frac{\omega_1 + \omega_2}{\sqrt{\omega_1 \omega_2 (1 + a_0 \beta)}} \\ A_0 \omega_n^2 = a_0 \omega_1 \omega_2 \rightarrow A_0 = \frac{a_0}{1 + a_0 \beta} \end{cases}$$

Properties of the General Laplace Biquad Transfer Function (a very well-studied function!)

Pole-Zero Diagram

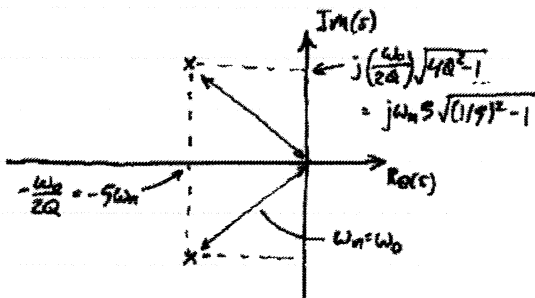

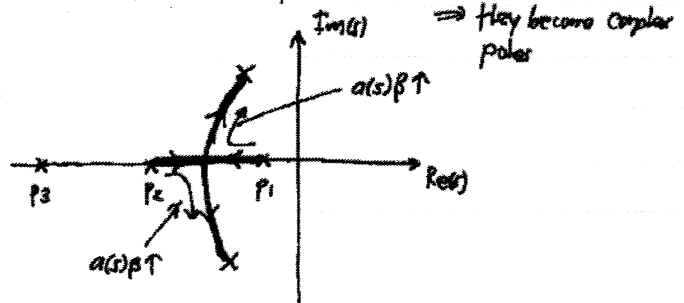Root Locus for FB Ckt: poles move as the loop gain increases



\(\Rightarrow\) they become complex poles

Time Domain Behavior

$$N_o(t) = A_0 V_i \left[ 1 - \frac{1}{\sqrt{1-\zeta^2}} e^{-\zeta \omega_n t} \sin(\sqrt{1-\zeta^2} \omega_n t + \phi) \right], \text{ where } \phi = \tan^{-1} \left[ \frac{\sqrt{1-\zeta^2}}{\zeta} \right]$$

For  $\zeta = \text{small} \rightarrow \phi = \frac{\pi}{2}$

For  $\zeta < 1$ : (for PM < 90°)

$$\% \text{ Overshoot} = \frac{\text{Peak Value} - \text{Final Value}}{\text{Final Value}} = \exp \left[ \frac{-\pi \zeta}{\sqrt{1-\zeta^2}} \right] \Rightarrow V_{overshoot} = V_0 \exp \left[ \frac{-\pi \zeta}{\sqrt{1-\zeta^2}} \right]$$


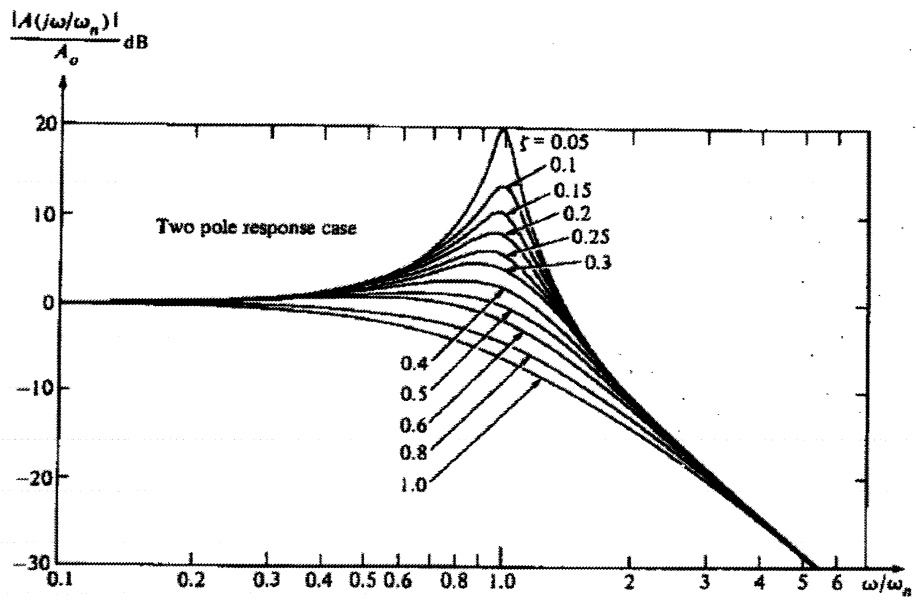


Figure C-2 Gain magnitude response for various values of  $\zeta$  for a second-order, low-pass system.

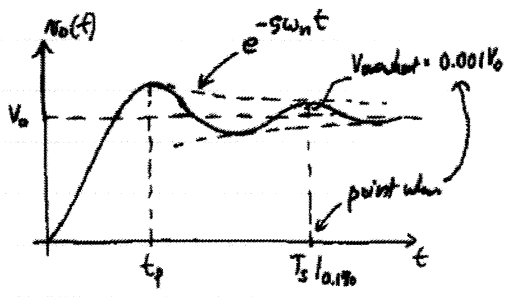

Find  $t_p$ :

$$\sqrt{1-\zeta^2} \omega_n t_p + \phi = \frac{3\pi}{2}$$

$[\zeta = \text{small} \rightarrow \phi \sim \frac{\pi}{2}] \Rightarrow t_p = \frac{\pi}{\omega_n \sqrt{1-\zeta^2}}$

Approximate Determination of 0.1% Settling Time -

$$V_{overshoot} e^{-\zeta \omega_n (T_s - t_p)} = 0.001 V_o \rightarrow T_s = t_p - \frac{1}{\zeta \omega_n} \ln \left[ \frac{0.001 V_o}{V_{overshoot}} \right]$$

$$s = -\frac{1}{\omega_n (T_s - t_p)} \ln \left[ \frac{0.001 V_o}{V_{overshoot}} \right]$$

Determine  $\phi_n = f(s)$  -

→ first get an expression for loop transmission:

$$A(s) = \frac{a(s)}{1 + a(s)\beta} \rightarrow a(s) = A(s) + a(s)A(s)\beta \rightarrow a(s) = \frac{A(s)}{1 - \beta A(s)}$$

$$\rightarrow a(s)\beta = \frac{\beta A(s)}{1 - \beta A(s)} = \frac{\beta A_0 \omega_n^2}{s^2 + 2\zeta \omega_n s + \omega_n^2 - \beta A_0 \omega_n^2} = \frac{\omega_n^2}{s^2 + 2\zeta \omega_n s} = \frac{\omega_n^2}{s(s + 2\zeta \omega_n)}$$

$[ \beta \approx \frac{1}{A_0} ]$ 
↑
↑

pole @ origin
LHP pole


⇒ get freq. at which  $|a(s)\beta| = 1 \rightarrow \omega_u$  =  $\omega_{ult}$

$$a(j\omega)\beta = \frac{\omega_n^2}{-\omega^2 + j25\omega_n\omega} \Rightarrow |a(j\omega)\beta| = \frac{\omega_n^2}{\sqrt{\omega^4 + \omega^2 45\omega_n^2}}$$

$$[|a(j\omega_u)\beta| = 1] \Rightarrow \frac{\omega_n^4}{\omega_u^4 + 45\omega_n^2\omega_u^2} = 1 \rightarrow \omega_u^4 + 45\omega_n^2\omega_u^2 - \omega_n^4 = 0$$

Solve quadratic:  $\omega_u = \omega_n \left[ \sqrt{45^2 + 1} - 25 \right]^{1/2}$

Find expression for phase:

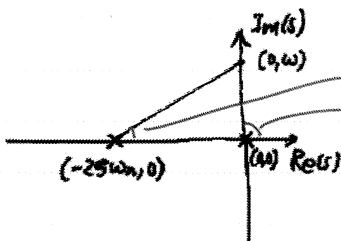

$$\phi = -\tan^{-1}\left(\frac{\omega}{0}\right) - \tan^{-1}\left(\frac{\omega}{25\omega_n}\right) = -90^\circ - \tan^{-1}\left(\frac{\omega}{25\omega_n}\right)$$

For Phase Margin:

$$\phi_m = 180^\circ + \phi|_{\omega=\omega_u} = 90^\circ - \tan^{-1}\left(\frac{\omega_u}{25\omega_n}\right)$$

$$\tan(90^\circ - \phi_m) = \frac{\omega_u}{25\omega_n}$$

$$[\tan(A+90^\circ) = -\frac{1}{\tan A}] \Rightarrow -\frac{1}{\tan(-\phi_m)} = \frac{\omega_u}{25\omega_n}$$

$$[\tan^{-1}(-x) = -\tan^{-1}x] \Rightarrow \phi_m = \tan^{-1}\left(\frac{25\omega_n}{\omega_u}\right) \quad \omega_{ult}$$

$$\text{or } \phi_m = \cos^{-1}\left[\sqrt{45^2 + 1} - 25\right]$$

Thus:

$$S = \frac{1}{2} \frac{\omega_{ult}}{\omega_n} \tan \phi_m$$

$$\Rightarrow T_s = t_p - \frac{2}{\omega_n \tan \phi_m} \ln \left[ \frac{0.001V_o}{V_{in,shot}} \right]$$

$\omega_{ult}$

(ignoring effects of slew rate)

⇒ But there's more to it than this. See the following papers:

- ① B.V. Kamath, P.G. Moyer, and P.R. Gray, "Relationship between frequency response and settling time of operational amplifiers," IEEE J. of Solid-State Ckts., vol. SC-9, no. 6, pp. 377-382, Dec. 1974.
- ② R.J. Apfel and P.R. Gray, "A fast-settling monolithic operational amplifier using doublet compression techniques," IEEE J. of Solid-State Ckts., vol. SC-9, no. 6, pp. 332-340, Dec. 1974.