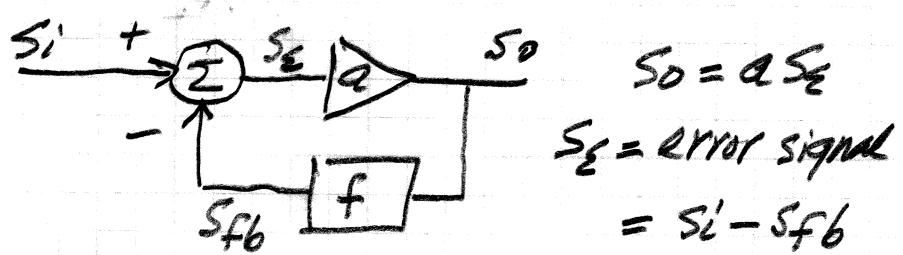


Feedback:Benefits of negative FB:

- ① Stabilizes closed-loop gain,  $A$ , against parameter changes and active device variations.

$$\therefore \frac{S_o}{S_i} = A = \frac{\alpha}{1+\alpha f}$$

loop transmission

$$A = \frac{\alpha}{1+\alpha f} \Rightarrow \frac{dA}{da} = \frac{(1+\alpha f) - \alpha f}{(1+\alpha f)^2} = \frac{1}{(1+\alpha f)^2}$$

For a change in open-loop gain,  $\delta\alpha$ :

$$\frac{\delta A}{\delta\alpha} = \frac{1}{(1+\alpha f)^2} \Rightarrow \delta A = \frac{\delta\alpha}{(1+\alpha f)^2} \quad (\text{much smaller than } \delta\alpha)$$



So, the fractional change is:

$$\boxed{\frac{\delta A}{A} = \frac{\delta\alpha}{\alpha^2}} \quad \therefore \text{gain sensitivity decreased by } \frac{1}{1+\alpha f} \approx \frac{1}{\alpha f} = \frac{1}{f}$$



Generally, closed-loop gain values are very accurate!

- ② Modifies  $R_i$  and  $R_o$  — i.e., improves these values according to the type of amplifier implemented.

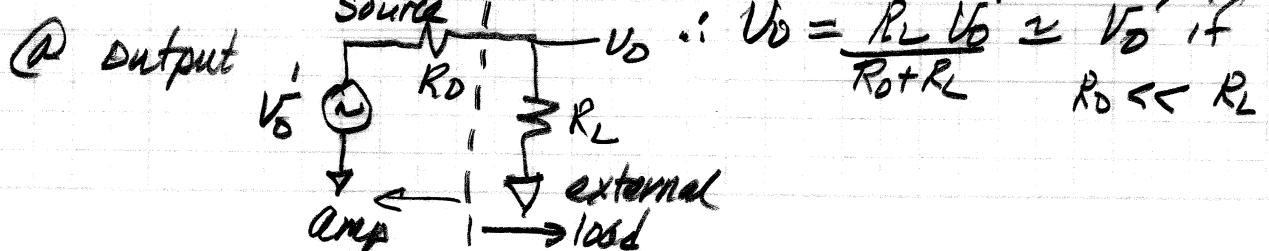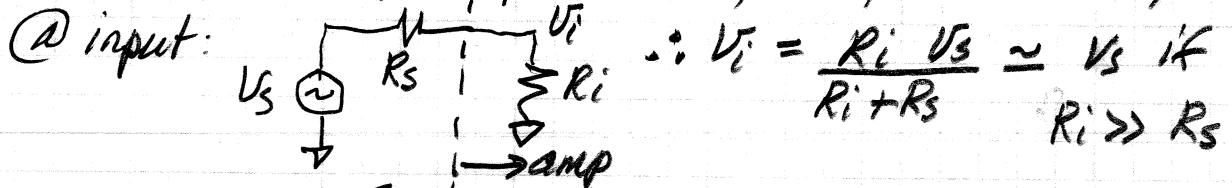Example: Voltage amplifier; i.e., Voltage in  $\rightarrow$  Voltage out



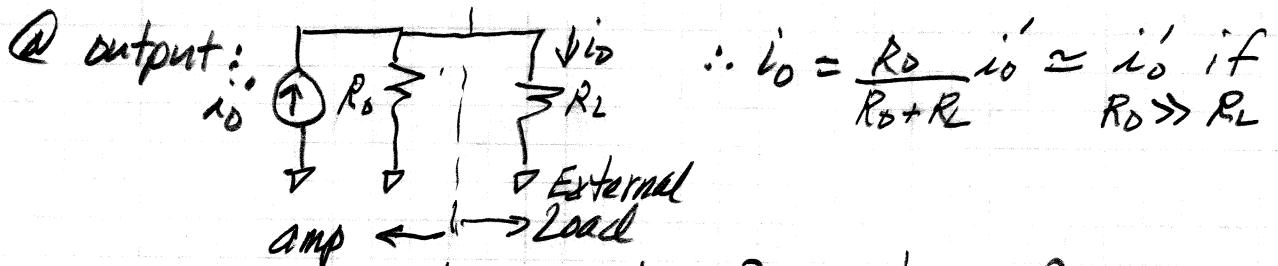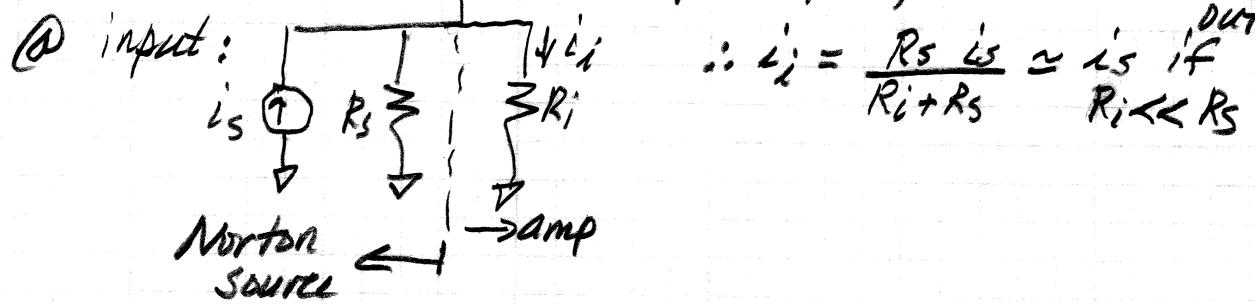Another example: Current amplifier, i.e., Current in  $\rightarrow$  Current out




Summary:

type	$R_i$	$R_o$
$V-V$ (Voltage Amp)	High	Low
$V-I$ (transconductance)	High	High
$I-V$ (transresistance)	Low	Low
$I-I$ (current amp)	Low	High

- Key Point: Negative FB can be used to tailor  $R_i$  and  $R_o$  for a specific type of amplifier

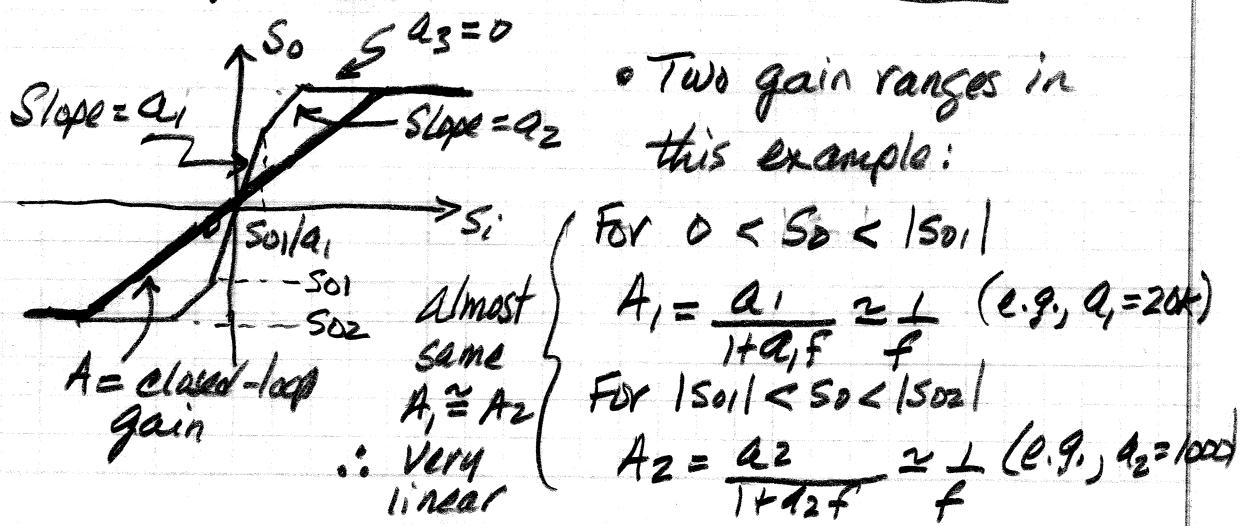(3) Negative FB to reduce distortion, increase linearity

- Consider a general open-loop transfer function:




④ Use negative FB to increase Bandwidth

- ① Gain is reduced - reduction factor equal to the amount of gain stabilization, distortion reduction, etc.; i.e., gain reduced by  $(1+af)$ .
- ② Feedback causes stability problems (if not compensated properly).

• Inspection Analysis of Feedback Circuits

• Identification of Feedback Types

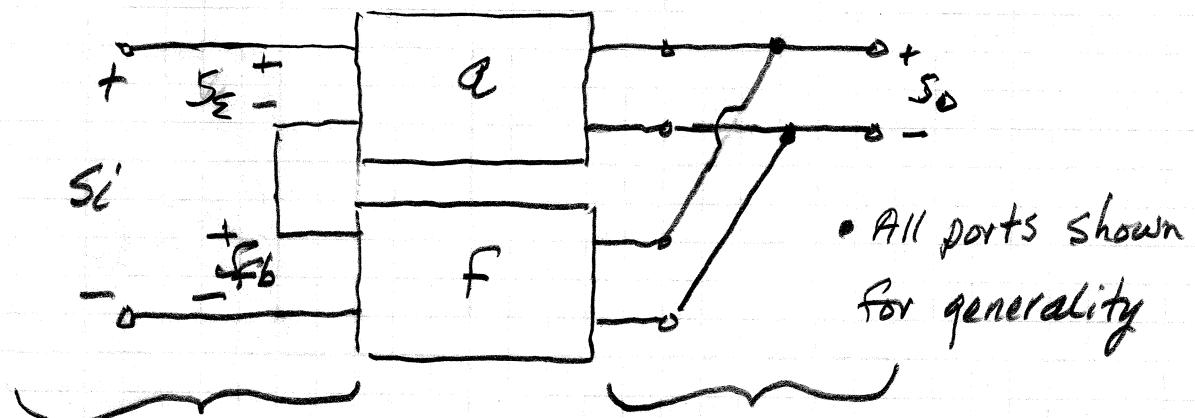

Series Connection

- Feedback network port in series with amplifier port must go through both the FB port and the Amplifier port to get from the (+) input to the (-) input (often ground)

Shunt connection

- Feedback network port in shunt with amplifier port can go from the (+) output to the (-) output either through the amplifier port or the feedback network port


• Steps to identification:

(i) Check for negative Feedback


(ii) Identify type of Feedback at input and output

- Examples of Feedback Circuits:

- First, a basic amplifier: (TWO CE stages)

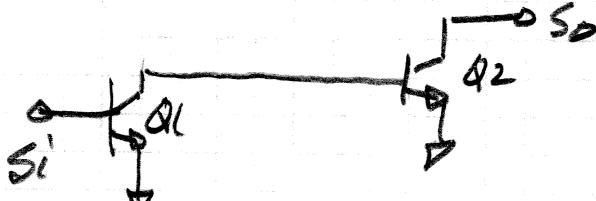

Example 1:

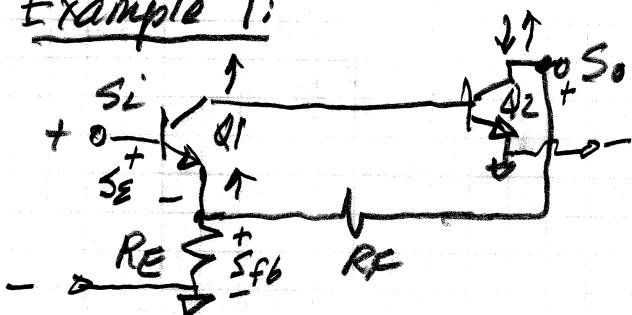

Type?


Series at input — must go through  $Q_1$  and  $R_E$  to go from (+) to (-) input terminals

Shunt at output — Either from (+) output terminal to (-) through  $Q_2$  or  $R_F$  and  $R_E$

Negative FB?

Yes, follow around loop

Example 2:

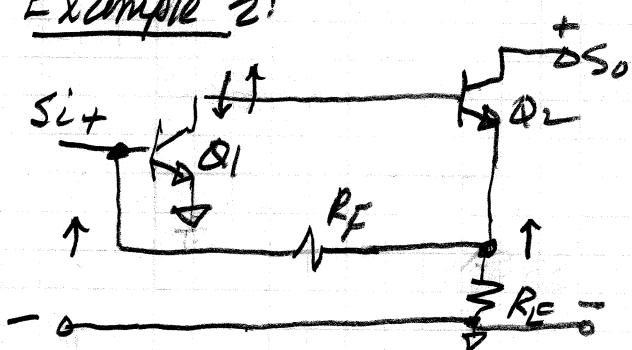

Negative FB?

Yes, follow around loop

Shunt at input — Either from (+) input to ground (emitter) or from (+) to (-) (ground) through  $R_F$  and  $R_E$


Series at output — must go through  $Q_2$  and  $R_E$  to go from (+) output terminal to (-) output terminal.

Shunt at input — same as above


Shunt at output

Example 3:


Same circuit except take output between  $R_F$  and  $R_E$ .

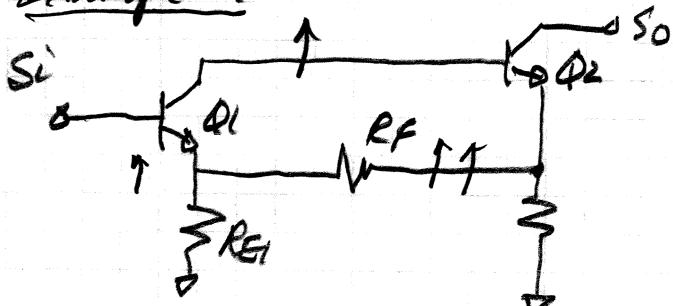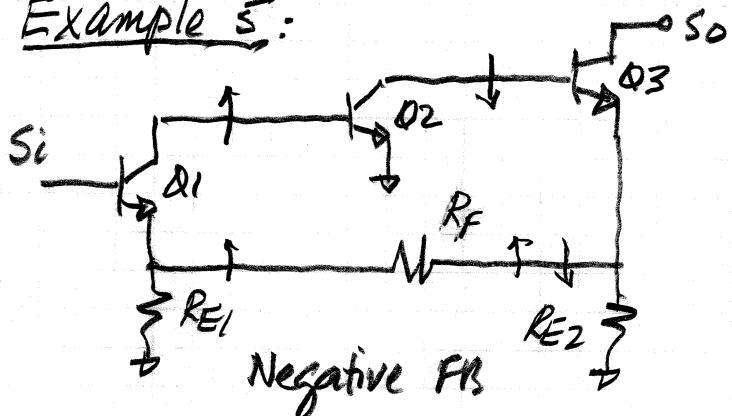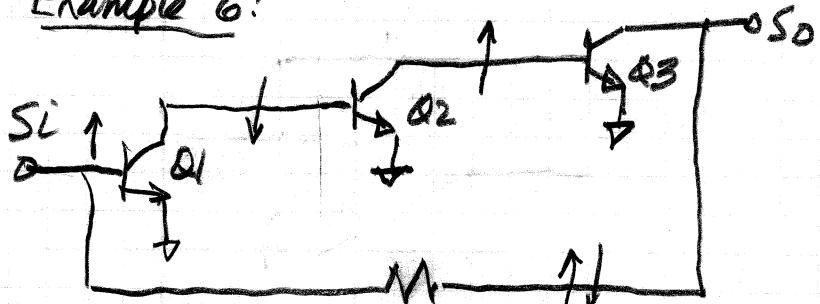Example 4:Series at inputSeries at output

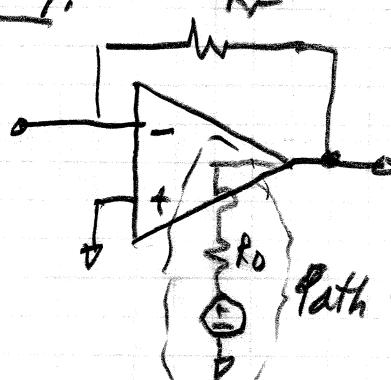
But, what about feedback?  
No, positive feedback -  
follows around loop

Example 5:

(add extra stage  
to get negative  
feedback)


Series at inputSeries at outputExample 6:

Yes, negative FB.

Shunt at inputShunt at outputExample 7:Shunt at inputShunt at output

Yes, negative FB

Path to ground through opamps.

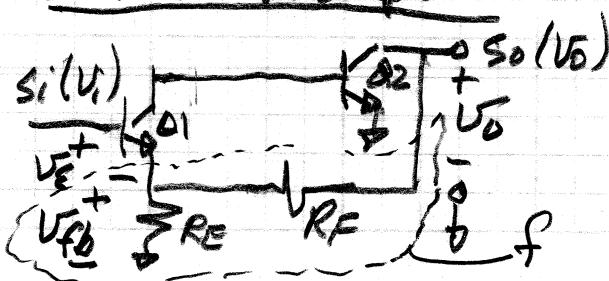Back to Example 1:


Series-Shunt: i.e., Voltage-Voltage  
Amp

$$V_{fb} = \frac{RF}{RE + RF} V_o$$

$$V_E = V_i - V_{fb}$$

$$V_i = V_{fb} + V_E$$

## Back to Example 2:

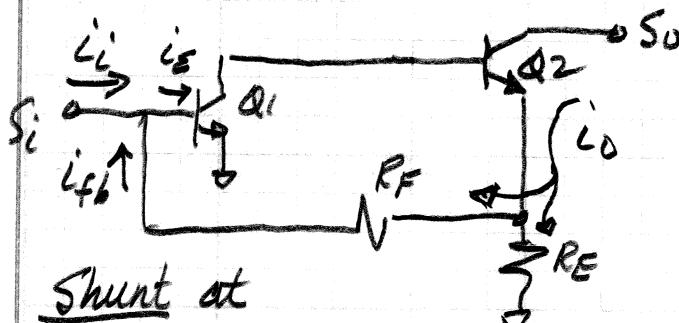

Series at output :  
Current as shown


Shunt at  
input : current as shown

### Effect of Feedback on $Z_i$ and $Z_o$ :

Example: Series-shunt feedback

Assumption (for now): Feedback network has ideal impedances;

i.e., does not load basic amplifier

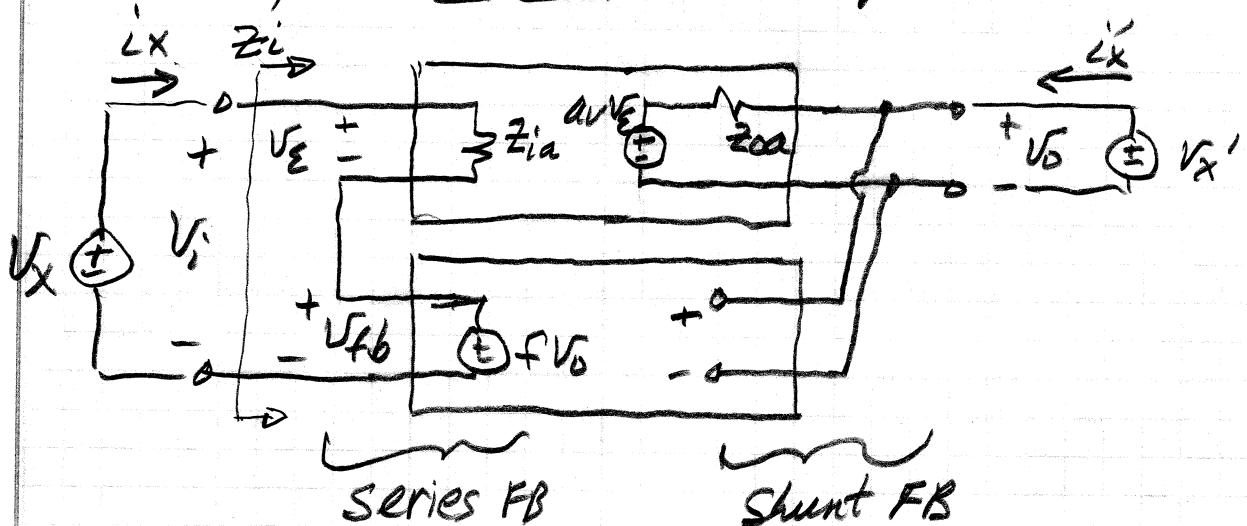

### Find the transfer function: (Ideal with no loading effects)

$$V_E = V_i - V_{fb} \quad \left. \begin{array}{l} \\ \end{array} \right\}$$

$$V_O = a_V V_E$$

$$V_{fb} = f V_O$$

$$\Rightarrow \frac{V_O}{V_i} = \frac{a_V}{1 + a_V f}$$

(as expected)

### Find the input impedance, $Z_i$ :

Apply a test source  $V_x$  as shown.

$$V_x = V_E + V_{fb} = V_E + f V_O = V_E (1 + a_V f)$$

loop gain

$$\text{Now, } i_x = \frac{V_E}{Z_{ia}} \rightarrow Z_i' = \frac{i_x}{V_E} = \frac{V_E(1 + \alpha_f)}{V_E/Z_{ia}}$$

- Open-loop opamp input impedance increased by  $(1 + \alpha_f)$  = loop gain when we use a series connection at the input. Thus, voltage input amp
- Find the closed-loop output impedance  $Z_o$ : (short input)

$$Z_o = \frac{V_x'}{i_x'} \quad V_\Sigma + V_{fb} = 0$$

$$V_\Sigma + fV_x' = 0 \quad V_\Sigma = -fV_x'$$


$$i_x' = \frac{V_x' - \alpha_f V_\Sigma}{Z_{oa}} = \frac{V_x' + \alpha_f V_x'}{Z_{oa}}$$

$$\therefore Z_o = \frac{V_x'}{i_x'} = \frac{Z_{oa}}{1 + \alpha_f}$$

closed-loop  
output impedance

- open-loop output impedance decreased by  $(1 + \alpha_f)$   
Thus, voltage output amplifier.

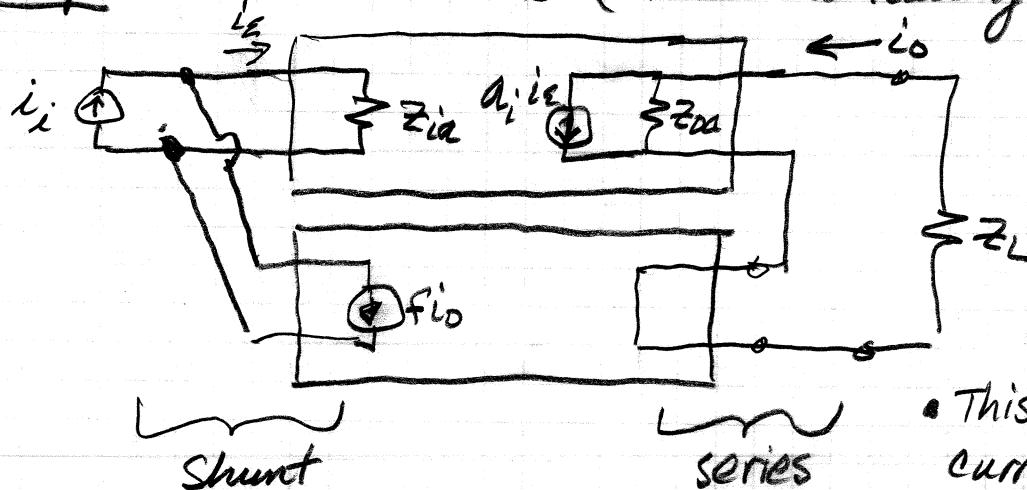Example: Shunt-Series FB (Assume no loading)



Transfer function:

$$i_o = a_i i_\Sigma = a_i (i_i - i_{fb}) = a_i (i_i + f_i i_o)$$


$$\therefore \frac{i_o}{i_i} = \frac{a_i}{1 + a_i f} \quad (\text{as expected})$$

Similarly,  $Z_i = \frac{Z_{ia}}{1 + a_{if}}$  and  $Z_o = Z_{oa}(1 + a_{if})$

- Same approach to analyze transconductance ( $V \rightarrow I$ ) and transresistance ( $I - V$ ) closed-loop amplifiers

- Now, consider the effects of loading impedances:

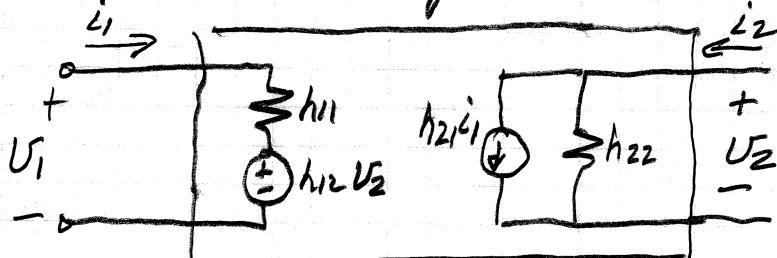- Take any nonidealities in the feedback network and move them into the forward amplifier: use h-parameter networks for  $a$  and  $f$ :



Defining equations:

$$U_i = h_{11} i_1 + h_{12} U_2$$

$$i_2 = h_{21} i_1 + h_{22} U_2$$

- For series-shunt closed-loop amp.


Elements:  $h_{11} = \frac{U_i}{i_1} \Big|_{U_2=0}$

$$h_{12} = \frac{U_i}{U_2} \Big|_{i_1=0}$$

$$h_{21} = \frac{i_2}{i_1} \Big|_{U_2=0}$$

$$h_{22} = \frac{i_2}{U_2} \Big|_{i_1=0}$$

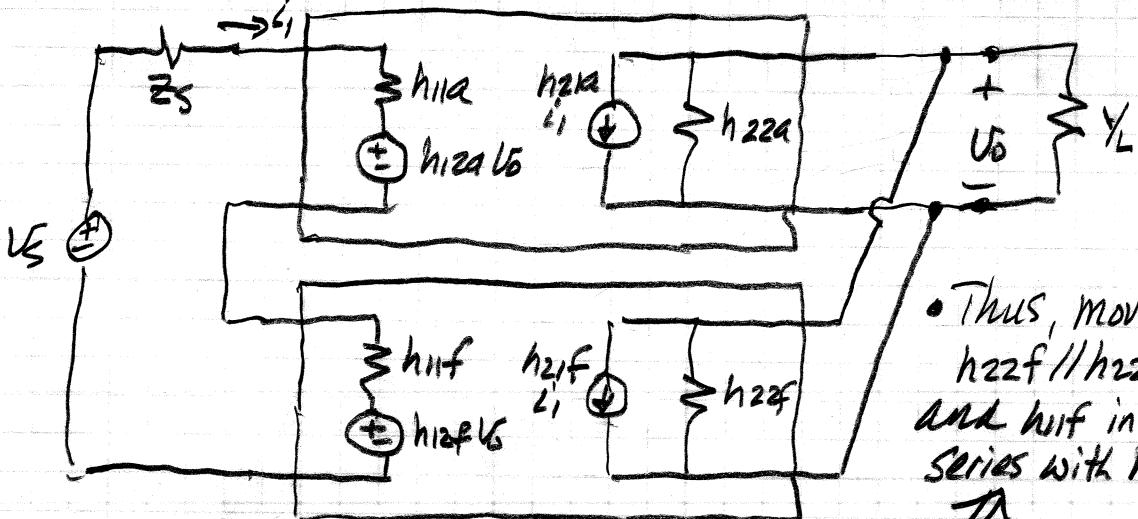- h-parameter representation of series-shunt FB circuit



- Thus, move  $h_{22f}/h_{22a}$  and  $h_{12f}$  in series with  $h_{11a}$

- In general, amplifiers and feedback networks uni-directional:

$$\therefore |h_{12a}| \ll |h_{12f}| \text{ and } |h_{21f}| \ll |h_{21a}|$$

(neglect  $h_{22a}$ ) (neglect  $h_{21f}$ )