
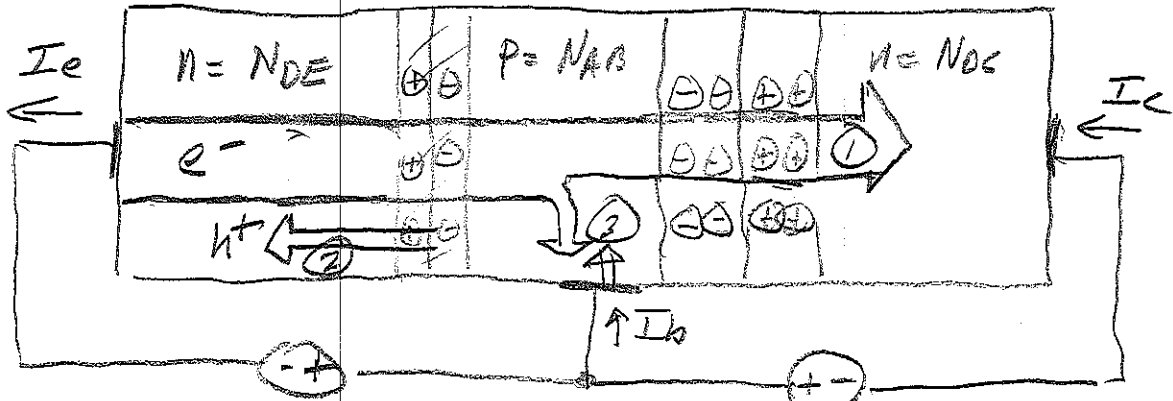


(2) F.A.R. 10^{15} 10^{16} 10^{14}

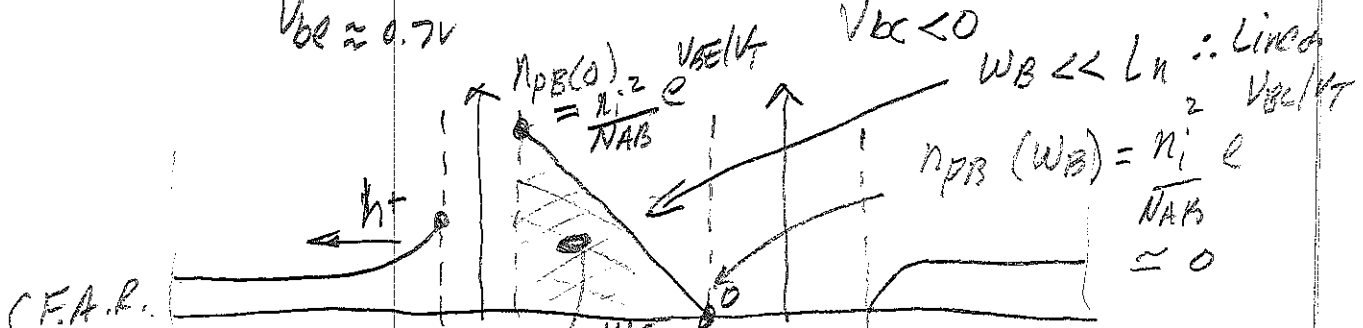

$V_{BE} \approx 0.7V$

$V_{BC} < 0$



F.A.R.
 $V_{BE} \approx 0.7V$
 V_{BC} negative

$Q_E \equiv$ minority carrier base charge


- (1) electrons injected from emitter - to base that reach collector
- (2) holes injected from base to emitter
- (3) Recombination of holes & electrons in base.

$\beta_F =$ forward current gain in F.A.R.

$$\beta_F = \frac{(1)}{(2) + (3)}$$

≈ 100 (typical value)

F.A.R. Large-signal models

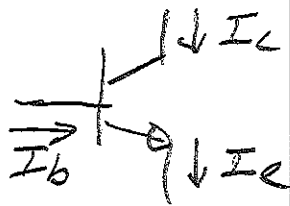

$$I_C = \beta_F I_B$$

$$I_E = I_C + I_B \quad (\text{KCL})$$



$$= (\beta_F + 1) I_B$$

$$= \left(I_C + \frac{I_C}{\beta_F} \right) = \left(\frac{\beta_F + 1}{\beta_F} \right) I_C$$



$$I_C = \frac{\beta_F}{\beta_F + 1} I_E = \alpha_F I_E$$

• β_F typically 100


Models: (F.A.R.)

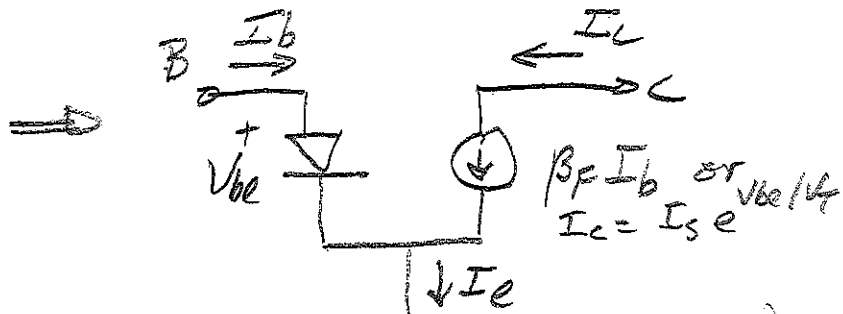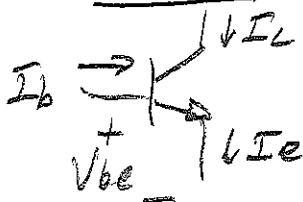

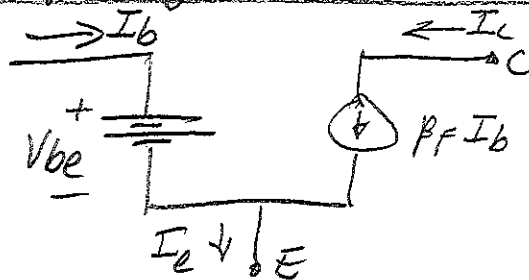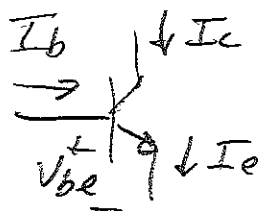
Often, we can simplify (e.g. for DC bias calcs):



Reason:

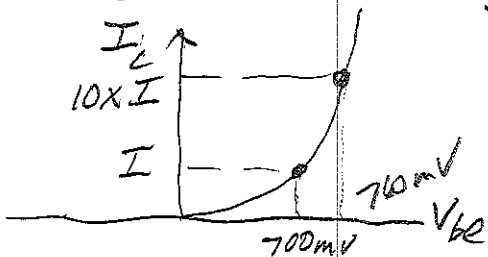

Pick a value: $V_{be} = 0.7V$

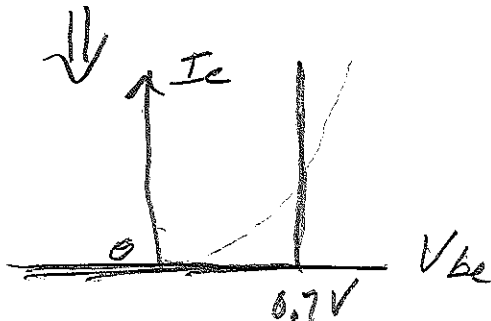




only 60 mV per decade of current

∴ 700 mV is good guess
SPICE for actual value

When determining dc operating point:

1. Assume F.A.R. (Check for cutoff - enough V_{be} ?)
 2. Determine V_{ce}
 3. If $V_{ce} > 0.2V$ ($V_{ce(sat)}$) \rightarrow OK it's F.A.R.
- Otherwise, Assume Saturation and start over.


IV Characteristics

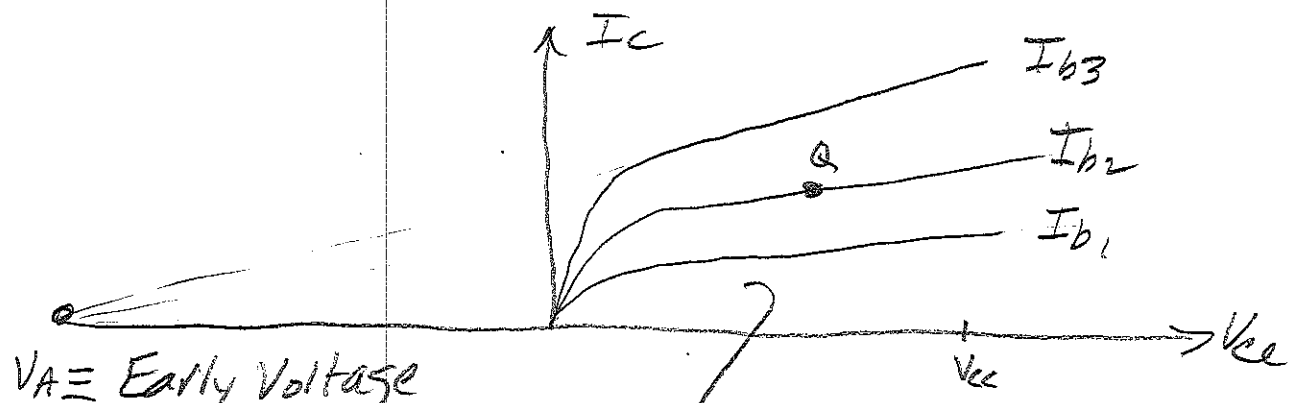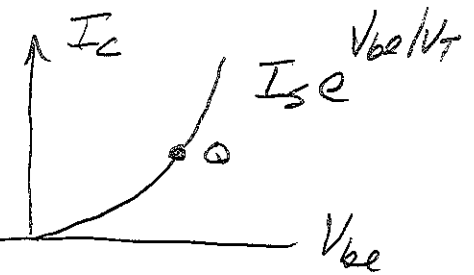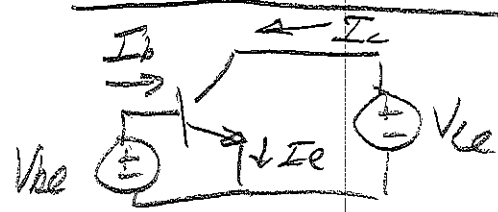

$V_A \equiv$ Early Voltage
(e.g., 60 volts)



$$I_C = I_{S e}^{V_{be}/V_T} \left(1 + \frac{V_{ce}}{V_A} \right)$$

Nomenclature:

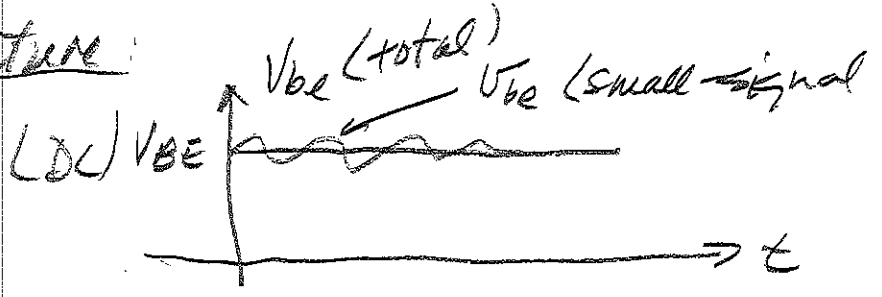

Early Effect:


Jim Early

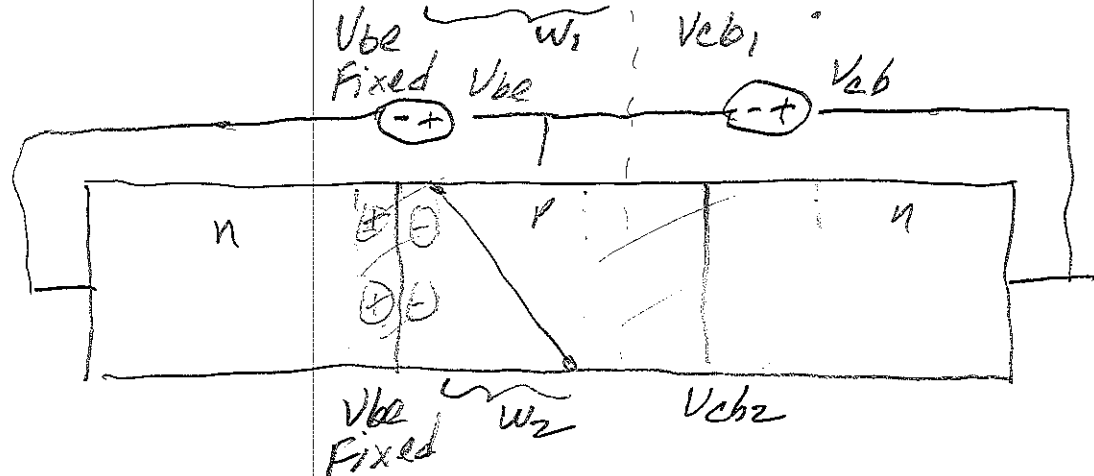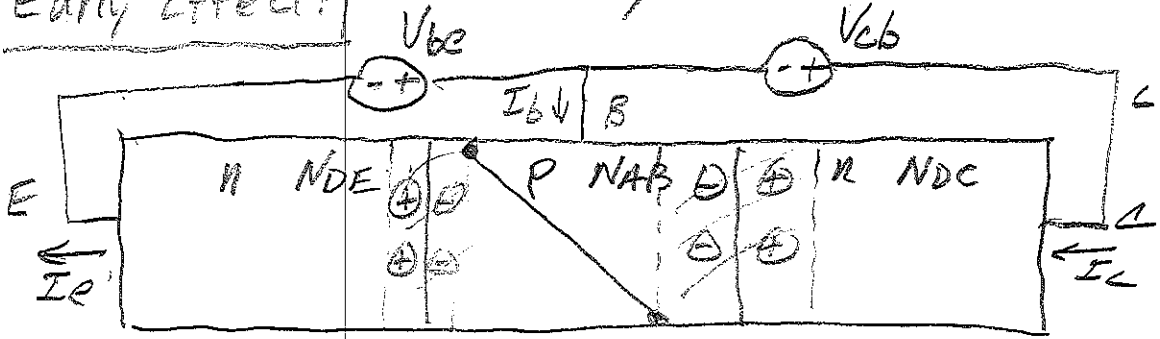

• I_c is due to diffusion current across base:

$$I_c = q A D_n \frac{\partial n_{PB}(x)}{\partial x} \approx \frac{n_i^2}{N_{AB}} e^{V_{be}/V_T}$$

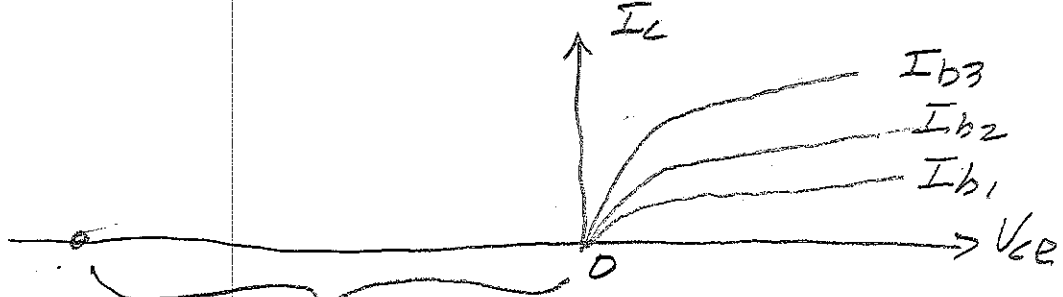For $V_{bc2} > V_{bc1}$, $W_2 < W_1$ ∴ $I_{c2} > I_{c1}$
Model of Early effect:



$V_A =$ Early voltage (typically, 50-100V)


$$I_c = I_s (e^{V_{be}/V_T} - 1) \left(1 + \frac{V_{ce}}{V_A} \right)$$

$$\approx I_s e^{V_{be}/V_T} \left(1 + \frac{V_{ce}}{V_A} \right) \text{ in F.A.K.}$$

"ARPAID"

Example of DC Bias Calculations:

Back to page 10 first -

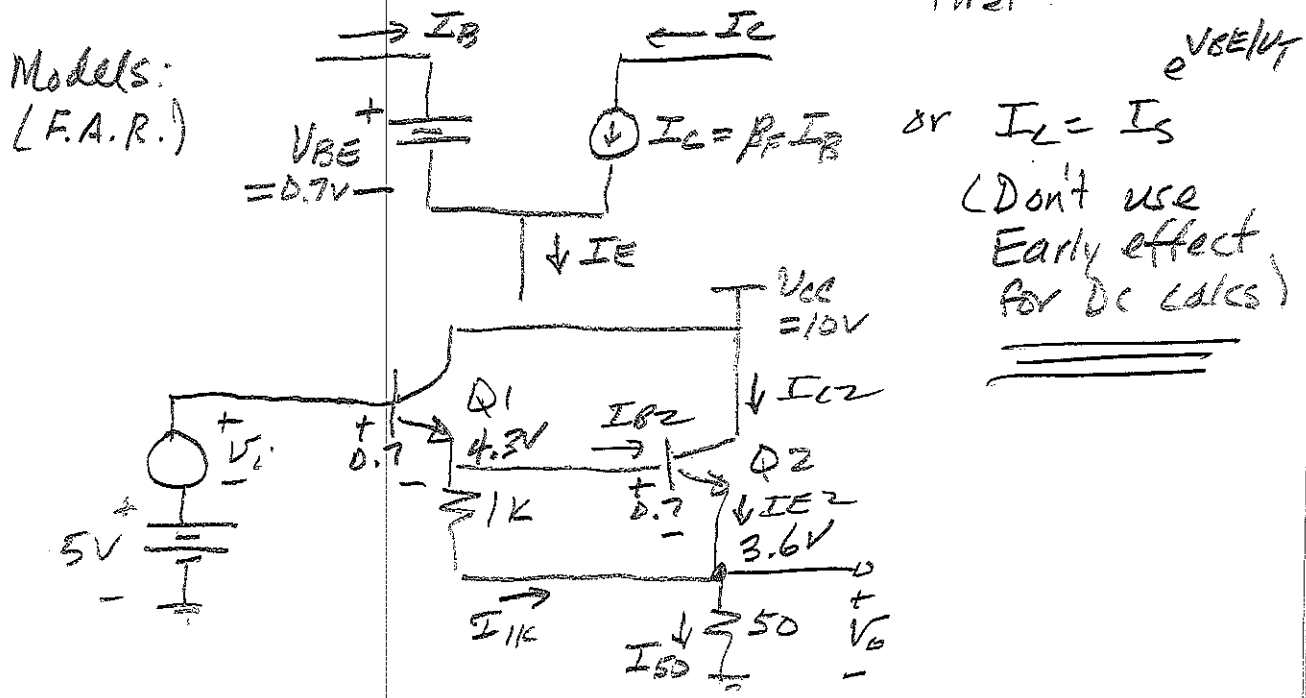

- Assume F.A.R.: $V_{BE} = 0.7V$; $V_{CE} > 0.2V$
 $\beta_F = 100$ Avoid saturation

• Look for V_{BE} 's to find voltages

• Calculate currents: $I_{50} = \frac{3.6V}{50} = 720\mu A$
 $I_{1k} = \frac{4.3 - 3.6}{1k} = 0.7\mu A$

KCL: $I_{E2} + I_{1k} = I_{50} \Rightarrow I_{E2} = (720 - 0.7)\mu A = 719.3\mu A$

$I_{C2} = \frac{\beta_F}{\beta_F + 1} I_{E2} = \frac{100}{101} (719.3\mu A) = 712.2\mu A$

$I_{B2} = \frac{I_{C2}}{\beta_F} = \frac{712.2\mu A}{100} = 7.12\mu A$

KCL: $I_{E1} = I_{1k} + I_{B2} = 0.7\mu A + 7.12\mu A = 7.82\mu A$

$I_{C1} = \frac{\beta_F}{\beta_F + 1} I_{E1} = \frac{100}{101} (7.82\mu A) = 7.74\mu A$



$I_{B1} = I_{C1} / \beta_F = 7.74\mu A / 100 = 77.4\mu A$

Check: $V_{CE1} = V_{CC} - 4.3V = 5.7V$; $V_{CE2} = 10 - 3.6 = 6.4V$
 OK. $> 0.2V$ $> 0.2V$

SAMSUNG

Low-Frequency small-signal model:

Bias Point:

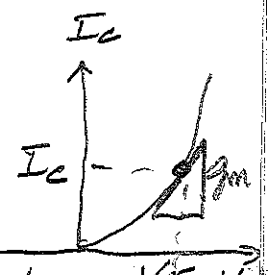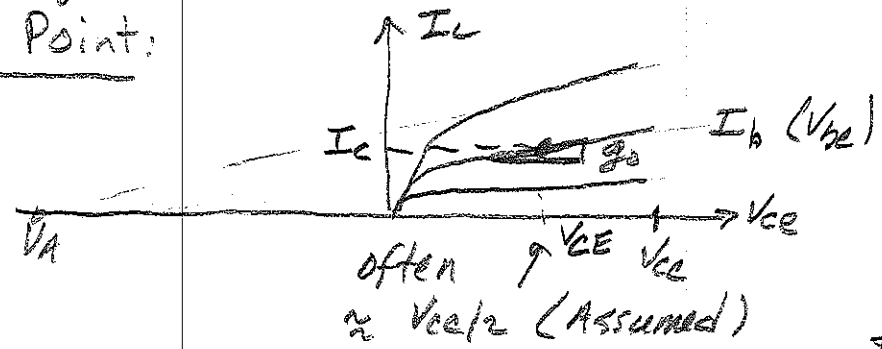

Small-signal parameters:

$$g_m = \left. \frac{\partial I_C}{\partial V_{BE}} \right|_{Q \text{ point}} = \frac{\partial}{\partial V_{BE}} \left[I_S e^{V_{BE}/V_T} \right] \quad (\text{neglect Early effect})$$

$$= \frac{I_S}{V_T} e^{V_{BE}/V_T} = \frac{I_C}{V_T} \quad \leftarrow g_m$$


$$g_{\pi} = \left. \frac{\partial I_B}{\partial V_{BE}} \right|_Q = \frac{1}{\beta_F} \left. \frac{\partial I_C}{\partial V_{BE}} \right|_Q = \frac{g_m}{\beta_F} \quad \leftarrow g_{\pi}$$

$$r_{\pi} = \frac{1}{g_{\pi}} = \frac{\beta_F}{g_m} \quad \leftarrow r_{\pi}$$

$$g_o = \left. \frac{\partial I_C}{\partial V_{CE}} \right|_Q = \frac{\partial}{\partial V_{CE}} \left[I_S e^{V_{BE}/V_T} \left(1 + \frac{V_{CE}}{V_A} \right) \right] \quad \leftarrow g_o$$


$$= \frac{I_S}{V_A} e^{V_{BE}/V_T} = \frac{I_C}{V_A + V_{CE}} \approx \frac{I_C}{V_A}$$
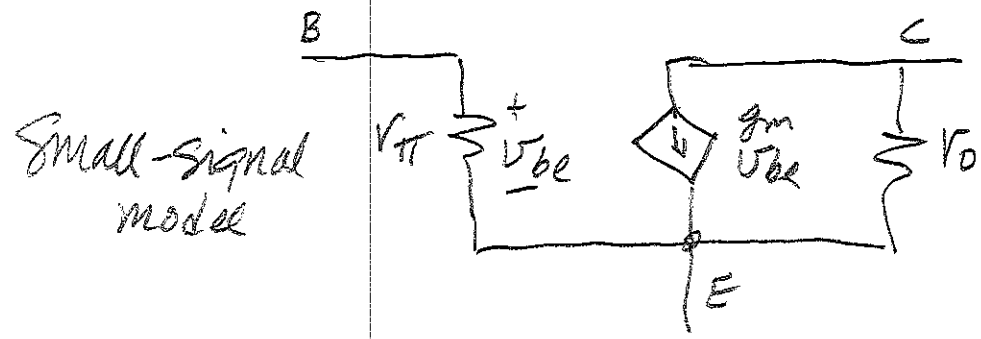
$$r_o = \frac{1}{g_o} = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} \quad \leftarrow r_o$$



Capacitances:

Recall: $C = \frac{dQ}{dV}$ (Gerald)

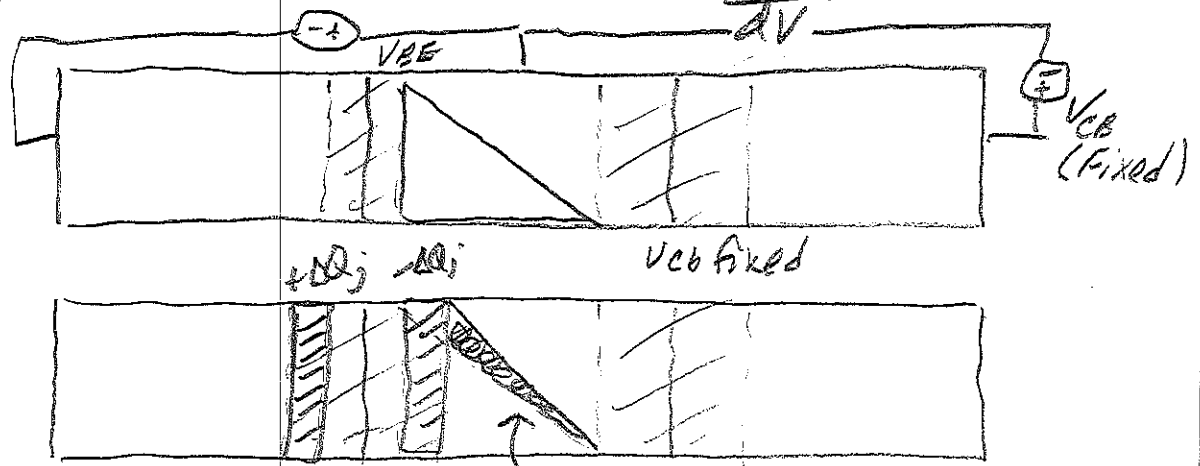


Changes in depletion region capacitance C_{je}

Change in stored minority carrier base charge

$C_B = \tau_F g_m$

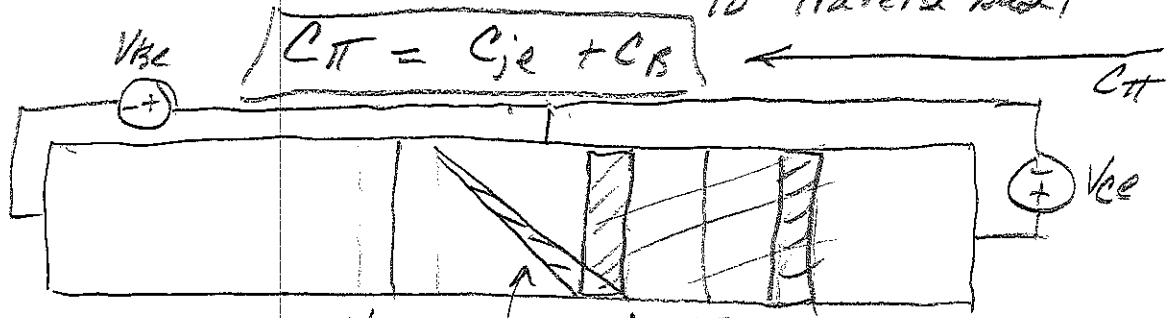τ_F = Base transit time (Average time for electron to traverse base)




$C_T = C_{je} + C_B$

V_{be} fixed ΔQ



Change in depletion capacitance is negligible because large C negative V_{cb}

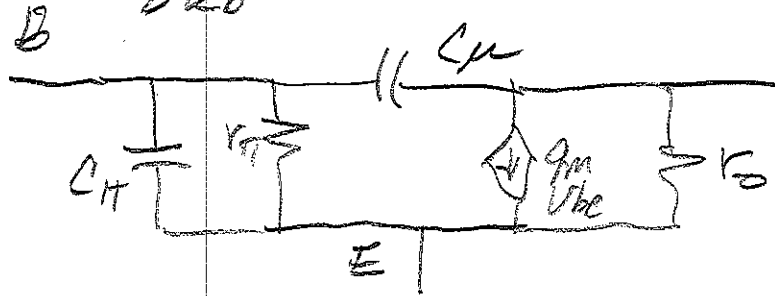$\frac{\partial Q_B}{\partial V_{cb}} = C_{\mu}$




MOSFETS:

Structure:

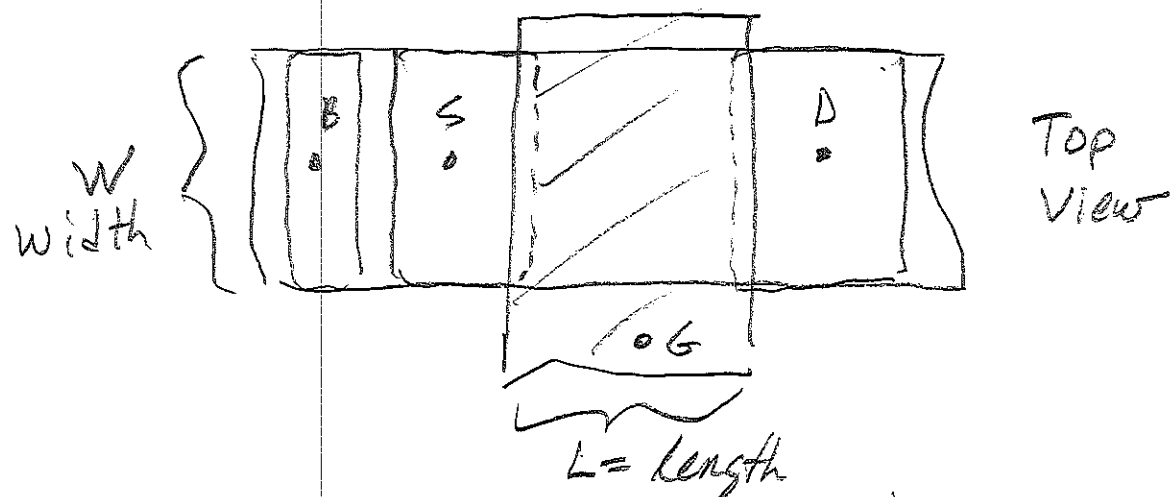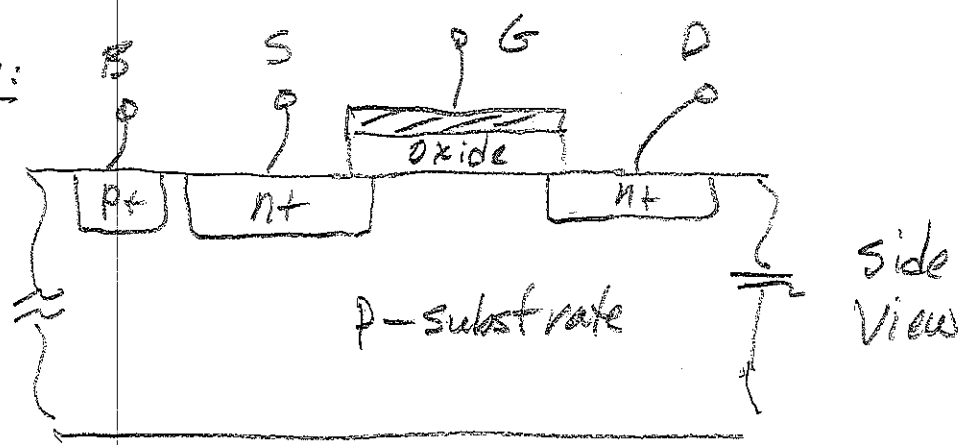

- Unlike BJT, Designer controls both W and L so long as they meet or exceed minimum dimensions



Symbol:

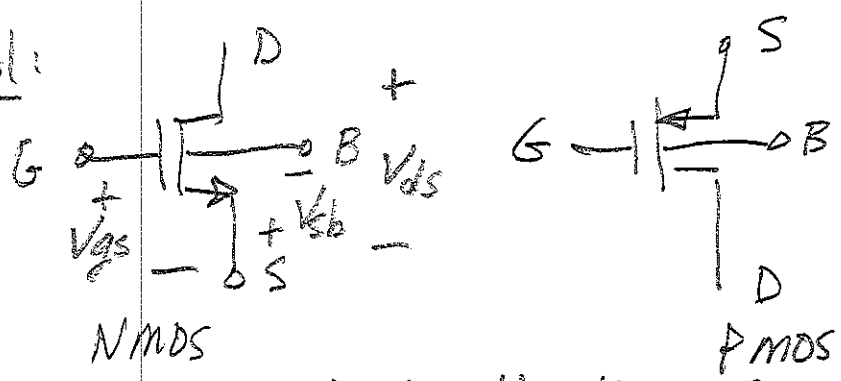

- Arrow on source indicates direction of conventional current flow


Regions of Operation:

(A) Cutoff

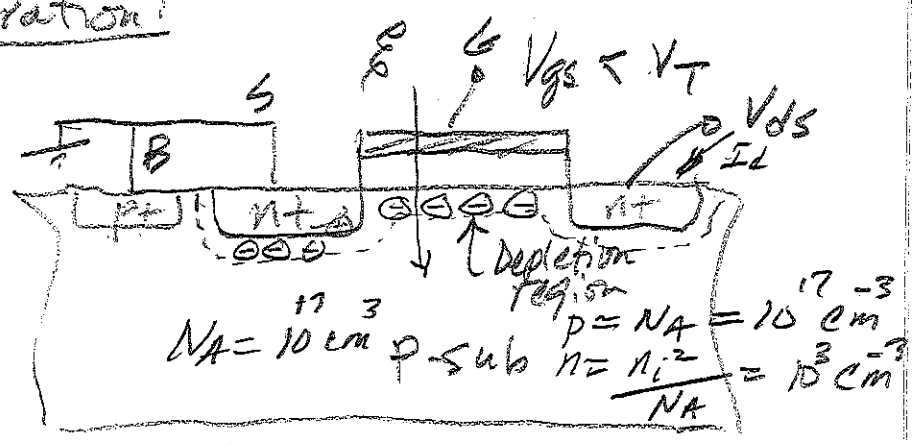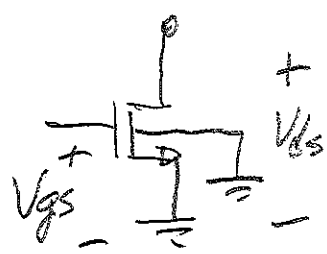

no layer of mobile electrons to connect drain to source. $\therefore I_d = 0$


(B) At threshold $V_{gs} = V_t$

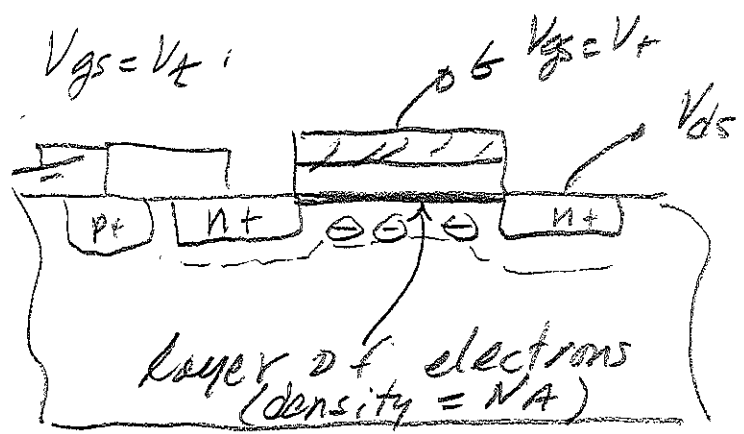

At edge of conduction (square-law model) but still $I_d = 0$

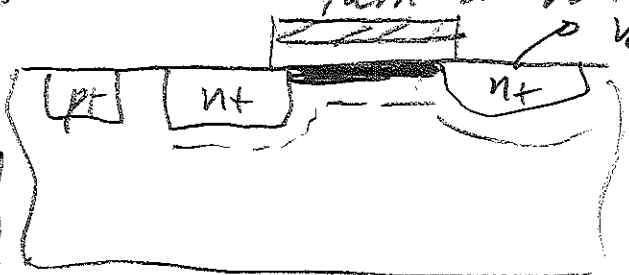(C) ON with $V_{gs} > V_t$ but $(V_{gs} - V_t) \ll V_{ds}$ (small V_{ds})
 For $V_{gs} > V_t$ and $V_{ds} < (V_{gs} - V_t)$
 Excess voltage or turn-on voltage

$I_d = \mu_n C_{ox} \left(\frac{W}{L}\right) \left[(V_{gs} - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right]$






μ_n = electron mobility in channel
 C_{ox} = gate oxide capacitance per unit area
 $K_n' = \mu_n C_{ox}$

* * *

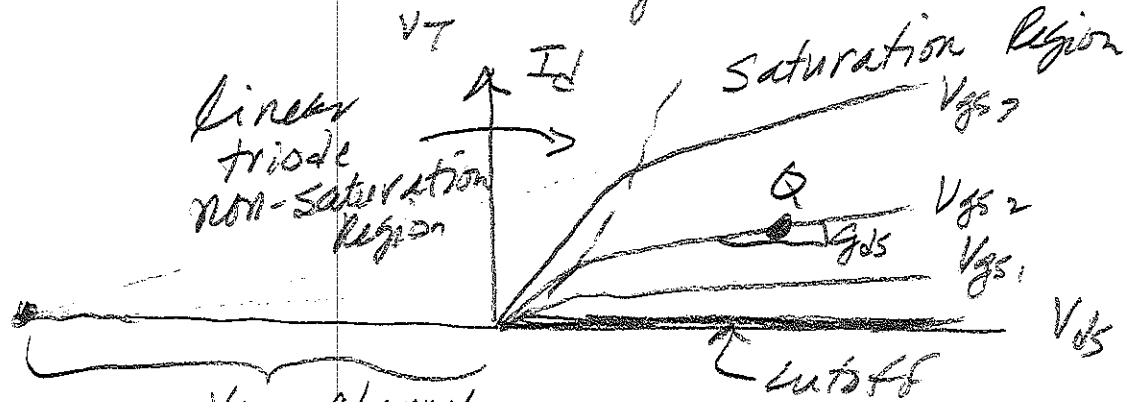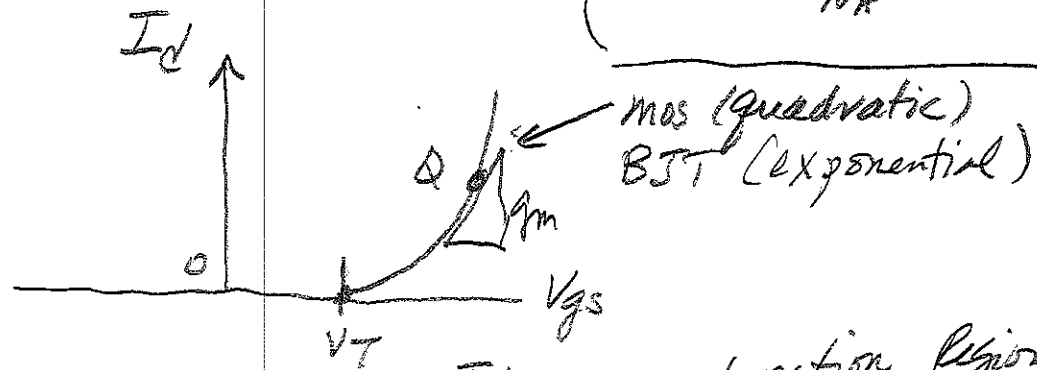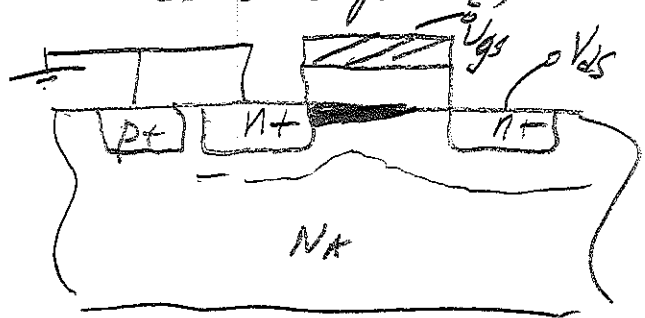(D) ON with $V_{gs} > V_t$ and $V_{ds} \geq (V_{gs} - V_t)$

$$I_d = \frac{K'}{2} \left(\frac{W}{L}\right) (V_{gs} - V_t)^2$$



$V_A =$ channel-length modulation
(aka Early Voltage)

Non-Sat. $I_d = K' \left(\frac{W}{L}\right) \left[(V_{gs} - V_t) V_{ds} - \frac{1}{2} V_{ds}^2 \right] \left\{ \begin{array}{l} V_{gs} > V_t \\ V_{ds} < (V_{gs} - V_t) \end{array} \right.$

Sat $I_d = \frac{K'}{2} \left(\frac{W}{L}\right) [(V_{gs} - V_t)^2] \left[1 + \frac{V_{ds}}{V_A} \right]$

$$V_T = V_{T0} + \delta \left[\sqrt{V_{sb} + 2\phi_f} - \sqrt{2\phi_f} \right]$$

$\delta \equiv$ Body-effect parameter

$$\phi_f = \frac{kT}{q} \ln \frac{N_A}{n_i}$$

Small-signal parameters (low frequency):
In saturation:

$$g_m = \frac{\partial I_D}{\partial V_{GS}} \bigg|_Q = \frac{\partial}{\partial V_{GS}} \left[\frac{K'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 \right]$$

neglect channel-length modulation

$$g_m = K' \left(\frac{W}{L}\right) (V_{GS} - V_T)$$

g_m - Form 1

But, $I_D = \frac{K'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$

SO $g_m = \frac{2 I_D}{(V_{GS} - V_T)^2} \cdot (V_{GS} - V_T) = \frac{2 I_D}{(V_{GS} - V_T)}$ g_m Form 2 (Similar to BJT)

OR $g_m = K' \left(\frac{W}{L}\right) \sqrt{\frac{2 I_D}{K' \left(\frac{W}{L}\right)}} = \sqrt{2 K' \left(\frac{W}{L}\right) I_D}$ g_m Form 3

• All three forms are useful. Form 3 will be used most often

$$g_{ds} = \frac{\partial I_D}{\partial V_{DS}} \bigg|_Q = \frac{\partial}{\partial V_{DS}} \left[K' \left(\frac{W}{L}\right) (V_{GS} - V_T)^2 (1 + \lambda V_{DS}) \right]$$
$$= \lambda K' \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$
$$= \frac{\lambda I_D}{1 + \lambda V_{DS}} \approx \lambda I_D$$
 g_{ds}

$$r_{ds} = \frac{1}{g_{ds}} \approx \frac{1}{\lambda I_D}$$

