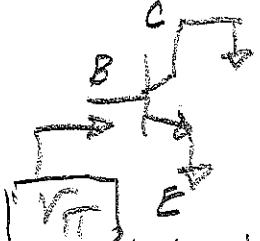


Today:

- Inspection analysis of basic stages
- CMOS gain stage analysis

Terminal resistances: (simple single transistor)



"looking into base"



"looking into collector"





$$\frac{1}{g_{mI} + g_{TII} + g_{OII}} \approx \frac{1}{g_{mI}}$$

"looking into emitter"



Now, let's extend by adding series resistances

→ (A) R_B

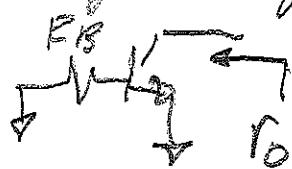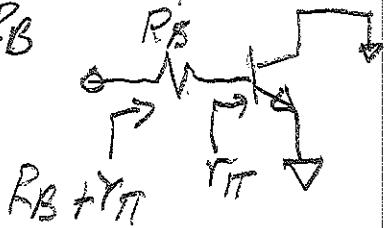

• Looking into emitter is slightly more complicated.

Form an equivalence:

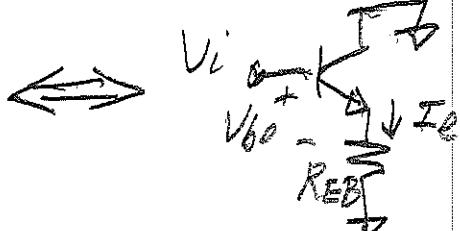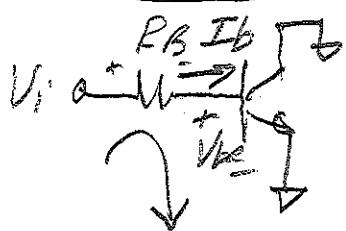

$$KCL: V_i = V_{be} + I_b R_B \quad KCL: V_i = V_{be} + I_e R_{EB}$$

$$= V_{be} + (P_F + 1) I_b R_{EB}$$

Equating \Rightarrow

$$R_{EB} = \frac{R_B}{P_F + 1}$$



∴ To move a resistance from in series with base to in series with emitter, divide its value by $(P_F + 1)$.

Likewise, from Emitter to base, multiply by $(P_F + 1)$.




Thus,

$$\Rightarrow \frac{1}{g_m + g_T + g_0} \approx \frac{1}{g_m}$$


$$\Rightarrow R_B / (B_F + 1)$$

$$\frac{1}{g_m + g_T + g_0} + \frac{R_B}{B_F + 1} \approx \frac{1}{g_m} + \frac{R_B}{B_F + 1}$$

\Rightarrow (B) R_C

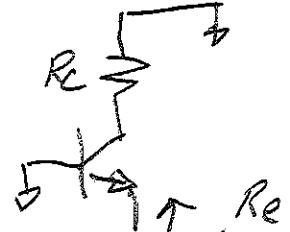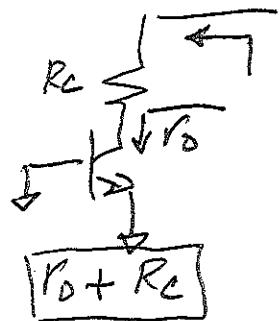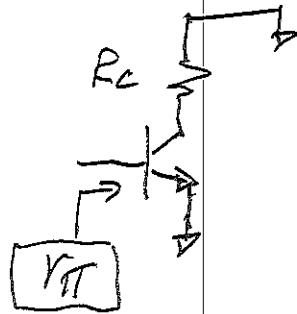

Somewhat complicated

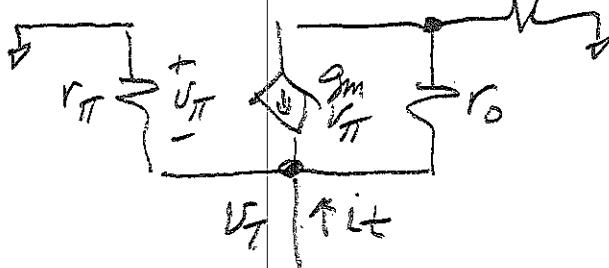

Write two KCL equations and solve:


$$R_e = \frac{g_0 + g_c}{g_c(g_m + g_\pi + g_0) + g_0 g_\pi} \approx \frac{1 + g_0/g_c}{g_m + \frac{g_0 g_\pi}{g_c}}$$

two cases: (i) R_C large $\approx r_o$ (i.e., $g_0 \approx g_c$)


$$\therefore R_e \approx \frac{2}{g_m}$$

or (ii) R_C small $\ll r_o$ (discrete implementation)
($g_c \gg g_0$)

$$\therefore R_e \approx \frac{1}{g_m}$$

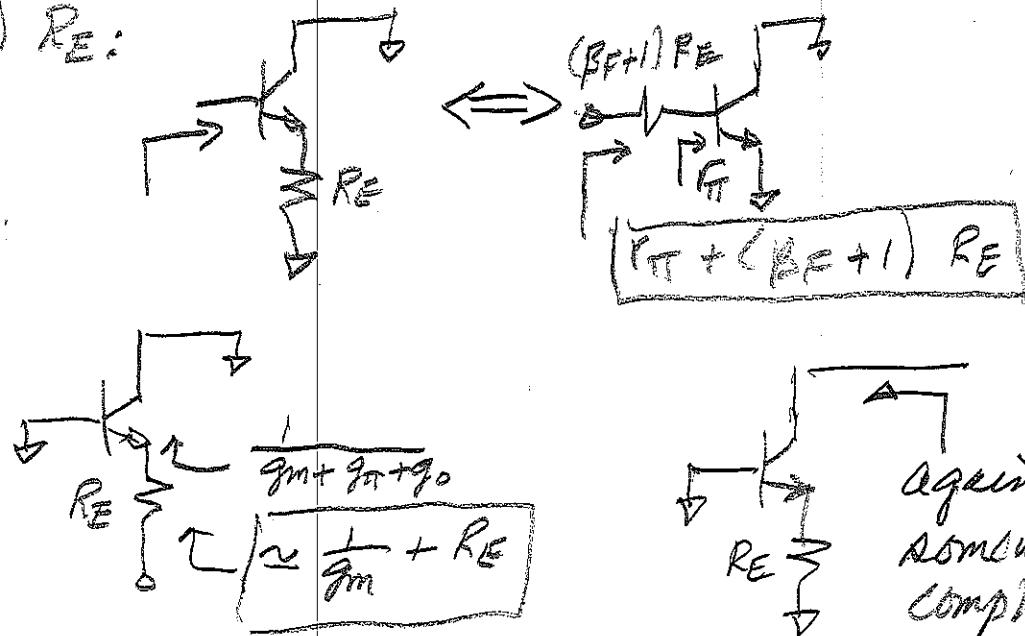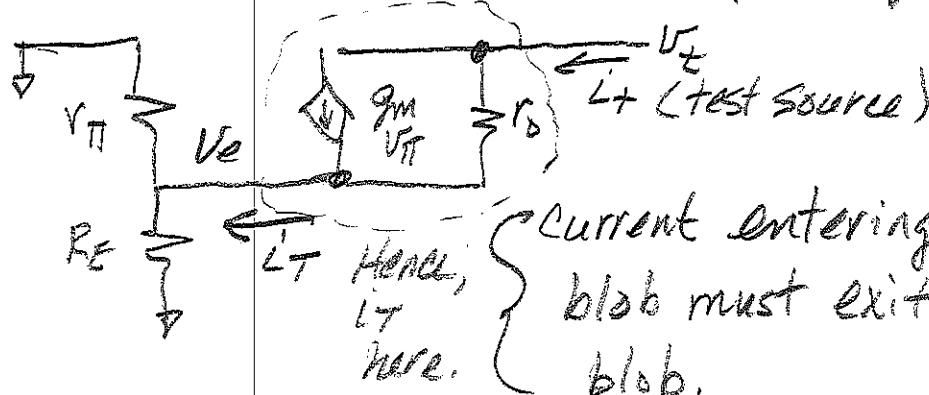(c) R_E :

Draw small-signal model (funny looking way):




$$\therefore \text{by inspection, } V_E = \frac{i_T}{(g_\pi + g_E)}$$

Now, KCL at collector:

$$\begin{aligned} i_T &= g_m V_\pi + g_o (V_t - V_E) \\ &= g_m (0 - V_E) + g_o (V_t - V_E) \\ &= -(g_m + g_o) V_E + g_o V_t \\ &= -(g_m + g_o) \frac{V_E}{g_\pi + g_E} + g_o V_t \end{aligned}$$

$$\begin{aligned} \therefore R_c &= \frac{V_E}{i_T} = \left(\frac{g_m + g_\pi + g_o + g_c}{g_\pi + g_E} \right) r_o = \left(\frac{g_m + g_E}{g_\pi + g_E} \right) r_o \\ &= \frac{(1 + g_m/g_E) r_o}{(1 + g_\pi/g_E)} = \frac{(1 + g_m R_E) r_o}{1 + g_m R_E/B_F} \approx \boxed{g_m R_E r_o} \end{aligned}$$

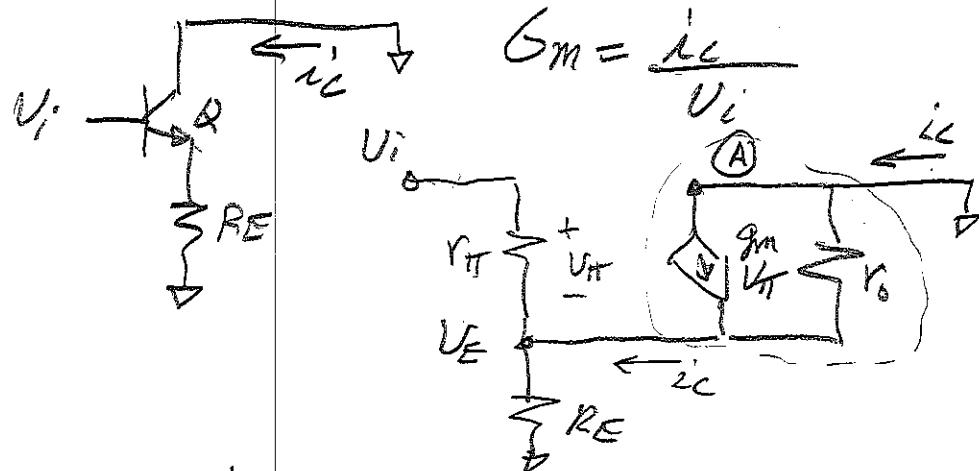- Small-signal transconductance with emitter degeneration, $G_m \neq g_m$:



$$V_E = \frac{i_c}{g_m + g_o} \quad (\text{By inspection})$$


Now, KCL at A:

$$\begin{aligned} i_c &= g_m V_{\pi} + g_o (0 - V_E) \\ &= g_m (V_i - V_E) + g_o (0 - V_E) \\ &= g_m V_i - V_E (g_m + g_o) \\ &= g_m V_i - \frac{(g_m + g_o)}{(g_m + g_o + g_E)} i_c \end{aligned}$$

$$\therefore G_m = \boxed{\frac{g_m}{1 + g_m R_E}}$$


Usually, $g_m R_E \gg 1 \Rightarrow \boxed{G_m \approx \frac{1}{R_E}}$

How do we see this by inspection.

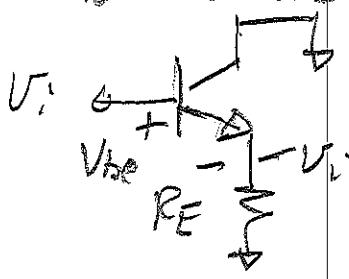

If we assume V_{BE} is constant at $V_{BE} = 0.7V$, then signal V_i appears across R_E
 $\therefore i_E = \frac{V_i}{R_E} \approx i_c \therefore G_m = \frac{1}{R_E}$

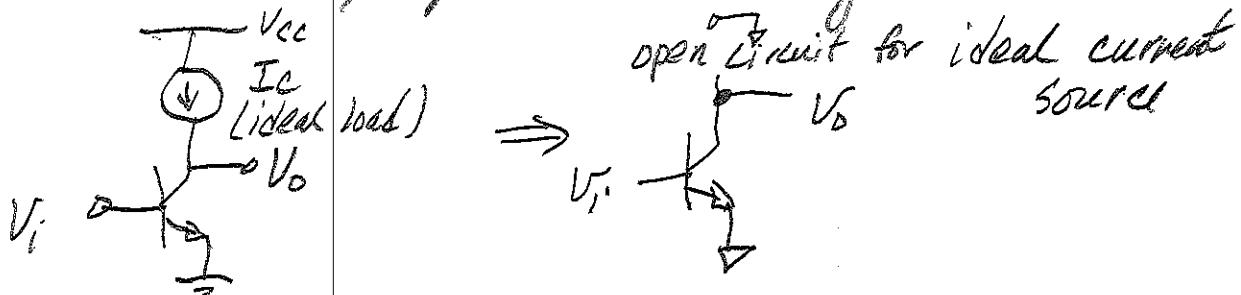
- An important voltage gain limitation = "open-circuit voltage gain" or "self gain"



Quick S.S. analysis: $A_v = \frac{V_o}{V_i} = -\left(\frac{g_m r_o}{1 + g_m r_o}\right)$

$$= -\frac{I_C}{V_T} \cdot \frac{V_A}{I_C} = -\frac{V_A}{V_T}$$

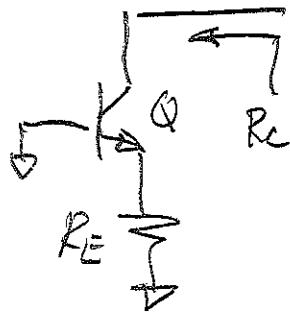- This is extraordinarily useful in inspection analysis:





Recall from previous analysis:

$$R_E \approx g_m R_E r_o \quad \text{(Bottom page 28)}$$

Rearrange: $R_E = (g_m r_o) R_E$

Series resistance is multiplied by self-gain of Q

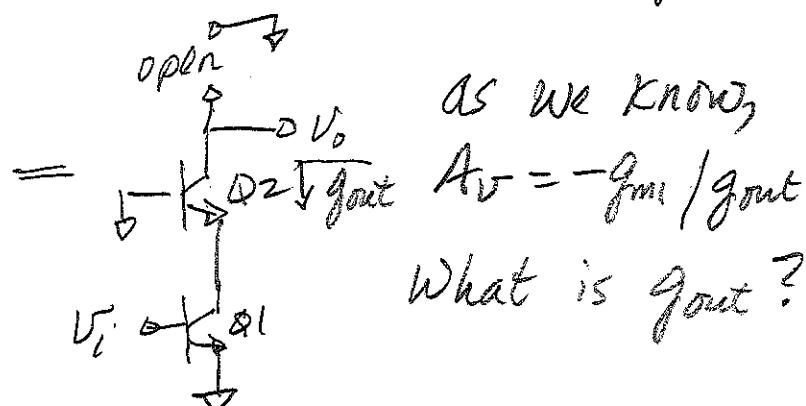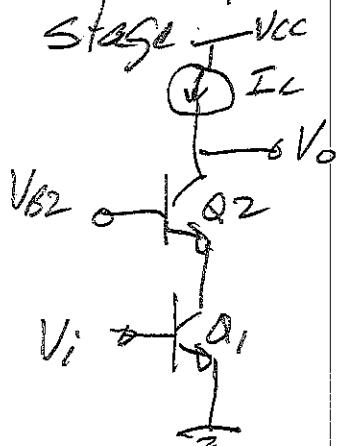
This is powerful. Consider a cascode gain stage:




As we know,

$$A_v = -g_m / g_{out}$$

What is g_{out} ?

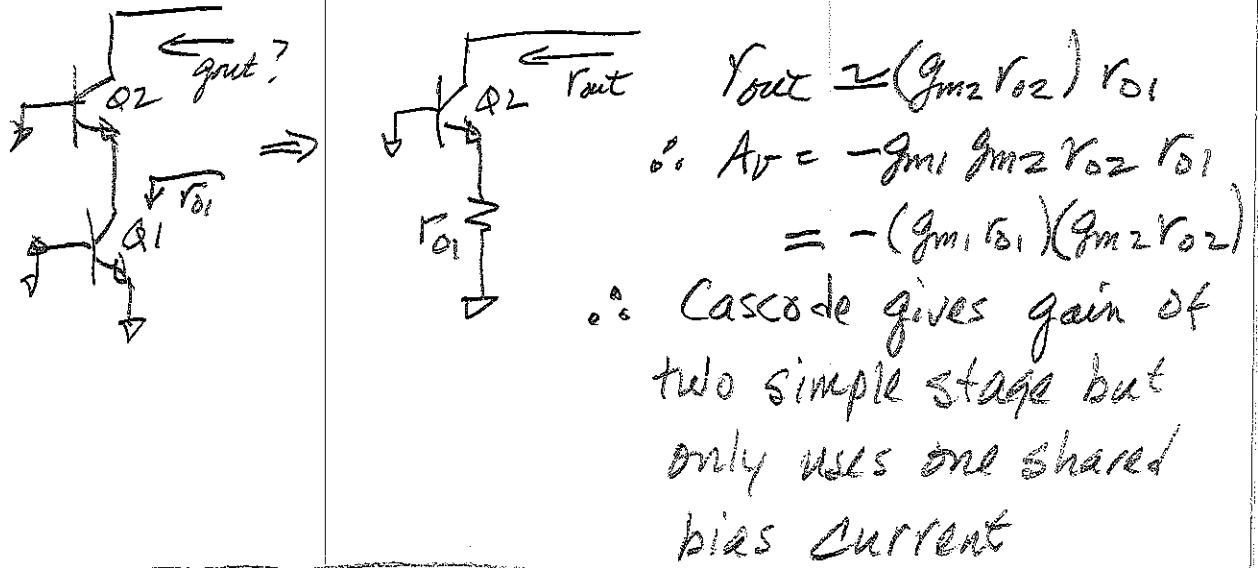

MOSFET Small-Signal models:

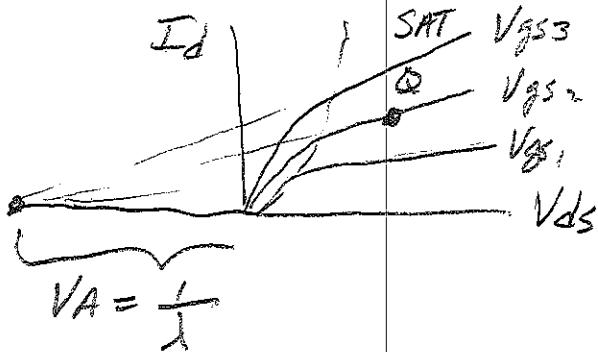

Saturation:

$$V_{gs} > V_T \text{ and } V_{ds} > (V_{gs} - V_T)$$

threshold
Voltage not
thermal voltage

$$I_d = \frac{k_n'}{2} \left(\frac{W}{L} \right) (V_{gs} - V_T)^2 (1 + \lambda V_{ds})$$

$$g_{ds} = \frac{\partial I_d}{\partial V_{ds}} \Big|_Q = \frac{\lambda I_d}{1 + \lambda V_{ds}} \approx \boxed{\lambda I_d} \quad \#1$$

Otherwise, including for DC calculations,
neglect channel-length modulation term:

$$I_d = \frac{k_n'}{2} \left(\frac{W}{L} \right) (V_{gs} - V_T)^2$$


$$g_m = \frac{\partial I_d}{\partial V_{gs}} \Big|_Q = \boxed{k_n' \left(\frac{W}{L} \right) (V_{gs} - V_T)} \quad \#1$$

$$= \boxed{\frac{2 I_d}{(V_{gs} - V_T)}} \quad \#2 \text{ (most likeBJT)}$$

$$= \sqrt{2 k_n' \left(\frac{W}{L} \right) I_d} \quad \#3$$

$$g_{mb} = \frac{\partial I_d}{\partial V_{bs}} \Big|_Q = \text{Back-gate transconductance}$$
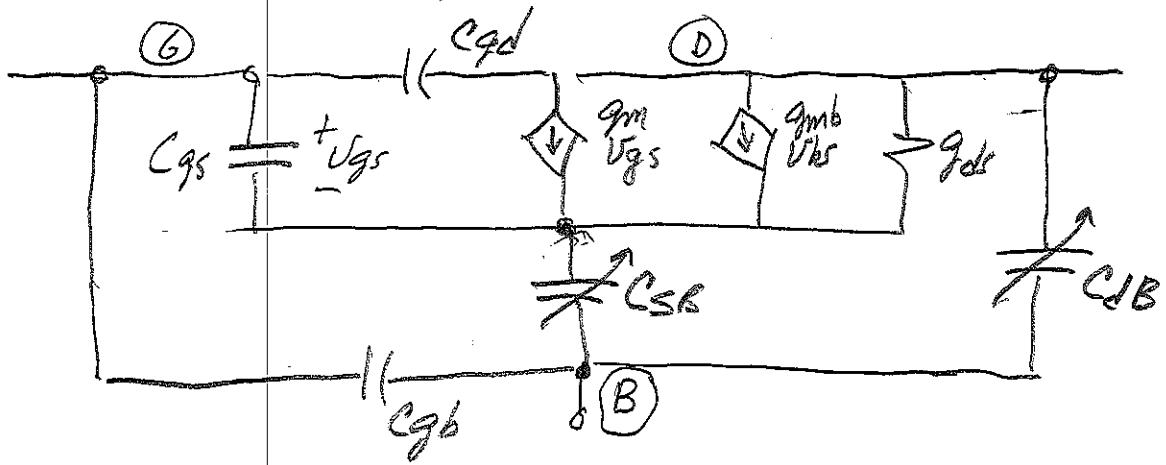
$$= \frac{\gamma}{2 + \sqrt{V_{sb} + 2\phi_f}} \cdot g_m$$



Complete MOSFET Small-signal model: