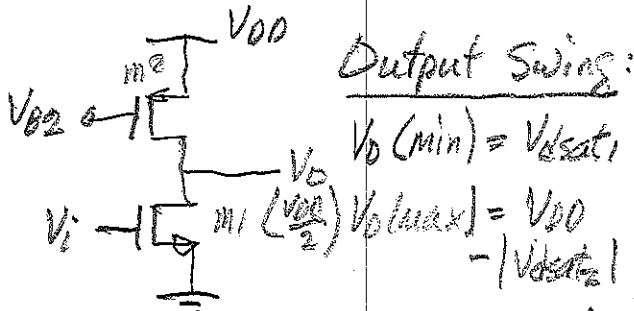


Multi-stage Amplifiers with Active Loads:

(A) PMOS Current Source  
load for NMOS CS Amp:

(B) NMOS Current Source  
load for PMOS CS Amp:




Output Swing:

$V_0(\min) = V_{dsat1}$

$V_0(\max) = V_{DD} - |V_{dsat2}|$

• DC level shift in pos. direction

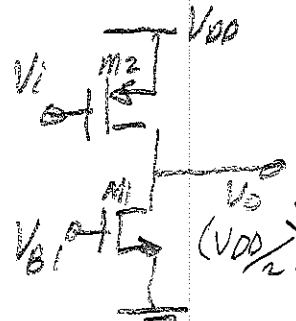$A_v = \frac{-g_{m1}}{g_{ds1} + g_{ds2}}$



Output Swing:


Same as (A)

• But, DC level shift in


neg. direction

$A_v = \frac{-g_{m2}}{g_{ds1} + g_{ds2}}$

A quick review on current sources:

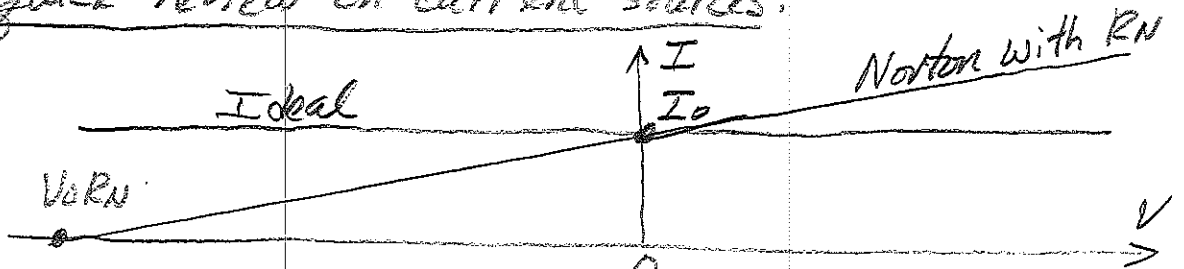

i) Ideal current source:

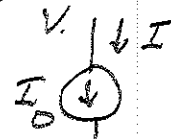



ii) Norton current source:



$I = I_0 + \frac{V}{R_N}$



$I=0 \Rightarrow V = -I_0 R_N =$  Thevenin voltage is very similar to Early voltage, etc.

Models: (A) NMOS

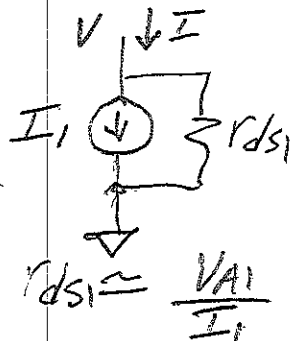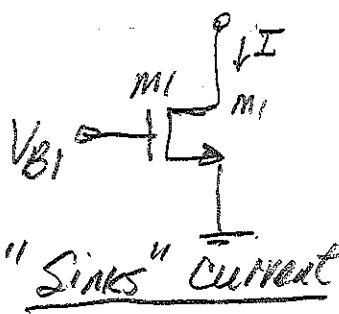

$r_{ds1} \approx \frac{V_{A1}}{I_1}$

(B) PMOS

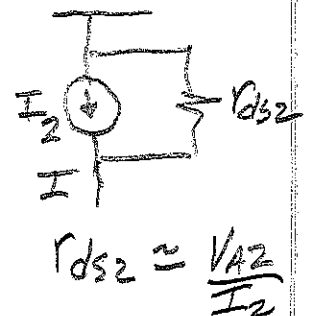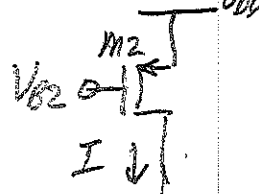


$r_{ds2} \approx \frac{V_{A2}}{I_2}$

"Sinks" current

"Sources" current


Multi-stage Amp with Active loads:

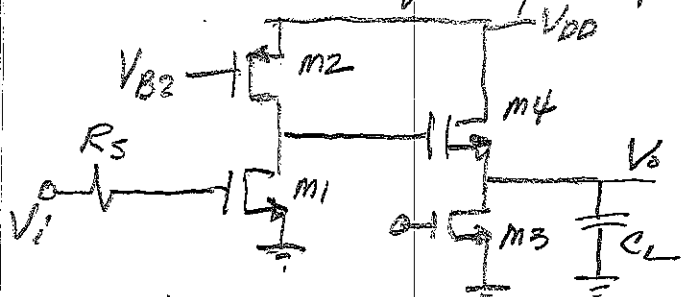Find: i) Input resistance; ii) output resistance; iii) frequency response (i.e., dominant pole freq.)




CS stage with PMOS active load

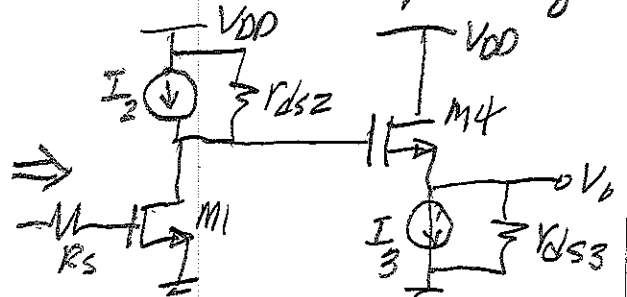CD stage (i.e., source follower) with NMOS active load



(Replace current sources with Norton sources with Norton

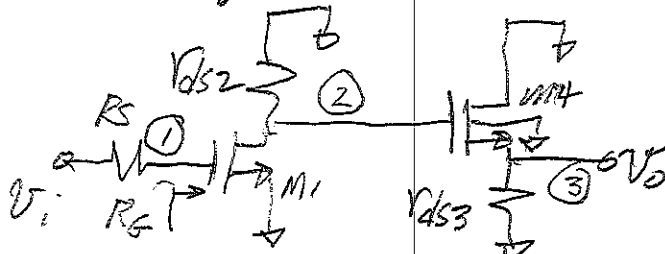AC equivalent circuit; (low freqs) <sup>equivalents</sup> m1 biased at I2; m4 biased at I3.



total voltage gain:


$$A_v = \frac{V_0}{V_i} = \frac{V_0}{V_1} \cdot \frac{V_2}{V_1} \cdot \frac{V_0}{V_2}$$

$$V_1 = \frac{R_g}{R_g + R_s} V_i ; V_2 = \frac{-g_{m1} V_1}{g_{ds1} + g_{ds2}} ; V_0 = \frac{g_{m4}}{g_{m4} + g_{mb4} + g_{ds4} + g_{ds3}}$$

$$\therefore A_v = 1 \cdot \frac{-g_{m1}}{g_{ds1} + g_{ds2}} \cdot \frac{g_{m4}}{g_{m4} + g_{mb4} + g_{ds4} + g_{ds3}}$$

$$A_v \approx - \frac{g_{m1}}{g_{ds1} + g_{ds2}} \cdot \frac{1}{1 + \eta} \quad (\text{neglect } g_{ds4} + g_{ds3} \text{ terms})$$

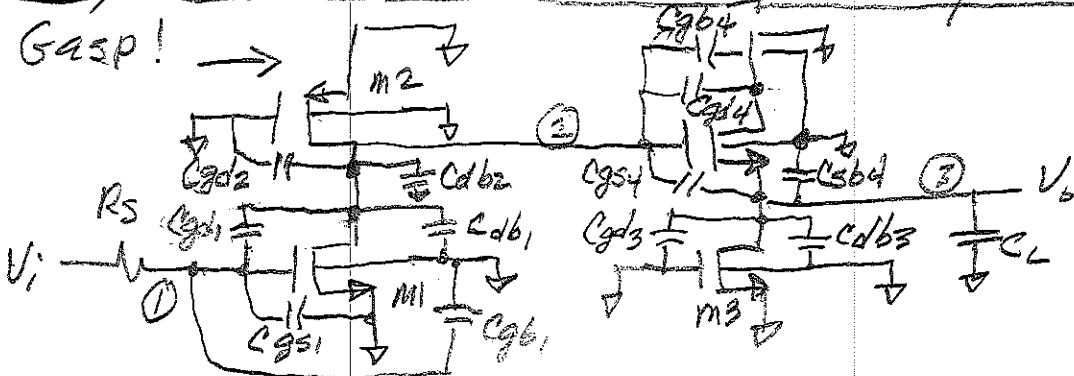Now, let's find the dominant pole frequency:



Gasp!

Now, before we apply ZVTC method to find dominant pole frequency, let's get the capacitance to ground at nodes ①, ② and ③: (Use Miller Effect as needed)

node ①:  $C_① = C_{gs1} + C_{gb1} + C_{m1}$  (Miller multiplied  $C_{gd1}$ )

$$C_{m1} = C_{gd1} (1 - A_{v0}) = C_{gd1} \left( 1 + \frac{g_{m1}}{g_{ds1} + g_{ds2}} \right)$$

$$\approx \left( \frac{g_{m1}}{g_{ds1} + g_{ds2}} \right) C_{gd1}$$

$$\therefore C_① \approx C_{gs1} + C_{gb1} + C_{gd1} \left( \frac{g_{m1}}{g_{ds1} + g_{ds2}} \right)$$

node ②:  $C_② = C_{x1} + C_{db1} + C_{gd2} + C_{db2}$   
 $+ C_{gd4} + C_{gb4} + C_{m4}$  (Miller mult.  $C_{gs4}$ )

$$C_{x1} = C_{gd1} \left( 1 - \frac{1}{A_{v0}} \right) \approx C_{gd1}$$

$$C_{m4} = C_{gs4} (1 - A_{v04})$$

$$\approx C_{gs4} \left( 1 - \frac{g_{m4}}{g_{m4} + g_{mb4}} \right)$$

$$\approx C_{gs4} \left( \frac{g_{mb4}}{g_{m4} + g_{mb4}} \right) = C_{gs4} \left( \frac{\eta}{1 + \eta} \right)$$

$$\therefore C_② \approx C_{gd1} + C_{db1} + C_{gd2} + C_{db2}$$

$$+ C_{gd4} + C_{gb4} + C_{gs4} \left( \frac{\eta}{1 + \eta} \right)$$

Fairly small term.

node ③:  $C_③ = C_{gd3} + C_{db3} + C_{sb4} + C_{x4} + C_L$

$$C_{x4} = C_{gs4} \left( 1 - \frac{1}{A_{v04}} \right)$$

(we will neglect negative caps)

$$\approx C_{gd3} + C_{db3} + C_{sb4} + C_L$$

Now, find the driving point resistances at each node:

node ①: By inspection:  $R_{①} = R_s \parallel R_{G1} \quad (R_{G1} = \infty)$   
 $= R_s$


node ②: By inspection:  $R_{②} = r_{ds1} \parallel r_{ds2} \parallel R_{G4}$   
 $= \frac{1}{g_{ds1} + g_{ds4}} \quad (R_{G4} = \infty)$

node ③: By inspection:  $R_{③} = \frac{1}{g_{m4} + g_{mb4} + g_{ds4} + g_{ds3}}$   
 $\approx \frac{1}{g_{m4} + g_{mb4}}$   
 $= \frac{1}{g_{m4} (1 + \eta_4)}$

∴ Dominant pole


$\omega_{3dB} = -A_1 = \frac{1}{\tau_{①} + \tau_{②} + \tau_{③}}$  where  $\tau_1 = R_{①} C_{①}$   
 $\tau_2 = R_{②} C_{②}$   
 $\tau_3 = R_{③} C_{③}$

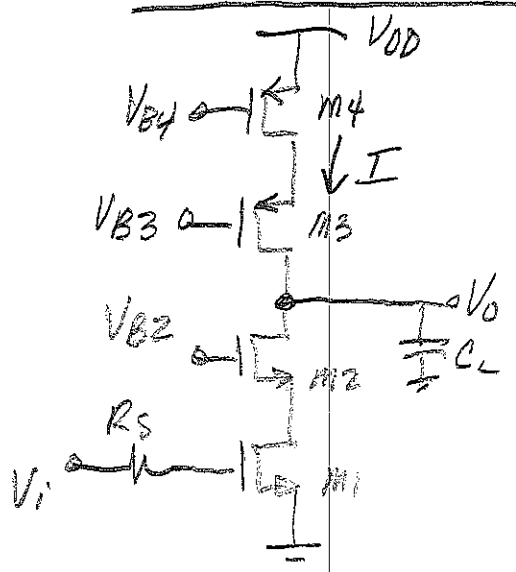• Now, let's consider a very important gain stage, the cascade CS stage:




Main Advantage: Very high voltage gain [like two cascaded CS stages; i.e.,  $A_v \sim (g_m r_o)^2$  for only one bias current, I].  
Drawback: Reduced output voltage swing; i.e., greater headroom required.

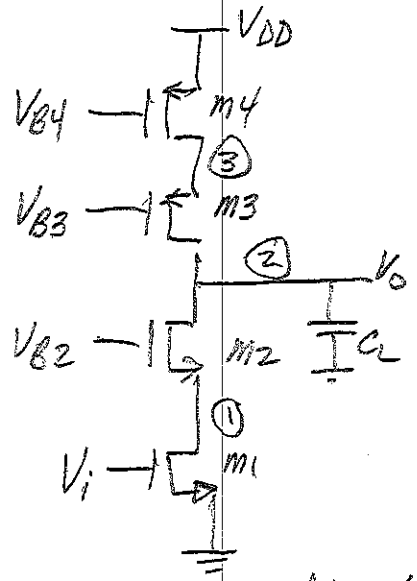Let's consider the output voltage swing limitation:



Observation: If we apply an input signal,  $v_i$ , the signal voltage at  $V_o$  is large because  $V_o$  is a very high impedance (i.e., high gain) node. The voltage swing at ① and ③ are small as we will see later. So, let's assume zero voltage signals at ① and ③ for now.


Consider DC bias conditions:

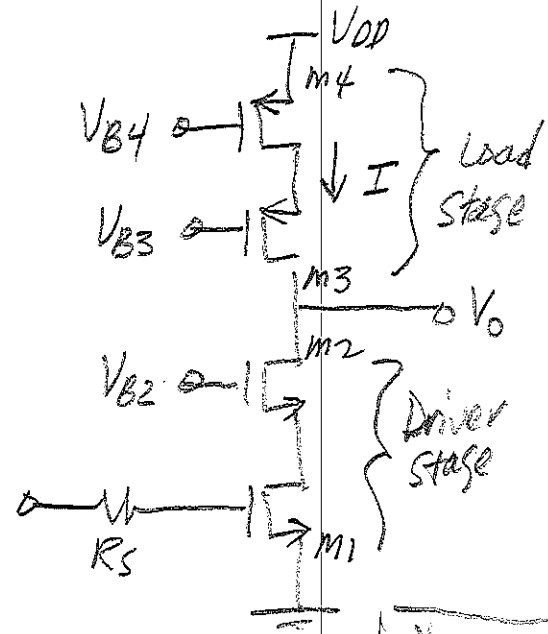

- Must assume  $V_o = V_{DD}/2$  because very high impedance node. \*
- Must keep  $M_1 - M_4$  in saturation as  $V_o$  swings from  $V_o(\min)$  to  $V_o(\max)$
- Let's consider  $M_1 - M_2$  cascode first:

\* Recall: For DC bias calculations use  $I = \frac{k'_n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$

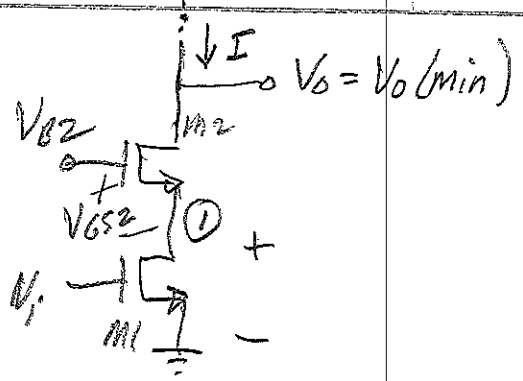Note: No  $V_{OS}$  so we have to assume  $V_o(DC) = \frac{V_{DD}}{2}$




- By inspection,  $V_0(\min) = V_{dsat1} + V_{dsat2}$
- But, we are assuming no signal at ① so  $V_{ds1} = V_{dsat1}$  is always true.

- Note that cascode device,  $M_2$ , sets the DC at ①: Side note:  $V_{gs} = V_T + (V_{gs} - V_T) = V_T + V_{dsat}$

$\therefore V_{\text{①}} = V_{B2} - V_{GS2} = V_{B2} - V_{T2} - V_{dsat2}$   
 But,  $V_{\text{①}} = V_{dsat1} \Rightarrow V_{B2} = V_{T2} + V_{dsat2} + V_{dsat1}$

- Design  $V_{B2}$  for  $V_{out}(\min) = 2V_{dsat}$   $\rightarrow$   $V_{B2} \approx V_{T2} + 2V_{dsat}$   $\leftarrow$

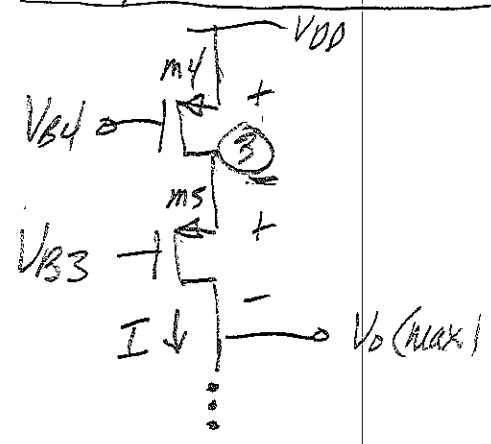• Now, consider the  $M_3$ - $M_4$  PMOS Cascode:



- $M_3$ - $M_4$  must remain in saturation for  $V_0 = V_0(\max)$
- By inspection,  $V_0(\max) = V_{DD} - |V_{dsat3}| - |V_{dsat4}|$
- Again, assume no voltage swing at node ③:


- Note that  $M_3$  sets DC bias voltage at ③:

$\therefore V_{\text{③}} = V_{B3} + V_{SG3} = V_{B3} + |V_{T3}| + |V_{dsat3}|$   
 But, we also want  $|V_{ds4}| = |V_{dsat4}|$

So, solving as before:  $V_{B3} = V_{DD} - 2|V_{dsat}|$   $\leftarrow$

- These DC designs for  $V_{B2}$  and  $V_{B3}$  are non trivial !!

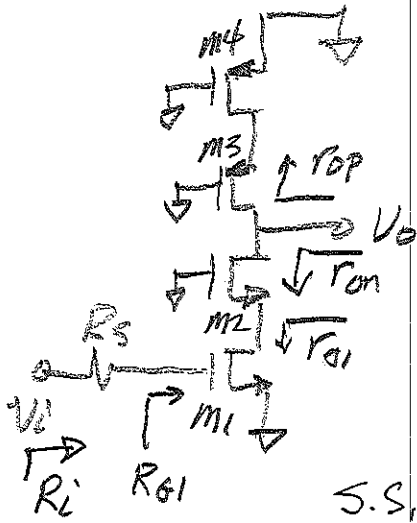
- Now, let's find: (i) Input resistance; (ii) output resistance; (iii) voltage gain and (iv) freq. response



(i)  $R_i = R_s + R_{G1} = R_s + \infty = \infty$

(ii)  $R_o = r_{on} \parallel r_{op}$

Recall this circuit:

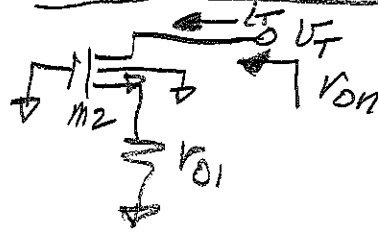

S.S. analysis  $\Rightarrow r_{on} = r_{o2} [1 + (g_{m2} + g_{mb2} + g_{o2}) r_{o1}]$

$\approx r_{o2} (g_{m2} + g_{mb2} + g_{o2}) r_{o1}$

$\approx r_{o1} [(g_{m2} + g_{mb2}) r_{o2}]$

$\approx r_{o1} (g_{m2} r_{o2})$

Self-gain of M2

So,  $R_o = r_{on} \parallel r_{op}$   
 $\approx r_{o1} (g_{m2} r_{o2})$   
 $\parallel r_{o4} (g_{m3} r_{o3})$

$\therefore R_o$  is very large impedance!

Let's do one more new circuit:

S.S. analysis yields:

$$R_{s2} = \frac{1 + g_{o2} R}{g_{m2} + g_{mb2} + g_{o2}}$$

limiting cases:

i)  $R=0 \Rightarrow R_{s2} = \frac{1}{g_{m2} + g_{mb2} + g_{o2}} \approx \frac{1}{g_{m2}}$

(Familiar case)


(ii) Let  $R = r_o$  (assume  $r_o = r_{o2}$  for simplicity)

$\Rightarrow R_{s2} = \frac{1 + g_{o2} r_o}{g_{m2} + g_{mb2} + g_{o2}} = \frac{2}{g_{m2} + g_{mb2} + g_{o2}} \approx \frac{2}{g_{m2}}$

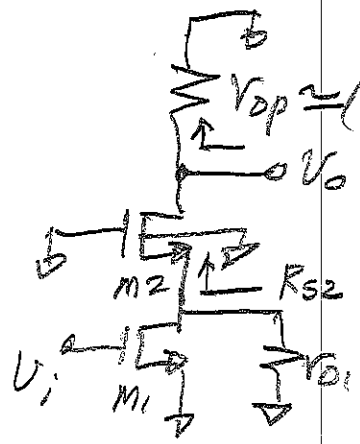(iii) Let  $R = N r_o = N r_{o2}$  (for simplicity)

\* Neat result to remember:  $\Rightarrow R_{s2} = \frac{1 + N g_{o2} r_o}{g_{m2} + g_{mb2} + g_{o2}} = \frac{N+1}{g_{m2} + g_{mb2} + g_{o2}} \approx \frac{N+1}{g_{m2}}$

Now, let's compute  $A_v = \frac{V_o}{V_i}$ :



note: The signal current generated by  $M_1$  is  $g_{m1}V_i$ . But, not all of that current flows through the high impedance output node because of current division between  $r_{o1}$  and  $R_{s2}$ . This effect

is often misunderstood and usually ignored, but it can be significant. From above:

$$R_{s2} = \frac{1 + g_{o2} r_{op}}{g_{m2} + g_{mb2} + g_{o2}} \quad (\text{Simplify: all } g_{mi} = g_m, g_{mbi} = g_{mb}, g_{oi} = g_o, \text{ etc.})$$

$$\rightarrow R_{s2} \approx \frac{1 + g_o g_m r_o^2}{g_m + g_{mb} + g_o} \approx \underline{\underline{r_o}}$$

• Thus, only half of  $g_{m1}V_i$  flows upwards into  $M_2$ :

Now, by inspection:

$$A_v = -\frac{1}{2} g_{m1} R_o = -\frac{1}{2} g_{m1} [r_{o1} (g_{m2} r_{o2}) \parallel r_{o4} (g_{m3} r_{o3})]$$

$$= -\frac{1}{2} g_{m1} \left[ \frac{1}{2} g_m r_o^2 \right] = -\frac{1}{4} \underbrace{(g_m r_o)^2}_{\text{Very large gain}}$$


• Thus,  $A_v$  of cascode gain stage is similar to that of two simple CS stages connected in cascode (i.e., in series)

ANIRUDH



Now, freq. response starting with dominant pole:

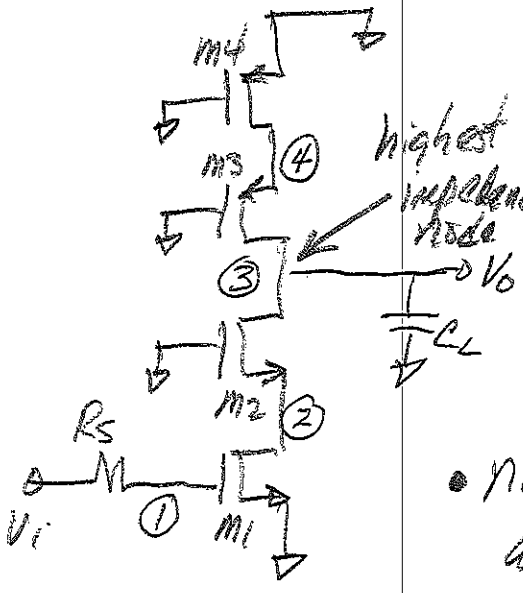ZVTC Method  $\rightarrow \omega_{-3dB} = \frac{1}{\tau_{(1)} + \tau_{(2)} + \tau_{(3)} + \tau_{(4)}}$




Before we do all of these computations, let's inspect to see if we need to:

- Node ①: Driving point resistance,  $R_{D1} = R_S$  (probably small)
  - Node ②: Based on our previous analysis  $R_{D2} \approx \frac{r_D}{2}$  (medium value)
  - Node ③:  $r_{o1} || r_{o2} = R_{D3} \approx g_{m2} r_{o2} r_{o1} || g_{m3} r_{o3} r_{o4} \approx \frac{r_D}{2} (g_m r_D)$  Very large Driving pt. Resistance.
  - Node ④: Same analysis as at node ②:  $R_{D4} \approx \frac{r_D}{2}$
- Note also that  $C_L$  is usually larger than the transistor capacitances.

Hence,  $\omega_{-3dB} \approx \frac{1}{\tau_{(2)}}$

$$\tau_{(3)} \approx [(g_{m2} r_{o2} r_{o1}) || (g_{m3} r_{o3} r_{o4})] [C_{gd2} + C_{db2} + C_{gd3} + C_{db3} + C_L]$$

Bode Plot:

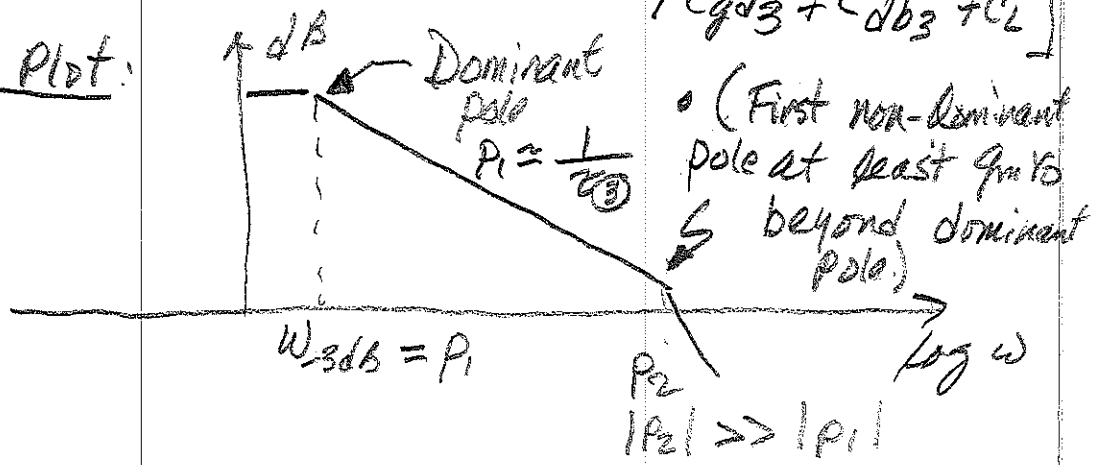


Now, near  $p_2$ ,  $C_L$  represents a low impedance: Example: let  $g_m r_o = 100$   
 $r_o = 1 M\Omega$

$Z_0$  at low freqs =  $r_{op} \parallel r_{on}$   
 $\approx \frac{1}{2} (g_m r_o) r_o = \frac{1}{2} (100) (1 M\Omega) = 50 M\Omega$

$|Z_c| = \left| \frac{1}{j\omega C_L} \right|$  at  $\omega_2 = 10^8$  rad/sec with  $C_L = 5 pF$

$\therefore |Z_c| = 2 k\Omega$  ← Now,  $V_o$  very low impedance!

Compared to  $r_{op}$ ,  $|Z_c|$  is very small at  $p_2$ . Thus, we can analyze the following circuit to get  $p_2$ :

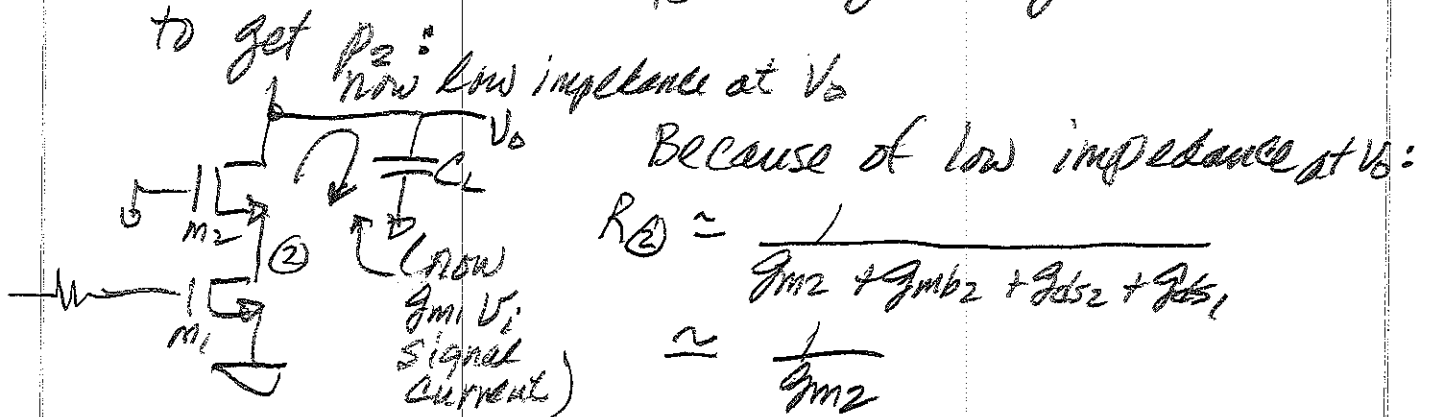

$\therefore \tau_2 = R_2 C_2$   
 $= \frac{1}{g_{m2}} [C_{x1} + C_{db1} + C_{gs2} + C_{sb2}]$

$\therefore p_2 \approx \frac{g_{m2}}{2C_{gd1} + C_{db1} + C_{gs2} + C_{sb2}}$

First non-dominant pole. (See bode plot on previous page)

\*  $\frac{V_2}{V_1} = \frac{-g_{m1}}{sC_2} \approx \frac{-g_{m1}}{g_{m2}} \approx -1 V/V$

$\therefore C_{m1} = C_{x1} \approx 2C_{gd1}$

"AMBA"