
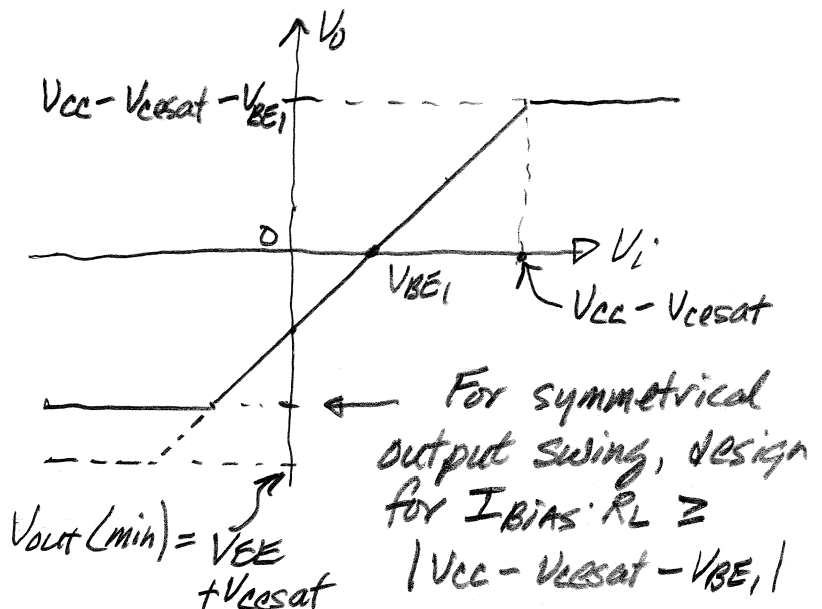




Output stages:

(A) Class-A (e.g., emitter follower):

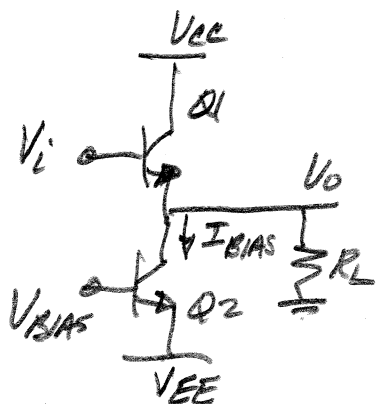


- Advantage: High linearity
- Disadvantages: Poor output swing for low supplies
 Poor efficiency - $\eta = \frac{P_{LOAD}}{P_{SUPPLY}} \leq 25\%$

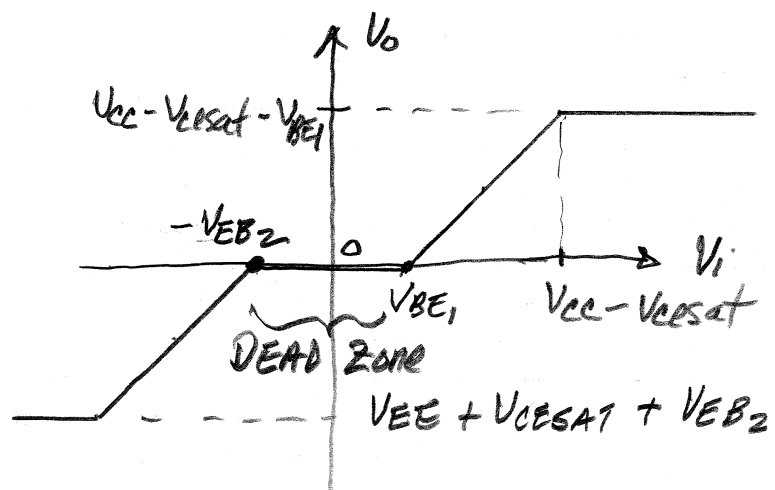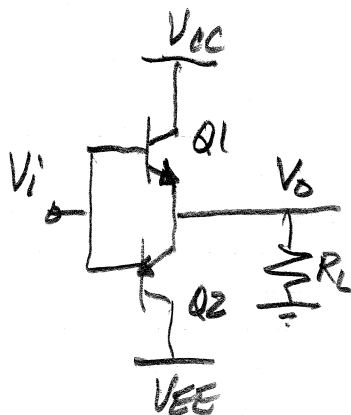(B) Class-B (e.g., complementary emitter followers):




- Advantage: Excellent power efficiency - $\eta = \frac{P_{LOAD}}{P_{SUPPLY}} \leq \frac{\pi}{4} \% = 78.5\%$
- Disadvantage: Severe crossover distortion.

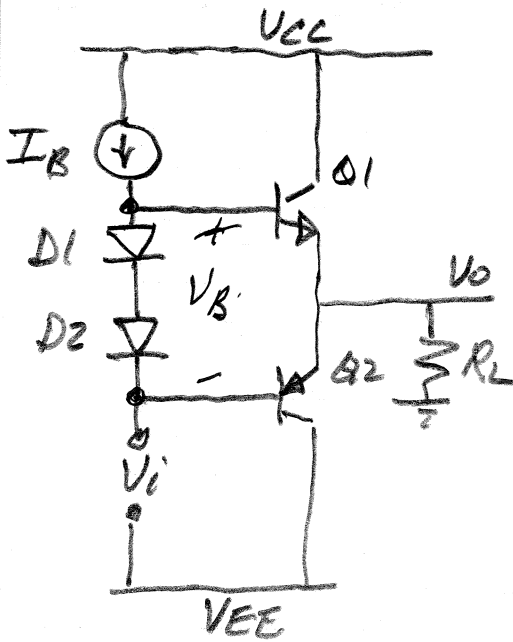
(c) Class-AB (e.g., 741 opamp output stage):



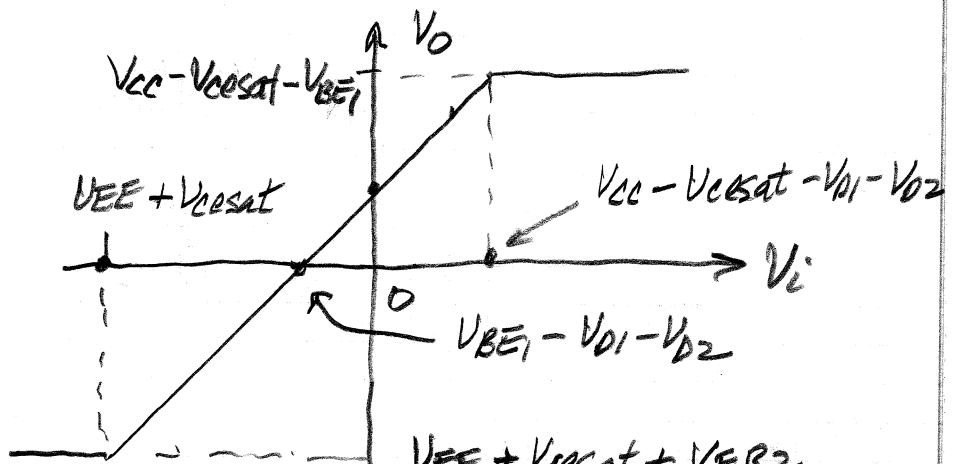With $\beta_{npn} = \beta_{pnp} = \infty$, $D1$ and $D2$ are biased with constant I_B . Thus, they generate a constant voltage, $V_B \approx 1.4V$, which is applied to $Q1$ and $Q2$. That is, $V_{D1} + V_{D2} = V_{BE1} + V_{BE2}$. Ideally, $Q1$ and $Q2$ are biased on with a small current to eliminate crossover distortion:



• Practical Implementation:

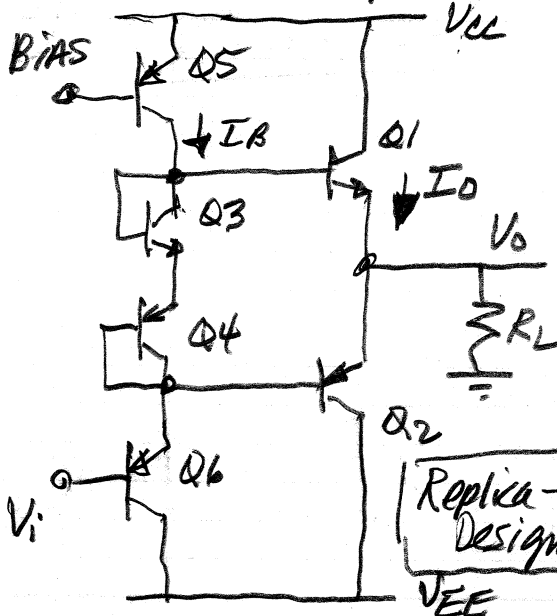

KVL: (R's very large)
 $V_{BE1} + V_{BE2} - V_{BE3} - V_{BE4} = 0$
 Assume: $A_{EB1} = n A_{EB3}$
 and $A_{EB3} = n A_{EB4}$
 $V_T \ln \frac{I_O}{I_{S1}} + V_T \ln \frac{I_O}{I_{S2}} - V_T \ln \frac{I_B}{I_{S3}} - V_T \ln \frac{I_B}{I_{S4}} = 0$
 $\therefore I_O = n I_B$

AMPAD™

• Stability and frequency Compensation in Opamps:


In general, Opamps are used in negative feedback loops

- Feedback sets DC bias level at output ∴ no large coupling or bypass capacitors needed.
- FB increases bandwidth (with reduced gain)
- FB increases linearity of input stage (e.g., emitter degeneration is a type of negative FB (i.e., series negative feedback))
- Gain determined by (passive) FB network and is usually based on resistor or capacitor ratios that are much more accurate than absolute opamp gain values.
- FB can improve temperature stability
- FB sets R_i and R_o

Input	Output	R_i	R_o	Type of Amp
Shunt FB	Shunt	Low	Low	$I \rightarrow V$; Transresistance
Shunt	Series	Low	High	$I \rightarrow I$; Current
Series	Shunt	High	Low	$V \rightarrow V$; Voltage
Series	Series	High	High	$V \rightarrow I$; Transconductance

• Motivations for frequency Compensation:

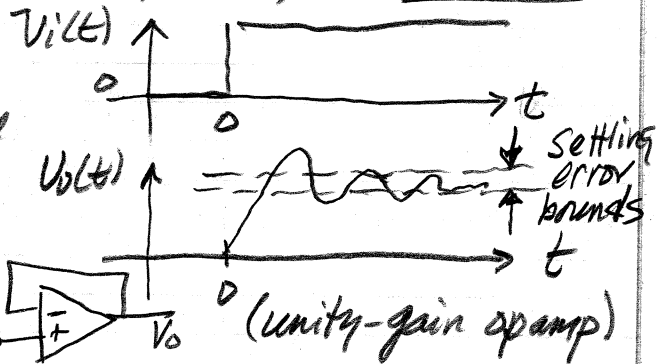
- Absolute closed-loop stability (i.e., no oscillation) with $V_{in} = 0$



- Control of settling time in high-accuracy sampled-data systems (e.g., SC A/D, etc.)

Problem: Any FB loop can become unstable under certain conditions - must frequency compensate to guaranteed stability in given, or worst-case operating condition.

Example: Non-inverting amplifier

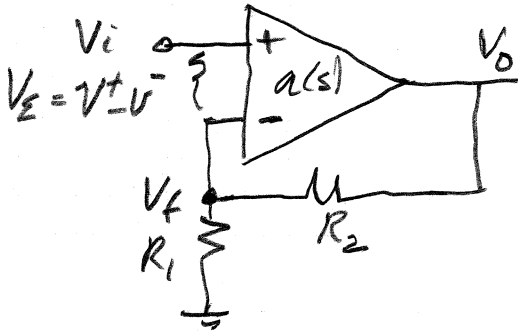



$a(s) \equiv$ open-loop opamp gain
 $V_f = \frac{R_1}{R_1 + R_2} V_o = F V_o \equiv$ Feedback Voltage

$V_E = V^+ - V^- = V_i - F V_o \equiv$ error voltage

$V_o = a(s) V_E$
 $= a(s) [V_i - F V_o]$

$\therefore A(s) \equiv$ closed-loop voltage gain $= \frac{V_o(s)}{V_i} = \frac{a(s)}{1 + a(s)F}$
 $= \frac{a(s)}{1 + T(s)}$ where $T(s) \equiv$ loop transmission
 and $T_0 \equiv$ loop gain at a specific frequency

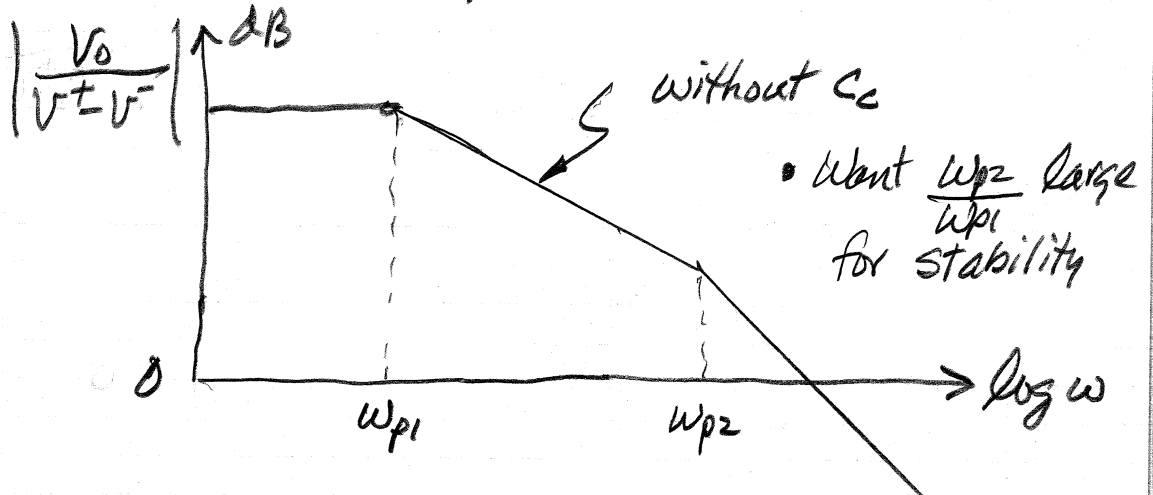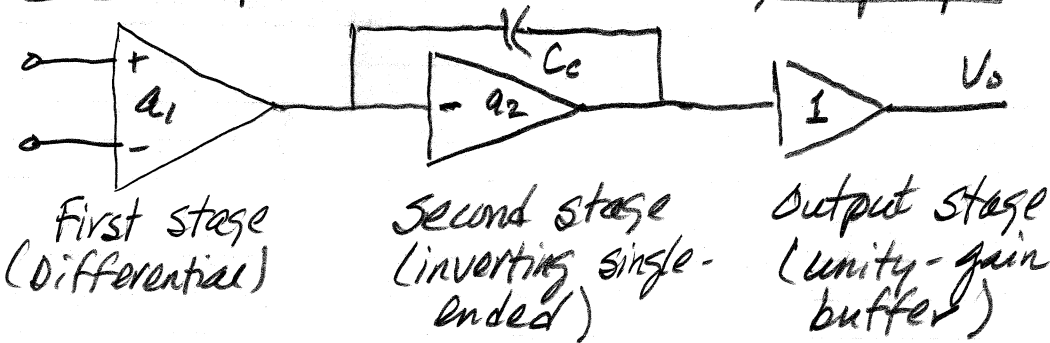• Miller Compensation in two-stage opamps



- Instability occurs when $A(s) \rightarrow \infty$

$$\therefore A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a(s)}{1 + T(s)} \rightarrow \frac{a(s)}{1 - 1} = \infty$$

$$\therefore \text{Loop transmission} = |a(s)f| = -1$$

- Also unstable if denominator is negative

In general: If $|a(s)f| \geq 1$ when $\angle a(s)f = -180^\circ$ the amplifier is unstable.

- This is a simplified version of Nyquist stability Criterion.

- Stability of Feedback Circuit using a single stage opamp

$$a(s) = \frac{a_0}{1 - s/p_1} \equiv \text{opamp transfer function}$$

$$\text{Thus, } A(s) = \frac{a(s)}{1 + a(s)f} = \frac{a_0}{1 + a_0f} \cdot \frac{1}{1 - \frac{s}{p_1(1 + a_0f)}}$$

$A_0 \equiv \text{closed-loop DC gain}$
 if $a_0f \gg 1$
 $A_0 \approx \frac{1}{f}$


BW increases by $(1 + a_0f)$

$$T_0 = a_0f = \text{loop gain at DC}$$





$$T(s) = a(s)f = \text{loop transmission (defined for general frequency)}$$

- Bode Plot: Use to find $\angle a(s)f$ when $|a(s)f| = 1$

This determines degree of Stability

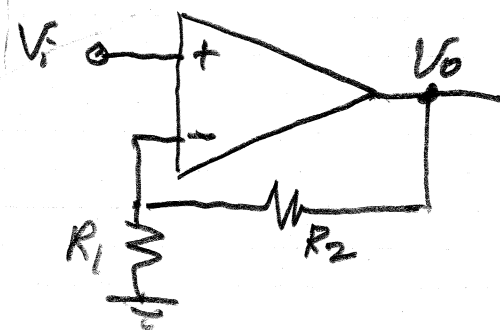

AMPAD

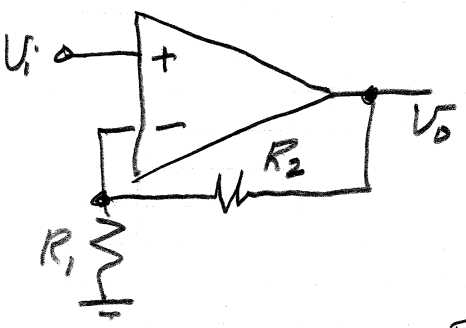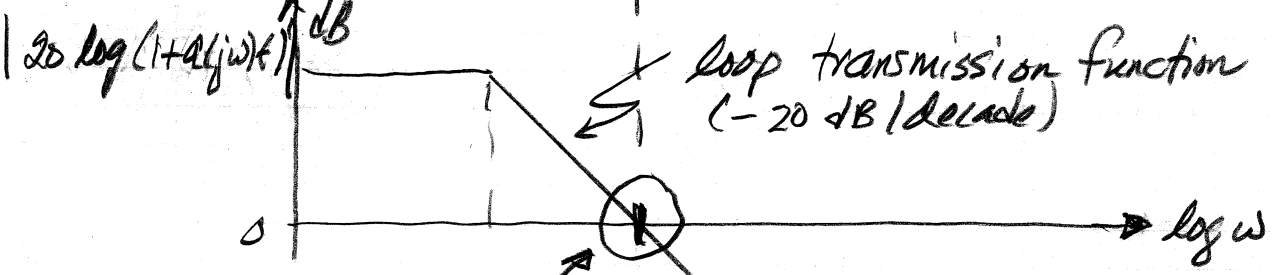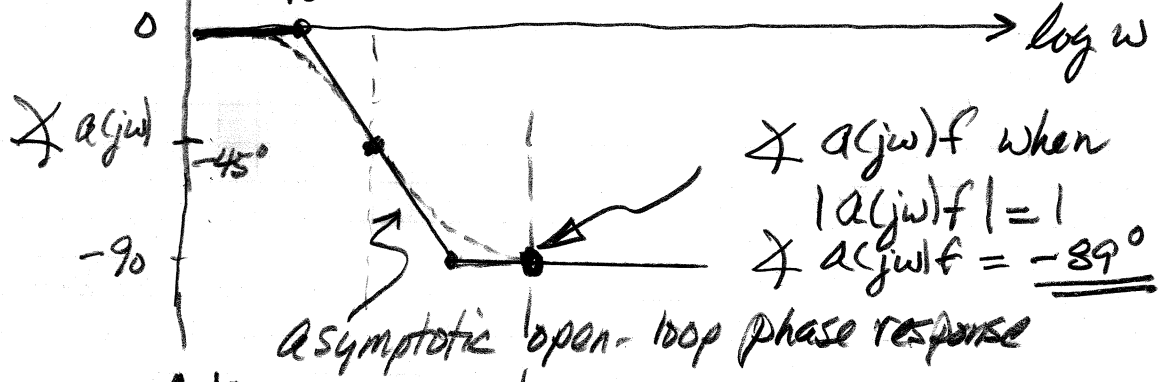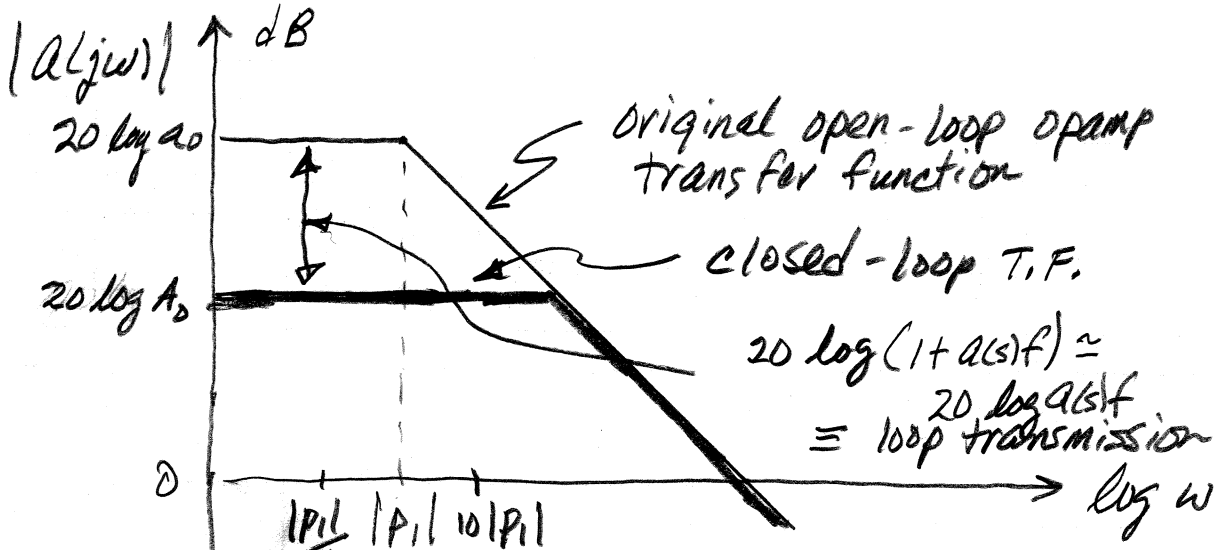

$$f = \frac{R_1}{R_1 + R_2}$$

Note: phase shift for loop transmission is same as that for open-loop opamp = $\angle(1 + a(j\omega)f)$
 $|a(j\omega)f| = 1$ at this freq.


- For a single-pole opamp, $\angle a(j\omega)f$ can never reach -180° (which converts negative FB to positive FB) so always stable. With $f = \text{constant}$.

o Real opamp has multiple poles:

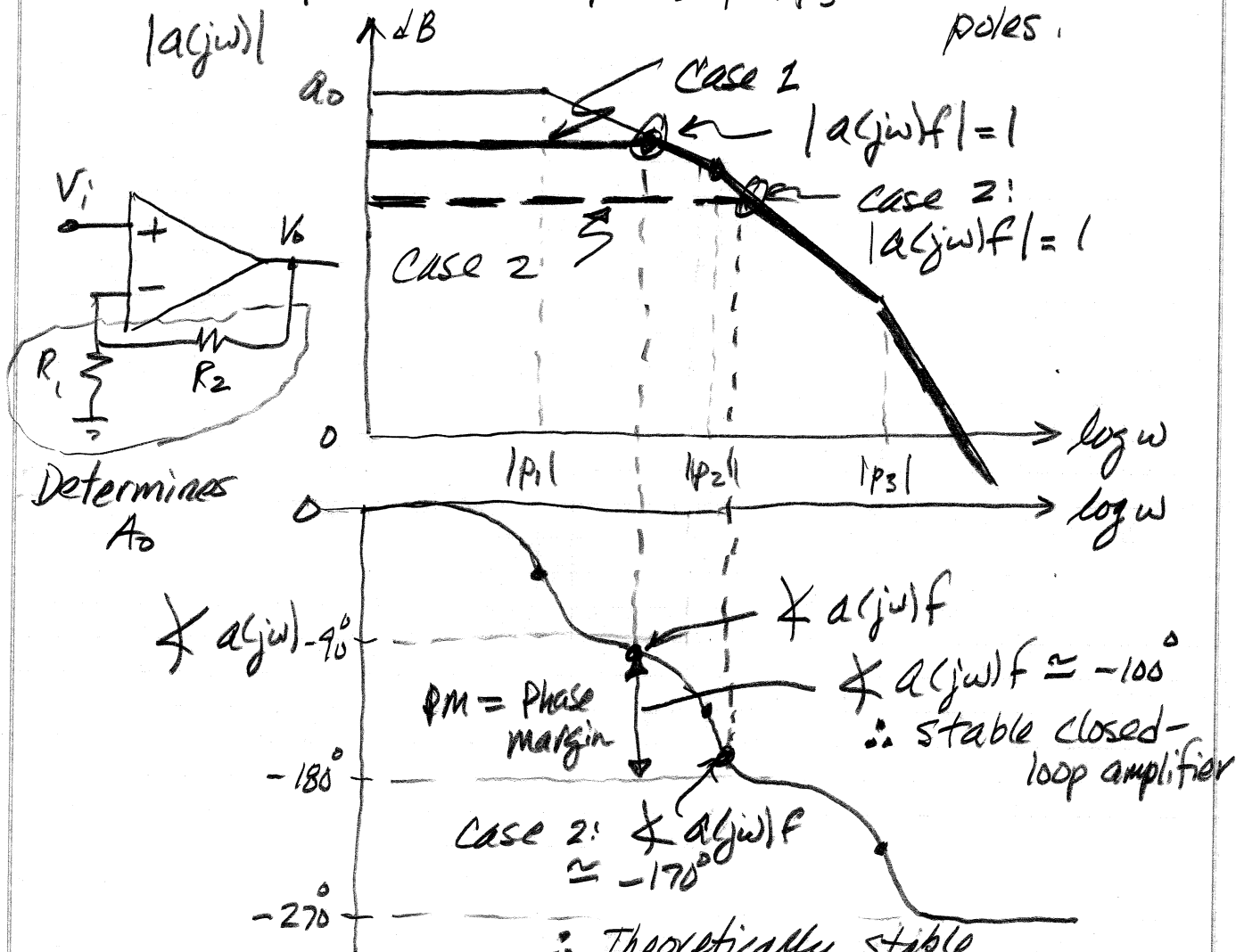- (i) Two-pole opamp - $\angle a(j\omega)f \rightarrow -180^\circ$ as $f \rightarrow \infty$
Theoretically, always stable but very, very marginal.
- (ii) With three or more poles, $\angle a(j\omega)f = -180^\circ$ at some frequency and $< -180^\circ$ beyond that frequency.

o Stability of Feedback circuit using three-stage opamp

Assume p_1 = dominant pole; p_2, p_3 = non-dominant poles.



Determines A_0

Case 1: Large closed-loop gain

Case 2: Smaller closed-loop gain

\therefore Theoretically stable but unsafe in the presence of PVT variations and possible load variations.

- For the general case where $d(s)$ has multiple poles:
 - (i) $A(s)$ has the same additional poles ($f = \text{constant}$)
 - (ii) at frequencies $> |p_1|(1+a_0f)$, the $A(s)$ curve just follows the $d(s)$ curve:

$$A(s) \cong \frac{A_0}{\left(1 - \frac{s}{|p_1|(1+a_0f)}\right) \left(1 - \frac{s}{|p_2|}\right) \left(1 - \frac{s}{|p_3|}\right)}$$

where $|p_1|(1+a_0f) < |p_2|$ as for case 1.

- Beyond this frequency, there is peaking in the closed-loop gain T.F. magnitude response

Definitions:

PM \equiv phase margin = $180^\circ + (\angle a(j\omega)f @ \text{frequency where } |a(j\omega)f| = 1)$

= 90° (Very stable - one-pole exponential behavior)

= 10° (Stable but not practical - too dangerous)

$\approx 60^\circ$ desired for minimum settling time

step response.

GM \equiv gain margin = $|a(j\omega)f| @ \text{frequency where } \angle a(j\omega)f = -180^\circ$. $|a(j\omega)f|$ should be less than 0 dB.

A good design value is GM = -12 dB.