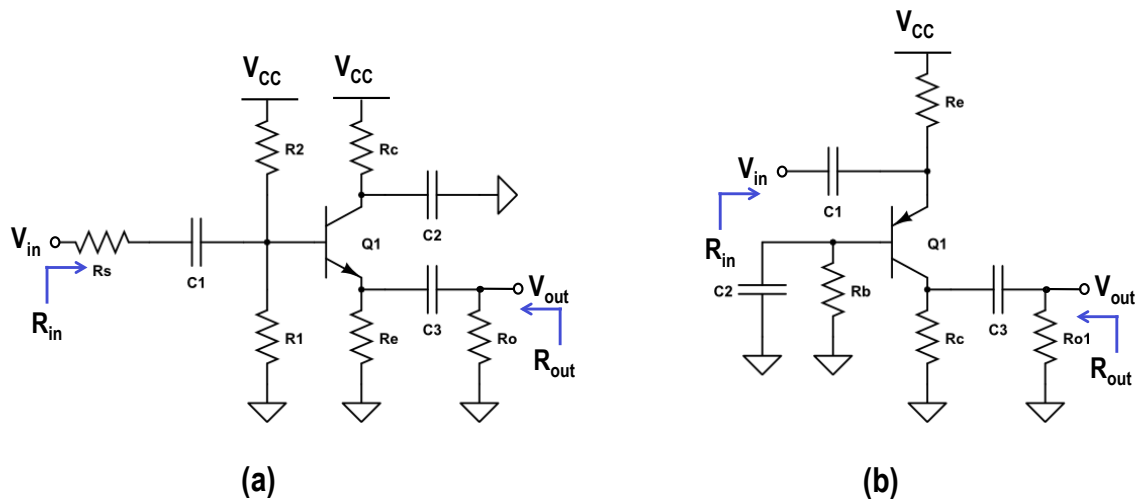


**PROBLEM SET #2**

*Issued: Tuesday, Sep. 9, 2015*


*Due (at 8 a.m.): Wednesday, Sep. 16, 2015, in the EE 140/240A HW box near 125 Cory.*

1. Use inspection analysis to write expressions for the input resistance  $R_{in}$ , output resistance  $R_{out}$ , and gain  $v_{out}/v_{in}$  for each of the amplifiers in Fig PS2.1. The expressions should be in terms of the given elements and parameters of the small-signal equivalent circuits (i.e.,  $g_m$ ,  $r_\pi$ ,  $r_o$ ,  $\beta$ , etc.) for the transistors used. For each circuit, assume that all capacitors shown have infinite values.



**Fig. PS1**

2. Use inspection analysis to write expressions for the input resistance  $R_{in}$ , output resistance  $R_{out}$ , and gain  $v_{out}/v_{in}$  for each the amplifiers in Fig. PS2. The expressions should be in terms of the given elements and parameters of the small-signal equivalent circuits (i.e.,  $g_m$ ,  $r_o$ , etc.) for the transistors used. For each circuit, assume that all the capacitors shown have infinite values. Ignore body-effect. For amplifier (c), assume  $R_s$  is much smaller than  $r_o$ .

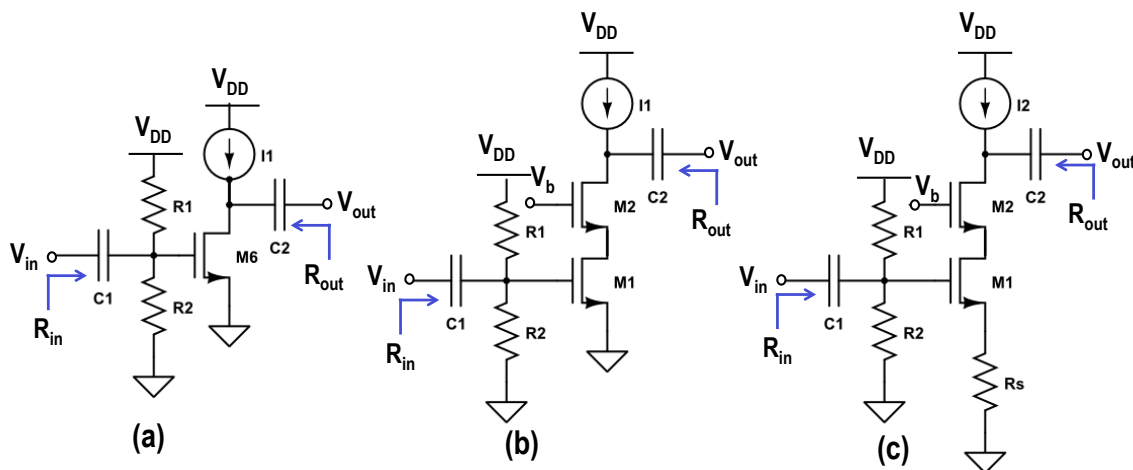

**Fig. PS2**

3. Consider the following questions using the parameter value list in Table PS.3. Assume all MOSFET share the same parameters except for the one specified. Ignore body-effect.
- Provide expressions for the input resistance  $R_{in}$ , output resistance  $R_{out}$ , and gain  $v_{out}/v_{in}$  for the amplifier in Fig. PS3. Assume  $V_b$  biases all the transistors properly in saturation region.
  - Redo Problem (a) with the amplifier shown in Fig. PS2-(b). Assume  $V_b$  biases all the transistors properly in saturation region.
  - Briefly compare the results you get from part (a) and (b) and identify advantages or disadvantages between the two amplifiers.

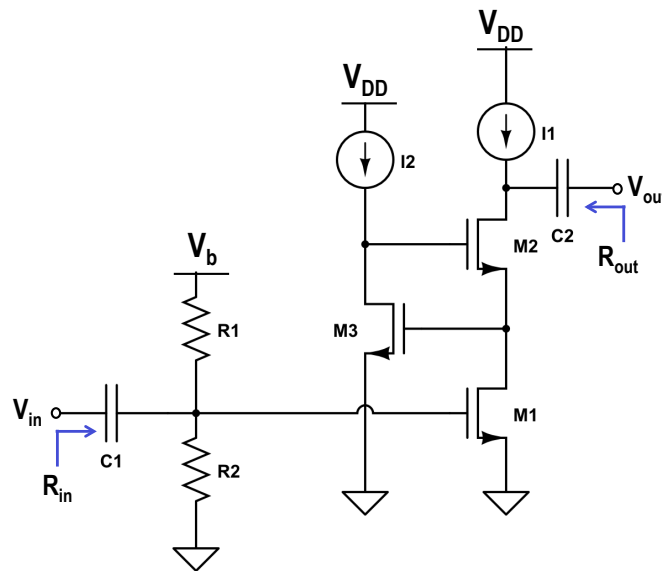


Fig. PS3

Parameter	Value	Parameter	Value
M1 Width ( $W$ )	$16\mu\text{m}$	Oxide relative permittivity ( $\epsilon_r$ )	3.9
M2 Width ( $W$ )	$8\mu\text{m}$	Channel Length	$0.2\text{ V}^{-1}$
		Modulation Coeff. ( $\lambda$ )	
M3 Width ( $W$ )	$8\mu\text{m}$	$R_1$	$10\text{k}\Omega$
Channel Length ( $L$ )	$0.8\mu\text{m}$	$R_2$	$20\text{k}\Omega$
Gate Dielectric Thickness ( $t_{ox}$ )	$60\text{\AA}$	$I_1$	$1\text{mA}$
Threshold Voltage ( $V_{TH}$ )	$0.6\text{V}$	$I_2$	$0.1\text{mA}$
Electron Mobility ( $\mu_n$ )	$1400\text{cm}^2/\text{Vs}$	$V_{DD}$	$3.3\text{V}$

Table. PS3

4. Suppose the BJTs in the two amplifiers of Fig. PS4 have the same  $\beta = 100$  and that they are properly biased by  $V_{b1}$  and  $V_{b2}$  such that the nominal bias current  $I_{C1} = I_{C2} = 0.5\text{mA}$ . Assume also that  $V_{b1}$  and  $V_{b2}$  are unstable, such that  $I_C$  varies by  $\pm 20\%$ . Ignore Early effect.
- (a) For both amplifiers, calculate the corresponding ranges of the input resistance  $R_{in}$ , output resistance  $R_{out}$ , and gain  $v_{out}/v_{in}$
- (b) Based on the result of problem 4-(a), briefly compare the two amplifiers, stating advantages and disadvantages of one over the other.

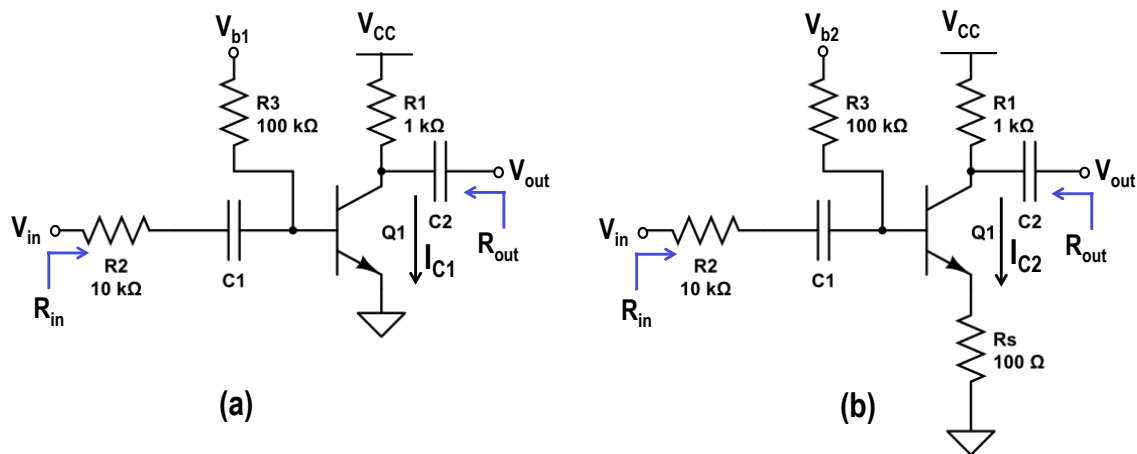


Fig. PS4