

PROBLEM SET #7

Issued: Friday, Oct. 16, 2015

Due (at 8 a.m.): Monday, Oct. 26, 2015, in the EE 140/240A HW box near 125 Cory.

1. A design error has resulted in a mismatch in the circuit of Fig. PS7-1. Specifically, M_2 has twice the W/L ratio of M_1 . If V_{id} is a small sine-wave signal, find an expression for
 - (a) I_{D1} and I_{D2} .
 - (b) V_{OV} for each of M_1 and M_2 .
 - (c) The differential gain A_{dm} in terms of R_D , I , and V_{OV} .

 


Fig. PS7-1

2. The differential amplifier in Fig. PS7-2 utilizes a resistor R_{SS} to establish a 1-mA dc bias current. Note that this amplifier uses a single 5-V supply and thus needs a dc common-mode voltage V_{CM} . Transistors M_1 and M_2 have $k'W/L = 2.5\text{mA/V}^2$, $V_t = 0.7\text{V}$, and $\lambda = 0$.
- Find the required value of V_{CM} .
 - Find the value of R_D that results in a differential gain A_{dm} of 8 V/V.
 - Determine the dc voltage at the drains
 - Determine the common-mode gain v_D/v_{CM} and CMRR for this amplifier. (Hint: You need to take $1/g_m$ into account.)
 - Use the common-mode gain found in (d) to determine the change in V_{CM} that results in M_1 and M_2 entering the triode region.

 


Fig. PS7-2

3. Fig. PS7-3 shows a high-gain op amp design with cascade devices. Let $I_{SS} = 1\text{mA}$, $V_{DD} = 3\text{V}$, $V_{B1} = 1.7\text{V}$ and $V_{B2} = 1.6\text{V}$. Assuming $\gamma = 0$ and $V_{ov,ISS} = 0.2\text{V}$, find the mid-band gain v_{out}/v_{in} , input common-mode range, and the output swing.

MOS Parameters:

$$\mu_n C_{ox} = \frac{135\mu\text{A}}{\text{V}^2}, \mu_p C_{ox} = \frac{38\mu\text{A}}{\text{V}^2} \quad V_{Tn} = 0.7\text{V}, V_{Tp} = -0.8\text{V}, \lambda_n = \lambda_p = 0.1,$$

$$\left(\frac{W}{L}\right)_{1,2,3,4} = \frac{100\mu\text{m}}{0.34\mu\text{m}}, \left(\frac{W}{L}\right)_{5,6,7,8} = \frac{100\mu\text{m}}{0.32\mu\text{m}}$$

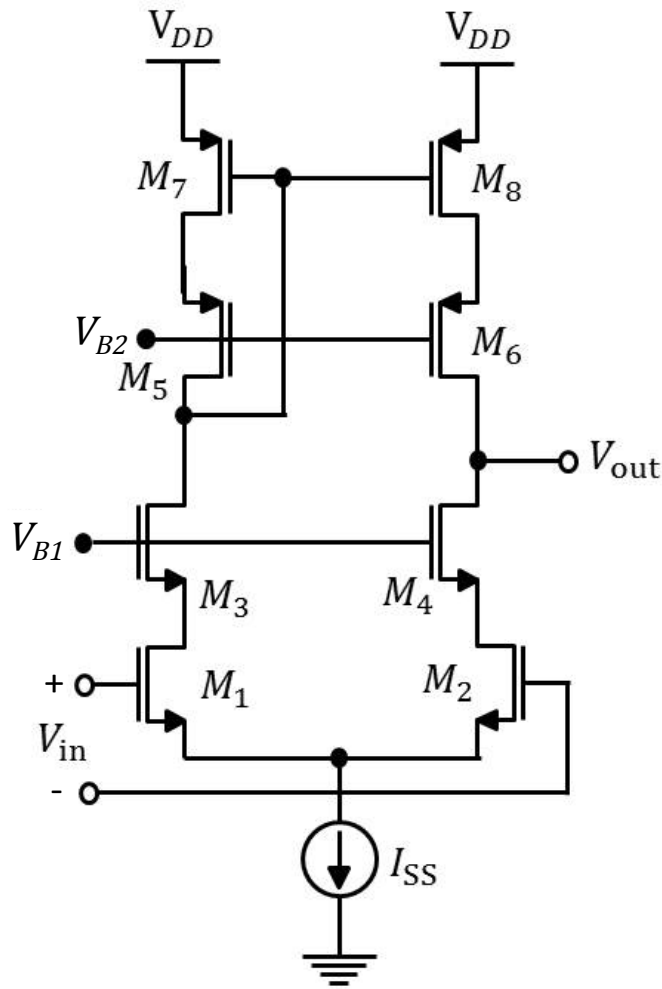


Fig. PS7-3

4. Fig. PS7-4 shows a two-stage CMOS op amp. Let $I_{REF} = 90\mu\text{A}$, $V_{DD} = V_{SS} = 2.5\text{V}$, and $C_C = 0$. Find the mid-band gain $v_o/(v_+ - v_-)$, input common-mode range, and the output swing.

MOS Parameters:

$$\mu_n C_{ox} = \frac{160\mu\text{A}}{\text{V}^2}, \mu_p C_{ox} = \frac{40\mu\text{A}}{\text{V}^2}, V_{Tn} = 0.7\text{V}, V_{Tp} = -0.8\text{V}, \lambda_n = \lambda_p = 0.1,$$

$$\left(\frac{W}{L}\right)_{1,2} = \frac{20\mu\text{m}}{0.8\mu\text{m}}, \left(\frac{W}{L}\right)_{3,4} = \frac{5\mu\text{m}}{0.8\mu\text{m}}, \left(\frac{W}{L}\right)_{5,7,8} = \frac{40\mu\text{m}}{0.8\mu\text{m}}, \left(\frac{W}{L}\right)_6 = \frac{10\mu\text{m}}{0.8\mu\text{m}}$$

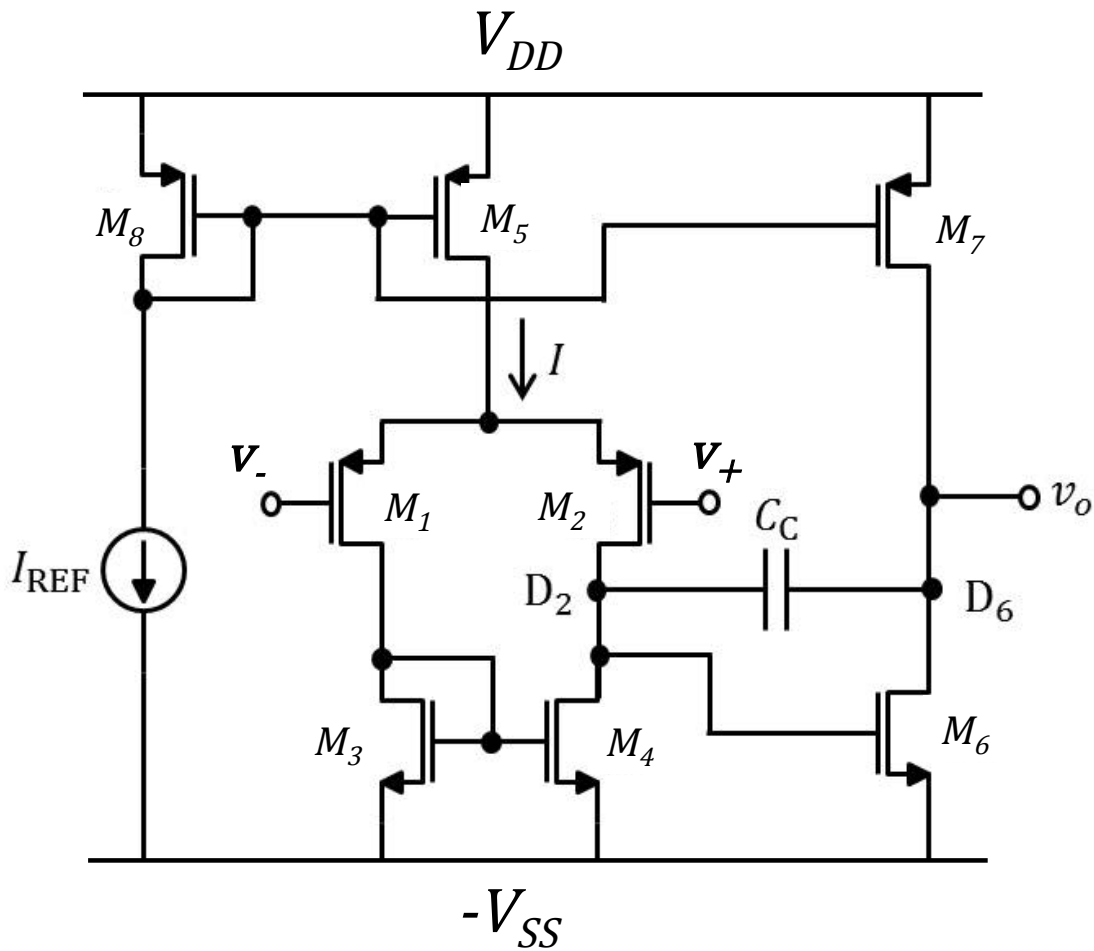


Fig. PS7-4

5. Fig. PS7-5 shows a multi-stage BJT OPamp design. BJTs $Q_1 - Q_9$ have the same size except for Q_6 , which is 4x larger than Q_9 . Ignore Early effect.

- Assuming $\beta \gg 1$ and $|V_{BE}| = 0.7V$, calculate the DC currents flowing through $Q_1 - Q_9$.
- Calculate the static power dissipation of this op amp.
- If transistors Q_1 and Q_2 have $\beta = 100$, what is the input bias current of this op amp?
- If $V_{CE(sat)} = 0.4V$, determine the input common-mode range of this op amp.
- Calculate the input resistance, mid-band gain v_o/v_{id} , and the output resistance of this op amp.

 


Fig. PS7-5