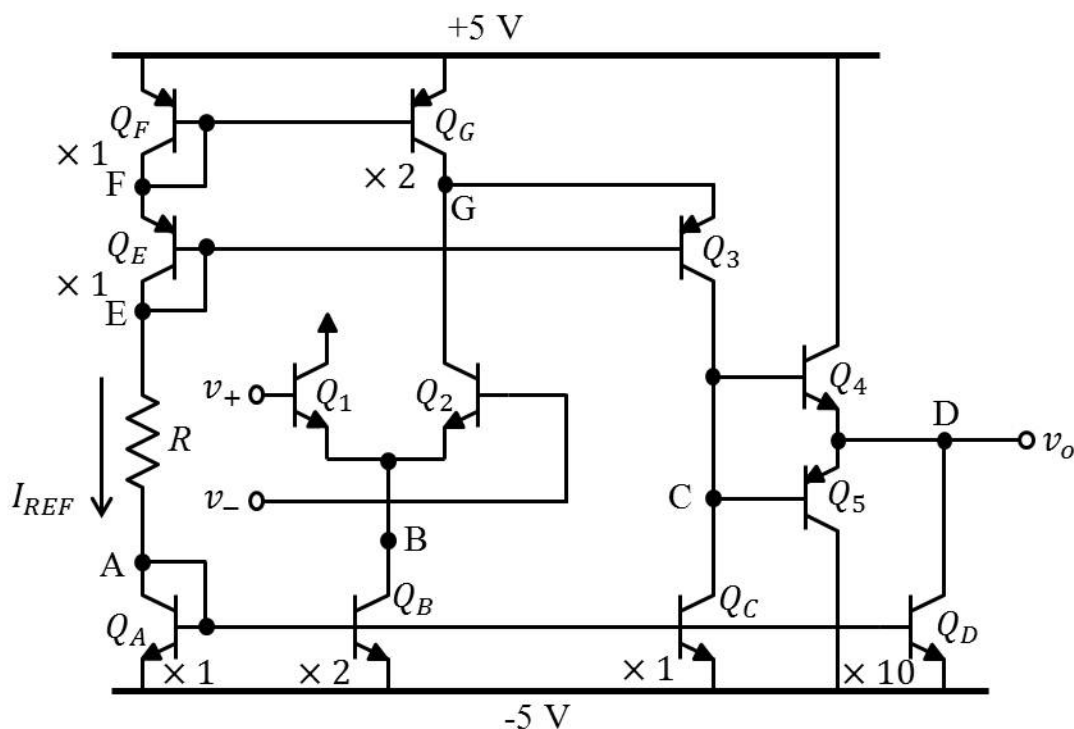


**PROBLEM SET #8**

*Issued: Tuesday, Nov. 3, 2015*

*Due (at 8 a.m.): Wednesday, Nov. 11, 2015, in the EE 140/240A HW box near 125 Cory.*

1. Fig. PS8-1 presents a BJT op amp with output stage. For all transistors  $|V_{BE}| = 0.7\text{V}$ ,  $\beta = 100$  and  $V_A = 200\text{V}$ .
  - (a) Determine the value of  $R$  such that  $Q_1$  and  $Q_2$  are biased with  $I_C = 100\mu\text{A}$ .
  - (b) Find the input resistance, output resistance, and voltage gain  $v_o/(v_+ - v_-)$ .
  - (c) Assuming  $|V_{CEsat}| = 0.3\text{V}$  for all the transistors, find the input common-mode range
  - (d) For no load, what is the range of available output voltages?
  - (e) Assuming  $Q_1$  or  $Q_2$  are allowed to cut-off, find the smallest load resistance that can be driven over the range you found in part (d).



**Fig. PS8-1**

2. Fig. PS8-2 presents a BJT op amp with compensation capacitor  $C_C$ . All transistors have  $\beta = 100$ ,  $|V_{BE}| = 0.7V$ , and  $V_A = \infty$ .
- Find the bias current  $I_C$  for each transistor.
  - Find the voltage gain  $v_o/(v_+ - v_-)$  of the amplifier with  $R_L = 10k\Omega$ .
  - With  $R_L$  as in (b), find the value of  $C_C$  to obtain a 3-dB frequency of 100 Hz.

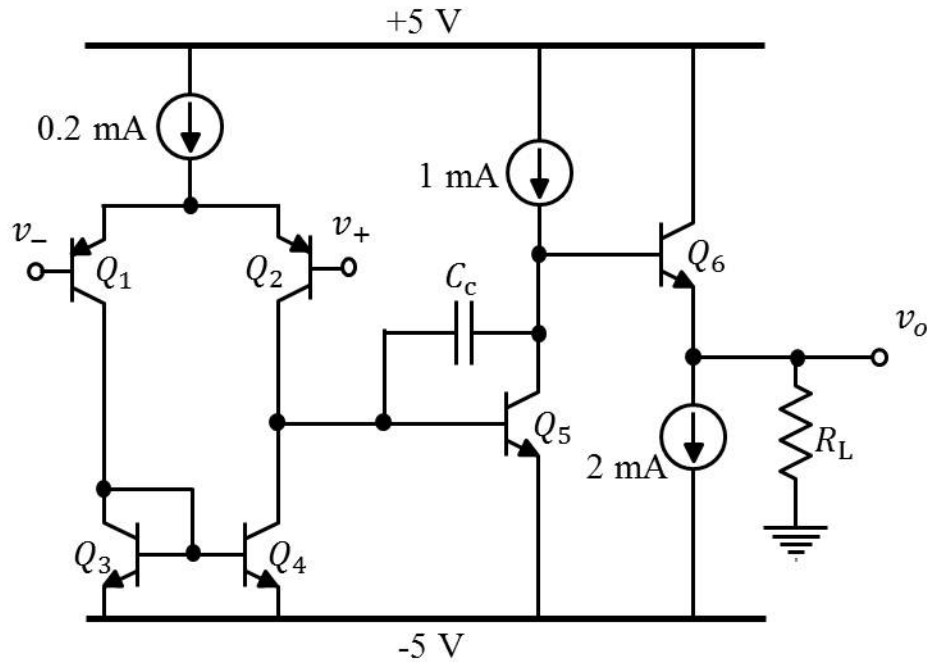


Fig. PS8-2

3. In the circuit of Fig. PS8-3,  $(W/L)_{1-4} = 100\mu\text{m}/0.5\mu\text{m}$ ,  $C_1 = C_2 = 0.5\text{pF}$ ,  $I_{SS} = 1\text{mA}$ ,  $\mu_n = 350\text{cm}^2/\text{V/s}$ ,  $\mu_p = 100\text{cm}^2/\text{V/s}$ ,  $t_{ox} = 9\text{nm}$ ,  $\epsilon_r = 3.9$ ,  $L_d = 0.08\mu\text{m}$ , and  $L_{eff} = L - 2L_d$ .
- (a) If a step voltage (as shown) is applied to the input of this circuit, find an expression for the time constant of its output response in terms of  $g_{m1-4}$ ,  $r_{o1-4}$ ,  $C_1$  and  $C_2$ .
- (b) What is the slew rate of this circuit?
- (c) With a 1-V step at the input, how long does it take for  $I_{D2}$  to reach  $0.1I_{SS}$ ? Before  $I_{D2}$  reaches  $0.1I_{SS}$ , you can assume that the current through  $C_1$  and  $C_2$  roughly equals  $I_{SS}$ .

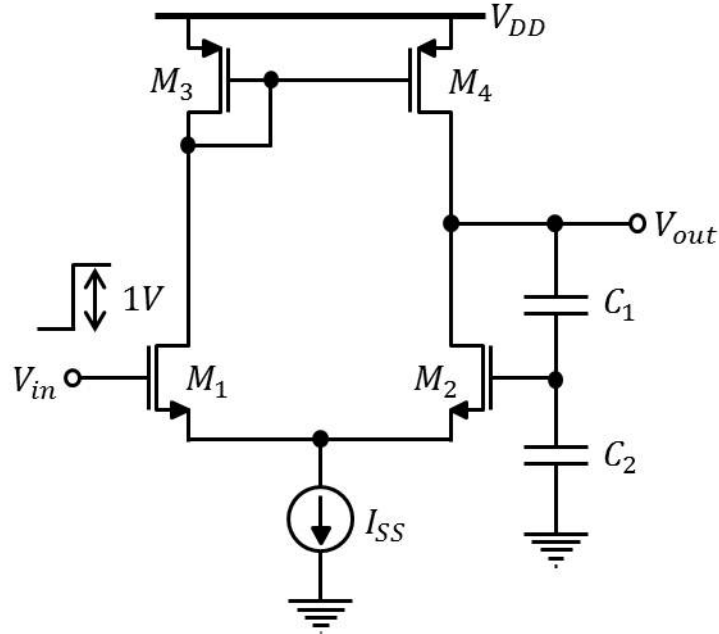


Fig. PS8-3

4. Write expressions for the low frequency closed-loop gains and poles of Fig. PS8-4 (a) and (b), where  $A(s)$  is the transfer function of a single pole amplifier (pole  $\omega_{p1}$ ) with a large low frequency gain of  $A_0$ .

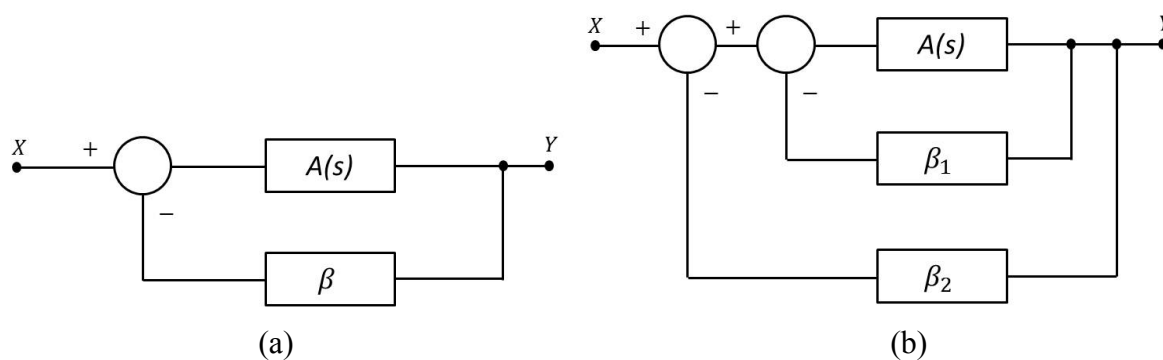


Fig. PS8-4