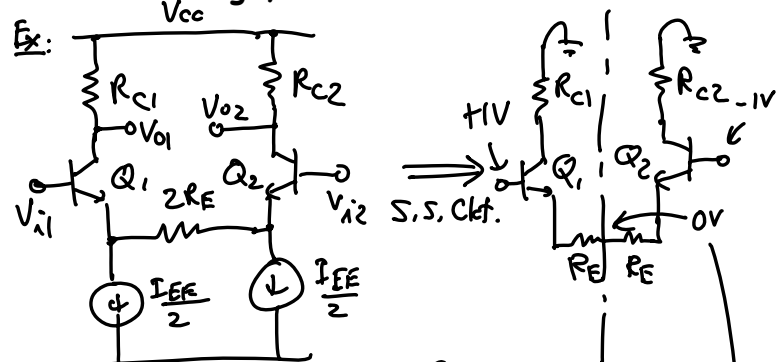


Announcements:

- No lecture Thursday, next week, 3/12
- Make up lecture on next Tuesday evening, at 7 p.m., in 247 Cory
- Homeworks now due at 8 p.m. on Tuesdays

Today:

- Diff pairs
- Offset Voltage,  $V_{os}$



$$V_{EE} \rightarrow r_{o1} = r_{o2} = r_o$$

$$Q_1 = Q_2 \rightarrow g_{m1} = g_{m2} = g_m$$

$$R_{C1} = R_{C2} = R_C$$


(i) Find the differential-mode gain: ( $A_{dm}$ )

D.P. Half Ckt.


$$\frac{(V_{od}/2)}{(V_{id}/2)} = -\frac{g_m(r_o || R_C)}{1 + g_m R_E}$$

$$A_{dm} = \frac{V_{o1} - V_{o2}}{V_{i1} - V_{i2}} = \frac{V_{od}}{V_{id}} = \frac{V_{od}}{V_{id}} = -\frac{g_m(r_o || R_C)}{1 + g_m R_E}$$

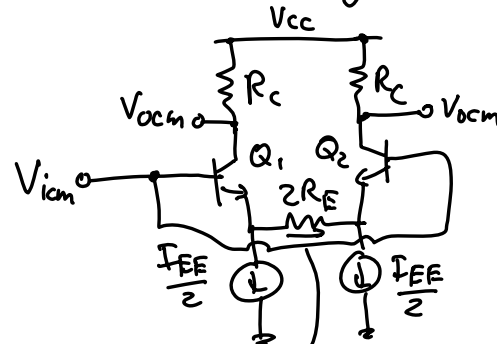(ii) Find the common-mode gain,  $A_{cm}$ :



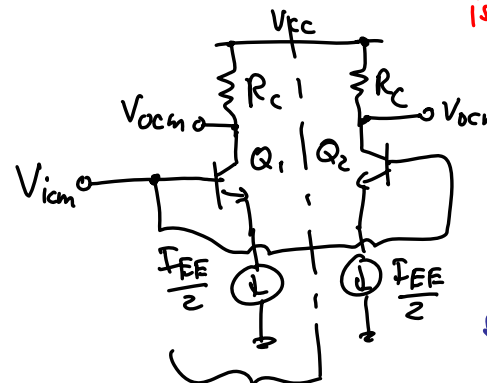How much current goes through this resistor?  
 $i_s = 0 \therefore$  the resistor effectively isn't there!



Common-Mode Half Ckt

for the ideal case!

$$A_{cm} = \frac{V_{oc}}{V_{ic}} = -\frac{g_m(r_o || R_C)}{1 + g_m(\infty)} = 0$$

In reality:

$$A_{cm} = \frac{V_{oc}}{V_{ic}} = -\frac{g_m(r_o || R_C)}{1 + g_m(2R_{EE})}$$

If there is a mismatch in the ckt., e.g.,  $R_{D1} \neq R_{D2}$ , then we can also define:

$$A_{cm-dm} \triangleq \text{common-mode input to differential-mode output gain}$$

$$= \frac{V_{od}}{V_{ic}} = \frac{V_{o1} - V_{o2}}{V_{i1}} = \frac{V_{o1} - V_{o2}}{V_{i2}} \quad (w/ V_{i1} = V_{i2})$$


$$A_{dm-cm} \triangleq \text{differential-mode input to common-mode output gain}$$

$$= \frac{V_{oc}}{V_{id}} = \frac{V_{oc}}{V_{i1} - V_{i2}} \quad [w/ V_{oc} = \frac{1}{2}(V_{o1} + V_{o2})]$$

You will be experiencing these in your HW.

$V_{os}$  of a Mismatched SCP  $\rightarrow$  First, go to prepared material on offset voltage & current.

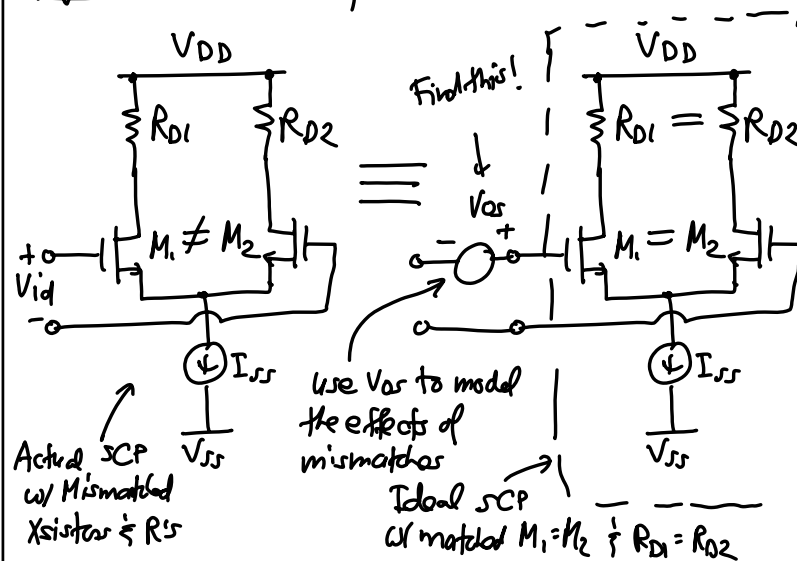
Objective: Derive an expression for  $V_{os}$ .



$V_{os}$  arises due to variations in:

- ①  $X_{static}, M_1 \neq M_2 \rightarrow \frac{W}{L} \neq V_t$  vary
- ②  $R_{D1} \neq R_{D2} \rightarrow$  cause variations in gain

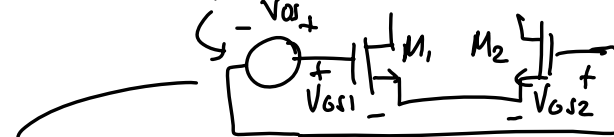Definition  $V_{os} = V_{id}$  needed to get  $V_{od} = 0V$  in this ckt.



$$\text{KVL: } V_{os} - V_{GS1} + V_{GS2} = 0$$

$$\therefore V_{os} = V_{GS1} - V_{GS2}$$

$$= V_{t1} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - V_{t2} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}}$$

$$V_{os} = V_{t1} - V_{t2} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox}(W/L)_1}} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox}(W/L)_2}} \quad (1)$$

Define difference and average quantities:

$$\Delta I_D = I_{D1} - I_{D2} \quad \Delta \left( \frac{W}{L} \right) = \left( \frac{W}{L} \right)_1 - \left( \frac{W}{L} \right)_2$$

$$I_D = \frac{I_{D1} + I_{D2}}{2} \quad \left( \frac{W}{L} \right) = \frac{1}{2} \left[ \left( \frac{W}{L} \right)_1 + \left( \frac{W}{L} \right)_2 \right]$$

$$\Delta V_t = V_{t1} - V_{t2}$$

$$V_t = \frac{1}{2}(V_{t1} + V_{t2})$$

$$\Delta R_D = R_{D1} - R_{D2}$$

$$R_D = \frac{1}{2}(R_{D1} + R_{D2})$$

Rearranging:

$$\begin{array}{l|l|l} I_{D1} = I_D + \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{\Delta(W/L)}{2} & V_{t1} = V_t + \frac{\Delta V_t}{2} \\ I_{D2} = I_D - \frac{\Delta I_D}{2} & \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{\Delta(W/L)}{2} & V_{t2} = V_t - \frac{\Delta V_t}{2} \end{array}$$

Substituting into (1):  $2I_D \left(1 + \frac{\Delta I_D}{2I_D}\right)$

$$V_{OS} = \Delta V_t + \sqrt{\frac{2(I_D + \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) + \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}} - \sqrt{\frac{2(I_D - \Delta I_D/2)}{\mu_n C_{ox} \left[\left(\frac{W}{L}\right) - \frac{1}{2} \Delta\left(\frac{W}{L}\right)\right]}}$$

$$\left[ V_{GS} - V_t = \sqrt{\frac{2I_D}{\mu_n C_{ox} (W/L)}} \right] \xrightarrow{\frac{W}{L} \left[1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}\right]} = \Delta V_t + (V_{GS} - V_t) \left\{ \frac{1 + \frac{\Delta I_D}{2I_D}}{1 + \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} - \frac{1 - \frac{\Delta I_D}{2I_D}}{1 - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)}} \right\}$$

Binomial Theorem:

$$(1+x)^m \xrightarrow{\eta = \text{small}} 1 + m\eta$$

$$V_{OS} = \Delta V_t + (V_{GS} - V_t) \left\{ \left(1 + \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) - \left(1 - \frac{1}{4} \frac{\Delta I_D}{I_D}\right) \left(1 + \frac{1}{4} \frac{\Delta(W/L)}{(W/L)}\right) \right\}$$

$$\cancel{1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} - \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}} - \cancel{1 + \frac{1}{4} \frac{\Delta I_D}{I_D} - \frac{1}{4} \frac{\Delta(W/L)}{(W/L)} + \frac{1}{16} \frac{\Delta I_D}{I_D} \frac{\Delta(W/L)}{(W/L)}}$$

$$= \Delta V_t + (V_{GS} - V_t) \left( \frac{1}{2} \frac{\Delta I_D}{I_D} - \frac{1}{2} \frac{\Delta(W/L)}{(W/L)} \right)$$

$$\therefore V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ \frac{\Delta I_D}{I_D} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

When  $V_{id} = V_{os} \rightarrow V_{od} = 0 \therefore I_{D1} R_{D1} = I_{D2} R_{D2}$

mis-match in  $I_D$  must be opposite that of  $R_D$

$$\therefore \frac{\Delta I_D}{I_D} = - \frac{\Delta R_D}{R_D}$$

$$V_{OS} = \Delta V_t + \frac{1}{2} (V_{GS} - V_t) \left\{ - \frac{\Delta R}{R} - \frac{\Delta(W/L)}{(W/L)} \right\}$$

Threshold Mismatch


Bias Independent

Geometric Variations (i.e., layout)

Scale or overdrive

$\Rightarrow$  Now, go to Bipolar Mismatch prepared material.

## MOSFET Source-Coupled Pair

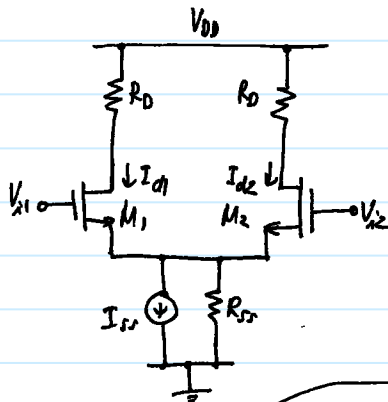

Assume:  $M_1$  &  $M_2$  are identical.

Find  $\Delta I_d = I_{d1} - I_{d2} = f(V_{id})$ .

$\Rightarrow$  approach: get  $V_{id} = f(\Delta I_d) \rightarrow$  then invert to get  $\Delta I_d = f(V_{id})$

$$I_{d1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{gs1} - V_t)^2 \Rightarrow V_{gs1} = V_t + \sqrt{\frac{2I_{d1}}{k}}$$

$$\therefore V_{id} = V_{gs1} - V_{gs2} = \sqrt{\frac{2I_{d1}}{k}} - \sqrt{\frac{2I_{d2}}{k}}$$

Define:

$$\begin{cases} \Delta I_d = I_{d1} - I_{d2} \\ I_d = \frac{I_{d1} + I_{d2}}{2} \end{cases} \Rightarrow \begin{cases} I_{d1} = I_d + \frac{\Delta I_d}{2} \\ I_{d2} = I_d - \frac{\Delta I_d}{2} \end{cases}$$

$$V_{id} = \sqrt{\frac{2(I_d + \frac{\Delta I_d}{2})}{k}} - \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{k}} \Rightarrow \frac{k}{2} V_{id}^2 = I_d + \frac{\Delta I_d}{2} - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2} + I_d - \frac{\Delta I_d}{2}$$

$$\frac{k}{2} V_{id}^2 = 2I_d - 2\sqrt{I_d^2 - \left(\frac{\Delta I_d}{2}\right)^2}$$

$\Rightarrow$  now rearrange to get  $\Delta I_d$  (algebra)

Solve for  $\Delta I_d$ :

$$\Delta I_d = \frac{k}{2} V_{id}^2 \left( \frac{2I_{ss}}{k/2} - V_{id}^2 \right)^{\frac{1}{2}} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{id} \sqrt{\left( \frac{2I_{ss}}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L}} \right) - V_{id}^2} = \Delta I_d$$

Large Signal Equation for Differential Output Current

Valid so long as the devices stay saturated:


$$|V_{id}| \leq \sqrt{\frac{2I_{ss}}{k}} = \sqrt{\frac{2I_{ss}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{2} (V_{GS} - V_t)$$

$V_{GS}$  for  $I_D = \frac{I_{ss}}{2}$

if true then input devices are both saturated

Thus, to extend the linear input range:

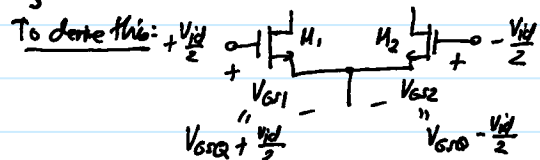- ①  $I_{ss} \uparrow \rightarrow (V_{GS} - V_t) \uparrow$
- ②  $W/L$
- ③  $L \uparrow$




When  $V_{id} \geq V_{GSQ} - V_t = \Delta V$  then  $M_2$  will cut-off

$\therefore V_{id} \leq 2(V_{GSQ} - V_t) \rightarrow$  to maintain saturation


$$V_{GSQ} - V_t = \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{2(I_d - \frac{\Delta I_d}{2})}{\mu_n C_{ox} \frac{W}{L}}} = \frac{V_{id}}{2}$$

Then plug in  $\Delta I_d$  & solve for  $V_{id}$
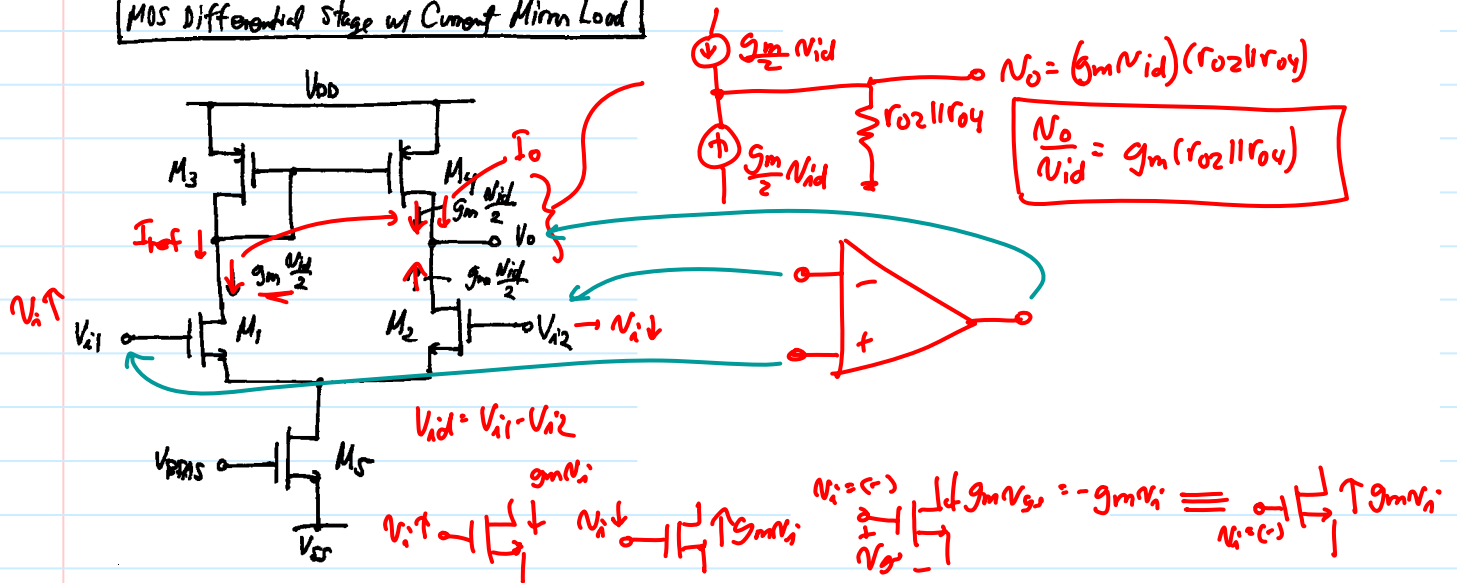
## MOS Differential Stage w/ Current Mirror Load



## CMRR -

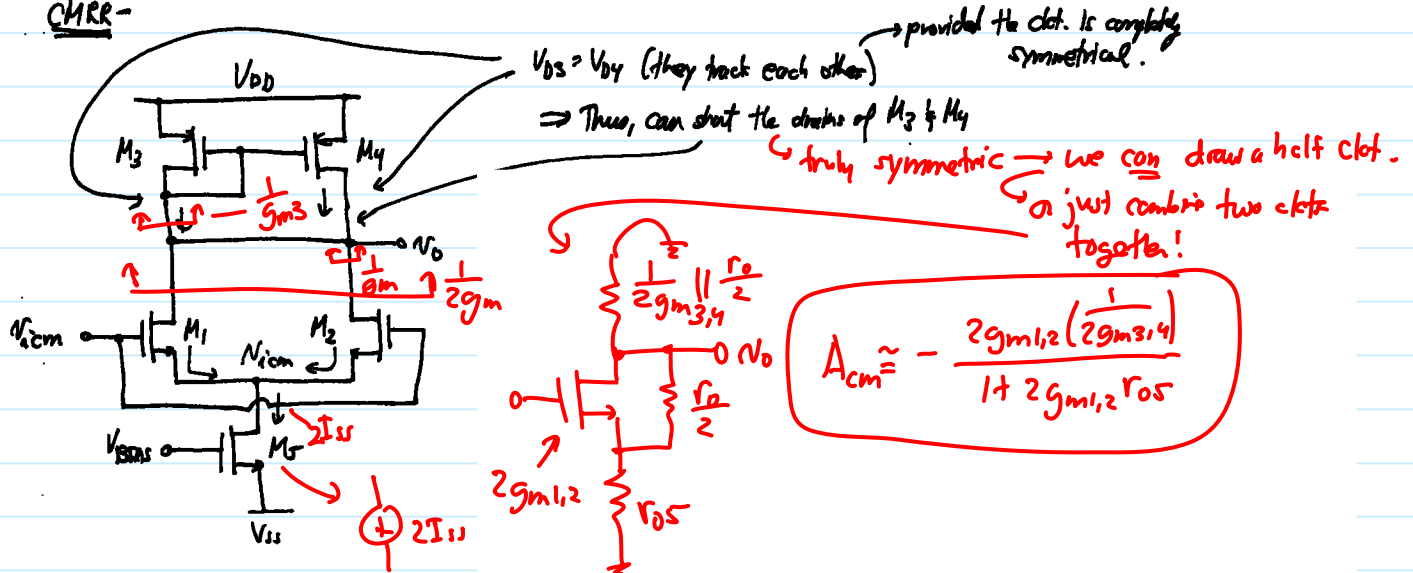

Thus:

$$CMRR = \left| \frac{A_{dm}}{A_{cm}} \right| = g_{m1,2} (r_{o1,2} || r_{o3,4}) (1 + 2g_{m1,2} r_{o5}) \left( \frac{g_{m3,4}}{g_{m1,2}} \right)$$

$$\rightarrow CMRR = (1 + 2g_{m1,2} r_{o5}) g_{m3,4} (r_{o1,2} || r_{o3,4})$$


Common-Mode Input Range - Range of input voltages in which all devices remain in saturation.

Low End - must keep  $M_5$  saturated

$$V_{icm(min)} = CMR- = V_{SS} + V_{DS5} + V_{GS1,2}$$

$$CMR- = V_{SS} + \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} (W/L)_5}} + V_{t1,2} + \sqrt{\frac{I_{SS}}{\mu_n C_{ox} (W/L)_{1,2}}}$$

High End - keep  $M_1, M_2$  saturated

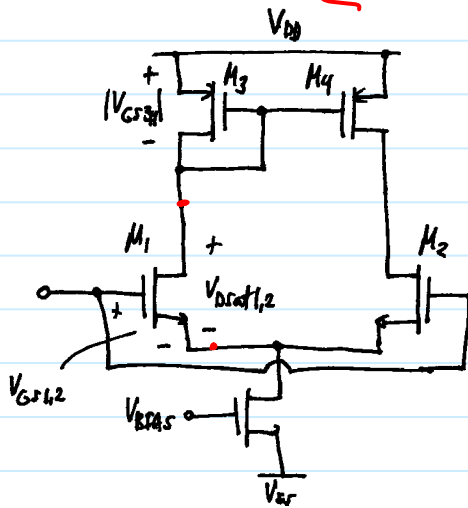

$$V_{icm(max)} = CMR+ = V_{DD} - |V_{GS3,4}| - V_{OV1,2} + V_{GS1,2}$$


$$V_{icm(max)} = CMR+ = V_{DD} - \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{3,4}}} - |V_{t3,4}| + V_{t1,2}$$

Device Mismatch Effects in Diff. Amplifiers

- ⇒ up to this point, we've assumed that  $Q_1$  &  $Q_2$  are perfectly matched  
 ⇒ in actual ckt., got device mismatches due to processing variations

The Result:

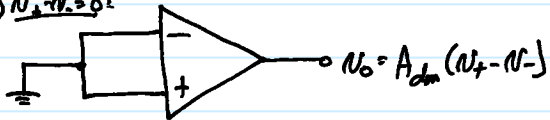①  $N_+ - N_- = 0$  → Output not zero when Input is zero →  $N_{od} \neq 0$  when  $N_{id} = 0$ !



Ideal Case:  $N_o = 0$

Reality:  $N_o \neq 0$ , even w/  $(N_+ - N_-) = 0$ !

② Input  $I_{B1} \neq I_{B2}$  if  $Q_1$  &  $Q_2$  not matched. (for BJT & JFET only.)


To model these effects, introduce:

① Input Offset Voltage,  $V_{os}$



② Input Offset Current,  $I_{os}$

Typ.  $I_{os} = 10 \text{ nA}$  for BJT

Typ. 1-5 nA for BJT

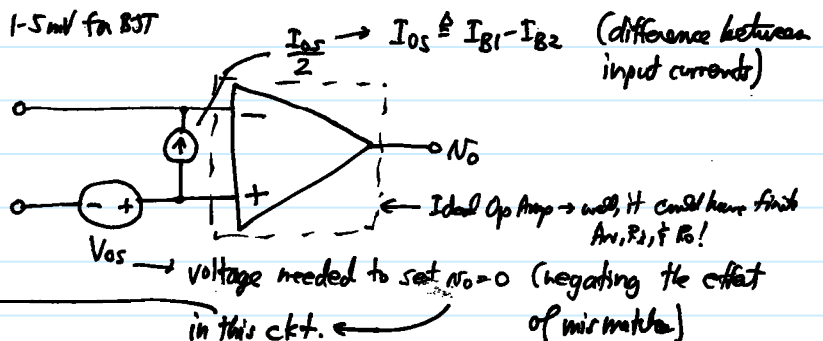Effect of  $V_{os}$  on Op Amp Ckt. -

Example. Integrator

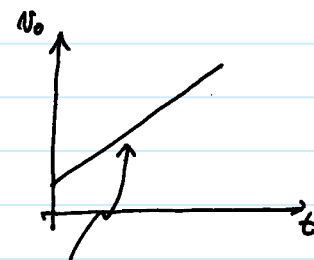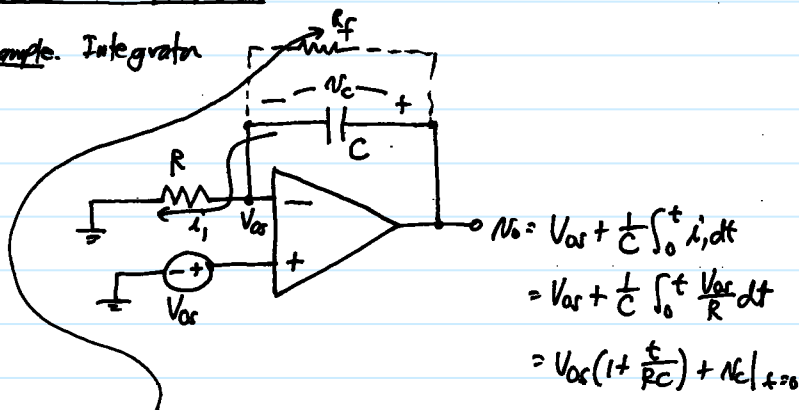


Fix: Place an  $R_f$  in shunt w/ the C

→ then  $N_o = V_{os} \left( 1 + \frac{R_f}{R} \right)$ , and railing doesn't happen


⇒ but, usually  $R_f$  is large to allow the C to dominate

the integrator Xfr Function  $\therefore N_o = V_{os} \left( 1 + \frac{R_f}{R} \right)$  can be quite large → still want  $V_{os}$  small

$V_{os}$  is even more important in setting the resolution of AD converters and other precision ckt.

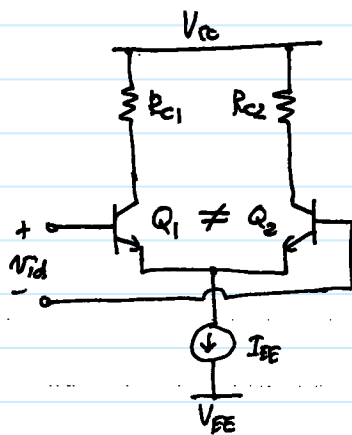$V_{OS}$  in a Mismatched ECPObjective: Derive an expression for  $V_{OS}$ .Actual ECP w/ Mismatched  $Q_1$  &  $Q_2$  &  $R$ 's

Equivalent to an ideal ECP + use  $V_{OS}$  &  $I_{OS}$  to model the effect of mismatches

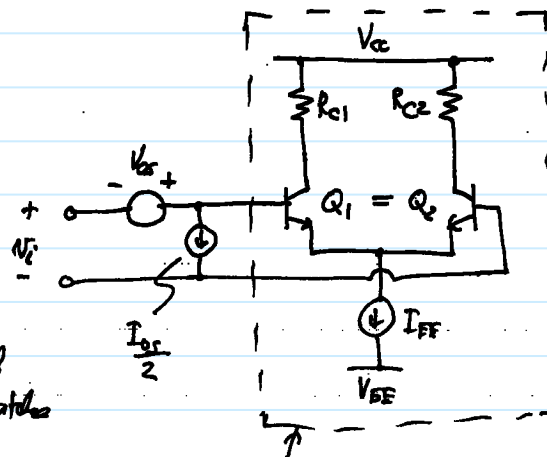Ideal ECP w/ Matched  $Q_1$  &  $Q_2$  and  $R_{C1} = R_{C2}$ Input Offset Voltage  $V_{OS}$  arises due to variations in:①  $Q_1 \neq Q_2 \rightarrow I_S \neq \beta$  vary:

$$I_S = \frac{q n_i^2 D_n A}{N_A W_B (V_{CB})}$$


"function of"

 $I_{S1} \neq I_{S2}$  can be caused by:

- (i)  $A_1 \neq A_2$  (etching tolerance limits)
- (ii)  $N_{A1} \neq N_{A2}$  (doping variations of base)
- (iii)  $W_B \neq f(V_{CB})$  (width variations exacerbated by  $V_{CB}$  diff)

②  $R_{C1} \neq R_{C2} \rightarrow$  cause gain variationDefinition.  $V_{OS} = V_{id}$  to get  $V_{od} = 0$ , which occurs when:

$$KVL: -V_{OS} - V_{be1} + V_{be2} = 0$$

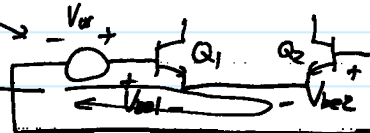

$$V_{OS} = V_{be1} - V_{be2} = V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}} = V_T \ln \left( \frac{I_{C1}}{I_{C2}} \frac{I_{S2}}{I_{S1}} \right)$$

Find  $\frac{I_{C1}}{I_{C2}}$  in terms of design elements:

$$[ \text{When } V_{id} = V_{OS} \rightarrow V_{od} = 0 ] \rightarrow V_{od} = (V_{CC} - I_{C1} R_{C1}) - (V_{CC} - I_{C2} R_{C2}) = 0$$

$$I_{C1} R_{C1} = I_{C2} R_{C2} \rightarrow \frac{I_{C1}}{I_{C2}} = \frac{R_{C2}}{R_{C1}}$$

$$V_{OS} = V_T \ln \left( \frac{R_{C2}}{R_{C1}} \frac{I_{S2}}{I_{S1}} \right)$$

This is an exact equation for  $V_{OS}$ . It's often more useful & intuitive to express this in terms of percent variations (and eventually standard deviations).



Convert to Percent Variation Form -

Define:  $R_c = \frac{R_{c1} + R_{c2}}{2}$ ,  $\Delta R_c = R_{c1} - R_{c2}$  } Objective: Express Var in terms of percent variations  $\frac{\Delta R_c}{R_c} \neq \frac{\Delta I_s}{I_s}$ .

$I_s = \frac{I_{s1} + I_{s2}}{2}$ ,  $\Delta I_s = I_{s1} - I_{s2}$  }

In general:  $\Delta X = X_1 - X_2$  }  $X_1 = X + \frac{\Delta X}{2}$   $\Rightarrow$  Thus:  $R_{c1} = R_c + \frac{\Delta R_c}{2}$ ,  $R_{c2} = R_c - \frac{\Delta R_c}{2}$

$X = \frac{X_1 + X_2}{2}$  }  $X_2 = X - \frac{\Delta X}{2}$   $I_{s1} = I_s + \frac{\Delta I_s}{2}$ ,  $I_{s2} = I_s - \frac{\Delta I_s}{2}$

With these formulations:

$$V_{OS} = V_T \ln \left[ \frac{R_{c2}}{R_{c1}} \frac{I_{s2}}{I_{s1}} \right] = V_T \ln \left\{ \frac{R_c - \frac{\Delta R_c}{2}}{R_c + \frac{\Delta R_c}{2}} \frac{I_s - \frac{\Delta I_s}{2}}{I_s + \frac{\Delta I_s}{2}} \right\} = V_T \ln \left\{ \frac{1 - \frac{\Delta R_c}{2R_c}}{1 + \frac{\Delta R_c}{2R_c}} \frac{1 - \frac{\Delta I_s}{2I_s}}{1 + \frac{\Delta I_s}{2I_s}} \right\}$$

$$\left[ \ln(1+x) \approx x - \frac{x^2}{2} + \frac{x^3}{3} - \dots \right] \Rightarrow V_{OS} \approx V_T \left\{ -\frac{\Delta R_c}{2R_c} - \frac{\Delta R_c}{2R_c} - \frac{\Delta I_s}{2I_s} - \frac{\Delta I_s}{2I_s} \right\}$$

taking the first term assuming  $\Delta R \ll R_c$  &  $\Delta I_s \ll I_s$

$$V_{OS} = V_T \left\{ -\frac{\Delta R_c}{R_c} - \frac{\Delta I_s}{I_s} \right\}$$

Since  $\frac{\Delta R_c}{R_c}$  and  $\frac{\Delta I_s}{I_s}$  are statistically <sup>varying</sup> parameters for a given process run & layout, one usually expresses terms in the form of variances when specifying  $V_{OS}$ :

$\rightarrow$  since  $\frac{\Delta R_c}{R_c} \neq \frac{\Delta I_s}{I_s}$  are uncorrelated, their variances add like powers:

$$\sigma_{Var} = V_T \sqrt{\sigma_{\Delta R_c/R_c}^2 + \sigma_{\Delta I_s/I_s}^2}$$

Ex: Typ.  $\sigma_{\Delta R_c/R_c} \sim 0.01$ ,  $\sigma_{\Delta I_s/I_s} \sim 0.05$

$$\therefore \sigma_{V_{OS}} = (26m) \sqrt{(0.01)^2 + (0.05)^2} = \underline{1.3mV} \quad \text{Typ. Var for BJT} \sim \underline{1-5mV}$$

V<sub>OS</sub> Drift w/ Temperature

$$\frac{dV_{OS}}{dT} = \frac{kT}{q} \left\{ -\frac{\Delta R_c}{R_c} - \frac{\Delta I_s}{I_s} \right\} \frac{1}{T} = \frac{Var}{T}$$

indep. w/ T      [in kelvin]

Ex:  $\frac{dV_{OS}}{dT} = \frac{1.3m}{300K} = 4.3 \mu V/^\circ C$  <sup>drift</sup> around  $T = 300K$ .

$I_{OS}$  in a Mismatched ECP

By Definition:  $I_{OS} = I_{B1} - I_{B2} = \frac{I_{C1}}{\beta_1} - \frac{I_{C2}}{\beta_2} = I_{OS}$

To express in percent variations:

$$\begin{cases} I_{C1} = I_C + \frac{\Delta I_C}{2} \\ I_{C2} = I_C - \frac{\Delta I_C}{2} \end{cases} \quad \begin{cases} \beta_1 = \beta + \frac{\Delta \beta}{2} \\ \beta_2 = \beta - \frac{\Delta \beta}{2} \end{cases}$$

$$\therefore I_{OS} = \frac{I_C + \frac{\Delta I_C}{2}}{\beta + \frac{\Delta \beta}{2}} - \frac{I_C - \frac{\Delta I_C}{2}}{\beta - \frac{\Delta \beta}{2}} = \frac{I_C}{\beta} \left\{ \frac{1 + \frac{\Delta I_C}{2I_C}}{1 + \frac{\Delta \beta}{2\beta}} - \frac{1 - \frac{\Delta I_C}{2I_C}}{1 - \frac{\Delta \beta}{2\beta}} \right\}$$

$$\left[ \frac{1}{1+x} \approx 1 - x + x^2 - \dots \right] \rightarrow = \frac{I_C}{\beta} \left\{ \left(1 + \frac{\Delta I_C}{2I_C}\right) \left(1 - \frac{\Delta \beta}{2\beta}\right) - \left(1 - \frac{\Delta I_C}{2I_C}\right) \left(1 + \frac{\Delta \beta}{2\beta}\right) \right\}$$

$$= \frac{I_C}{\beta} \left\{ 1 + \frac{\Delta I_C}{2I_C} - \frac{\Delta \beta}{2\beta} - \frac{\Delta I_C}{2I_C} \frac{\Delta \beta}{2\beta} - 1 + \frac{\Delta I_C}{2I_C} - \frac{\Delta \beta}{2\beta} + \frac{\Delta I_C}{2I_C} \frac{\Delta \beta}{2\beta} \right\}$$

$$I_{OS} = \frac{I_C}{\beta} \left\{ \frac{\Delta I_C}{I_C} - \frac{\Delta \beta}{\beta} \right\}$$


But for  $V_{od} = 0V \Rightarrow \frac{I_{C1}}{I_{C2}} = \frac{R_{C2}}{R_{C1}} \rightarrow \frac{\Delta I_C}{I_C} = - \frac{\Delta R_C}{R_C}$

$$\therefore I_{OS} = - \frac{I_C}{\beta} \left( \frac{\Delta R_C}{R_C} + \frac{\Delta \beta}{\beta} \right)$$

Ex: Typ:  $\sigma_{\Delta R_C} = 0.1$ ,  $\sigma_{\Delta \beta / \beta} = 0.01$

$$\Rightarrow I_{OS} = - \frac{I_C}{\beta} \left[ \sigma_{\Delta R_C}^2 + \sigma_{\Delta \beta / \beta}^2 \right]^{1/2} \approx -0.1 \frac{I_C}{\beta} \approx -0.1 I_B = I_{OS}$$
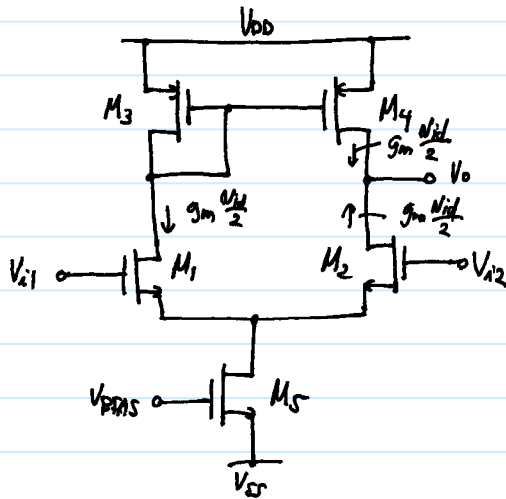
## MOS Differential Stage w/ Current Mirror Load



Small-Signal Gain: (similar to BJT)

$$\frac{V_o}{V_{id}} = g_{m2}(r_{o2} \parallel r_{o4}) = \frac{g_{m2}}{g_{ds2} + g_{ds4}} = \frac{\sqrt{2\mu_n C_{ox} (\frac{W}{L})_2 I_{D2}}}{\lambda_2 I_{D2} + \lambda_4 I_{D4}}$$

$$= \frac{\sqrt{\mu_n C_{ox} (\frac{W}{L})_2 I_{SS}}}{\frac{I_{SS}}{2} (\lambda_2 + \lambda_4)} \Rightarrow \frac{V_o}{V_{id}} = \frac{2}{\lambda_2 + \lambda_4} \sqrt{\frac{\mu_n C_{ox} (W/L)_2}{I_{SS}}}$$

$$\left[ \frac{\Delta(W/L)_{1,2}}{(W/L)_{1,2}} - \frac{\Delta(W/L)_{3,4}}{(W/L)_{3,4}} \right]$$

Offset Voltage -  $V_{OS} = V_{GS1} - V_{GS2}$  when  $V_{id} = 0V$ 

$$V_{OS} = \Delta V_{t1,2} + \Delta V_{t3,4} \left( \frac{g_{m3,4}}{g_{m1,2}} \right) + \frac{(V_{GS} - V_t)_{1,2}}{2} \left[ \frac{\Delta k_{1,2}}{k_{1,2}} + \frac{\Delta k_{3,4}}{k_{3,4}} \right]$$

Via similar derivation to what we just did

For small  $V_{OS}$ : ① small  $(V_{GS} - V_t)$ 

$$\text{② } g_{m3,4} < g_{m1,2} \rightarrow k_{3,4} < k_{1,2} \quad \frac{1}{2} \left( \frac{W}{L} \right)_{3,4} < \left( \frac{W}{L} \right)_{1,2}$$