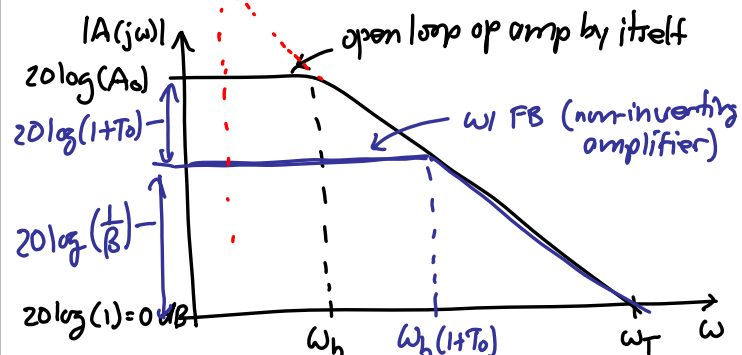


Finite Op Amp Gain & Bandwidth

For an ideal op amp, $A = \infty$.

In reality, the gain is given by: $A(s) = \frac{A_0}{1 + s/\omega_b}$



$\omega_T \triangleq$ unity gain frequency = freq. @ which $|A(j\omega)| = 1$ (= 0 dB)

At ω_T :

$$|A(j\omega_T)| = 1 = \frac{A_0}{\sqrt{1 + \left(\frac{\omega_T}{\omega_b}\right)^2}}$$

$$[\omega_T \gg \omega_b] \Rightarrow \frac{A_0}{\frac{\omega_T}{\omega_b}} = 1 \rightarrow \omega_T = A_0 \omega_b$$

Gain-Bandwidth Product


For $\omega \gg \omega_b$:

$$A(s) \approx \frac{A_0}{s} = \frac{A_0 \omega_b}{s} = \frac{\omega_T}{s} = \frac{f_T}{f} \quad \left[\begin{array}{l} \text{Integrate w/ time} \\ \text{Constant } \bar{c} = \frac{1}{\omega_T} \end{array} \right]$$

The unity gain bandwidth f_T is usually specified on op amp data sheets. Knowing f_T , one can easily determine the op amp gain at a given frequency f .

Frequency Response of Closed Loop Amplifiers

Example. Non-Inverting Amplifier

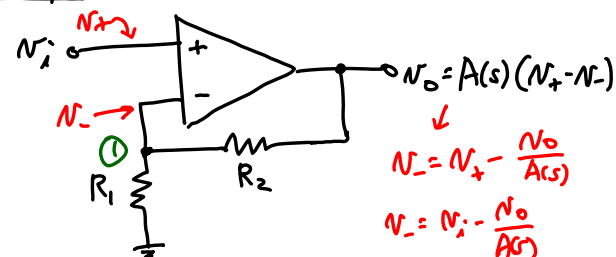

Find an expression for the gain as a function of frequency.

① Brute force derivation:

$$\text{KCL @ ①: } \frac{N_o - N_-}{R_2} = \frac{N_-}{R_1} \rightarrow \frac{N_o}{R_2} = N_- \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$


$$\frac{N_o}{R_2} = \left(N_i - \frac{N_o}{A(s)} \right) \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \rightarrow \frac{N_o}{N_i}(s) = \frac{1 + \frac{R_2}{R_1}}{1 + \frac{1}{A(s)} \left(1 + \frac{R_2}{R_1} \right)}$$


$$\left[A(s) = \frac{A_0}{1 + \frac{s}{\omega_b}} \right] \Rightarrow \frac{N_o}{N_i}(s) = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + \frac{s}{A_0 \omega_b \left(\frac{R_1 + R_2}{R_1} \right)}}$$

(after a lot of algebraic rearrangement)

Neg. FB Block Diagram

② More insightful way to do this:

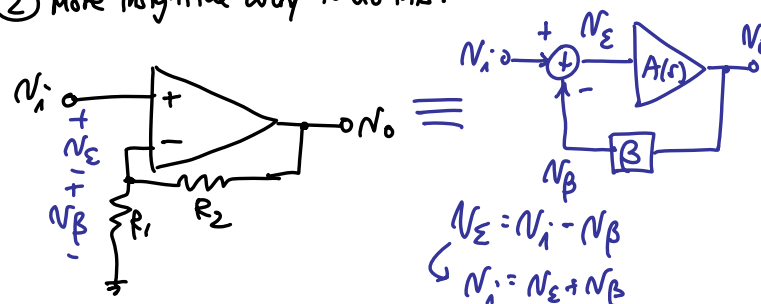

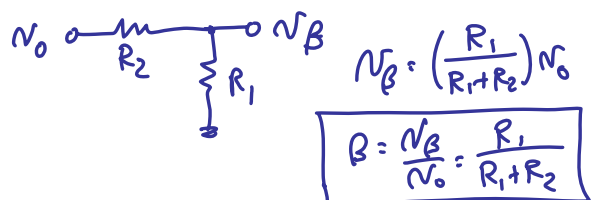

Recall from our previous FB analysis:

$$\frac{V_o}{V_i}(s) = \frac{A(s)}{1 + \beta A(s)}$$

$$\left[A(s) = \frac{A_o}{1 + \frac{s}{\omega_b}} \right] \rightarrow \frac{V_o}{V_i}(s) = \frac{\frac{A_o}{1 + \frac{s}{\omega_b}}}{1 + \beta \left(\frac{A_o}{1 + \frac{s}{\omega_b}} \right)}$$

$$\frac{V_o}{V_i}(s) = \frac{A_o}{1 + \beta A_o} \cdot \frac{1}{1 + \frac{s}{\omega_b(1 + \beta A_o)}}$$

closed loop dc gain term frequency shaping term

$T_o = \beta A_o \triangleq$ "loop gain" at $\omega = 0$
(i.e., at dc)

Plug in β :

$$\frac{V_o}{V_i}(s) \approx \frac{1}{\beta} \cdot \frac{1}{1 + \frac{s}{\omega_b \beta A_o}} = \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{1}{1 + \frac{s}{\omega_b A_o \left(\frac{R_1}{R_1 + R_2} \right)}} = \frac{V_o}{V_i}(s)$$

What if $A_o \neq \text{large}$?

can't say $\frac{A_o}{1 + \beta A_o} \approx \frac{1}{\beta}$

Need to increase the gain of our op amp!

Observations:

① Closed loop DC gain = $\frac{A_o}{1 + \beta A_o} = \frac{A_o}{1 + T_o} \approx \frac{A_o}{T_o}$
 i.e., the closed loop gain is reduced from the open loop gain by $1 + T_o \rightarrow$ show this on graph
 $[T_o \gg 1]$

② Alternatively, closed loop DC gain $\approx \frac{A_o}{\beta A_o} = \frac{1}{\beta} \quad [T_o \gg 1]$

③ ω_{-3dB} has increased from $\omega_b \rightarrow \omega_b(1 + \beta A_o) = \omega_b(1 + T_o)$
 To draw the Bode plot, just find the dc gain, draw a horizontal line across, then follow the open loop response after running into it!

④ Gain-BW Product = $\frac{A_o}{1 + \beta A_o} \omega_b(1 + \beta A_o) = A_o \omega_b = \omega_T$
 \therefore the Gain-BW product remains the same for the open & closed loop FB cases!