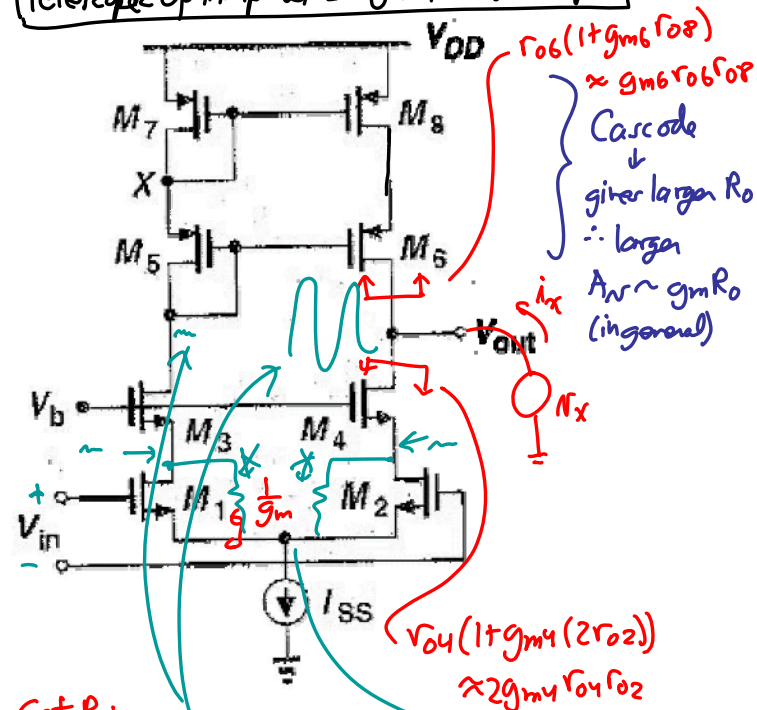


• Today: Higher Gain Op Amps

How can we increase gain?

- ① Cascode
- ② Cascade of amplifiers


Telescopic Op Amp w/ Single-Ended Output



Get  $R_o$ :

Due to huge difference in node resistance.

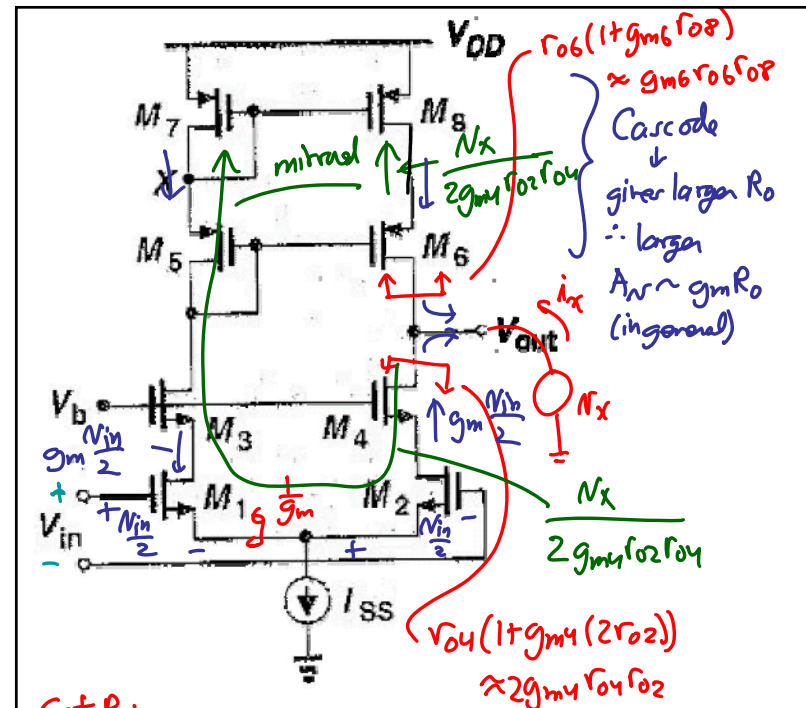These cascodes effectively shield the drains of  $M_1$  &  $M_2$  from large voltage excursions. This node stays still → virtual ground! → Do it this way later for the folded cascode.




Get  $R_o$ :

$$R_o = (g_{mN} r_{oN}^2) \parallel (g_{mP} r_{oP}^2)$$


$$G_m = \frac{i_{out}}{v_{in}} = g_m$$


$$\therefore \text{Gain} = A_v = g_{mN} \left[ (g_{mN} r_{oN}^2) \parallel (g_{mP} r_{oP}^2) \right]$$

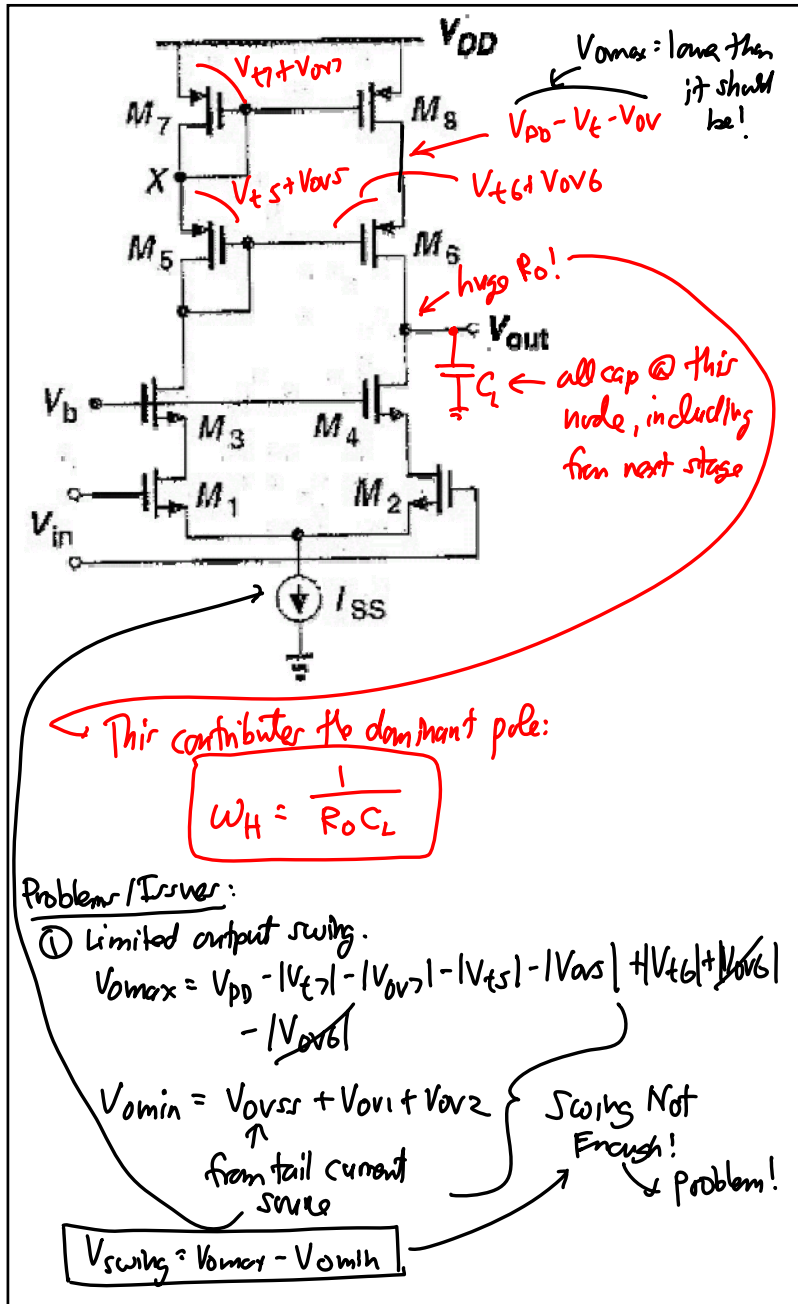↑ huge R!    ↑ huge R!  
gain will be big! ✓



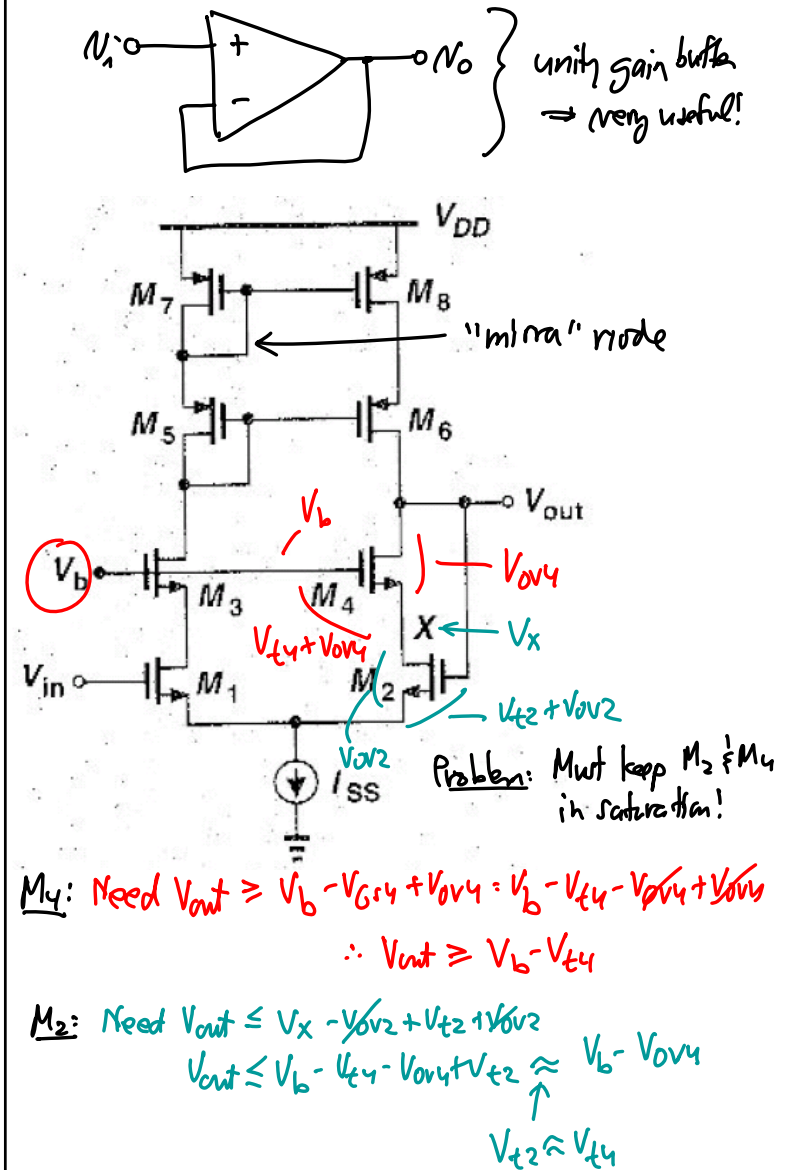Problem ②: Difficult to tie input to output!



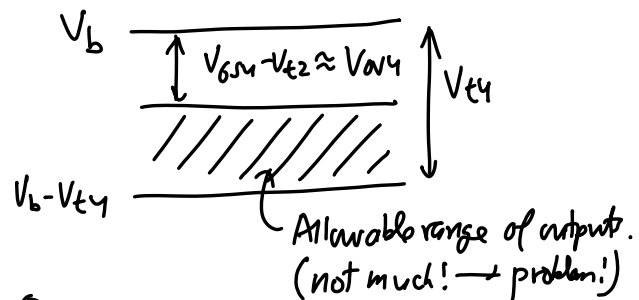


Problem ③:

Low freq. non-dominant pole associated w/ the "inter" node.  $\rightarrow$  will hurt stability in feedback ckt! (we'll cover this later)

Soln: use fully differential, fully balanced op amp

One solution to the above: use folded-cascode  $\rightarrow$  we'll do this later  
Another solution: 2-stage op amp

Classic 2-Stage Op Amp

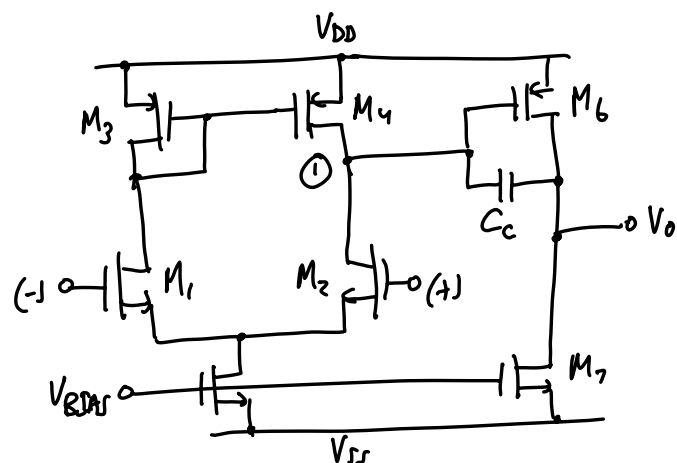


Gain -

$$\text{1st Stage: } A_{v1} = \frac{V_{O1}}{V_i} = -g_{m2}(r_{o2} \parallel r_{o4})$$

$$\text{2nd Stage: } A_{v2} = \frac{V_O}{V_{O1}} = g_{m6}(r_{o6} \parallel r_{o7})$$

$$A_v = A_{v1} A_{v2} = g_{m2}(r_{o2} \parallel r_{o4}) g_{m6}(r_{o6} \parallel r_{o7})$$

Freq. Response:

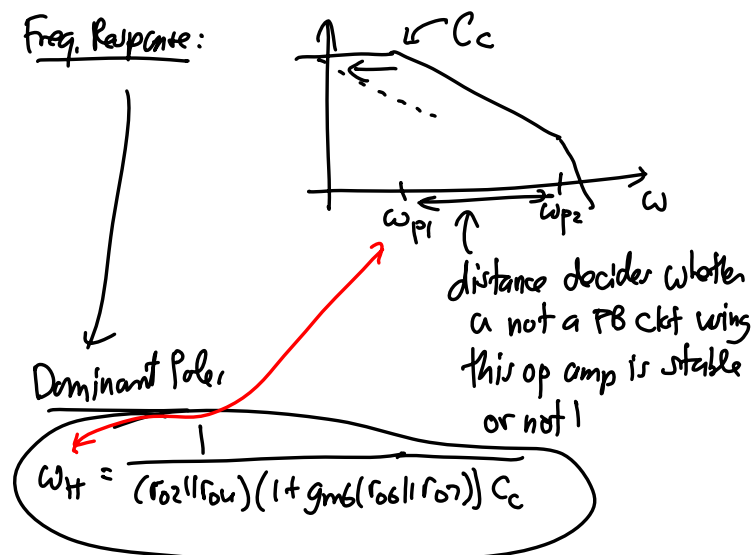

Output Swing:

$$V_{swing} = V_{DD} - V_{DS} - |V_{ov6}| - V_{ov7}$$